

# Components in wireless technology, 5XTC0

## Module 6

### Exercise: Amplifier matching using distributed components

Vojkan Vidojkovic



Technische Universiteit  
**Eindhoven**  
University of Technology

Where innovation starts


# Outline

- Amplifier design
  - Solution for problem 1 from assignment
- Matching using distributed components
- Amplifier matching using distributed

# Formula list available for exam

Power delivered to the load	$P_L = \frac{ V_2 ^2}{2Z_0} (1 -  \Gamma_L ^2)$
Input power to the network	$P_{in} = \frac{ V_1 ^2}{2Z_0} (1 -  \Gamma_{in} ^2)$
Input and output reflection coefficients of a transistor with a source and load: general case	$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$ $\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s}$
Input and output reflection coefficients of a transistor with a source and load: unilateral case	$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11}$ $\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22}$
Gain of the input matching network	$G_S = \frac{1 -  \Gamma_S ^2}{ 1 - \Gamma_{in}\Gamma_S ^2}$
Gain of the output matching network	$G_L = \frac{1 -  \Gamma_L ^2}{ 1 - S_{22}\Gamma_L ^2}$
Gain of the transistor (unilateral case)	$G_0 =  S_{21} ^2$
Transducer gain of the basic amplifier circuit (input matching, unilateral transistor, output matching)	$G_T = G_S G_0 G_L$ $G_{T,0dB} = G_{S,0dB} + G_{0,0dB} + G_{L,0dB}$
Maximum gain of the input and output matching networks	$G_{S,max} = \frac{1}{1 -  S_{11} ^2}$ $G_{L,max} = \frac{1}{1 -  S_{22} ^2}$
Maximum transducer power gain, unilateral case	$G_{TU,max} = \frac{1}{1 -  S_{11} ^2}  S_{21} ^2 \frac{1}{1 -  S_{22} ^2}$
Normalized gain factors $g_s$ and $g_L$	$g_s = \frac{G_S}{G_{S,max}} = \frac{1 -  \Gamma_S ^2}{ 1 - S_{11}\Gamma_S ^2} (1 -  S_{11} ^2)$ $g_L = \frac{G_L}{G_{L,max}} = \frac{1 -  \Gamma_L ^2}{ 1 - S_{22}\Gamma_L ^2} (1 -  S_{22} ^2)$
Center and radius of the constant gain circle for the input matching network	$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S) S_{11} ^2}$ $R_S = \frac{\sqrt{1 - g_S} (1 -  S_{11} ^2)}{1 - (1 - g_S) S_{11} ^2}$
Center and radius of the constant gain circle for the output matching network	$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) S_{22} ^2}$ $R_L = \frac{\sqrt{1 - g_L} (1 -  S_{22} ^2)}{1 - (1 - g_L) S_{22} ^2}$
Condition for "unconditionally stable" device, general case	for all $ \Gamma_L  < 1$ and $ \Gamma_S  < 1$ $\Rightarrow \begin{cases}  \Gamma_{in}  = \left  S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right  < 1 \\  \Gamma_{out}  = \left  S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right  < 1 \end{cases}$

Conditions for "unconditionally stable" device, unilateral case	$ \Gamma_m  =  S_{11}  < 1$ $ \Gamma_{out}  =  S_{22}  < 1$
Center and radius of the stability circles, load side	$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{ S_{22} ^2 -  \Delta ^2}$ (center), $R_L = \frac{ S_{12}S_{21} }{ S_{22} ^2 -  \Delta ^2}$ (radius), $\Delta = S_{11}S_{22} - S_{12}S_{21}$
Center and radius of the stability circles, source side	$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{ S_{11} ^2 -  \Delta ^2}$ (center), $R_S = \frac{ S_{12}S_{21} }{ S_{11} ^2 -  \Delta ^2}$ (radius), $\Delta = S_{11}S_{22} - S_{12}S_{21}$
Test for unconditional stability, general case	$ \Delta  =  S_{11}S_{22} - S_{12}S_{21}  < 1$ and $K = \frac{1 -  S_{11} ^2 -  S_{22} ^2 +  \Delta ^2}{2 S_{12}S_{21} } > 1$
Test for unconditional stability, unilateral case	$ S_{11}  < 1$ $ S_{22}  < 1$
Two-stage amplifier: Output noise and noise figure	$P_{N,total} = G_{A2} (G_{A1} P_{N,m} + P_{n1}) + P_{n2}$ $\Rightarrow F_{total} = \frac{P_{N,total}}{P_{N,m} G_{A1} G_{A2}} = 1 + \frac{P_{n1}}{P_{N,m} G_{A1}} + \frac{P_{n2}}{P_{N,m} G_{A1} G_{A2}}$ $F_{total} = F_1 + \frac{F_2 - 1}{G_{A1}}$ with $F_j = 1 + \frac{P_{nj}}{P_{N,m} G_{Aj}}$ , $j = 1, 2$
Noise figure of a 2-port amplifier	$F = F_{min} + \frac{r_N}{g_S} \left  \frac{y_S - y_{opt}}{y_S - y_{opt}} \right ^2$ $F = F_{min} + 4r_N \frac{ \Gamma_S - \Gamma_{opt} ^2}{(1 -  \Gamma_S ^2)  1 + \Gamma_{opt} ^2}$
Constant noise circles	$C_F = \frac{\Gamma_{opt}}{1 + N}$ $R_F = \frac{1}{1 + N} \sqrt{N^2 + N(1 -  \Gamma_{opt} ^2)}$ $\Delta F_n' = N = (F - F_{min}) \frac{ 1 + \Gamma_{opt} ^2}{4r_n} = \frac{ \Gamma_S - \Gamma_{opt} ^2}{1 -  \Gamma_S ^2}$

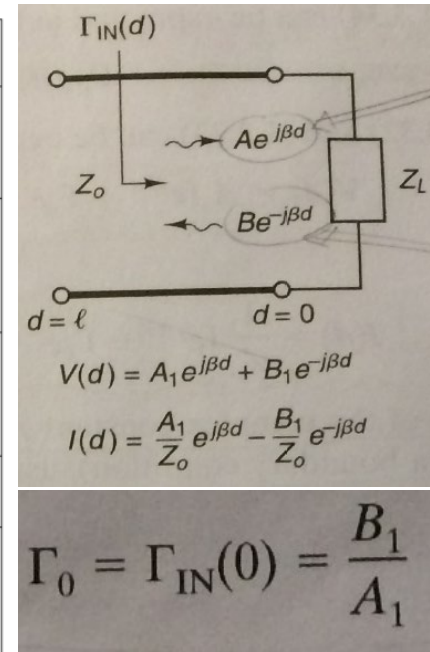

# Problem 1

## - Assignment, problem 1

A microwave amplifier is to be designed for  $G_{TU,max}$  using a bipolar transistor with:

$$S_{11}=0.4, \angle 130^\circ$$

$$S_{12} = 0$$

$$S_{21}=6, \angle 40^\circ$$

$$S_{22}=0.7, \angle -75^\circ$$

The S-parameters were measured in a  $50\ \Omega$  system at  $f=1\text{ GHz}$ ,  $V_{CE}=15\text{ V}$ , and  $I_C=15\text{ mA}$ .

- Determine whether this amplifier is unconditionally stable.
- Determine  $G_{TU,max}$ . Express your answer in dB.
- Determine the optimum source impedance and the optimum load impedance for maximum gain. Illustrate your answer in the Smith chart.
- Design a 2-element matching network at the input and a 2-element matching network at the output of the amplifier to reach conjugate matching to a  $50\ \Omega$  source and load impedance. Illustrate your answer on the Smith chart.
- Calculate the constant gain circle for  $G_L=1.5\text{ dB}$  and indicate it in the Smith chart.

# Problem 1: Solution

Problem 2:

$$\begin{aligned} S_{11} &= 0.4 e^{j130} \\ S_{12} &= 0 \\ S_{21} &= 6 e^{j40} \\ S_{22} &= 0.7 e^{j75} \end{aligned}$$

$$\begin{aligned} a) \quad \Delta &= S_{11} S_{22} - S_{12} S_{21} < 1 \\ K &= \frac{1 - |S_{11}|^2 - |S_{22}|^2 + \Delta^2}{2 |S_{12} S_{21}|} > 1 \end{aligned}$$

→ conditions for unconditional stability

$$\begin{aligned} \text{unilateral case: } |S_{11}| &= 0.4 < 1 \\ |S_{22}| &= 0.7 < 1 \end{aligned}$$

amplifier unconditionally stable

$$b) \quad G_{T, \max} = \frac{1}{1 - |S_{11}|^2} \cdot \frac{|S_{21}|^2}{1 - |S_{22}|^2}$$

→ unilateral case


$$G_{T, \max} = 1.2 \cdot 36 \cdot 2 = 86.4$$

$$G_{T, \max} [\text{dB}] = 10 \log G_{T, \max}$$

$$G_{T, \max} [\text{dB}] = 19.4 \text{ dB}$$

①
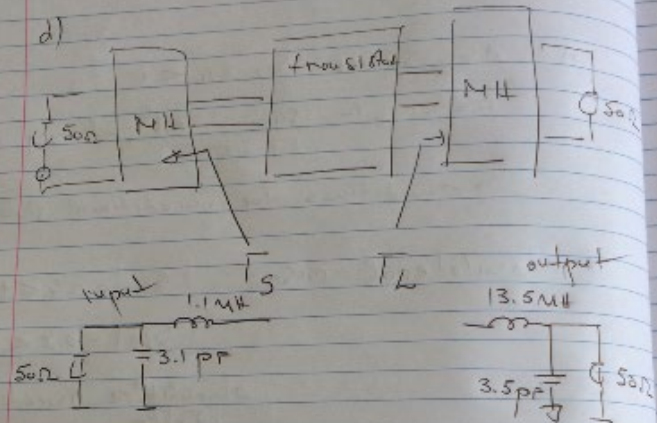
$$\begin{aligned} c) \quad \Gamma_S &= S_{11}^* = 0.4 e^{-j130} \\ \Gamma_L &= S_{22}^* = 0.7 e^{-j75} \end{aligned}$$



$$e) \quad G_L = 1.5 \text{ dB} \Rightarrow G_L = 1.41$$

$$G_{L, \max} = \frac{1}{1 - |S_{22}|^2} = 2$$


$$g_L = \frac{1.41}{2} = 0.71$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$


$$P_L = \frac{|1 - g_L| (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$



# Problem 1: Solution, matching at input

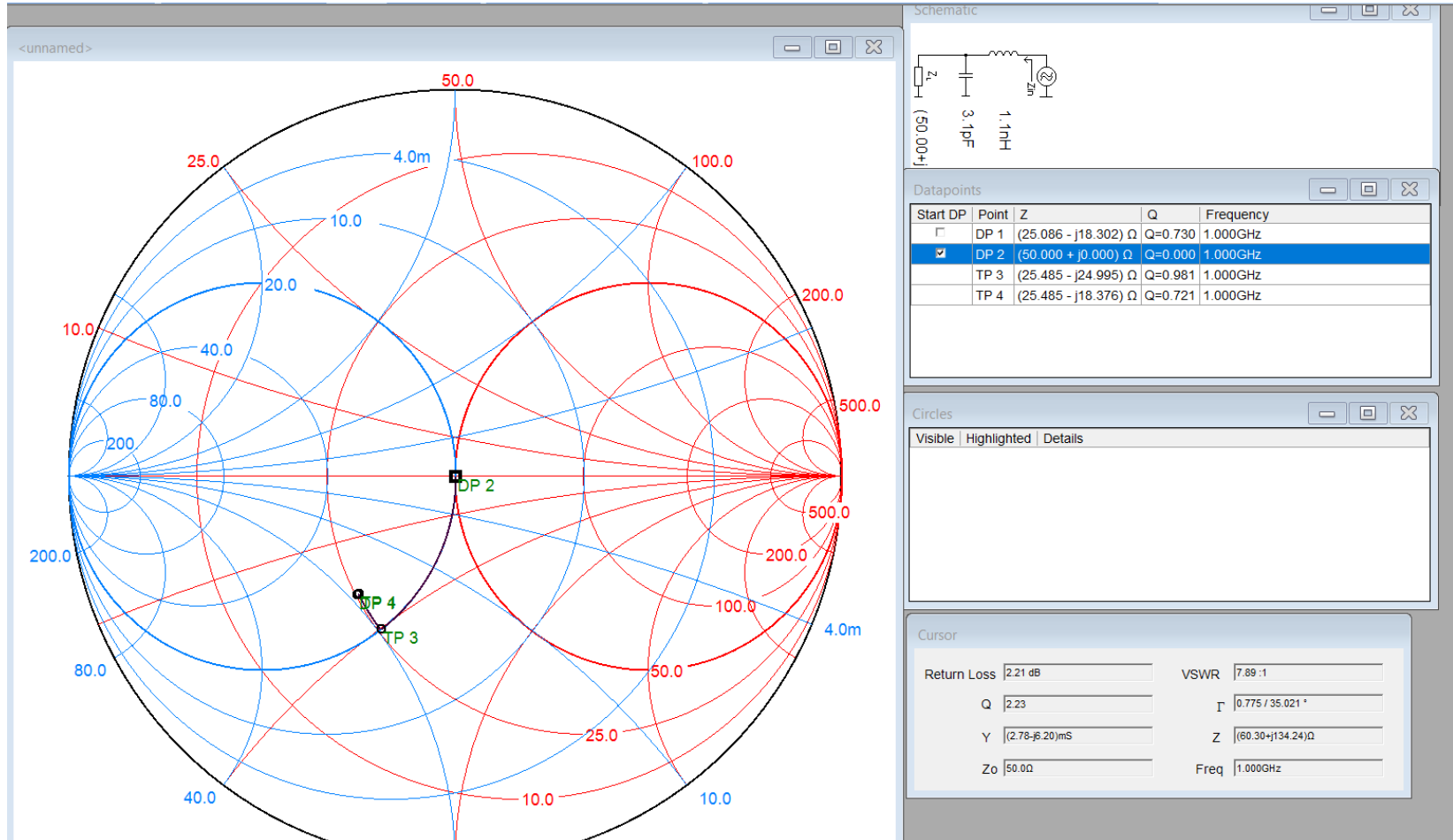

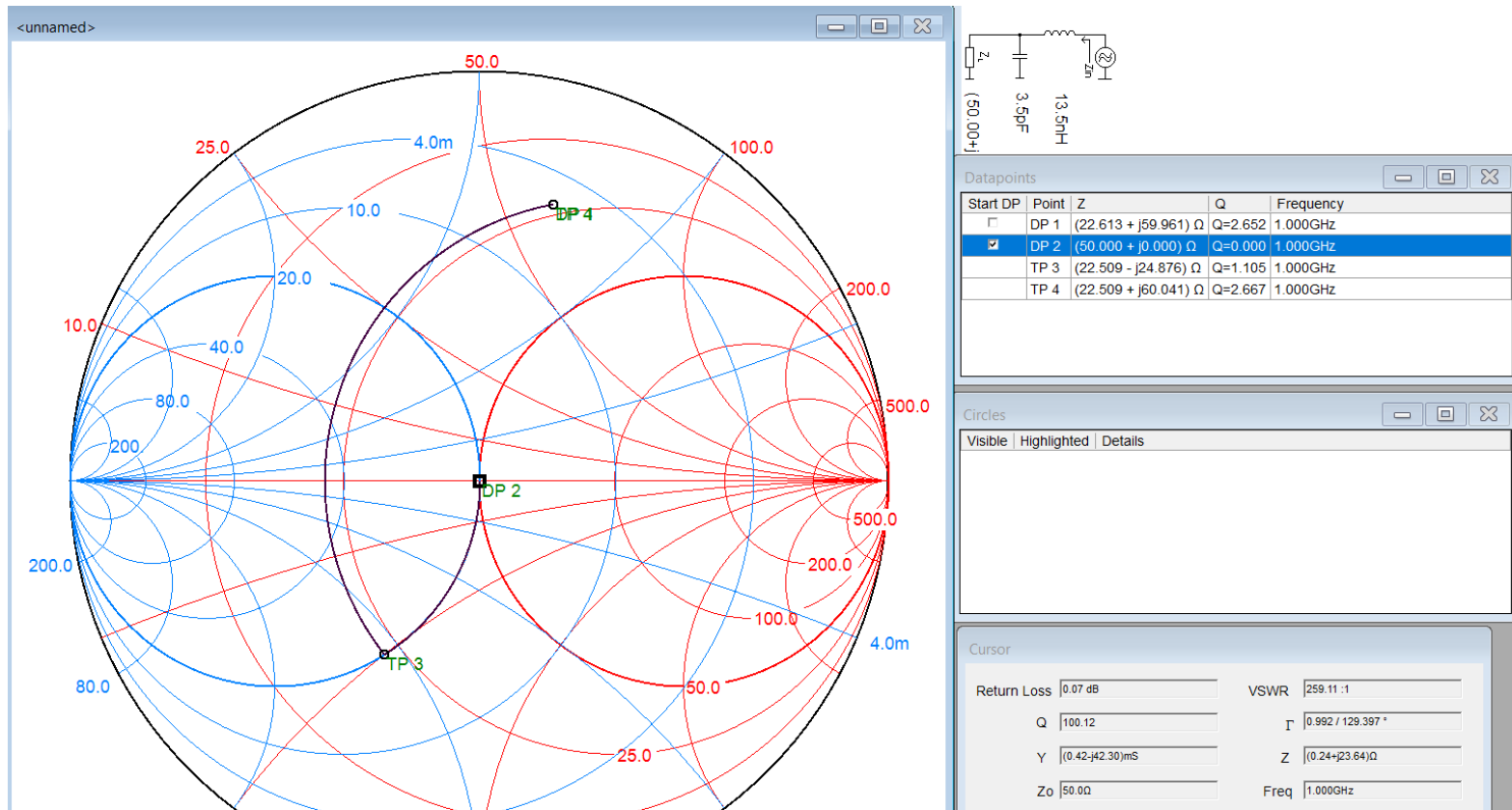
# Problem 1: Solution, matching at output


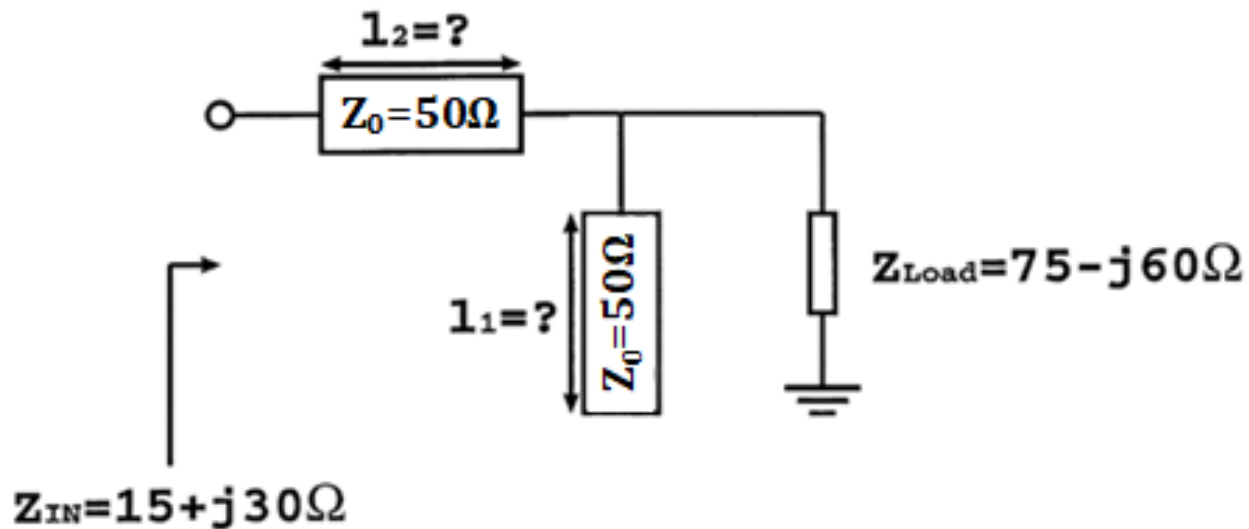
# Problem 2 - Matching using TL

Using the Smith chart, design a matching network with microstrip lines (open-circuited stub and series line) which transforms the load impedance  $Z_{\text{Load}}$  into the input impedance  $Z_{\text{IN}}$ . Choose shortest possible line length.





# Problem 2, Matching using TL - Solution

## Step 1

Shunt C with normalized admittance  $j(-0.35+0.95)=j0.6$


To realize normalized admittance of  $j0.6$  we need open TL of  $(0.25-0.165)\lambda=0.085\lambda$

$$l_1=0.085\lambda$$

## Step 2

We need series TL with length  $(0.09+0.12)\lambda=0.21\lambda$

$$l_2=0.21\lambda$$

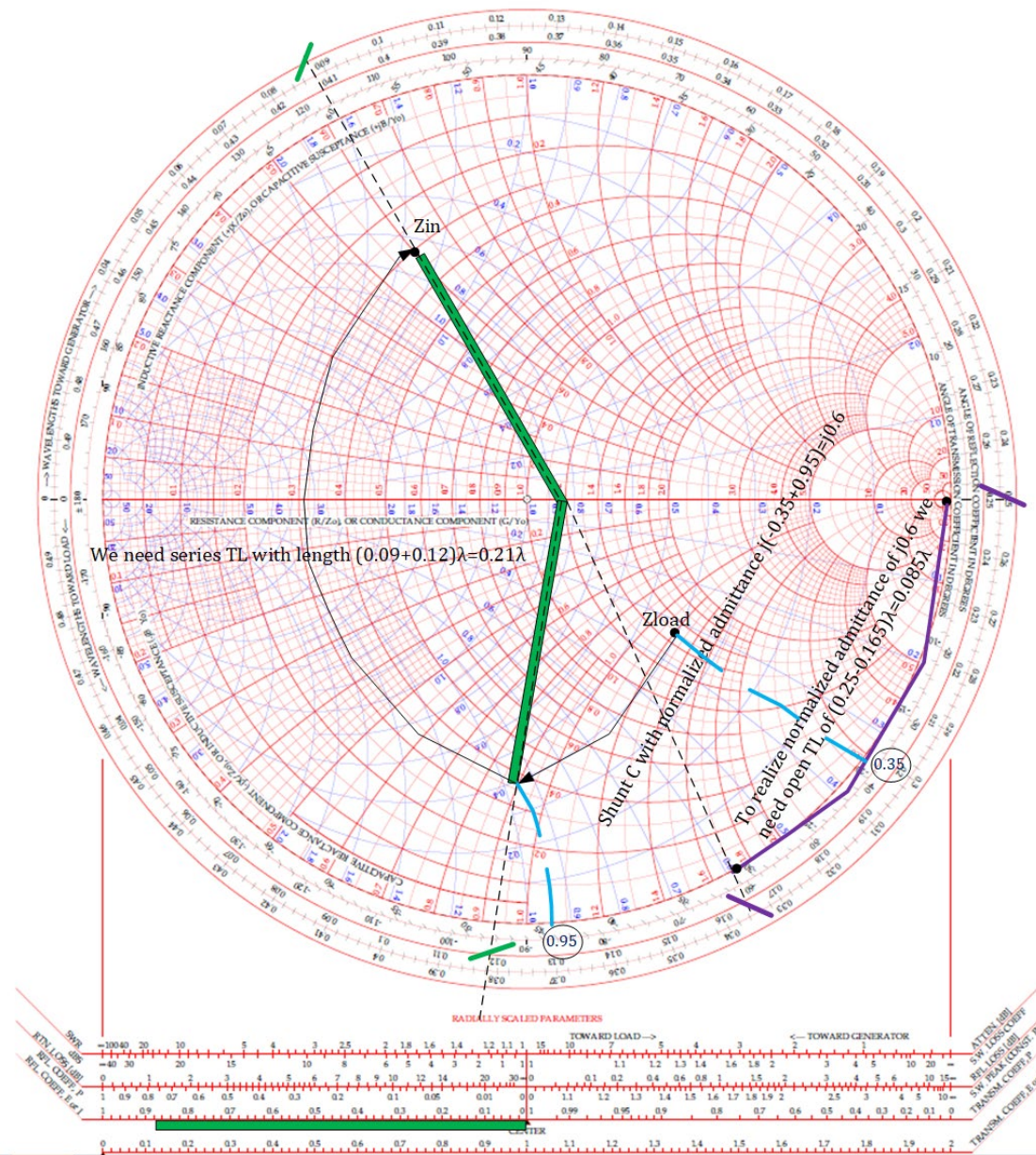

# Example 12.4 book of Pozar – solution (1/4)

Next, we use (11.59) and (11.61) to compute the center and radius of the 2 dB noise figure circle:

$$N = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{\text{opt}}|^2 = \frac{1.58 - 1.445}{4(20/50)} |1 + 0.62 \angle 100^\circ|^2$$

$$= 0.0986,$$

$$C_F = \frac{\Gamma_{\text{opt}}}{N + 1} = 0.56 \angle 100^\circ$$

$$R_F = \frac{\sqrt{N(N + 1 - |\Gamma_{\text{opt}}|^2)}}{N + 1} = 0.24.$$

This noise figure circle is plotted in Figure 11.15a. Minimum noise figure ( $F_{\min} = 1.6$  dB) occurs for  $\Gamma_S = \Gamma_{\text{opt}} = 0.62 \angle 100^\circ$ .

Next we calculate data for several input section constant gain circles. From (11.52),

$G_S(\text{dB})$	$g_S$	$C_S$	$R_S$
1.0	0.805	$0.52 \angle 60^\circ$	0.300
1.5	0.904	$0.56 \angle 60^\circ$	0.205
1.7	0.946	$0.58 \angle 60^\circ$	0.150


These circles are also plotted in Figure 11.15a. We see that the  $G_S = 1.7$  dB gain circle just intersects the  $F = 2$  dB noise figure circle, and that any higher gain will result in a worse noise figure. From the Smith chart the optimum solution is then  $\Gamma_S = 0.53 \angle 75^\circ$ , yielding  $G_S = 1.7$  dB and  $F = 2.0$  dB.

For the output section we choose  $\Gamma_L = S_{22}^* = 0.5 \angle 60^\circ$  for a maximum  $G_L$  of

$$G_L = \frac{1}{1 - |S_{22}|^2} = 1.33 \approx 1.25 \text{ dB}.$$

The transistor gain is

$$G_0 = |S_{21}|^2 = 3.61 = 5.58 \text{ dB},$$

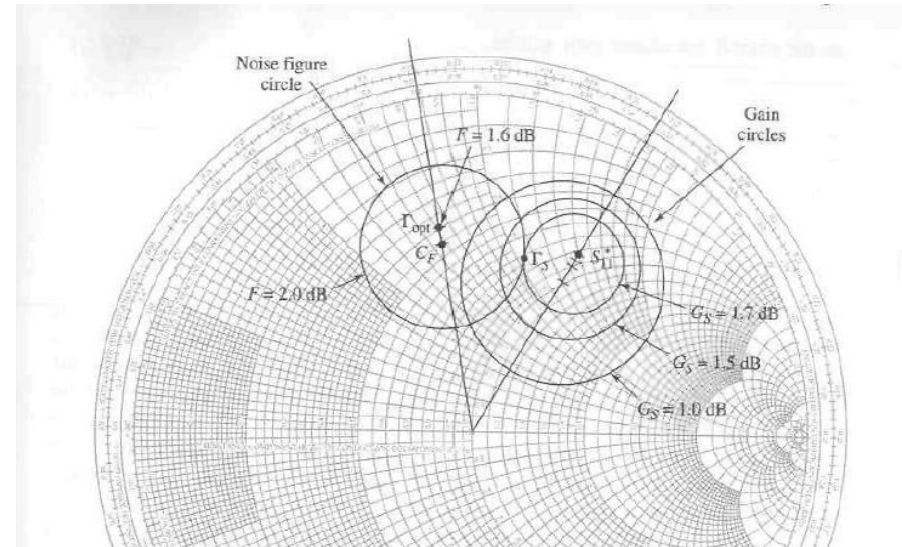


$$G_T = G_S + G_0 + G_L [\text{dB}] = 8.5 \text{ dB}$$




# Example 12.4 book of Pozar – solution (2/4)

## Input matching network

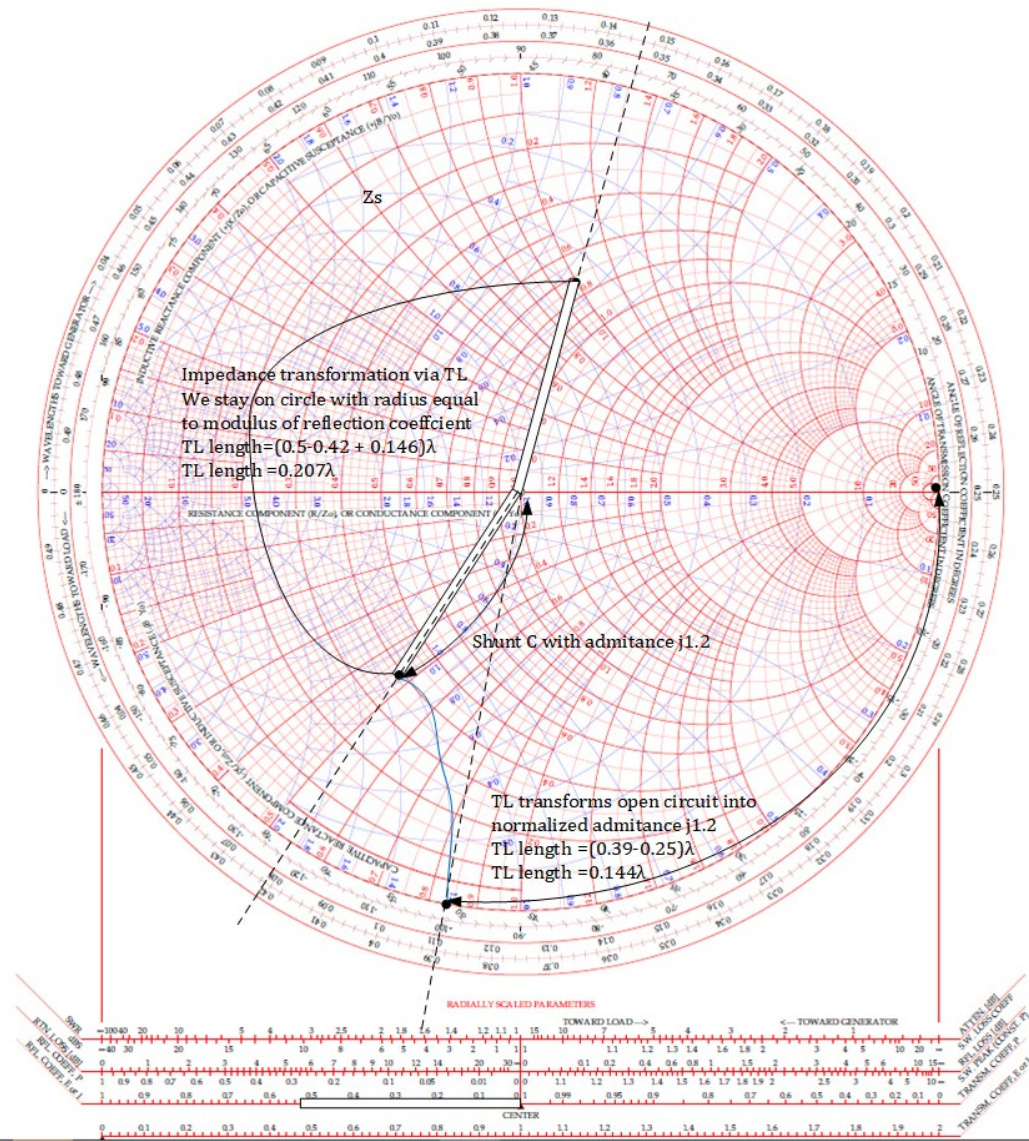


# Example 12.4 book of Pozar – solution (3/4)

## Output matching network

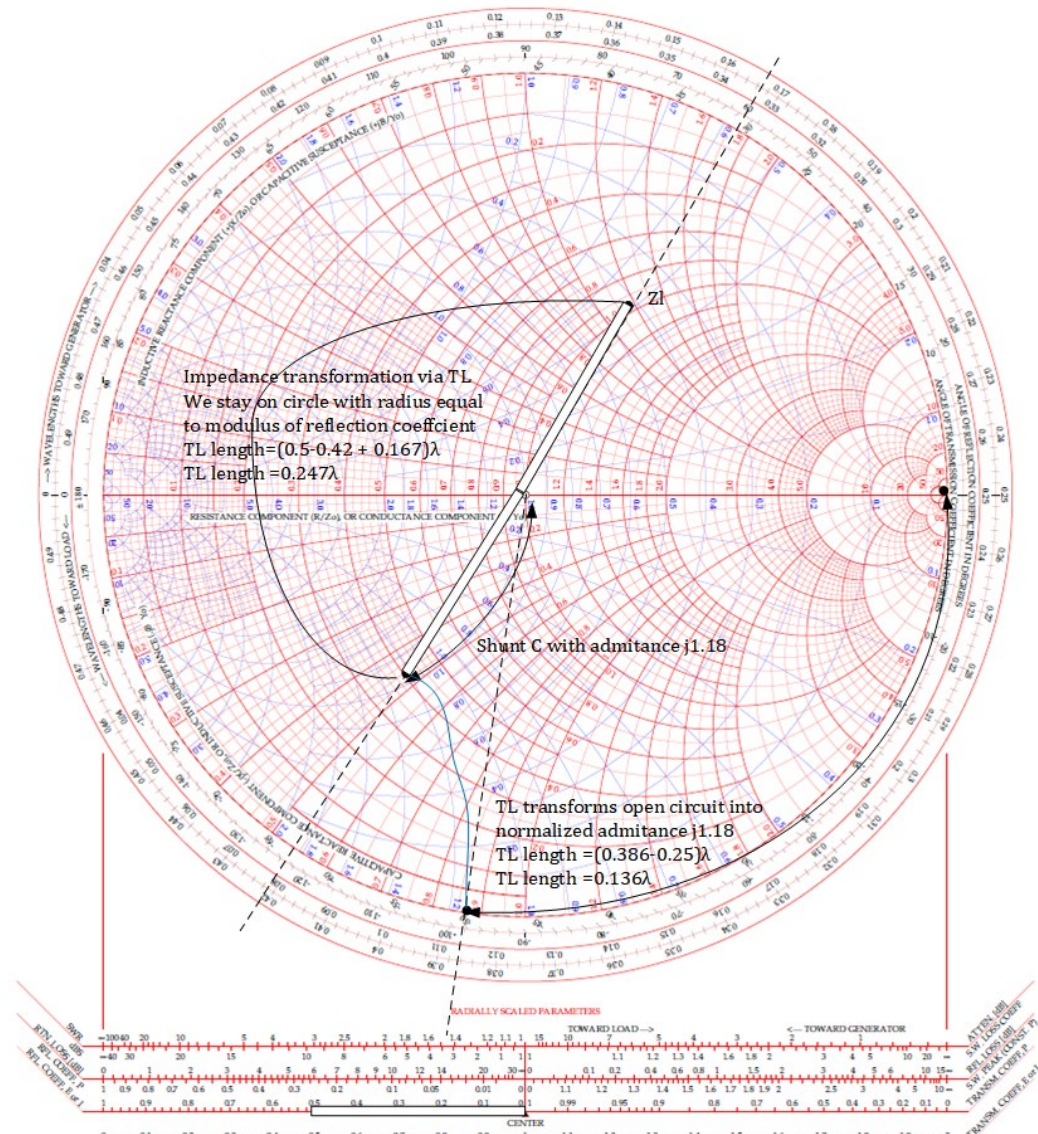

# Example 12.4 book of Pozar – solution (4/4)

## Amplifier schematic

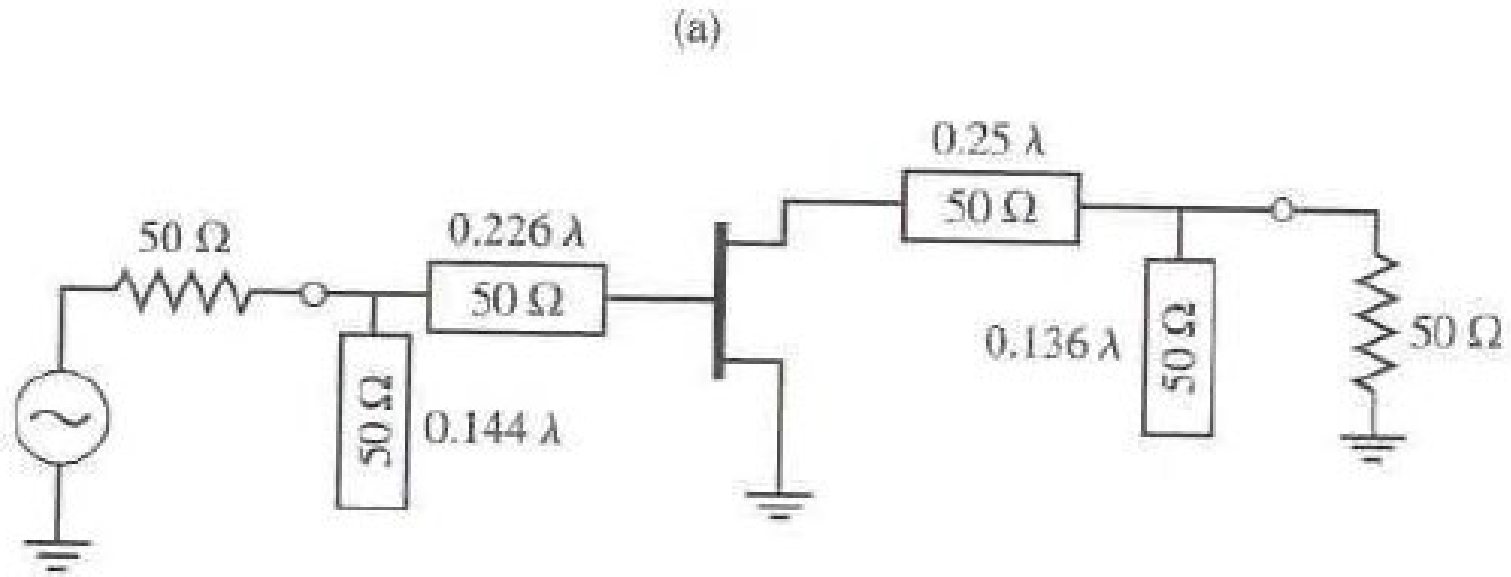

# Amplifier design – matching using TL

## Example 12.3 book of Pozar

### EXAMPLE 11.3 Conjugately Matched Amplifier Design

Design an amplifier for maximum gain at 4.0 GHz using single-stub matching sections. ~~Calculate and plot the input return loss and the gain from 3 to 5 GHz.~~ The GaAs FET has the following  $S$  parameters ( $Z_0 = 50 \Omega$ ):

$f$ (GHz)	$S_{11}$	$S_{21}$	$S_{12}$	$S_{22}$
3.0	$0.80 \angle -89^\circ$	$2.86 \angle 99^\circ$	$0.03 \angle 56^\circ$	$0.76 \angle -41^\circ$
4.0	$0.72 \angle -116^\circ$	$2.60 \angle 76^\circ$	$0.03 \angle 57^\circ$	$0.73 \angle -54^\circ$
5.0	$0.66 \angle -142^\circ$	$2.39 \angle 54^\circ$	$0.03 \angle 62^\circ$	$0.72 \angle -68^\circ$



# Amplifier design - matching using TL

## Example 12.3 book of Pozar – Solution (1/4)

Example 11.3, book of Pozar, page 620

Maximum transducer power gain → Review

$$G_T = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_S \Gamma_{in}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

$$G_{T_{max}} \quad \Gamma_{in} = \Gamma_S^* \\ \Gamma_{out} = \Gamma_L^*$$

$$\Gamma_S^* = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1} \quad \text{page 620} \\ \text{© Pozar}$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^*$$

$$C_2 = S_{22} - \Delta S_{11}^*$$

$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

We first check the stability of the transistor by calculating  $\Delta$  and  $K$  at 4.0 GHz:

$$\Delta = S_{11} S_{22} - S_{12} S_{21} = 0.488 \angle -162^\circ,$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12} S_{21}|} = 1.195.$$

### 11.3 Single-Stage Transistor Amplifier Design

Since  $|\Delta| < 1$  and  $K > 1$ , the transistor is unconditionally stable at 4.0 GHz. There is no need to plot the stability circles.

For maximum gain, we should design the matching sections for a conjugate match to the transistor. Thus,  $\Gamma_S = \Gamma_{in}^*$  and  $\Gamma_L = \Gamma_{out}^*$ , and  $\Gamma_S$ ,  $\Gamma_L$  can be determined from (11.43):

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1} = 0.872 \angle 123^\circ$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2} = 0.876 \angle 61^\circ,$$

Then the effective gain factors of (11.19) can be calculated as

$$G_S = \frac{1}{1 - |\Gamma_S|^2} = 4.17 = 6.20 \text{ dB},$$

$$G_0 = |S_{21}|^2 = 6.76 = 8.30 \text{ dB},$$



$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} = 1.67 = 2.22 \text{ dB}.$$

So the overall transducer gain will be

$$G_{T_{max}} = 6.20 + 8.30 + 2.22 = 16.7 \text{ dB}.$$

# Amplifier design - matching using TL
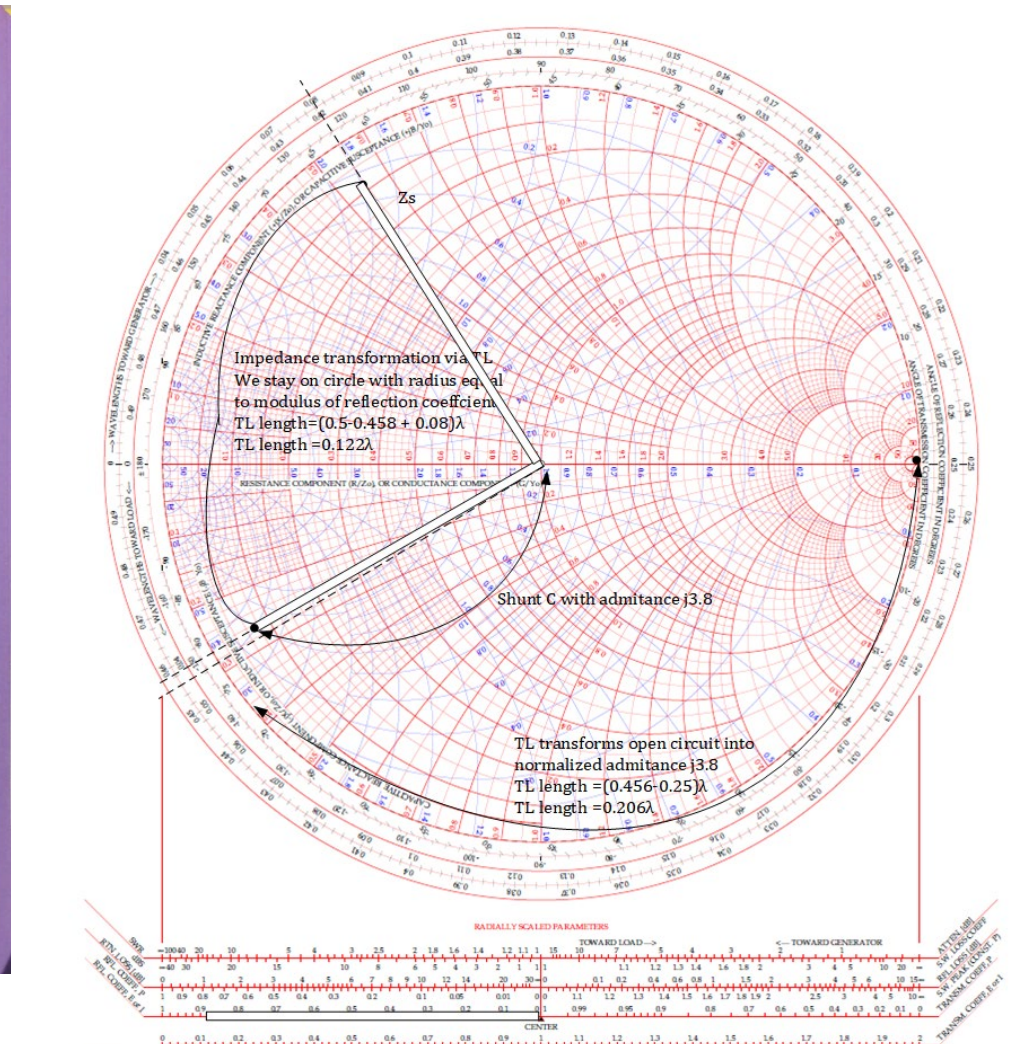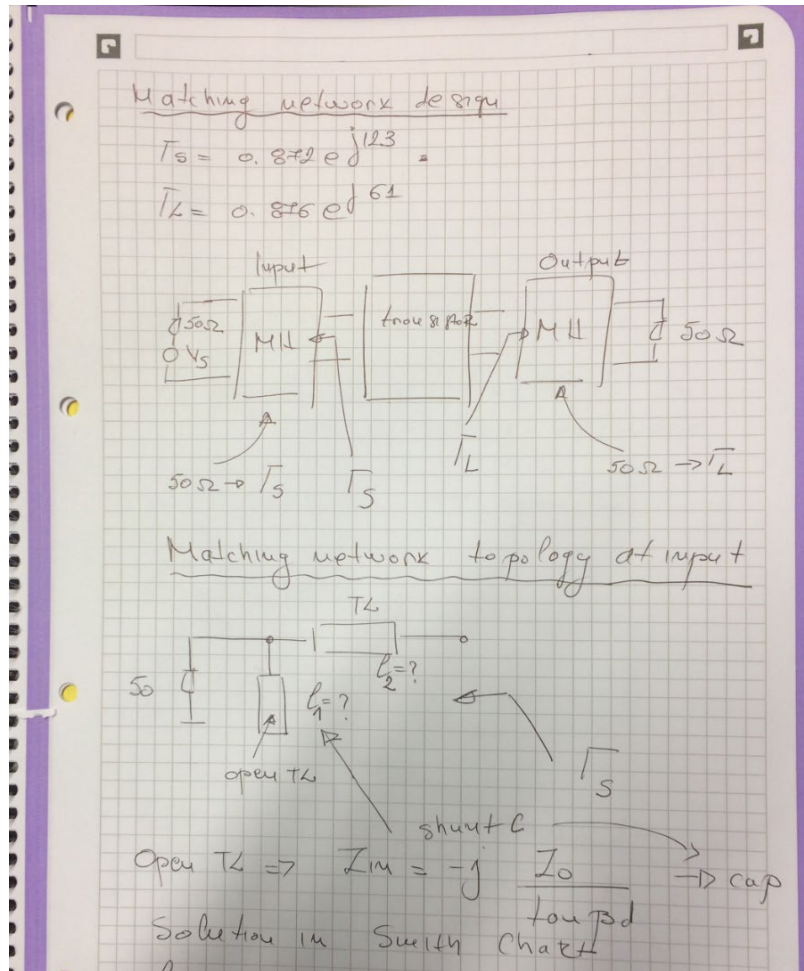
## Example 12.3 book of Pozar – Solution (2/4)






# Amplifier design - matching using TL

## Example 12.3 book of Pozar – Solution (3/4)

Matching network topology at output

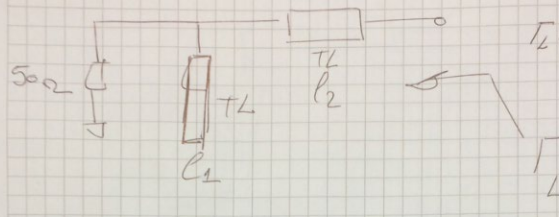


$Z_L = 0.8 + j0.61$

$l_1 \rightarrow$  the same length as in input matching network

$l_1 = 0.108 \lambda \rightarrow$  open TL


$l_2 = 0.207 \lambda$

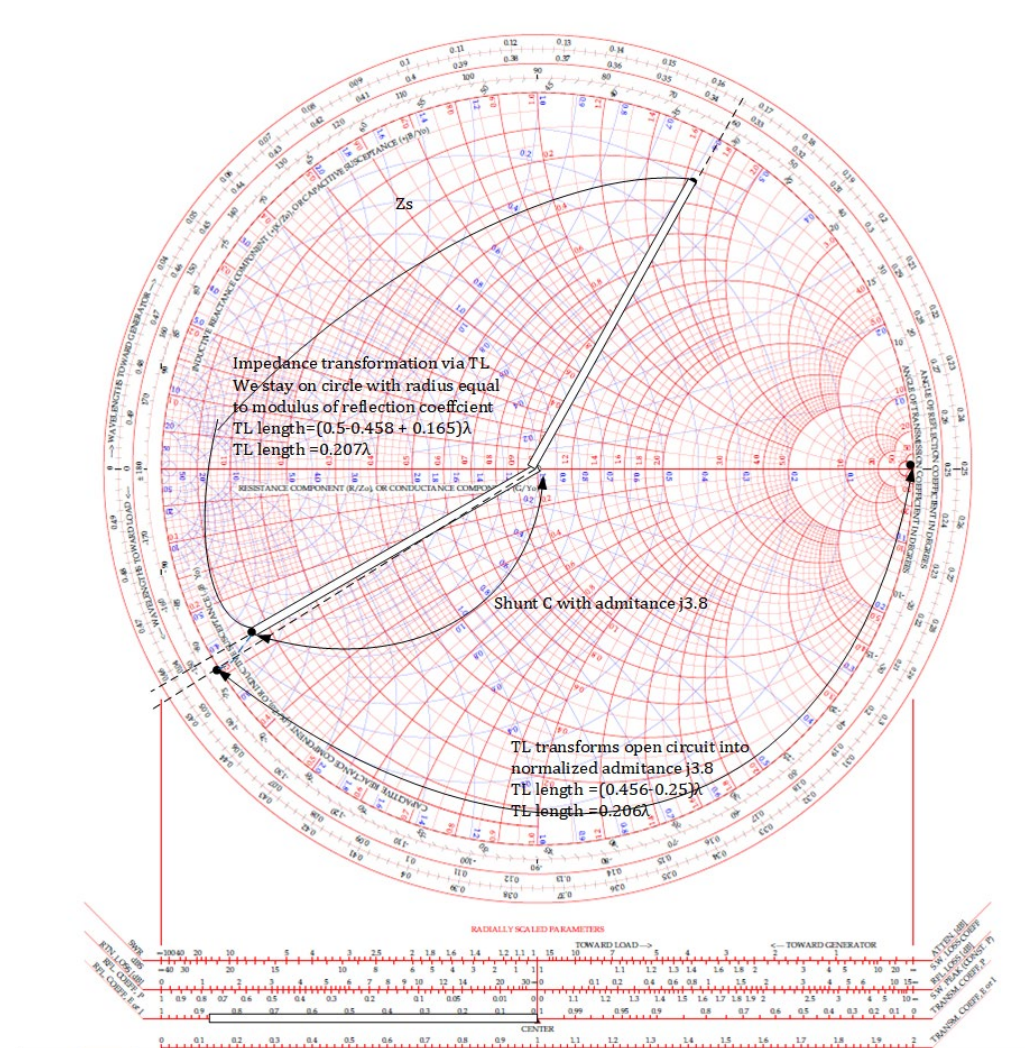$Z_{in, \text{open TL}} = -j \frac{Z_0}{\tan \beta l}$



# Amplifier design
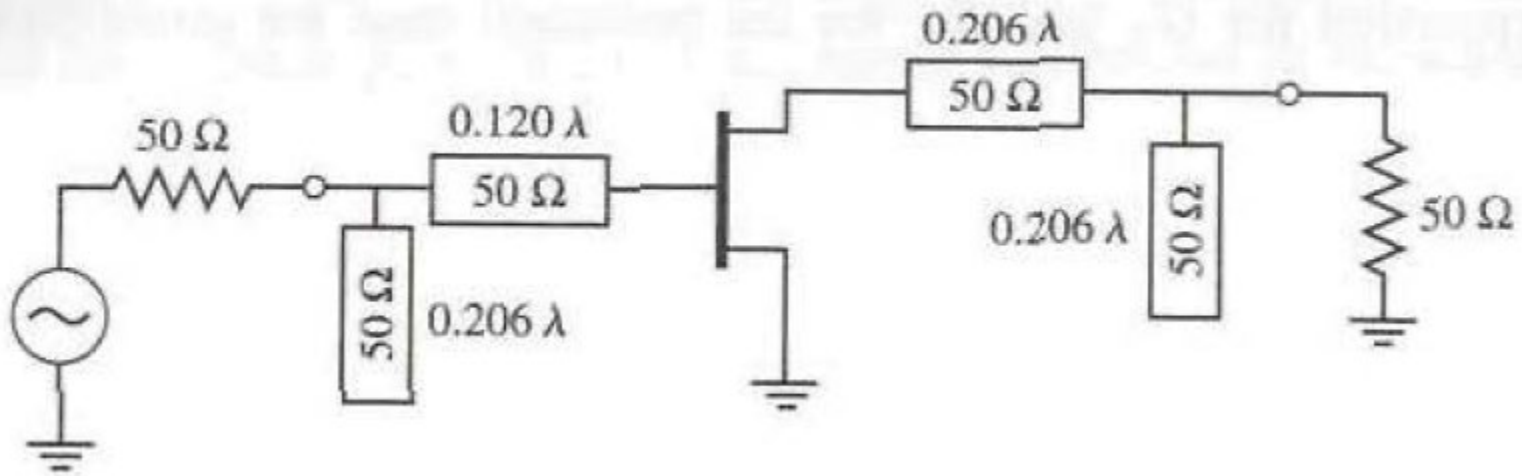
## Example 12.3 book of Pozar – Solution (4/4)



## Example 11.5 book of Pozar

A GaAs FET is biased for minimum noise figure, and has the following  $S$  parameters and noise parameters at 4 GHz ( $Z_0 = 50\ \Omega$ ):  $S_{11} = 0.6\angle -60^\circ$ ,  $S_{21} = 1.9\angle 81^\circ$ ,  $S_{12} = 0.05\angle 26^\circ$ ,  $S_{22} = 0.5\angle -60^\circ$ ;  $F_{\min} = 1.6\text{ dB}$ ,  $\Gamma_{\text{opt}} = 0.62\angle 100^\circ$ ,  $R_N = 20\ \Omega$ . For design purposes, assume the device is unilateral, and calculate the maximum error in  $G_T$  resulting from this assumption. Then design an amplifier having a 2.0 dB noise figure with the maximum gain that is compatible with this noise figure.

## Example 11.4 book of Pozar

Design an amplifier to have a gain of 11 dB at 4.0 GHz. Plot constant gain circles for  $G_S = 2$  dB and 3 dB, and  $G_L = 0$  dB and 1 dB. Calculate and plot the input return loss and overall amplifier gain from 3 to 5 GHz. The FET has the following  $S$  parameters ( $Z_0 = 50 \Omega$ ):

$f$ (GHz)	$S_{11}$	$S_{21}$	$S_{12}$	$S_{22}$
3	$0.80 \angle -90^\circ$	$2.8 \angle 100^\circ$	0	$0.66 \angle -50^\circ$
4	$0.75 \angle -120^\circ$	$2.5 \angle 80^\circ$	0	$0.60 \angle -70^\circ$
5	$0.71 \angle -140^\circ$	$2.3 \angle 60^\circ$	0	$0.58 \angle -85^\circ$



# Example 11.4 book of Pozar - Solution


Since  $S_{12} = 0$  and  $|S_{11}| < 1$  and  $|S_{22}| < 1$ , the transistor is unilateral and unconditionally stable. From (11.48) we calculate the maximum matching section gains as

$$G_{S_{\max}} = \frac{1}{1 - |S_{11}|^2} = 2.29 = 3.6 \text{ dB},$$

$$G_{L_{\max}} = \frac{1}{1 - |S_{22}|^2} = 1.56 = 1.9 \text{ dB}.$$

The gain of the mismatched transistor is

$$G_o = |S_{21}|^2 = 6.25 = 8.0 \text{ dB},$$

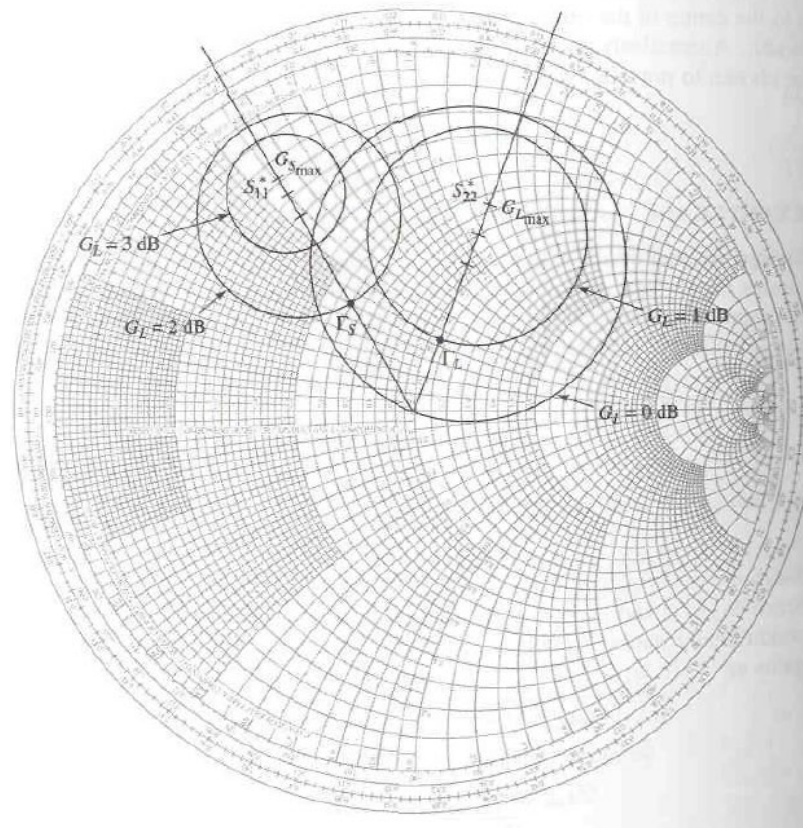

## Chapter 11: Design of Microwave Amplifiers and Oscillators

so the maximum unilateral transducer gain is

$$G_{TU_{\max}} = 3.6 + 1.9 + 8.0 = 13.5 \text{ dB}.$$

Thus we have 2.5 dB more gain than is required by the specifications.

We use (11.49), (11.52), and (11.53) to calculate the following data for the constant gain circles:

$G_S = 3 \text{ dB}$	$g_S = 0.875$	$C_S = 0.706 \angle 120^\circ$	$R_S = 0.166$
$G_S = 2 \text{ dB}$	$g_S = 0.691$	$C_S = 0.627 \angle 120^\circ$	$R_S = 0.294$
$G_L = 1 \text{ dB}$	$g_L = 0.806$	$C_L = 0.520 \angle 70^\circ$	$R_L = 0.303$
$G_L = 0 \text{ dB}$	$g_L = 0.640$	$C_L = 0.440 \angle 70^\circ$	$R_L = 0.440$

