

---

# 5XCC0 Biopotential and Neural Interface Circuits

Acquisition of neural signals


Eugenio Cantatore

---

# Outline


- Basic neurophysiology
- Example of a Neural Field Potential acquisition system
- Examples of Action Potentials acquisition systems

# Neuron structure

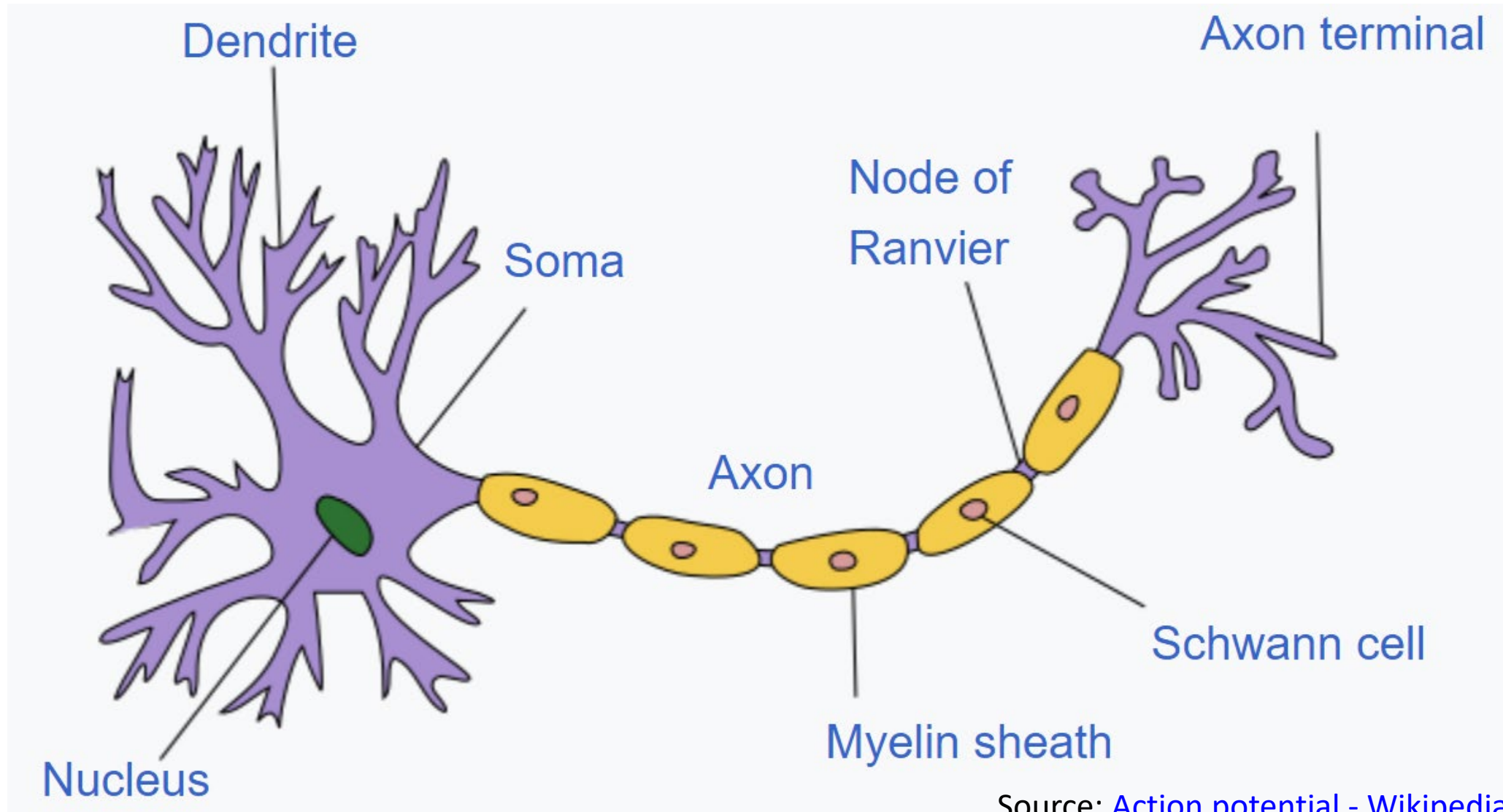

Source: [Action potential - Wikipedia](#)



# Synapses

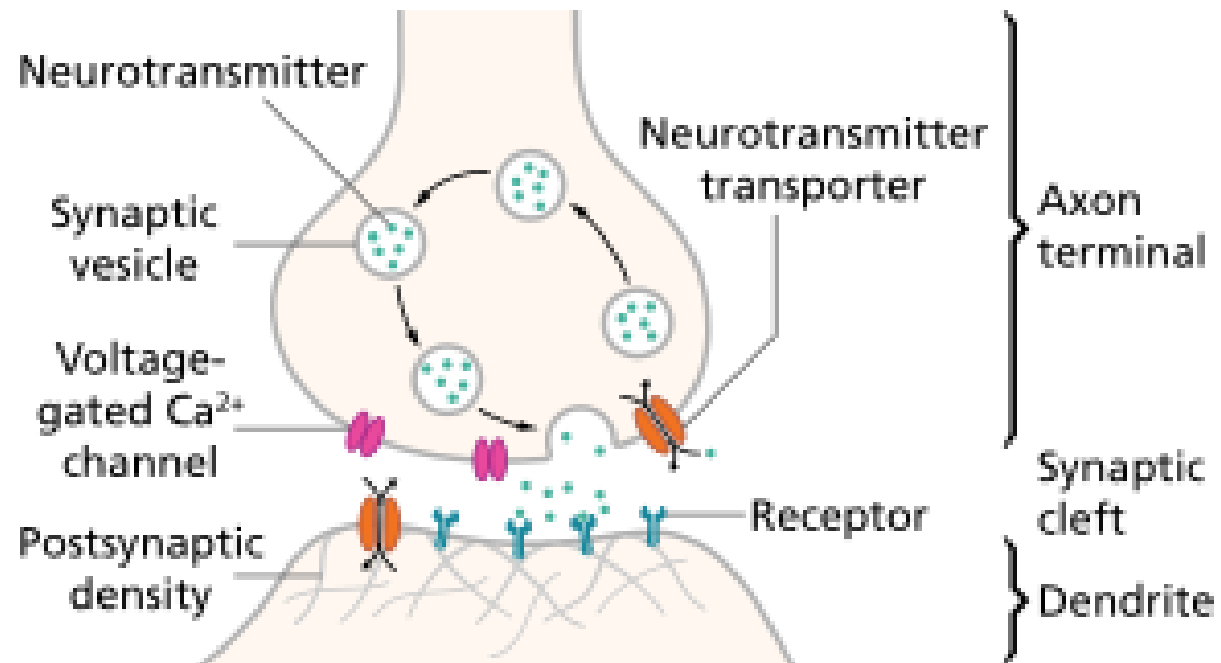

Source: [Action potential - Wikipedia](#)


# Action potential

Charges at rest state

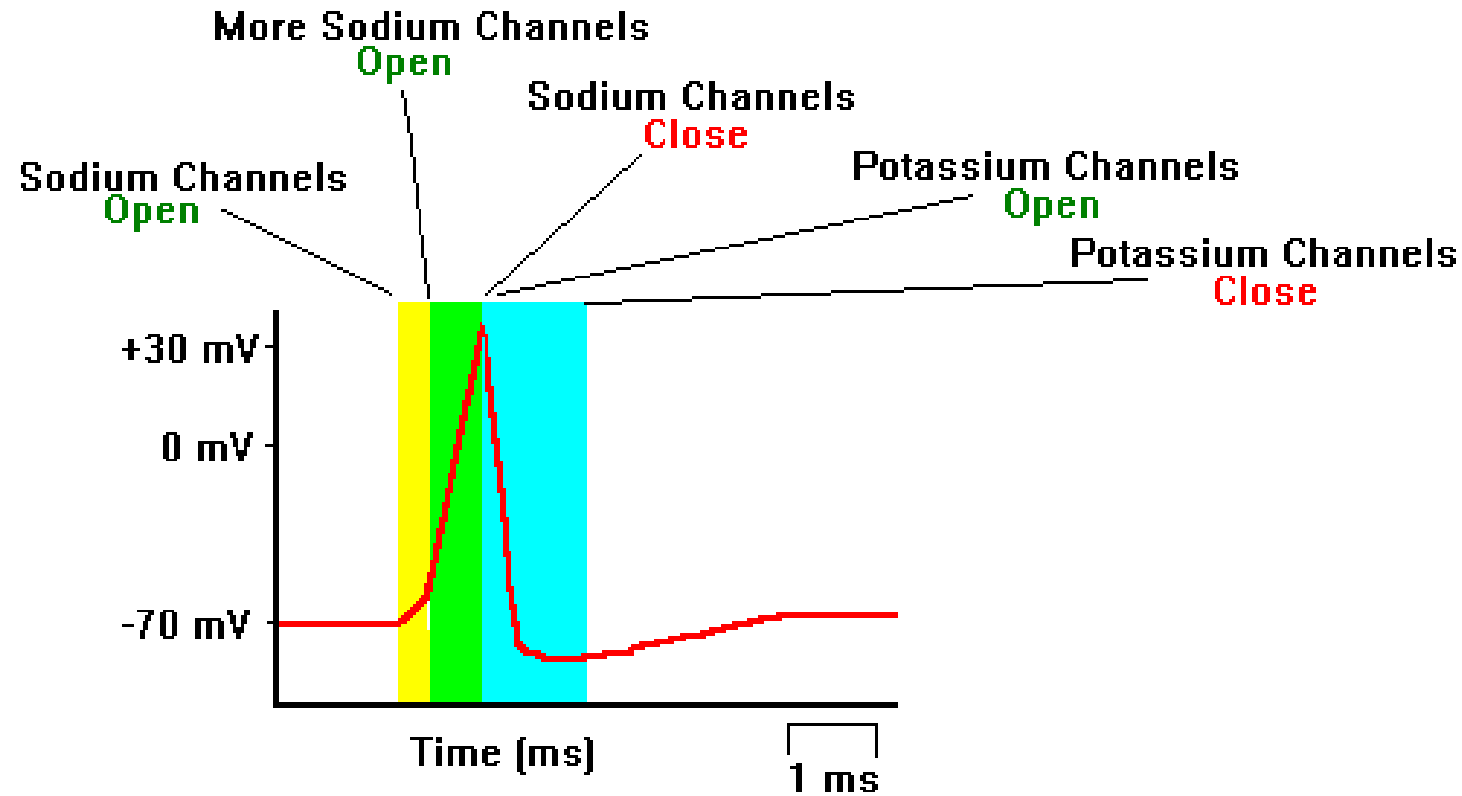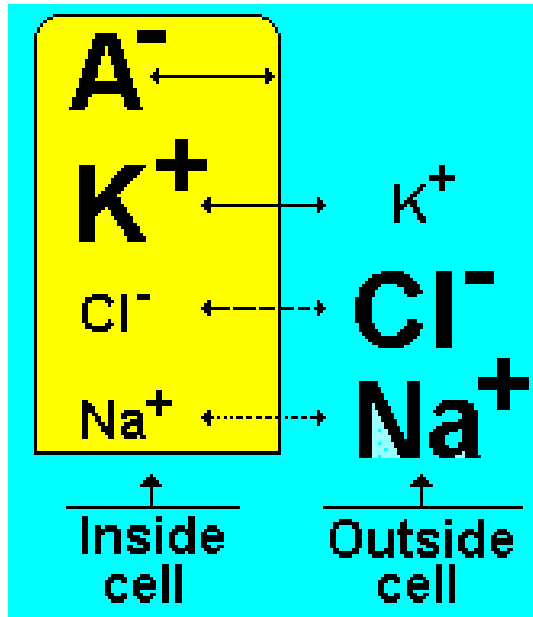


Source: [Neuroscience For Kids - action potential](#)
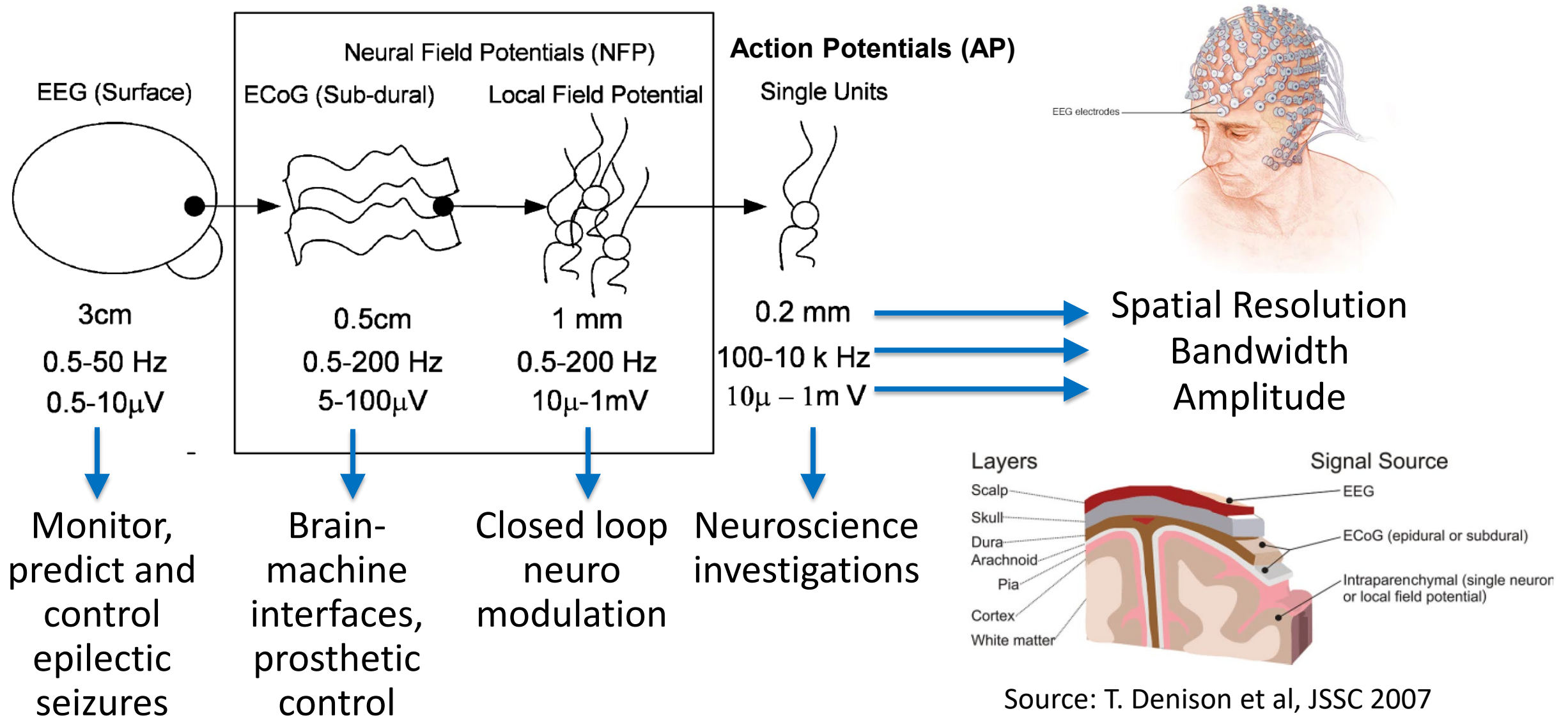
# Neural signals with application examples




# Deep Brain Stimulation

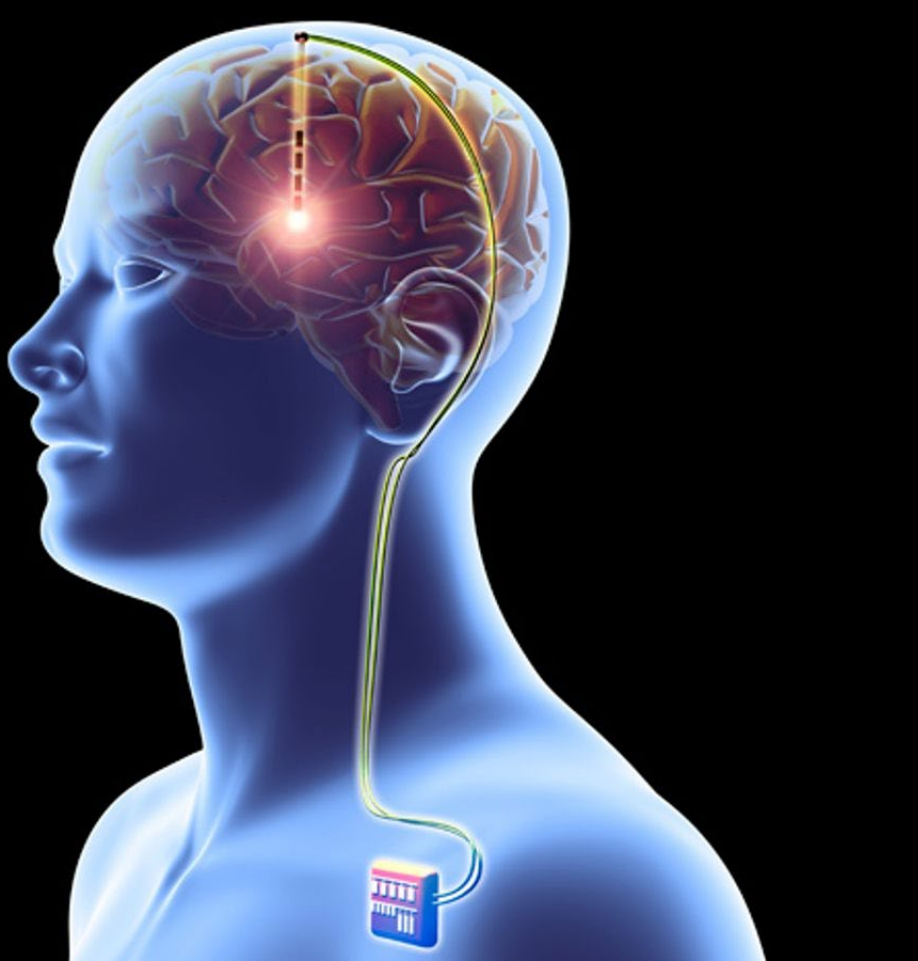

- Parkinson's disease
- Essential tremor
- Dystonia
- Epilepsy
- Obsessive-compulsive disorder
- [Amazing DBS Before & After | 225-769-2200 | Baton Rouge Parkinson's Specialists - YouTube](#)
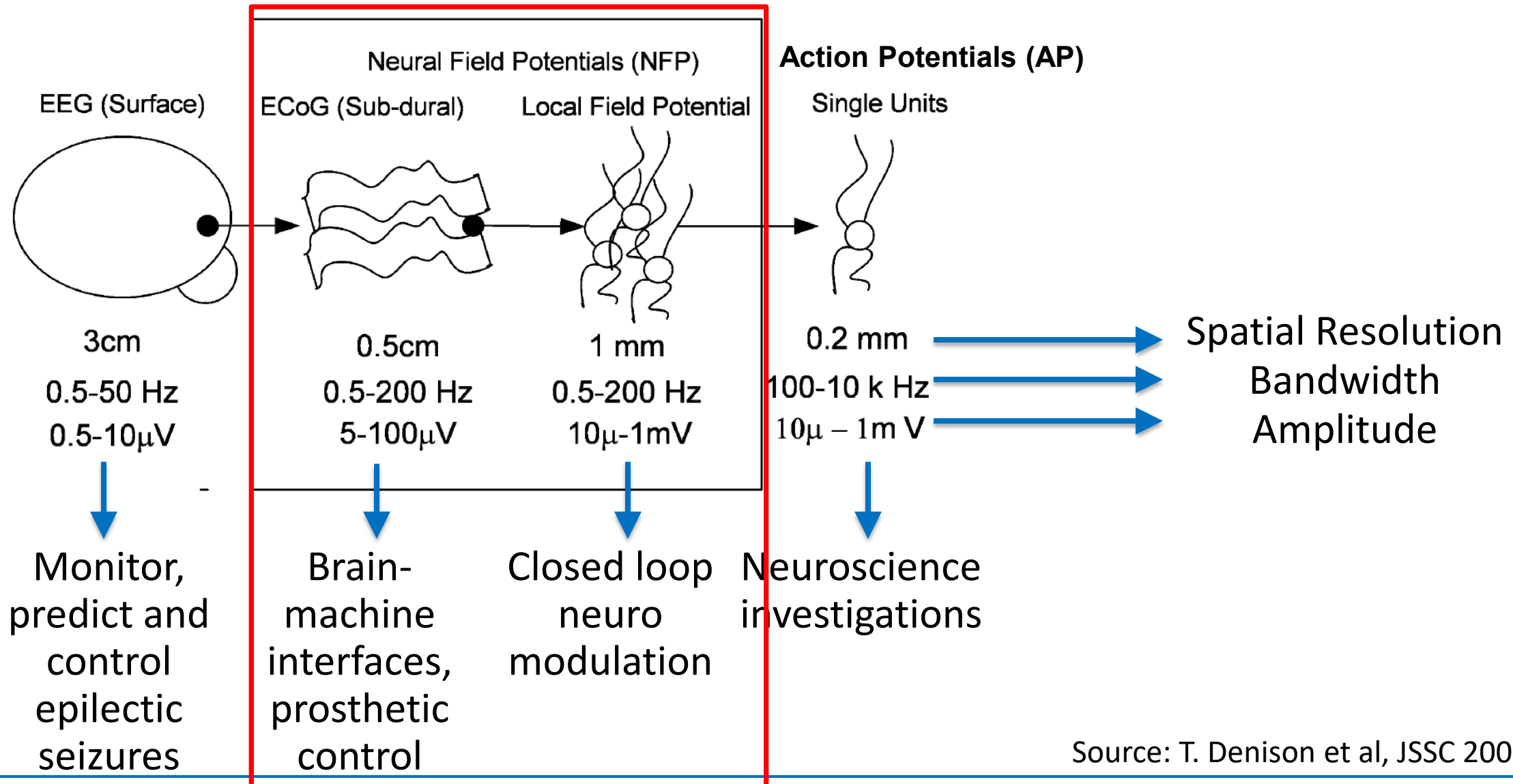
# Neural signals with application examples



Source: T. Denison et al, JSSC 2007



# Example of a NFP acquisition system

2934

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 42, NO. 12, DECEMBER 2007


## A $2\ \mu\text{W}$ 100 nV/rtHz Chopper-Stabilized Instrumentation Amplifier for Chronic Measurement of Neural Field Potentials

Tim Denison, Kelly Consoer, Wesley Santa, Al-Thaddeus Avestruz, John Cooley, and Andy Kelly, *Member, IEEE*

- Medtronic work, meant for future applications:
  - Neuro prosthesis
  - Closed-loop neuromodulation (Epilepsy, Parkinson's)

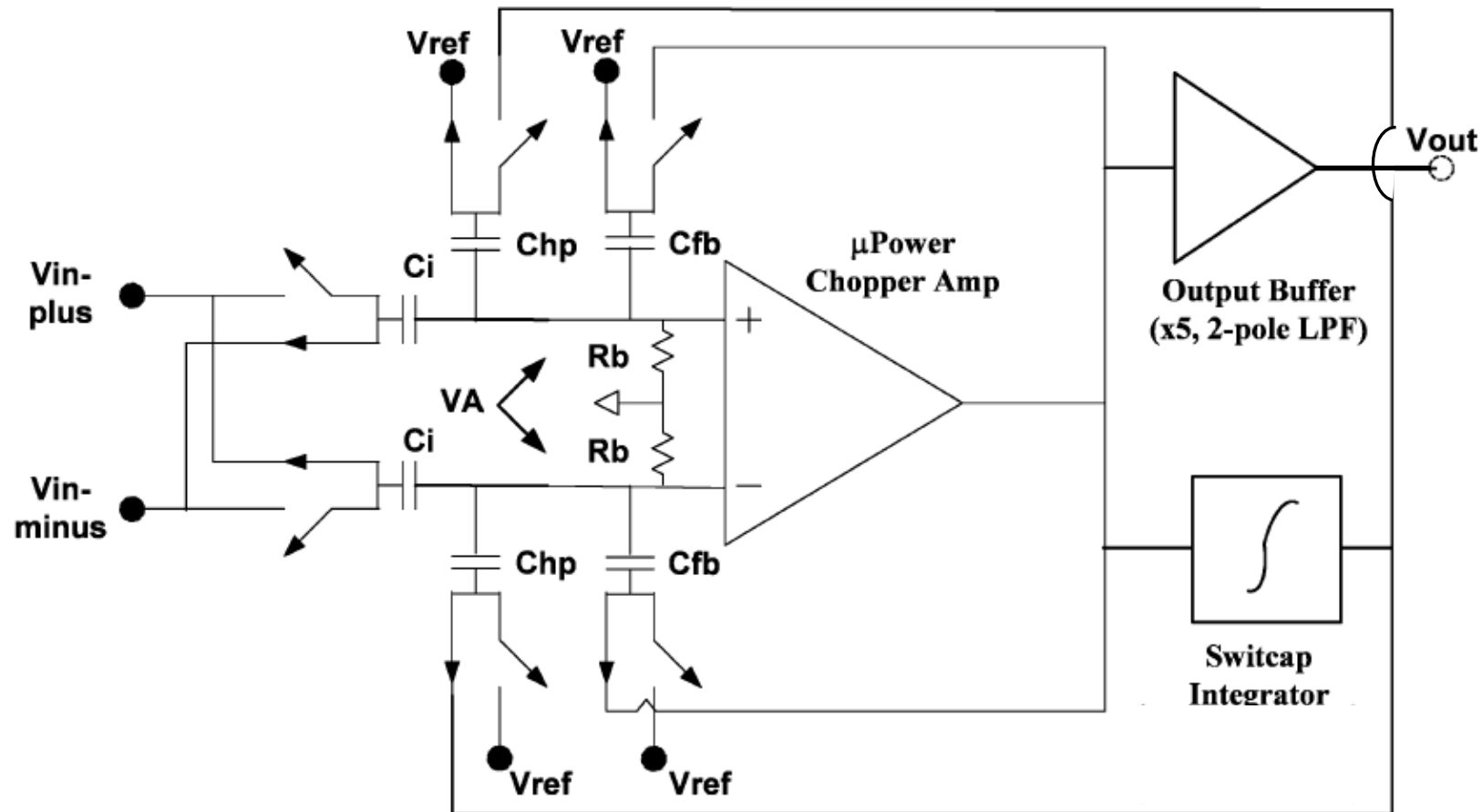
# Example of a NFP acquisition system

- Based on a capacitive-feedback amplifier


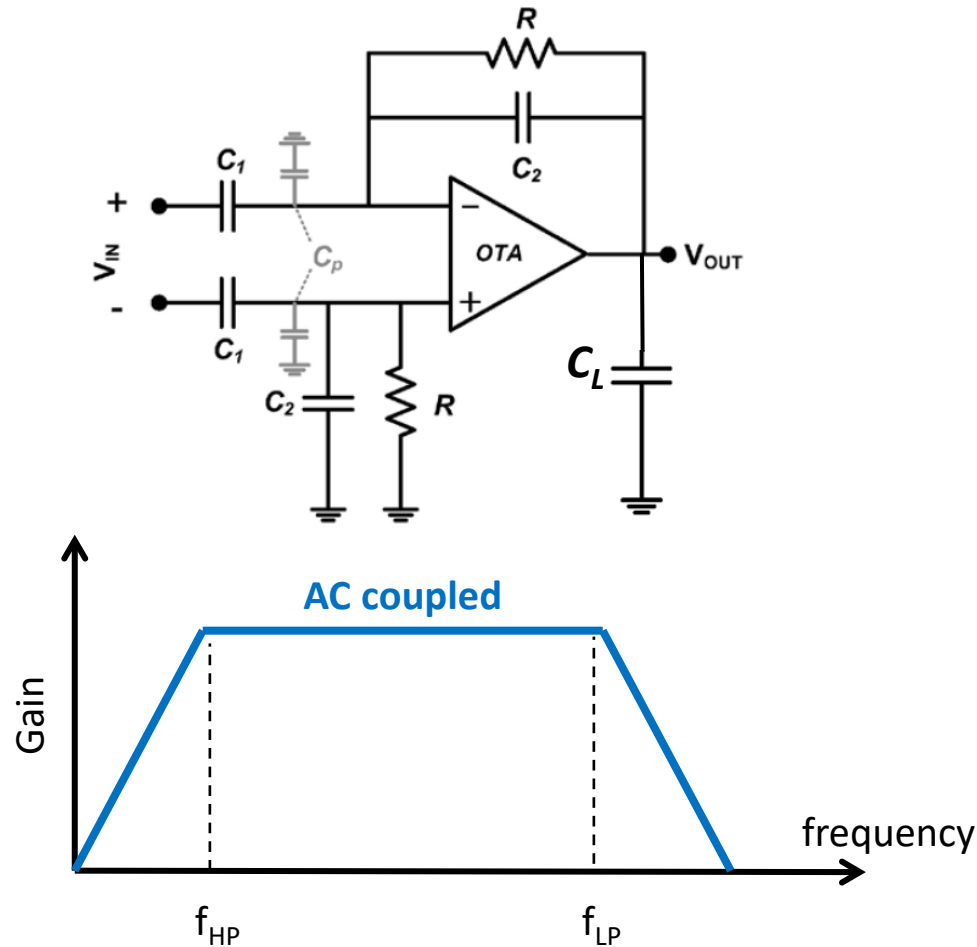
# Example of a NFP acquisition system

- Main properties of capacitive-feedback amplifier



$$A_0 = \frac{C_1}{C_2} \quad (\text{in band})$$

$$f_{HP} = \frac{1}{2\pi RC_2}$$

$$f_{LP} \approx \frac{g_m}{2\pi A_0 C_L}$$


$$v_{IRN}^2 = \left( \frac{C_1 + C_2 + C_p}{C_1} \right)^2 v_{OTA}^2$$

$$Z_{in} \approx \frac{1}{j\omega C_1}$$
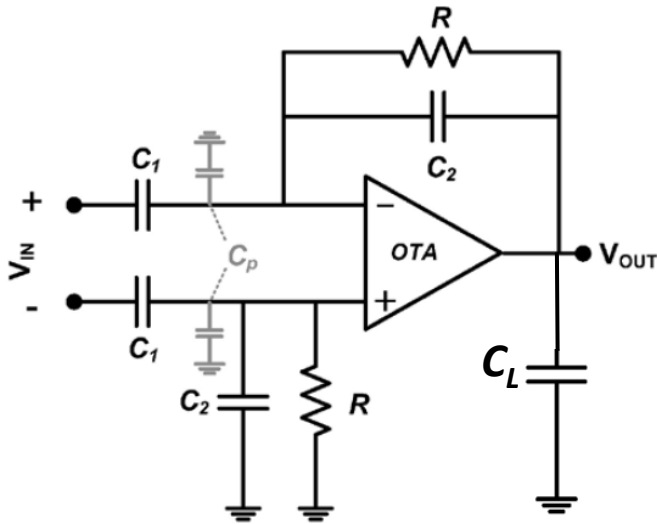
# Example of a NFP acquisition system

- Important trade-offs:


- To improve  $1/f$  noise, increase area of OTA input transistors
- This increases  $C_p$  and thus worsens  $V_{\text{IRN}}$



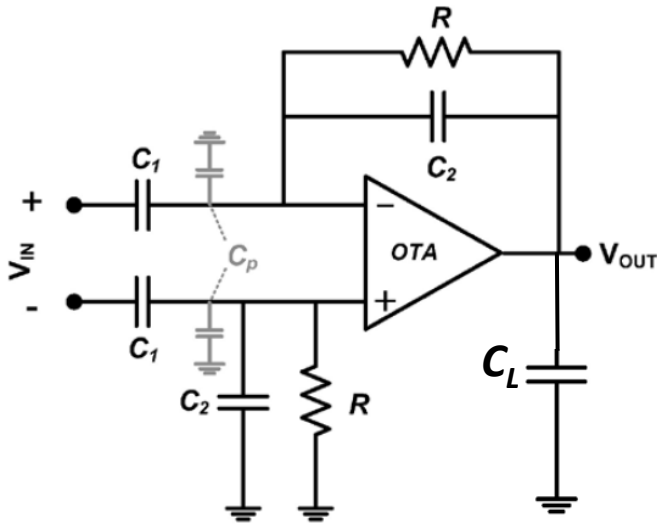
# Example of a NFP acquisition system

- Important trade-offs:

- To improve  $1/f$  noise, apply chopping
- Chopping increases the frequency of the signal applied to  $C_1$  and thus results in larger input current and lower input impedance




# Intermezzo: chopping in time domain

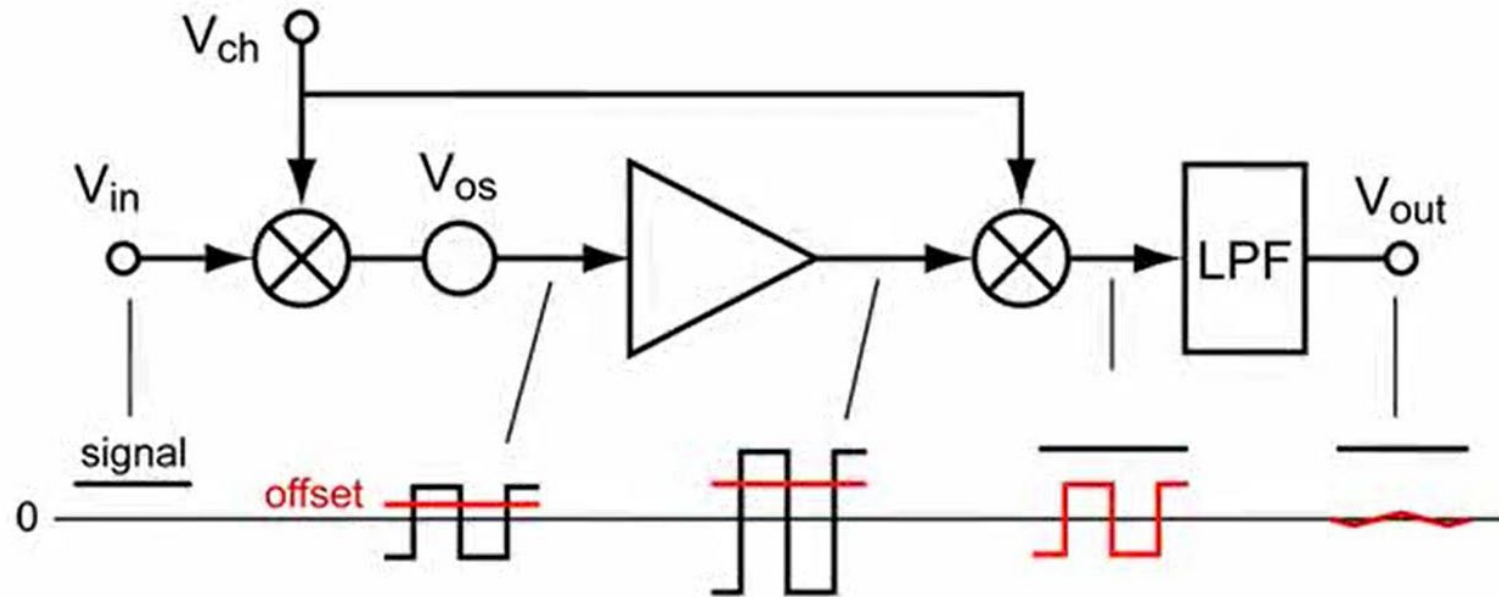

- Chopping duty cycle must be exactly 50% to avoid a DC component in the modulated offset at the output.

Source: [K. Makinwa, Dynamic-Offset Cancellation Techniques in CMOS](#)

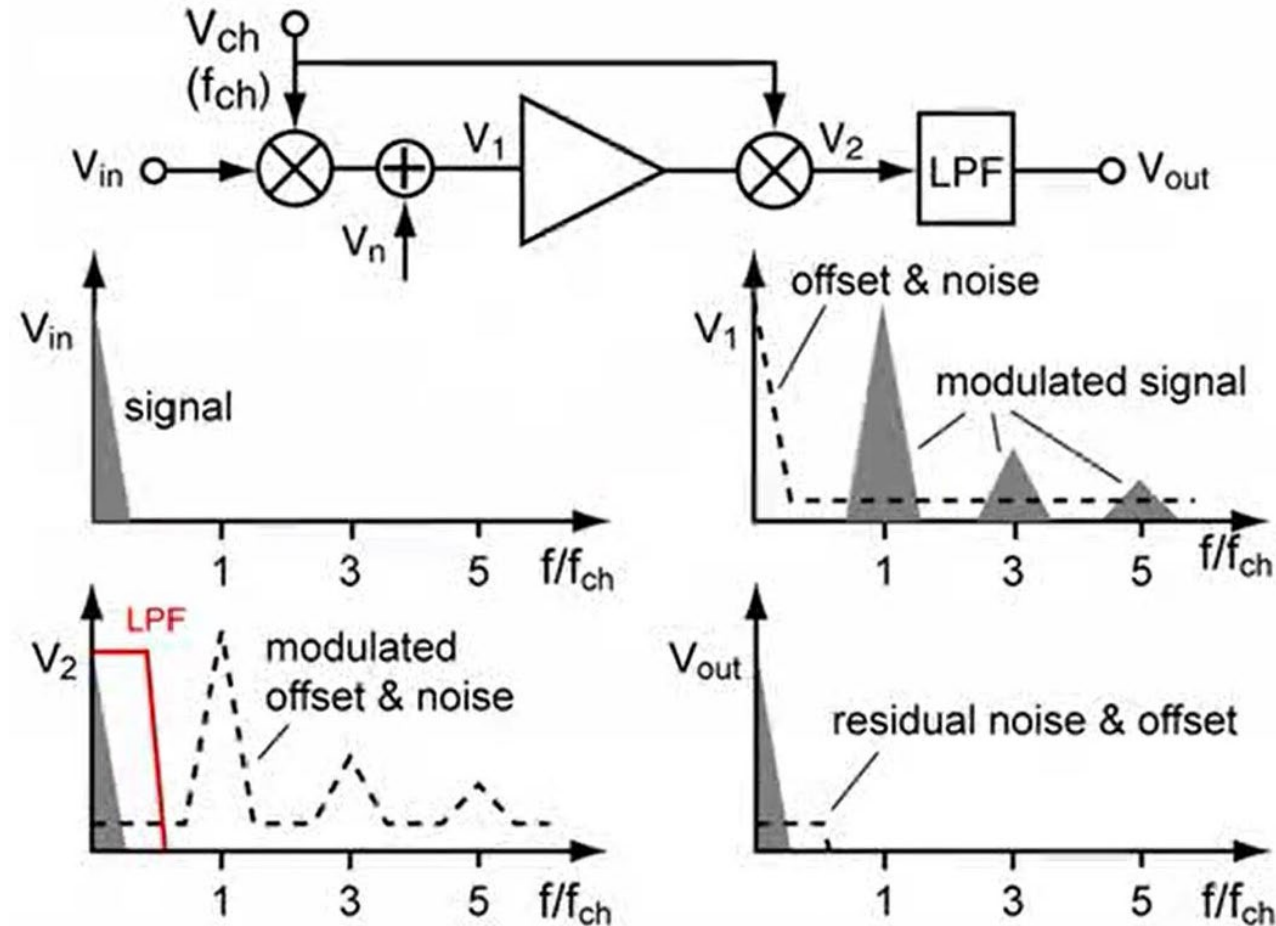
# Intermezzo: chopping in frequency domain



Source: [K. Makinwa, Dynamic-Offset Cancellation Techniques in CMOS](#)
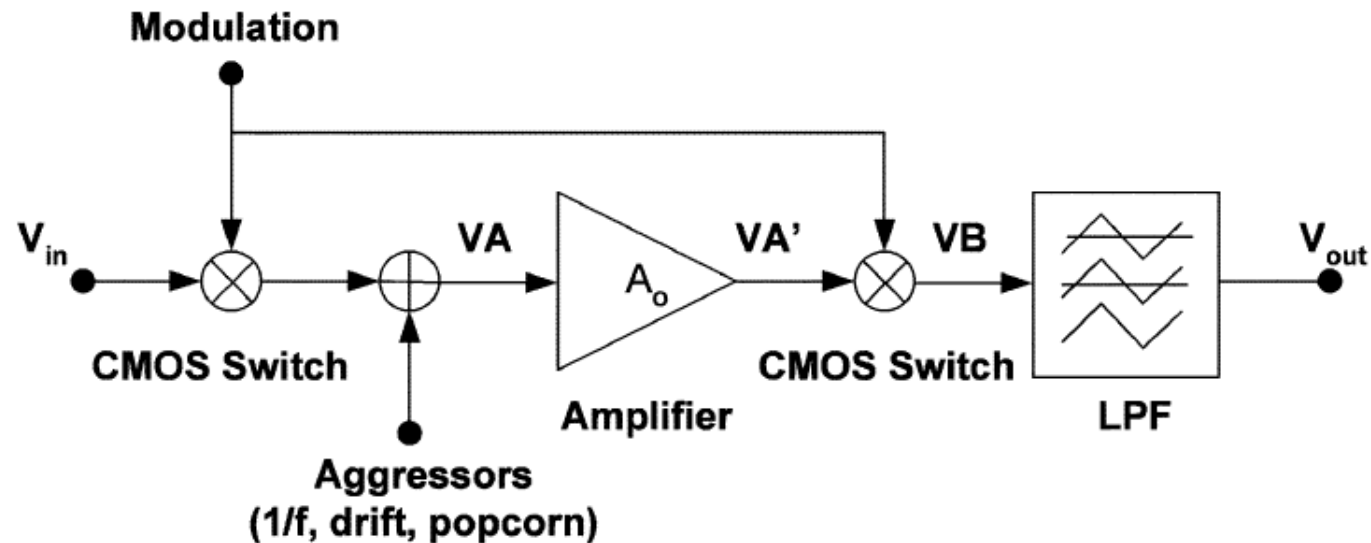
# Example of a NFP acquisition system


- Drawbacks of chopping:
  - The amplifier must have large bandwidth to cope with the chopped signal
  - Due to incomplete settling the gain when chopping is applied is not  $A_0$




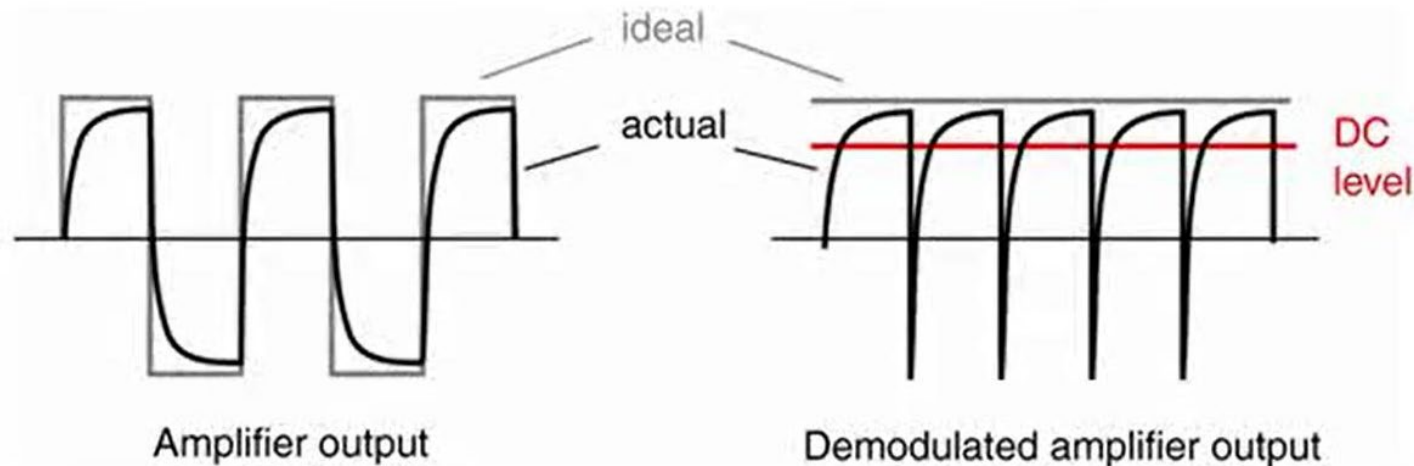
# Example of a NFP acquisition system

- Drawbacks of chopping:
  - The amplifier must have large bandwidth to cope with the chopped signal
  - Due to incomplete settling the gain when chopping is applied is not  $A_0$




Source: [K. Makinwa, Dynamic-Offset Cancellation Techniques in CMOS](#)

# Example of a NFP acquisition system

- To restore an accurate gain:

- Apply feedback

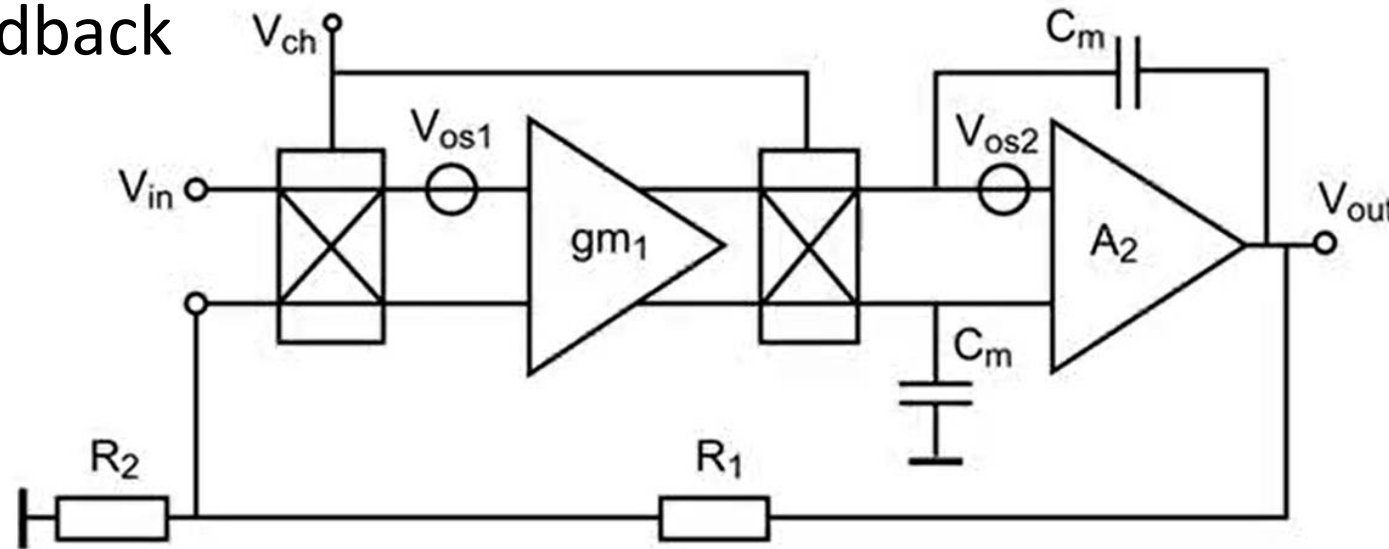


- Resistor ratio accurately determines the gain
- Miller capacitance help to suppress ripple
- DC gain of first stage must be large enough to suppress  $V_{os2}$  at input
- Higher chopping frequency reduces ripple

Source: [K. Makinwa, Dynamic-Offset Cancellation Techniques in CMOS](#)

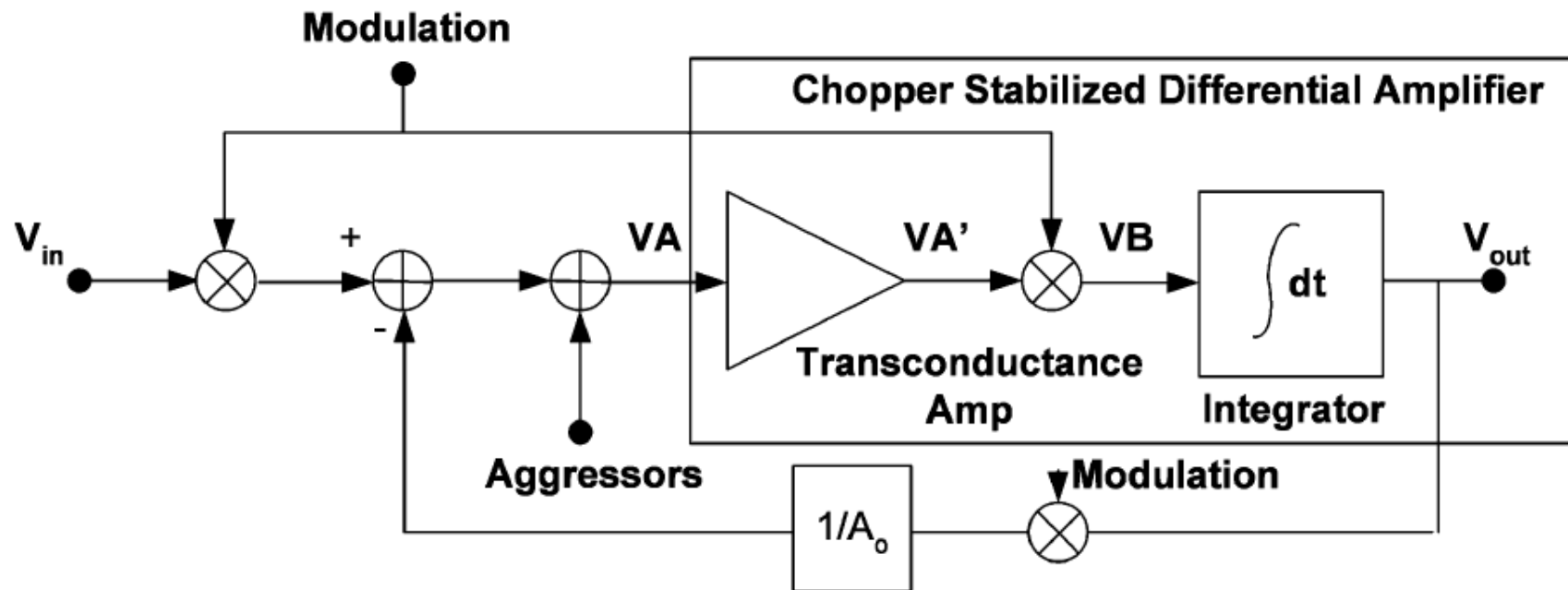
# Example of a NFP acquisition system

- To restore an accurate gain:
  - Apply feedback



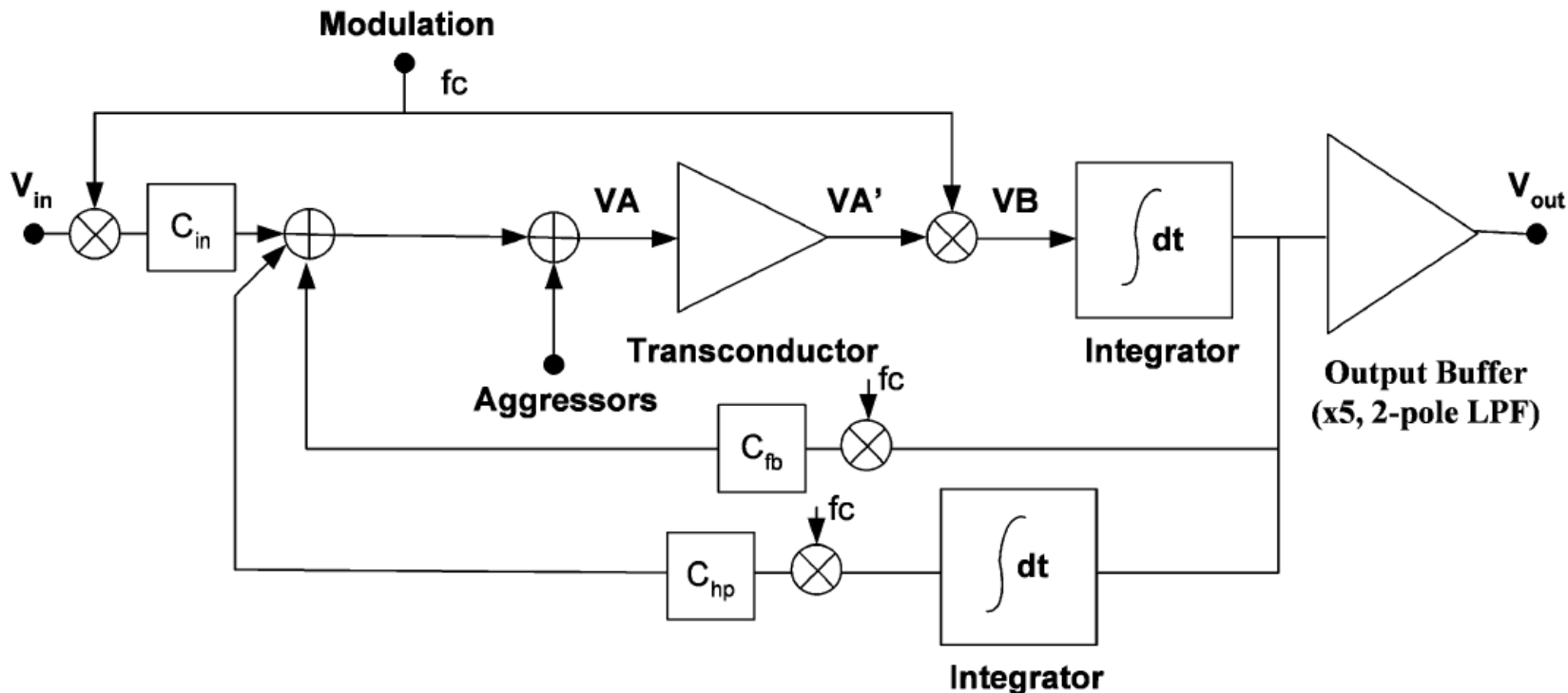
# Example of a NFP acquisition system

- Using an integrator in the feedback
  - Feedback in the chopped domain enables use of capacitors as passives
  - A high-pass behavior can be obtained




# Example of a NFP acquisition system

- Resulting schematic

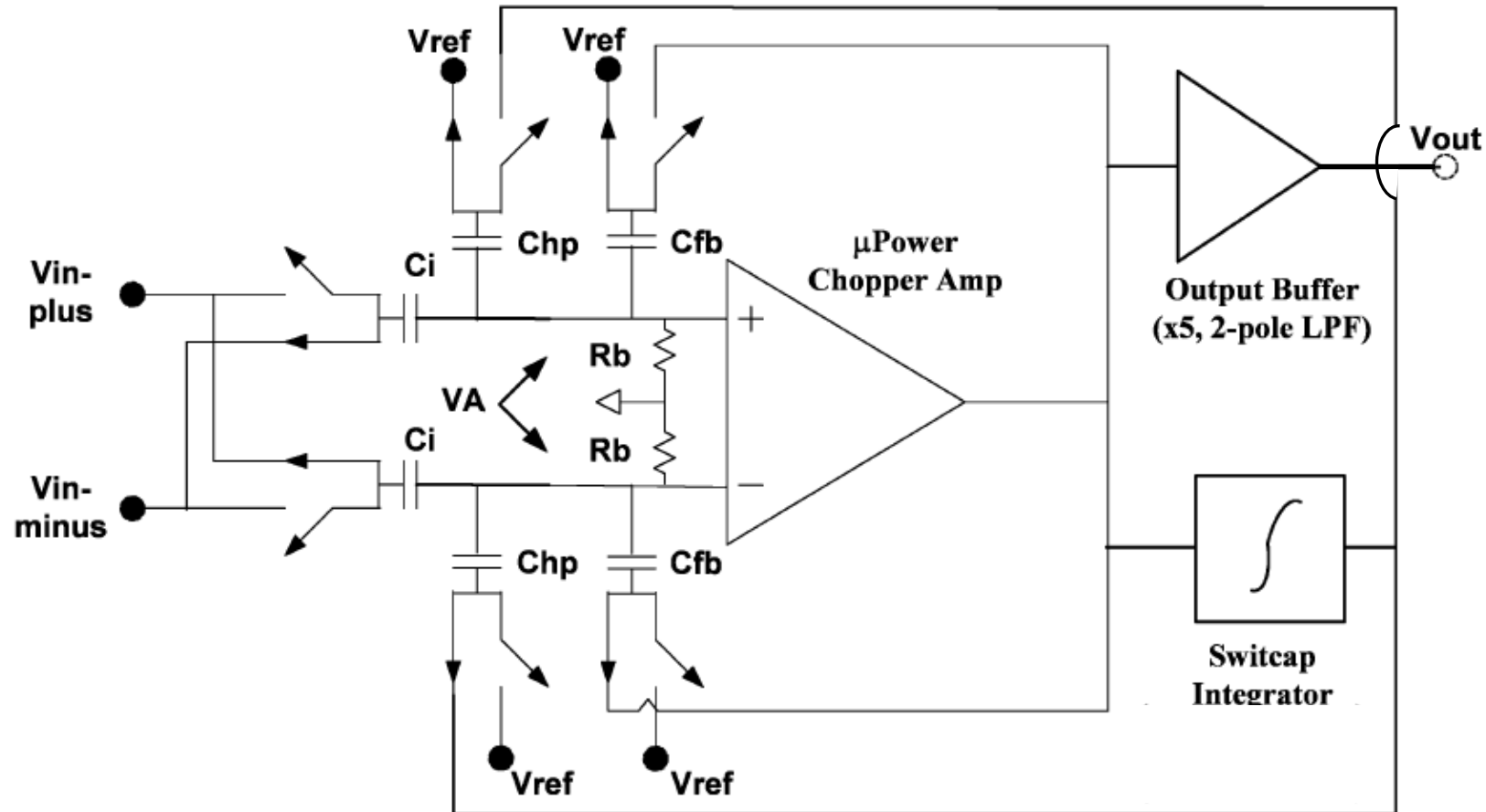

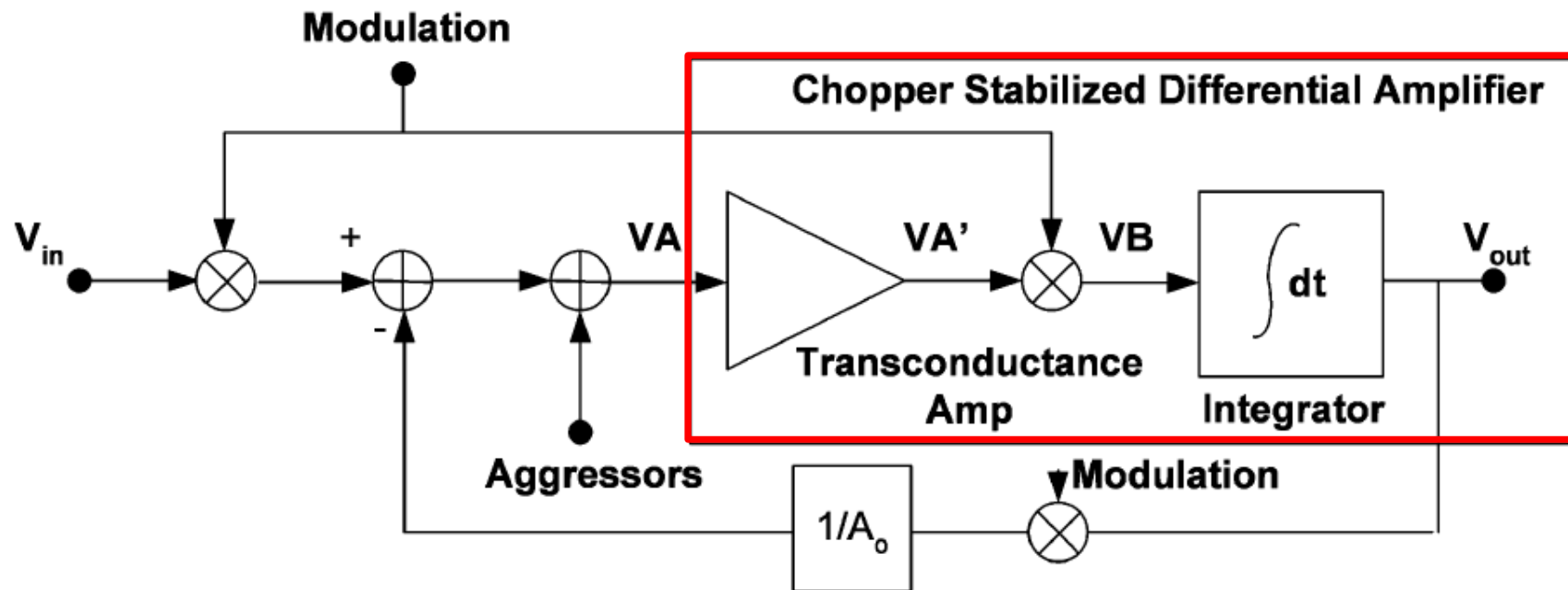
# Example of a NFP acquisition system

- To restore an accurate gain:
  - Apply feedback
  - Feedback in the chopped domain enables use of capacitors as passives





# Example of a NFP acquisition system

- Amplifier schematic

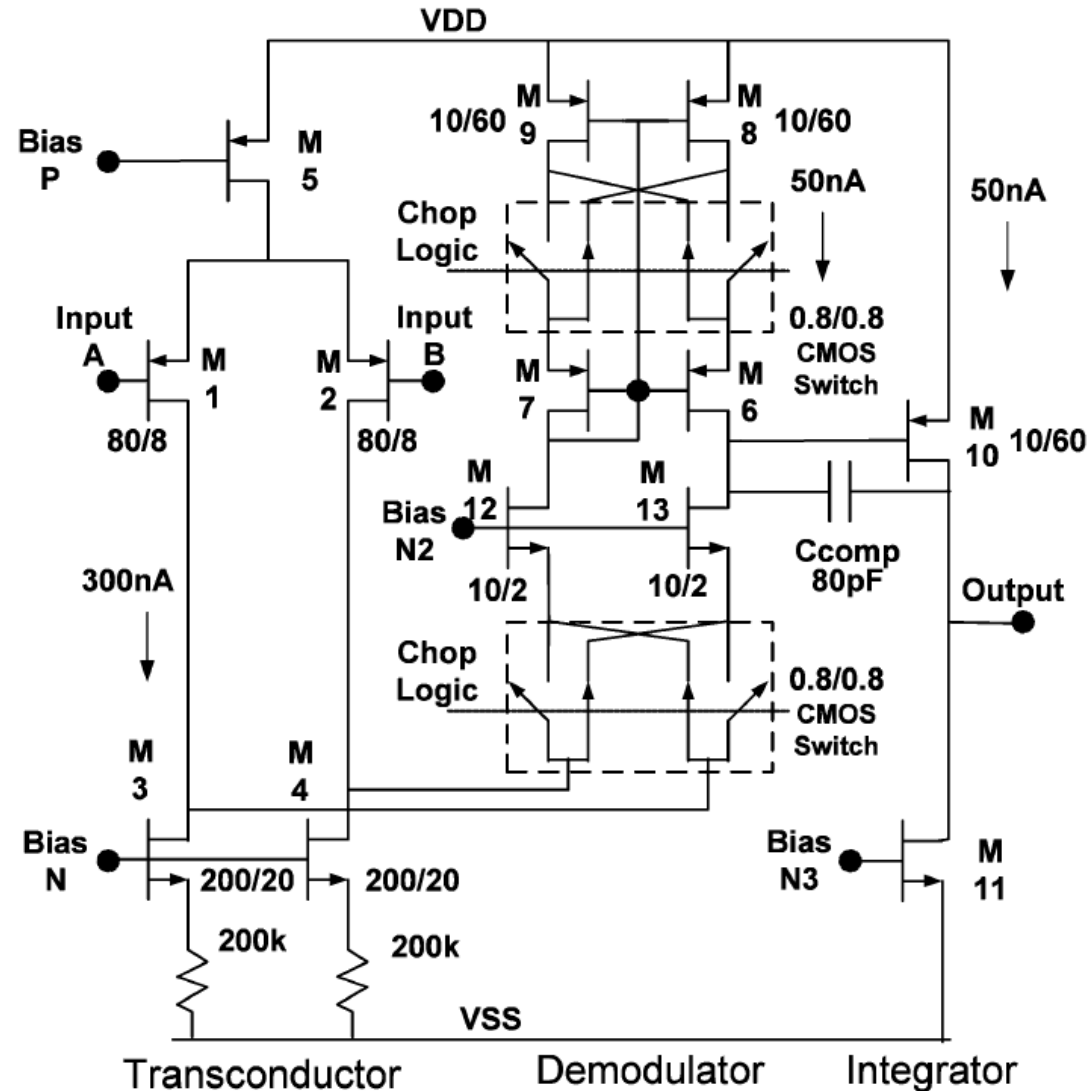

# Example of a NFP acquisition system



- Implementation of  $R_b$

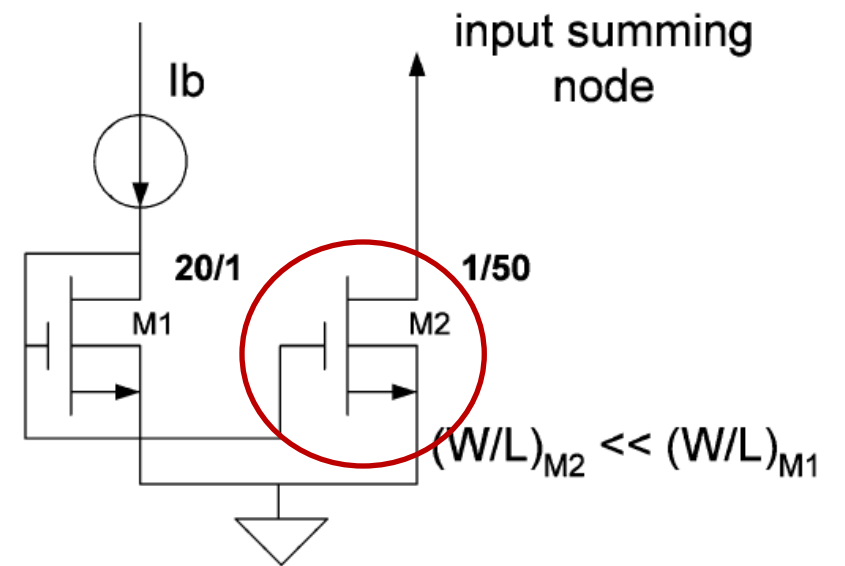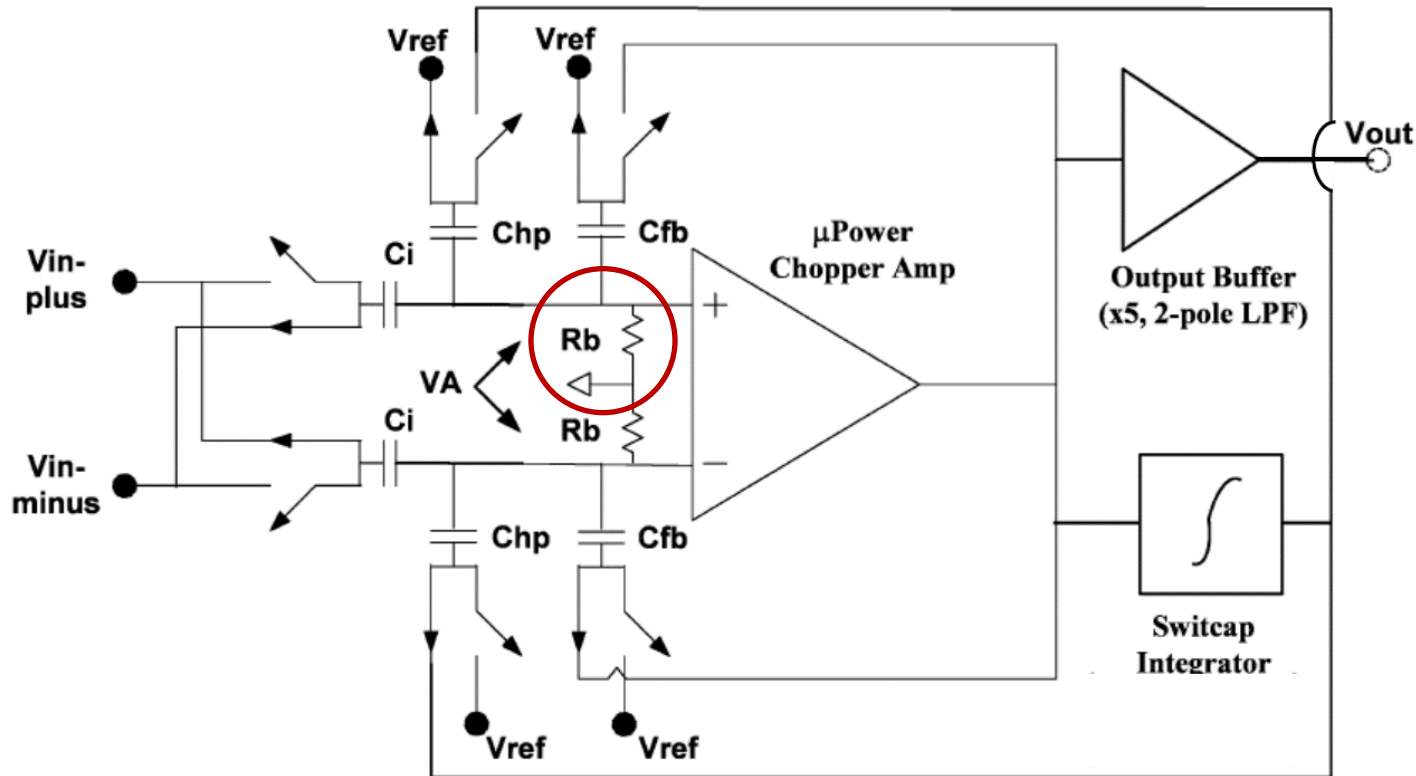



# Example of a NFP acquisition system

- Implementation results

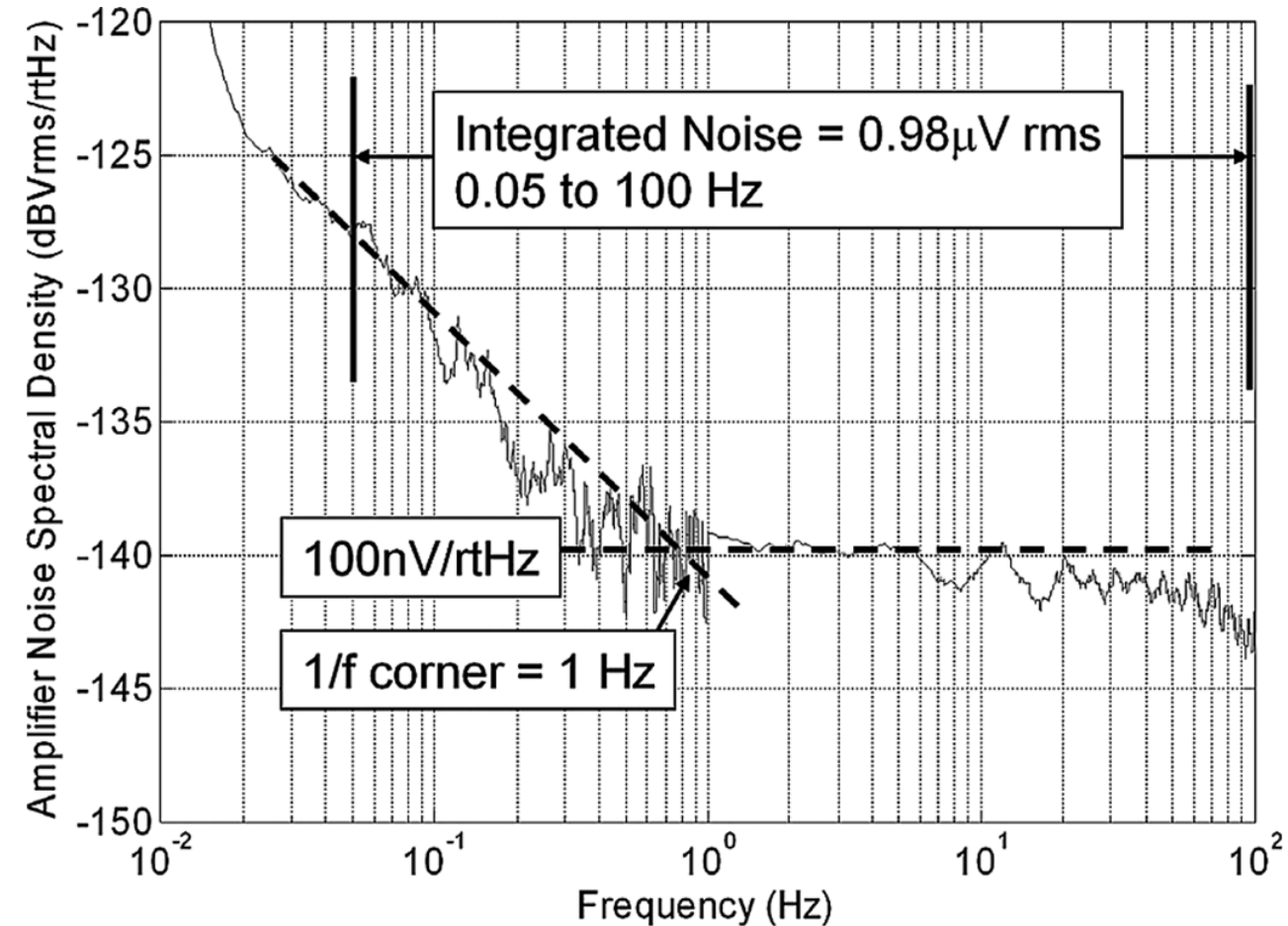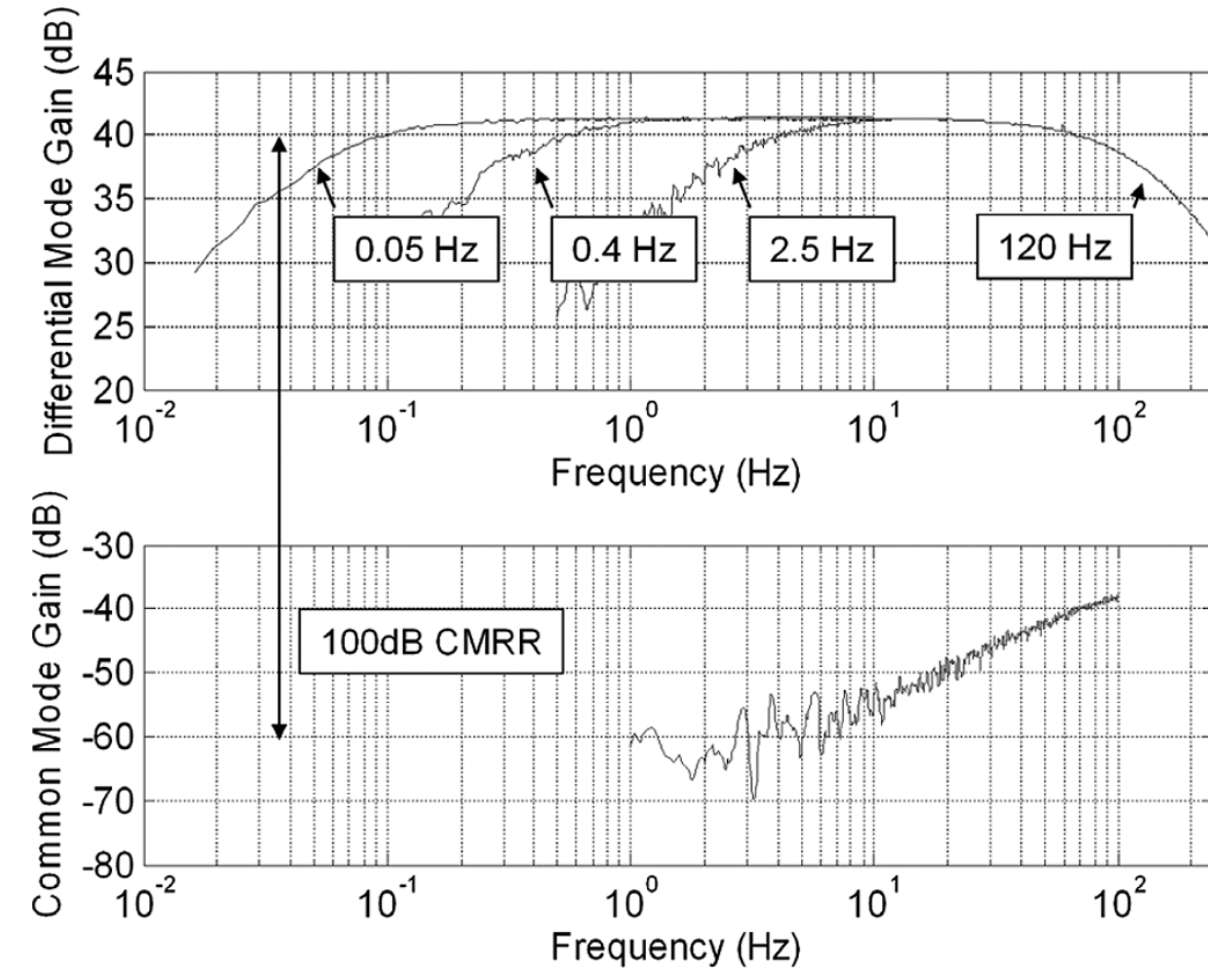

# Example of a NFP acquisition system

- Specifications and their experimental validation

BIOPOTENTIAL AMPLIFIER SPECIFICATIONS

Specification	Value	Units/Comments
Supply Voltage	1.7 to 3.3	Volts
Supply Current	1.0	uA
Gain	40 (min)	dB
Noise	1.5	$\mu$ V rms , 0.05 to 100Hz
CMRR	> 80	dB (DC to 60Hz)
Nonlinearity	< 0.1%	Harmonic Distortion
Aliasing	< -40	dB (compared to baseband)
Functional Range	20 to 45	Celsius
High-Pass Corners	0.05, 0.4, 2.5	Hz, no external components
Electrode Polarization	15, 50	mV (DC headroom)
Lowpass Corner Freq	150	Hz / corner frequency

KEY BIOPOTENTIAL AMPLIFIER RESULTS


Specification	Value	Units/Comments
Supply Voltage	1.8 to 3.3	Volts
Supply Current	1.0	uA
Gain	41, 50.5	dB (High polarization), (Diagnostic)
Noise	0.95	$\mu$ V rms , 0.05 to 100Hz
CMRR	> 80 > 100	SE dB (DC to 60Hz) DE dB (DC to 100Hz)
Nonlinearity	< 0.1%	Harmonic Distortion (5 mV input)
Aliasing	< -50	dB (compared to baseband)
NEF	4.6 / 5.4	Diagnostic / Sense-Stim Modes
High-Pass Corners	0.05, 0.4, 2.5	Hz, digitally programmable No external components
Lowpass Corner	180	Hz (-6dB, 2-pole filter)

# Exercise 1


- Discuss whether this statement is correct or not and explain your answer:
  - In a biopotential interface circuit using chopping, the chopping frequency must be larger if the required total input integrated noise level is reduced
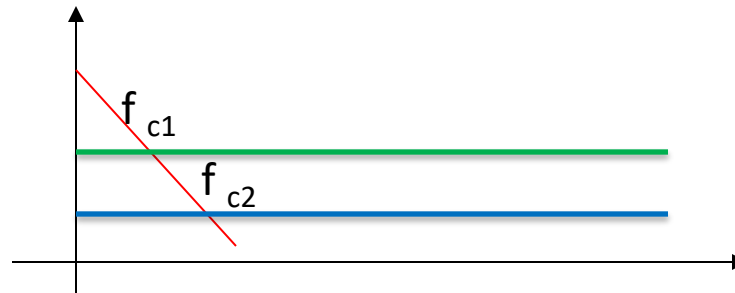
# Exercise 1: answer

- The statement is correct:
  - In a circuit using chopping the residual noise after applying chopping is due to white noise (slide 15)
  - To reduce the input integrated noise, thus, one must lower the white noise level (for instance, from green to blue here below), e.g. increasing the current in the input transistors
  - This approach decreases the thermal noise but has little effect on the  $1/f$  noise. Therefore, the noise corner is pushed to higher frequencies ( $f_{c1} \rightarrow f_{c2}$ ). To be effective, chopping must be performed at frequencies higher than the noise corner, thus the chopping frequency must increase.


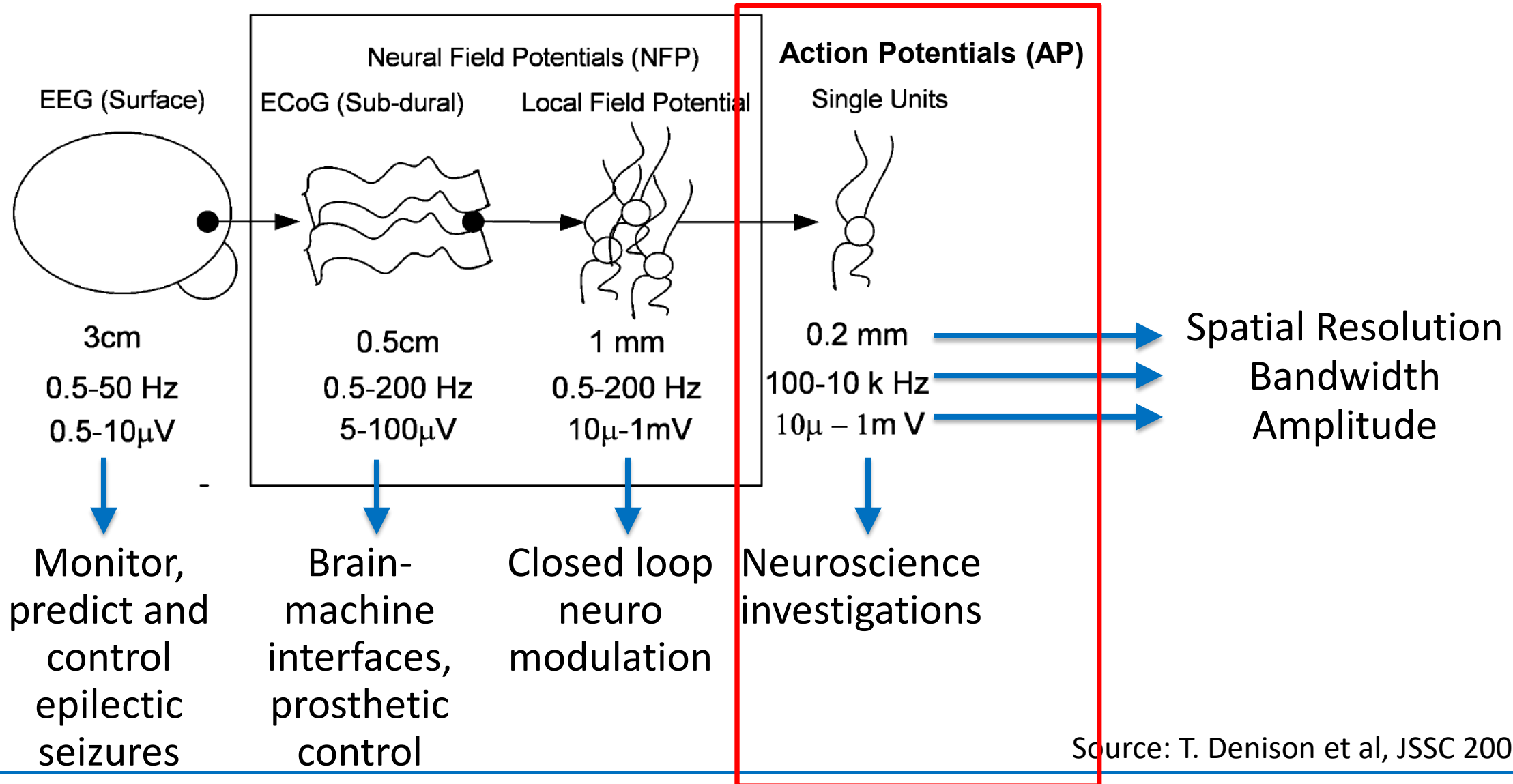
# Neural signals with application examples



# Example of an AP acquisition system

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 42, NO. 1, JANUARY 2007

123


## A Low-Power Integrated Circuit for a Wireless 100-Electrode Neural Recording System

Reid R. Harrison, *Member, IEEE*, Paul T. Watkins, *Student Member, IEEE*, Ryan J. Kier, *Student Member, IEEE*,  
Robert O. Lovejoy, Daniel J. Black, *Student Member, IEEE*, Bradley Greger, *Member, IEEE*, and  
Florian Solzbacher, *Member, IEEE*

- University of Utah work, related to Utah array development


# Example of an AP acquisition system

- System overview

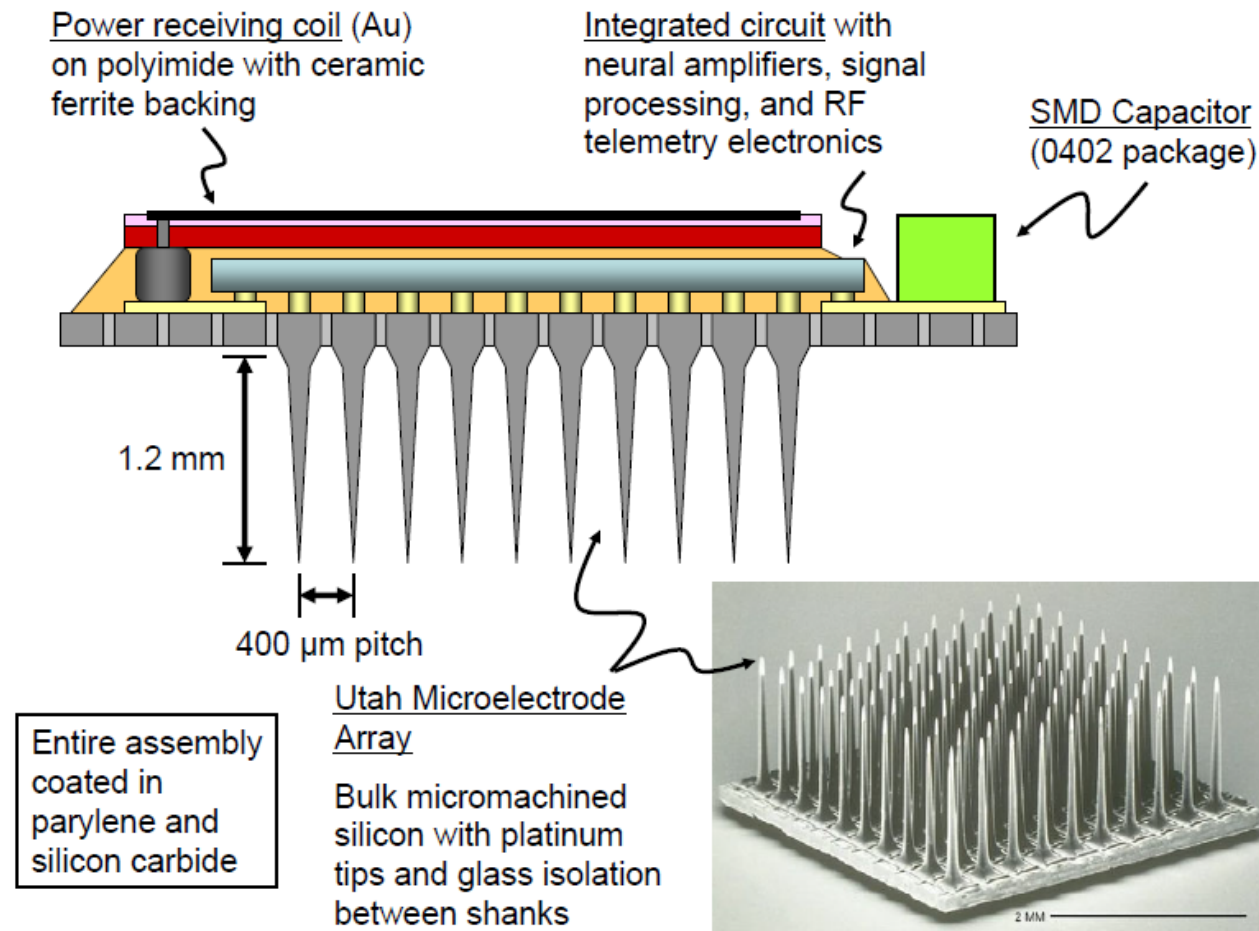

# Example of an AP acquisition system


- Block diagram

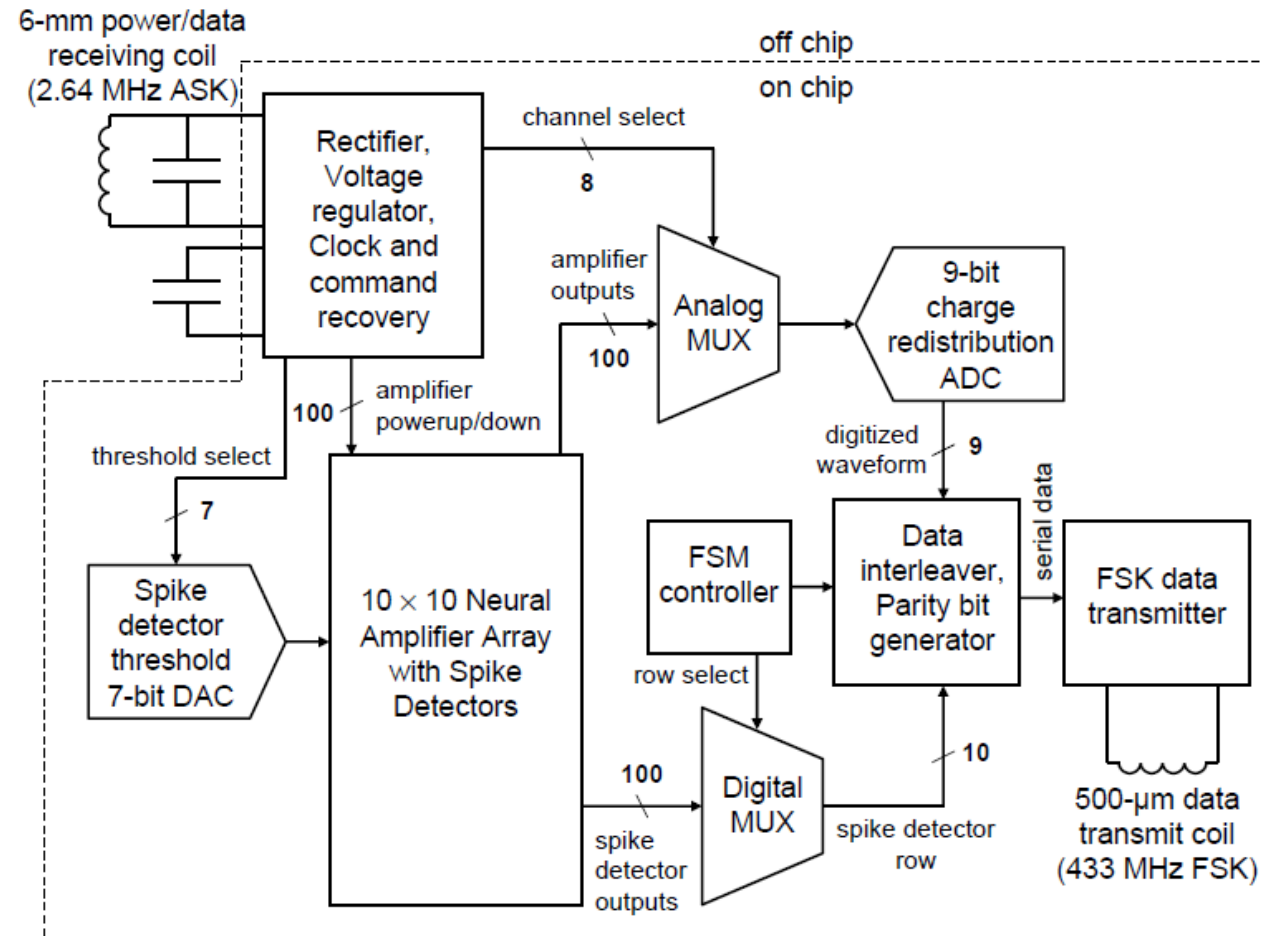




# Example of an AP acquisition system

- Chip photos

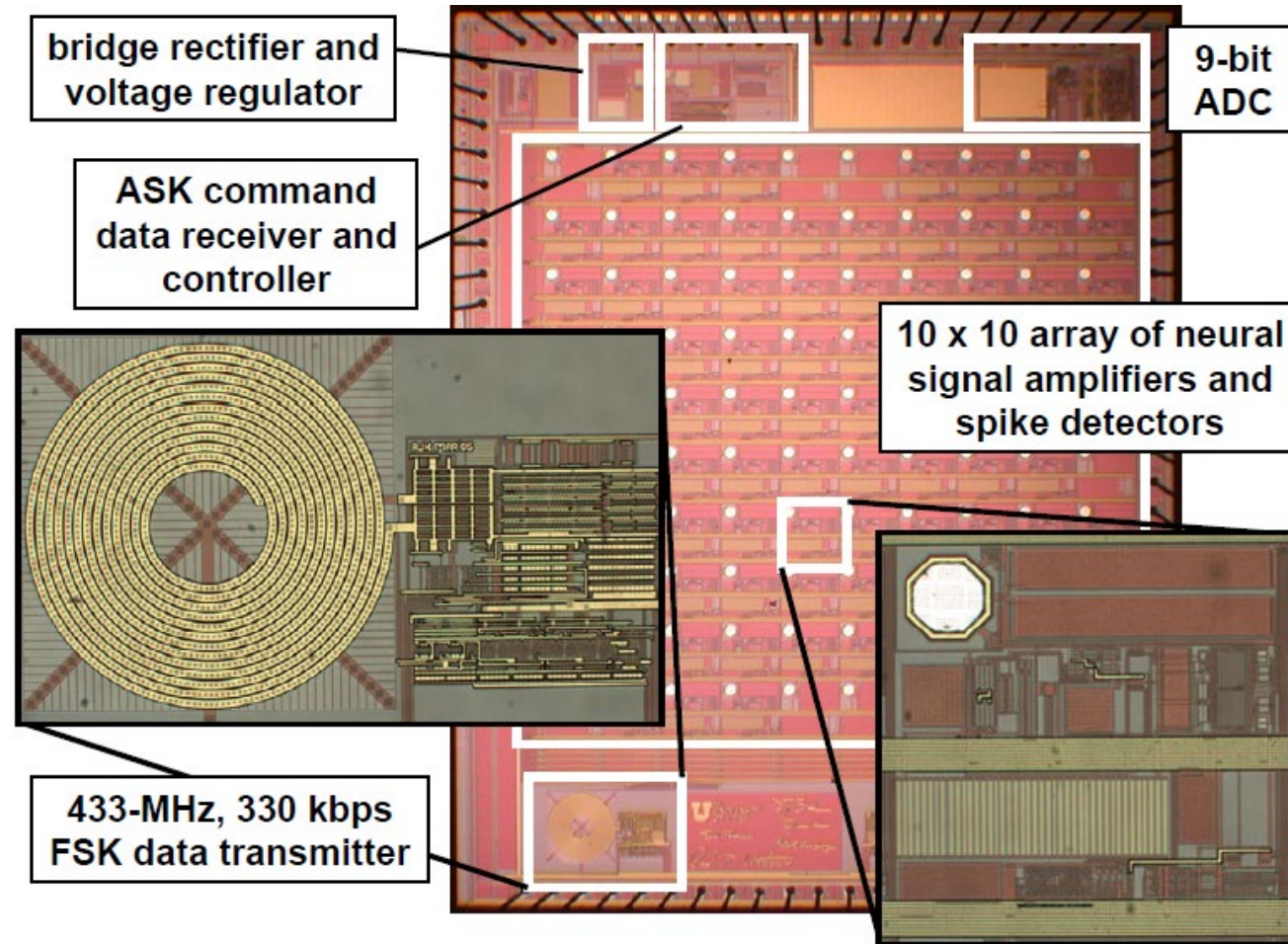


# Example of an AP acquisition system

- Single channel amplifier schematic

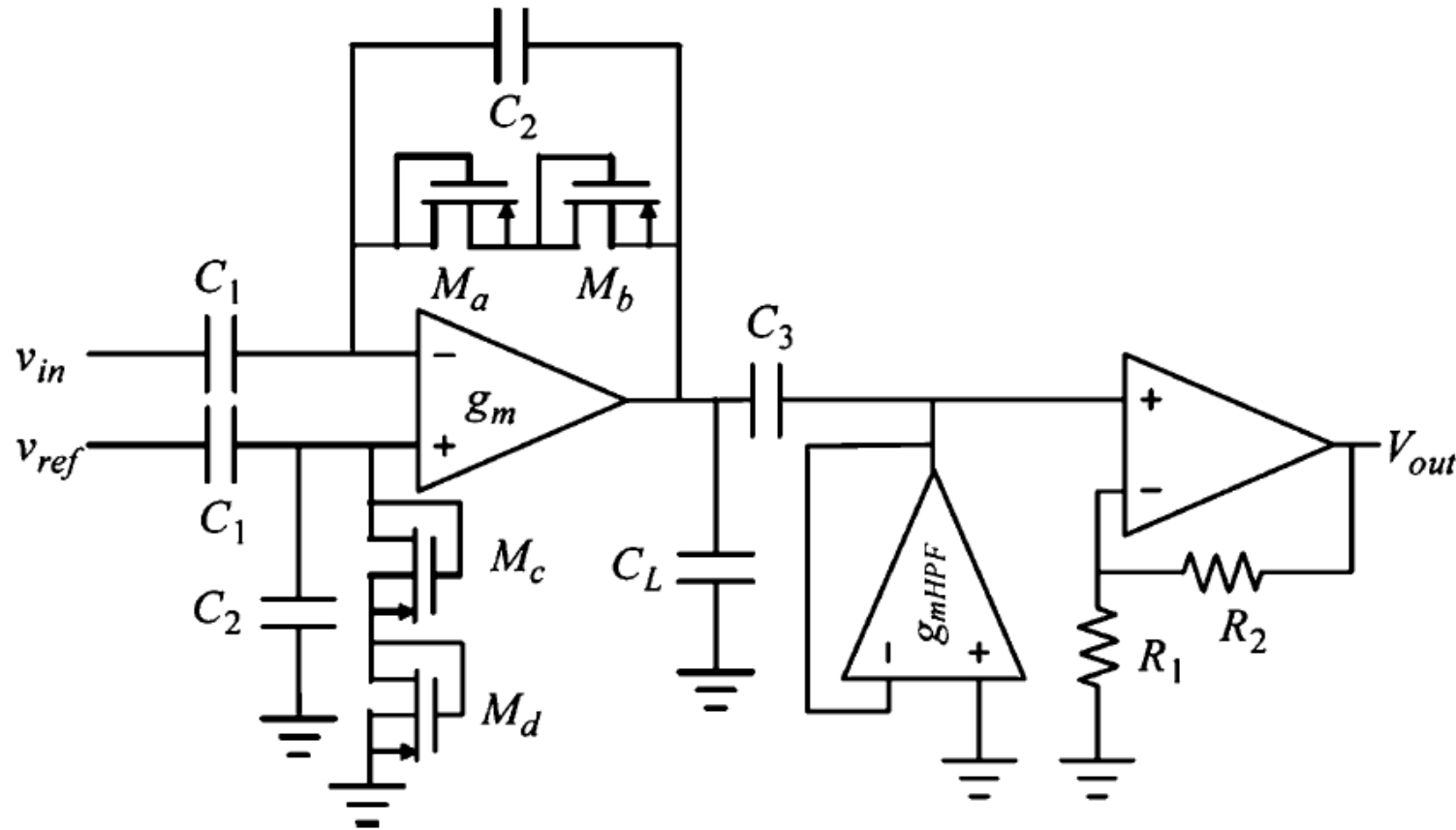
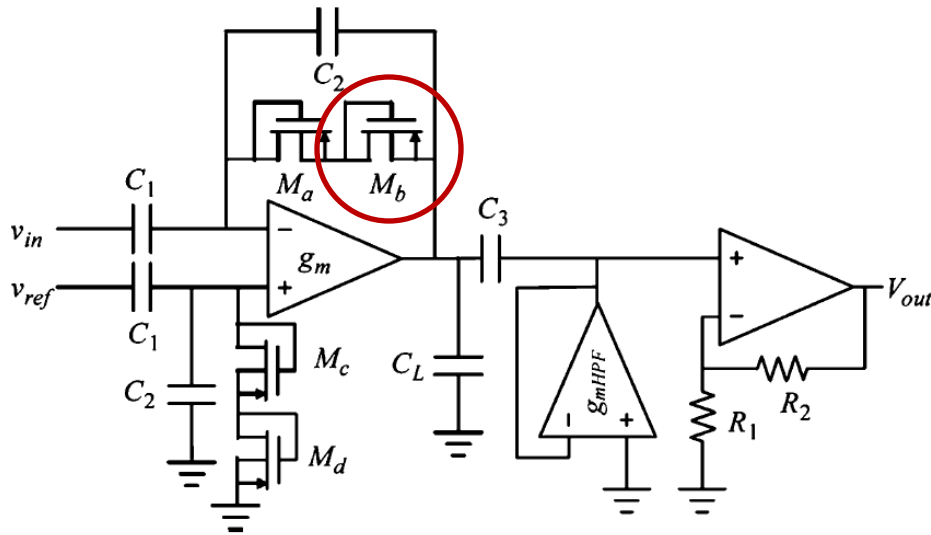
# Example of an AP acquisition system

- Pseudo resistors (diode-connected PMOS in off bias):  
+ Very large  $R_{eq} \approx 100G\Omega$



- + Very compact
- Very nonlinear
- Extreme PVT dependance
- Light dependent
- Leakage dependent

# Example of an AP acquisition system

- Measurement results:

Integrated Neural Interface IC Measured Performance	
Power/command signal frequency	2.64 MHz
Minimum required receive coil voltage amplitude	5.7 V (peak)
3.3-V voltage regulator dropout ( $I_L = 3$ mA)	250 mV
Load regulation ( $I_L = 2$ -10 mA)	0.15 %
Line regulation ( $V_{unreg} = 3.5$ V – 8.0 V)	<0.30 %/V
Maximum command input data rate (ASK)	6.5 kbps
Number of Channels/Electrodes	88 signal, 12 ground
Neural Signal Amplifier Gain	60.1 dB (1.1 – 5 kHz)
Input Referred Noise	5.1 $\mu$ Vrms
Individual Amplifier Supply Current	12.8 $\mu$ A
ADC resolution (LSB = 2.4 $\mu$ V electrode referred)	9 bits
ADC sampling rate	15.0 kSamples/s
ADC INL/DNL error (codes 50-511)	$\pm 0.8$ LSB/ $\pm 0.6$ LSB
Spike detector threshold resolution (LSB = 4.8 $\mu$ V electrode referred)	7 bits
FSK data transmission frequency	433 MHz
FSK data rate	330 kbps
Received signal power at distance of 13 cm	-86 dBm
Total chip power dissipation	13.5 mW
Total chip area (0.5- $\mu$ m, 2P3M CMOS)	27.3 mm <sup>2</sup>

# High spatial resolution AP acquisition system

248



IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 49, NO. 1, JANUARY 2014

## An Implantable 455-Active-Electrode 52-Channel CMOS Neural Probe

Carolina Mora Lopez, Alexandru Andrei, Srinjoy Mitra, Marleen Welkenhuysen, Wolfgang Eberle, *Senior Member, IEEE*, Carmen Bartic, Robert Puers, *Fellow, IEEE*, Refet Firat Yazicioglu, *Member, IEEE*, and Georges G. E. Gielen, *Fellow, IEEE*

- Shank probe with high count of measurement sites

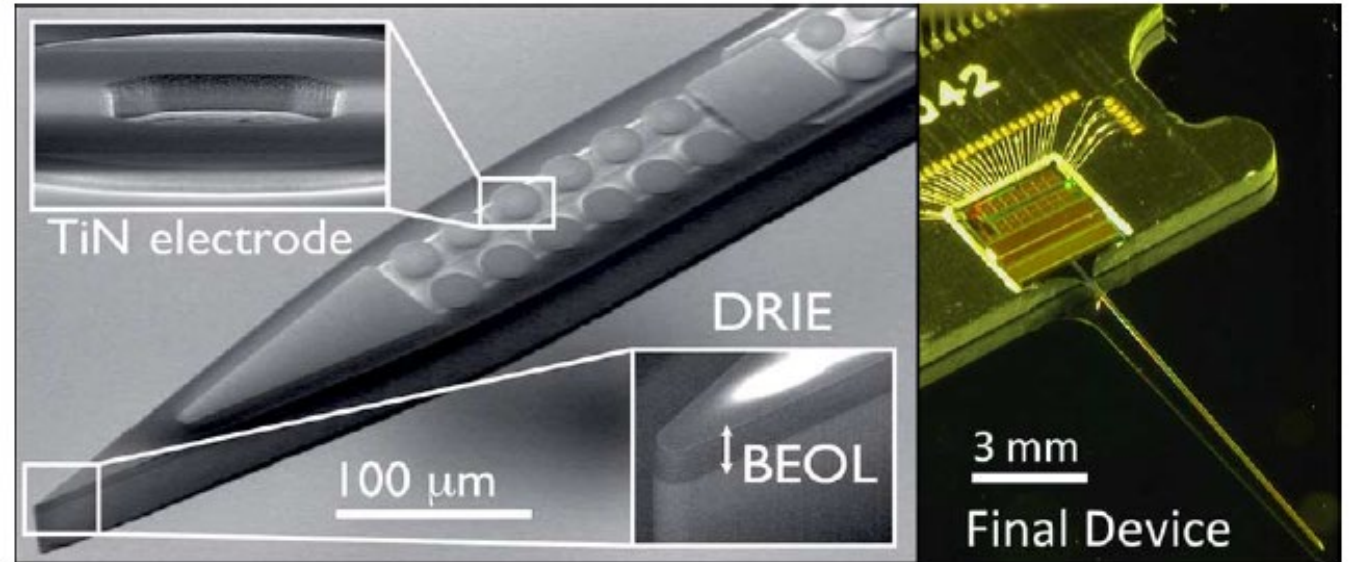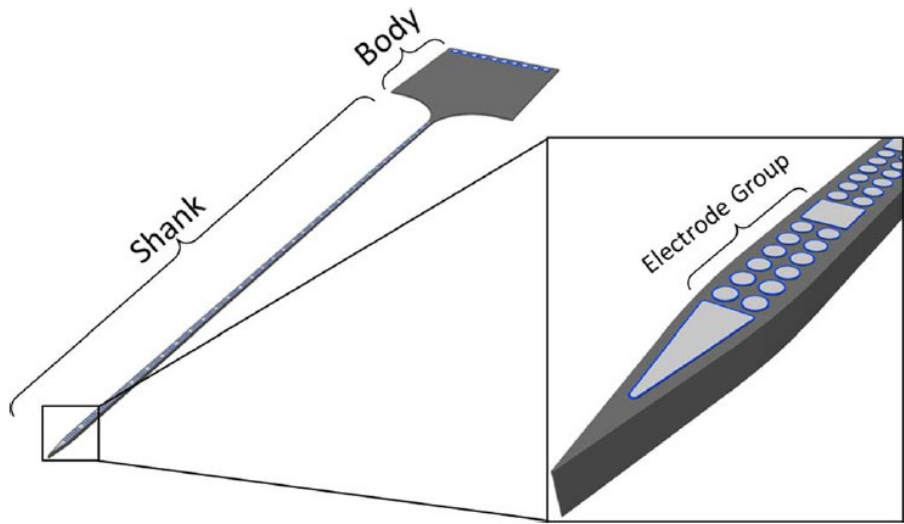
# High spatial resolution AP acquisition system



- Shank probe with high count of measurement sites




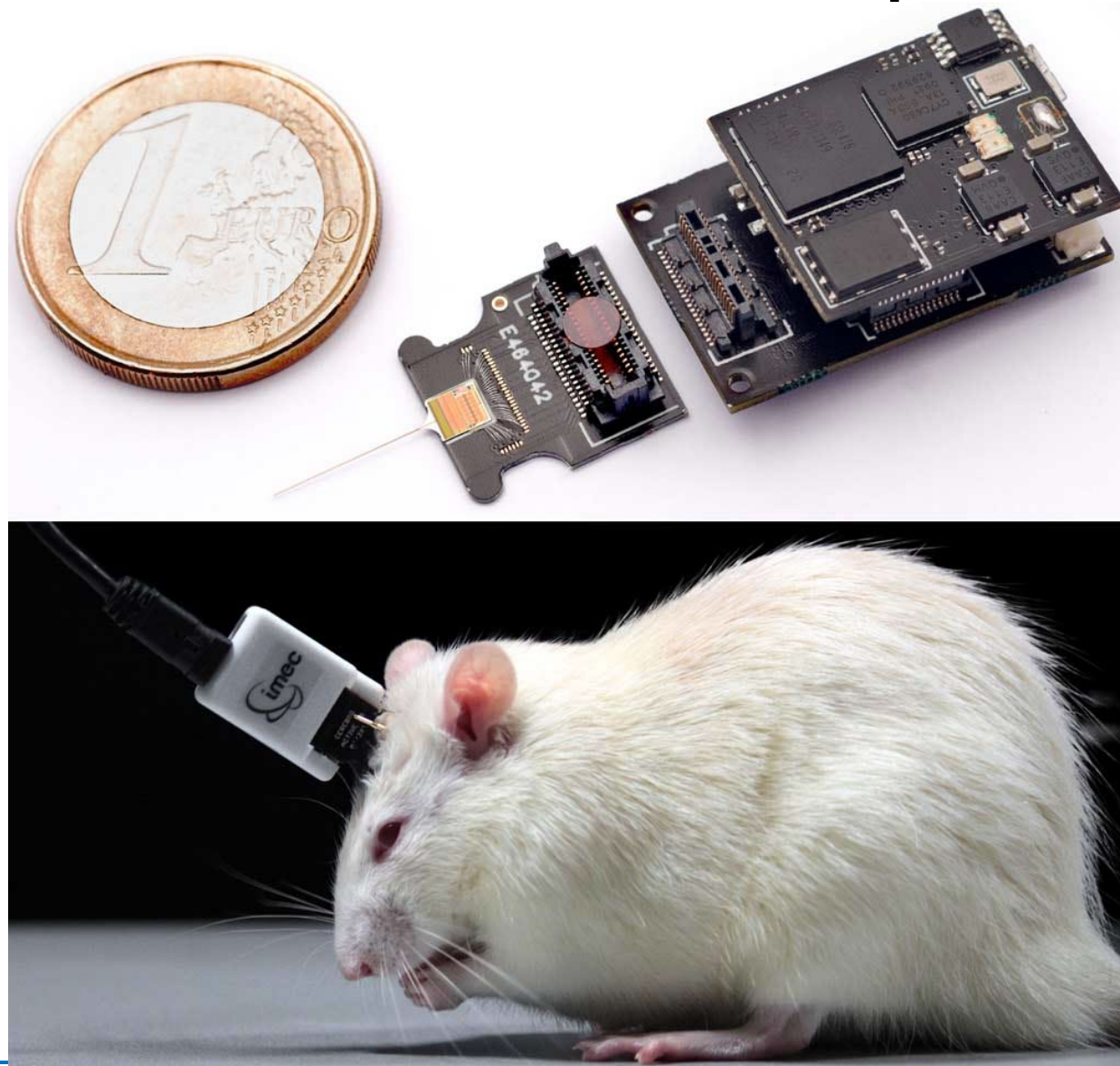
# High spatial resolution AP acquisition system



# High spatial resolution AP acquisition system


- Interference and cross-talk issues

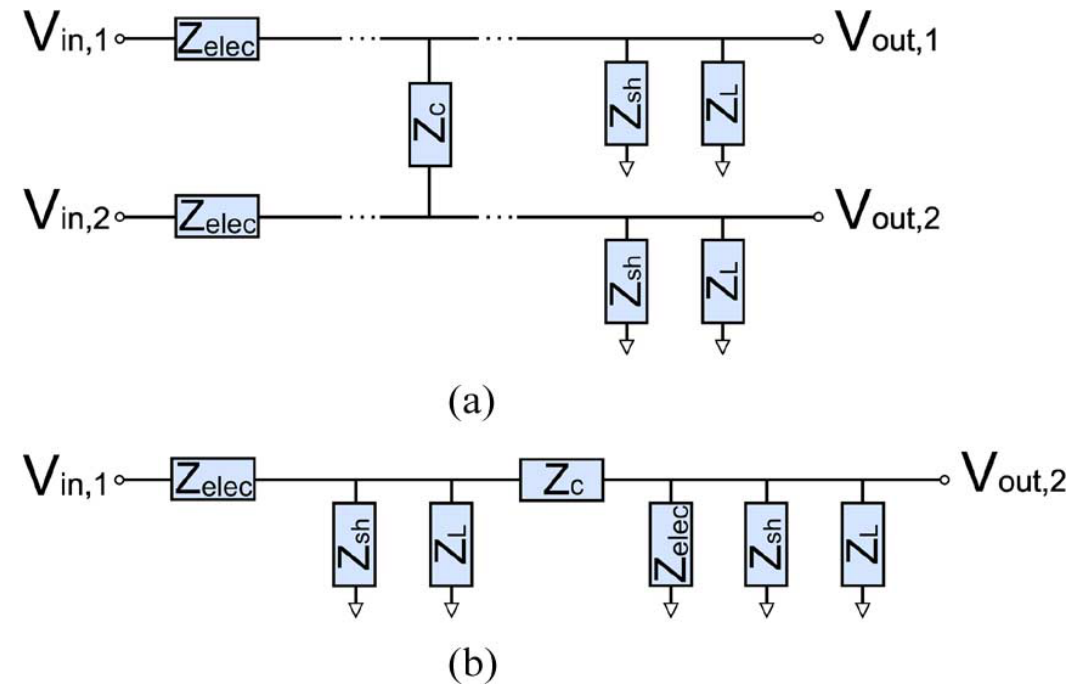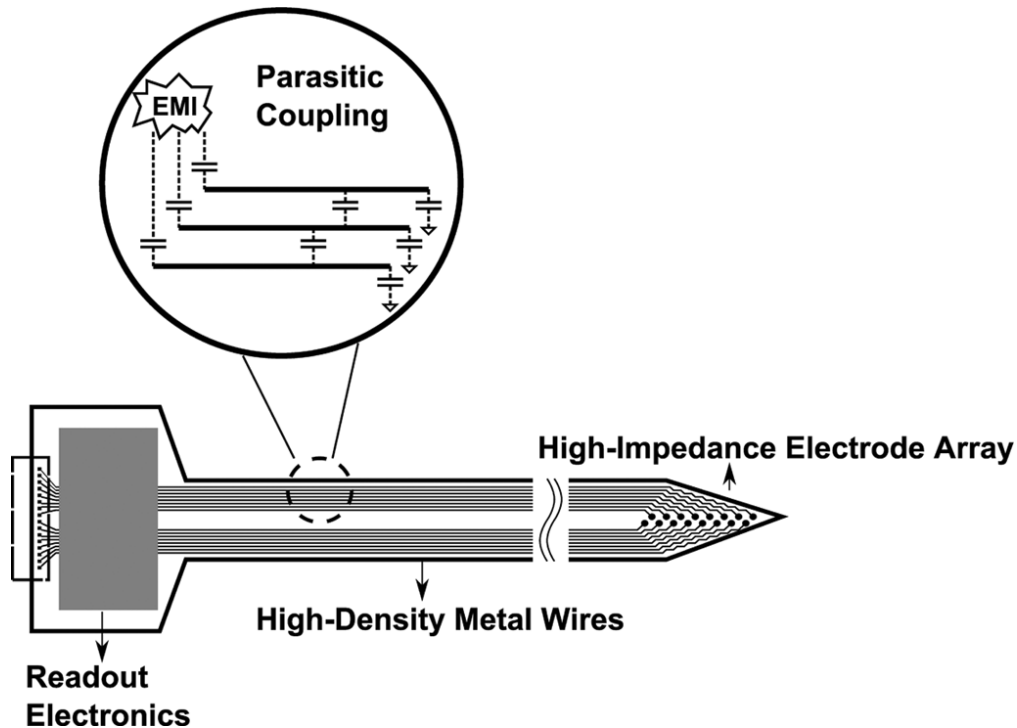



# High spatial resolution AP acquisition system


- Interference and cross-talk issues

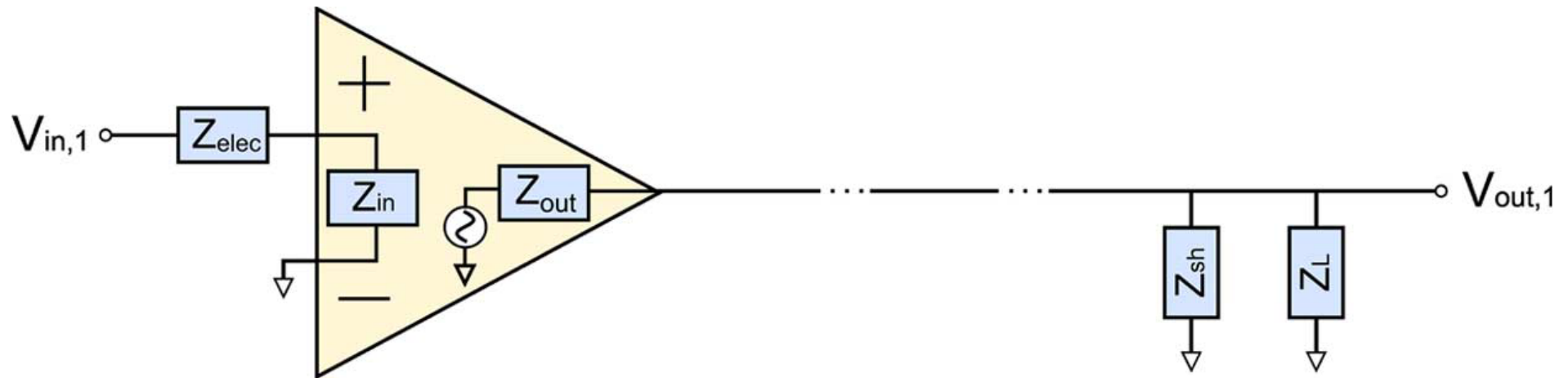

- Active electrodes


# High spatial resolution AP acquisition system

- System block diagram

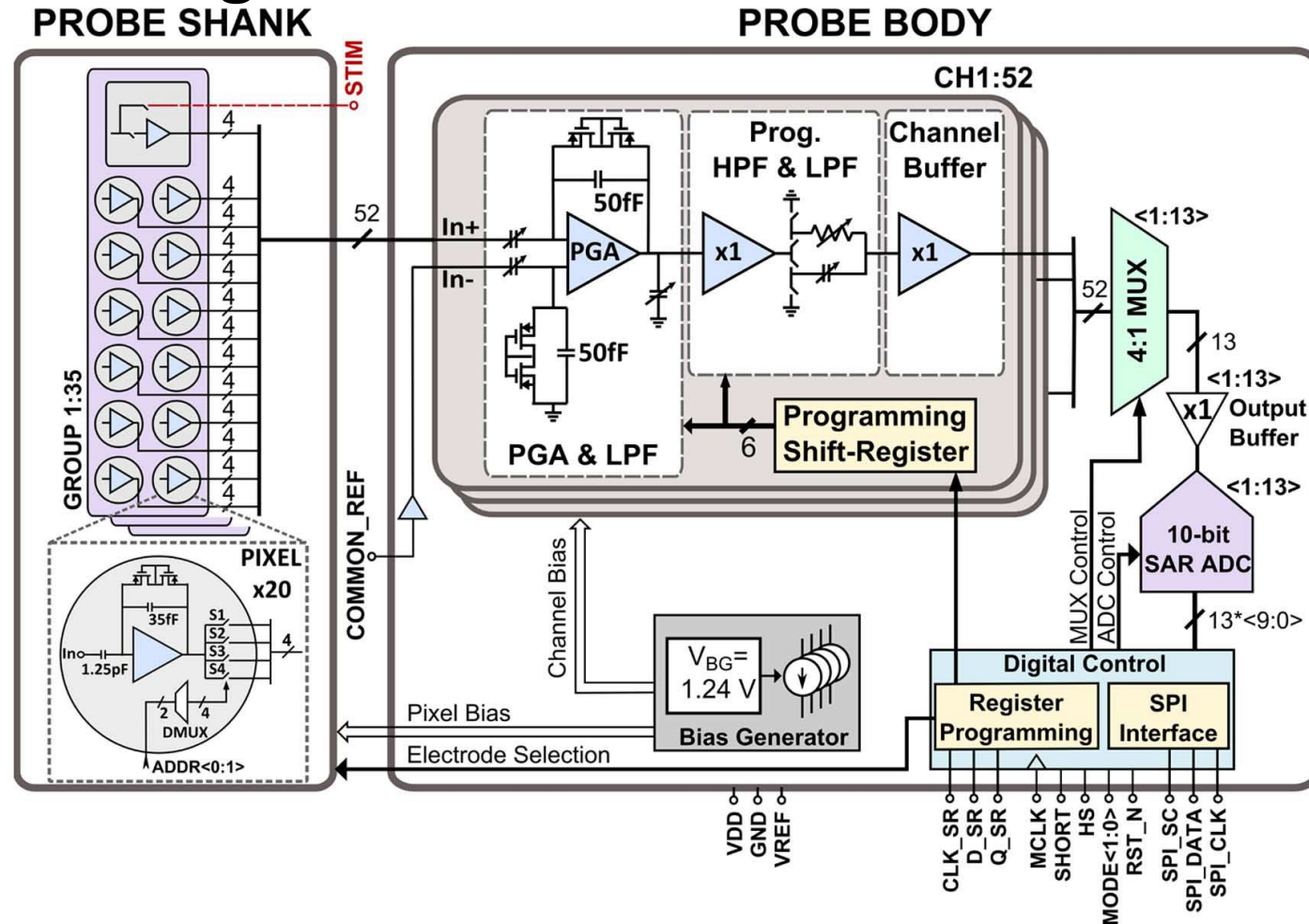

# High spatial resolution AP acquisition system

- Active electrode schematic

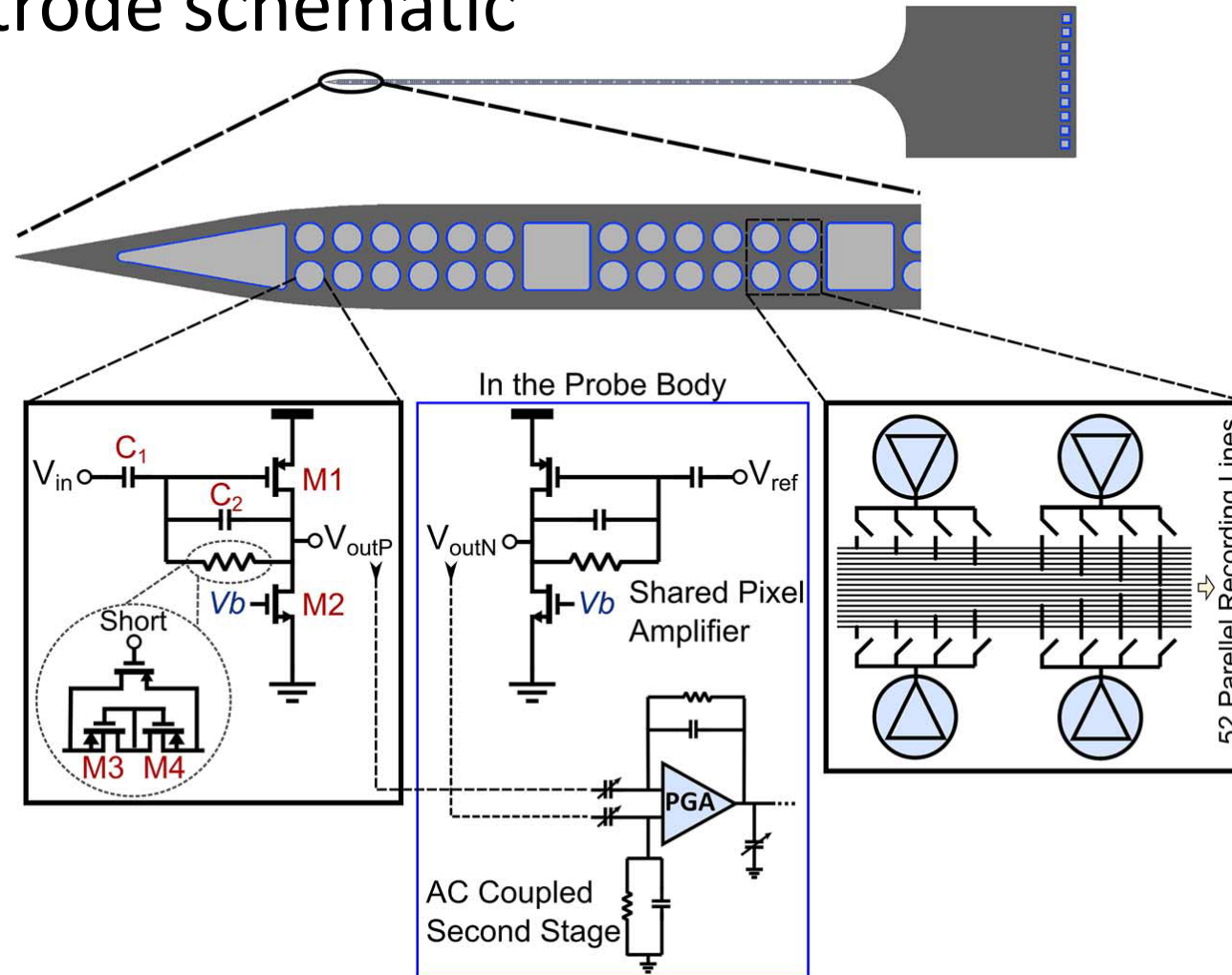

# High spatial resolution AP acquisition system

- Measured results

Parameter	Measured Value					
	[33]	[4]	[13]	[10]	[39]	This Work
<i>Probe Shank</i>						
No./Type Electrodes	--	8 <sup>A</sup> Passive	64 Passive	257 <sup>B</sup> Passive	--	<b>455 Active</b>
Electrode Area ( $\mu\text{m}^2$ )	--	100	108	1963.5	--	<b>78.6/491</b>
Electrode Pitch ( $\mu\text{m}$ )	--	100	28	60	--	<b>35</b>
Crosstalk (dB)	--	--	-84	--	--	<b>-44.8</b>
<i>Readout Electronics</i>						
No./Type Channels	1 <sup>D</sup>	8 Integrated	64 Hybrid <sup>C</sup>	128 Hybrid <sup>C</sup>	96 <sup>D</sup>	<b>52 Integrated</b>
Supply Voltage (V)	0.5	3	3	--	1.2	<b>1.8</b>
Total Power/Ch ( $\mu\text{W}$ )	5.04	94.5	351.6	39.1	67.7	<b>27.84</b>
Total Area/ Ch ( $\text{mm}^2$ )	0.013	0.625	0.45	--	0.26	<b>0.19</b>
<i>Analog Front-End (Pixel Amplifier + Recording Channel)</i>						
Power ( $\mu\text{W}$ )	5.04 <sup>E</sup>	68	--	--	35	<b>7.02</b>
Input Noise ( $\mu\text{V}_{\text{rms}}$ )	4.9	8.9	2	3.7	2.2	<b>3.2</b>
NEF	5.99	16	--	--	4.5	<b>3.08</b>
PEF= NEF <sup>2</sup> ·V <sub>DD</sub>	17.96	771	--	--	24.3	<b>17.13</b>
Gain	32	1000	194	70.8	630	<b>30-4000</b>
HP Corner (Hz)	300	300	1.3	1	1/280	<b>0.5/200/300/500</b>
LP Corner (Hz)	10000	10000	6400	10000	10000	<b>200/6000</b>
THD	2%	--	--	--	--	<b>1% (@ 18mV<sub>pp</sub>)</b>
CMRR/PSRR (dB)	75/64	--	83/84	--	--	<b>60/76</b>
<i>ADC</i>						
Resolution/ENOB (bit)	8/7.2	5/--	--	--	10/9.7	<b>10/9.2</b>
DNL (LSB)	0.55	0.33	--	--	0.29/-0.37	<b>0.23/-0.15</b>
INL (LSB)	--	0.5	--	--	0.28/-0.33	<b>0.42/-0.35</b>
Sam. Rate (kS/s)	20	160 (8 Ch)	--	--	31.25	<b>120 (4 Ch)</b>

<sup>A</sup> A 3-D array of 256 sites is achieved by mechanical assembly of 4 multi-shank (8) probes.

<sup>B</sup> In a multi-shank (4) probe with 1028 sites.


<sup>C</sup> Hybrid: Readout circuits are in a separate ASIC.

<sup>D</sup> Neural recording ASIC, not integrated with a neural probe.

<sup>E</sup> Includes ADC.
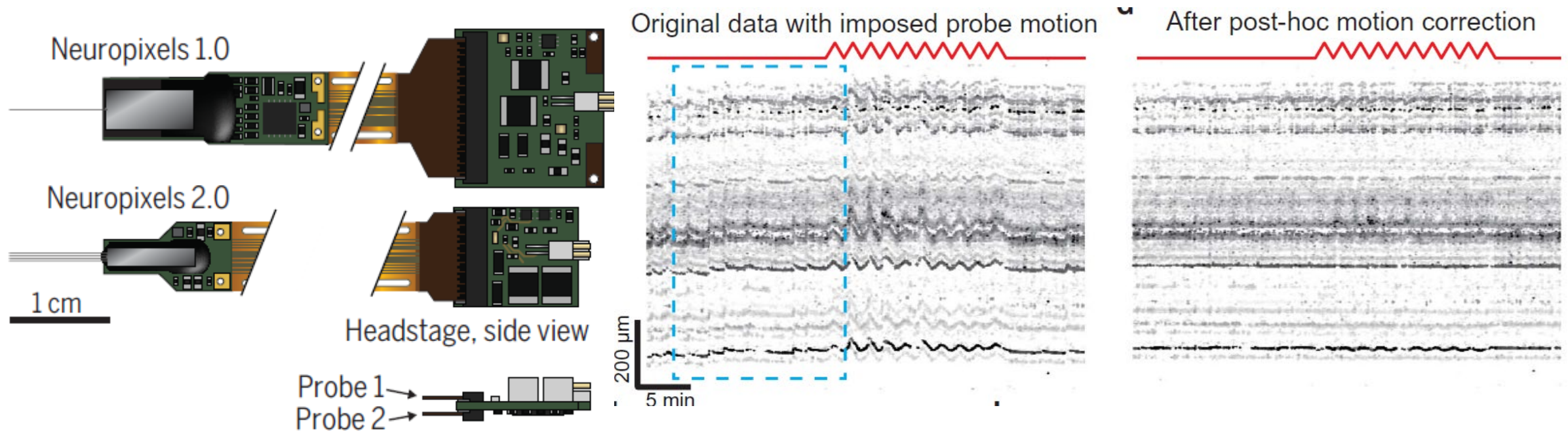
# High spatial resolution AP acquisition system

- Pros: possible to follow brain functioning with neuron resolution
- Cons: difficult to do this for a long time in chronic implants



Source: Steinmetz et al., Science 372, 258 (2021)

# Exercise 2

- Answer the following questions:
  - a) Why is it possible in the paper by Harrison to avoid chopping and in the one by Denison not?
  - b) In the paper by Harrison, why is it a very good idea to add after the amplifier a Gm-C high pass filter?
  - c) In the same paper, why the same impedance used in the feedback branch is added between ground and the positive input of the amplifier?
  - d) Which amplifier is more efficient, the one by Denison or the one by Harrison?
  - e) Why does the paper by Mora Lopez use a PMOS common source in the active electrode amplifier?



# Exercise 2: answers

- a) As the paper by Harrison deals with Action Potentials, which are signals at relatively high frequency ( $>100\text{Hz}$ ), he can filter out the low frequency spectrum and get rid of the  $1/f$  noise in this way. The paper by Denison deals with NFPs, which are at very low frequency (their spectrum extends below  $1\text{Hz}$ ), and thus Denison cannot use this method to attenuate the effect of  $1/f$  noise.
- b) The Gm-C filter indeed implements the high-pass behavior that cancels at the output the  $1/f$  noise added by the electronics.
- c) In this way, the impedance seen from the input  $V_{\text{in}}$  to ground is made as similar as possible (matching) to the one seen from  $V_{\text{ref}}$  to ground. Then, if a common mode disturbance is applied to  $V_{\text{in}}$  and  $V_{\text{ref}}$ , it will appear at the differential amplifier inputs still as common mode and will be rejected by the CMRR. An imbalance between the two branches would result in a different voltage at the amplifiers inputs for the same input disturbances at  $V_{\text{in}}$  and  $V_{\text{ref}}$ , and thus parts of the input common node would be converted to a differential signal and would propagate to the output. Please note that the amplifier output is low impedance (and thus almost at ground for the signal) due to the feedback applied.
- d) Calculate the NEF for both amplifiers to answer this question. The BW by Harrison is  $1.1\text{kHz}$ - $5\text{kHz}$ .
- e) Because it needs to implement an amplifier that is very compact, due to the space restrictions in the neural probe.

# Summary

- Capacitive feedback amplifiers for neural interfaces
- Design trade-offs
- Advantages and problems caused by chopping
- Active vs. passive electrodes