

Components in wireless technology, 5XTC0

Module 5
**Exercise: Design of amplifiers
and low-noise amplifiers**

Vojkan Vidojkovic



Technische Universiteit
Eindhoven
University of Technology

Where innovation starts


Outline

- Matching networks
- Amplifier design
- Low-noise amplifier dsign

Formula list available for exam

Power delivered to the load	$P_L = \frac{ V_2^+ ^2}{2Z_0} (1 - \Gamma_L ^2)$
Input power to the network	$P_m = \frac{ V_1^+ ^2}{2Z_0} (1 - \Gamma_m ^2)$
Input and output reflection coefficients of a transistor with a source and load: general case	$\Gamma_m = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$ $\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_3}{1 - S_{11}\Gamma_3}$
Input and output reflection coefficients of a transistor with a source and load: unilateral case	$\Gamma_m = \frac{V_1^-}{V_1^+} = S_{11}$ $\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22}$
Gain of the input matching network	$G_S = \frac{1 - \Gamma_S ^2}{ 1 - \Gamma_m\Gamma_S ^2}$
Gain of the output matching network	$G_L = \frac{1 - \Gamma_L ^2}{ 1 - S_{22}\Gamma_L ^2}$
Gain of the transistor (unilateral case)	$G_0 = S_{21} ^2$
Transducer gain of the basic amplifier circuit (input matching, unilateral transistor, output matching)	$G_T = G_S G_0 G_L$ $G_{T,dB} = G_{S,dB} + G_{0,dB} + G_{L,dB}$
Maximum gain of the input and output matching networks	$G_{S_{max}} = \frac{1}{1 - S_{11} ^2},$ $G_{L_{max}} = \frac{1}{1 - S_{22} ^2}.$
Maximum transducer power gain, unilateral case	$G_{TU_{max}} = \frac{1}{1 - S_{11} ^2} S_{21} ^2 \frac{1}{1 - S_{22} ^2}$
Normalized gain factors g_s and g_L .	$g_S = \frac{G_S}{G_{S_{max}}} = \frac{1 - \Gamma_S ^2}{ 1 - S_{11}\Gamma_S ^2} (1 - S_{11} ^2),$ $g_L = \frac{G_L}{G_{L_{max}}} = \frac{1 - \Gamma_L ^2}{ 1 - S_{22}\Gamma_L ^2} (1 - S_{22} ^2).$
Center and radius of the constant gain circle for the input matching network	$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S) S_{11} ^2},$ $R_S = \frac{\sqrt{1 - g_S}(1 - S_{11} ^2)}{1 - (1 - g_S) S_{11} ^2}$
Center and radius of the constant gain circle for the output matching network	$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) S_{22} ^2},$ $R_L = \frac{\sqrt{1 - g_L}(1 - S_{22} ^2)}{1 - (1 - g_L) S_{22} ^2}$
Condition for "unconditionally stable" device, general case	for all $ \Gamma_L < 1$ and $ \Gamma_S < 1$ $\Rightarrow \begin{cases} \Gamma_m = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} < 1 \\ \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_3}{1 - S_{11}\Gamma_3} < 1 \end{cases}$

Conditions for "unconditionally stable" device, unilateral case	$ \Gamma_m = S_{11} < 1$ $ \Gamma_{out} = S_{22} < 1$
Center and radius of the stability circles, load side	$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{ S_{22} ^2 - \Delta ^2}$ (center), $R_L = \left \frac{S_{12}S_{21}}{ S_{22} ^2 - \Delta ^2} \right $ (radius). $\Delta = S_{11}S_{22} - S_{12}S_{21}$
Center and radius of the stability circles, source side	$C_S = \frac{(S_{11} - \Delta S_{21}^*)^*}{ S_{11} ^2 - \Delta ^2}$ (center), $R_S = \left \frac{S_{12}S_{21}}{ S_{11} ^2 - \Delta ^2} \right $ (radius) $\Delta = S_{11}S_{22} - S_{12}S_{21}$
Test for unconditional stability, general case	$ \Delta = S_{11}S_{22} - S_{12}S_{21} < 1$ and $K = \frac{1 - S_{11} ^2 - S_{22} ^2 + \Delta^2}{2 S_{12}S_{21} } > 1$
Test for unconditional stability, unilateral case	$ S_{11} < 1$ $ S_{22} < 1$
Two-stage amplifier: Output noise and noise figure	$P_{N_{total}} = G_{A2}(G_{A1}P_{N,m} + P_{n1}) + P_{n2}$ $\Rightarrow F_{total} = \frac{P_{N_{total}}}{P_{N,m}G_{A1}G_{A2}} = 1 + \frac{P_{n1}}{P_{N,m}G_{A1}} + \frac{P_{n2}}{P_{N,m}G_{A1}G_{A2}}$ $F_{total} = F_1 + \frac{F_2 - 1}{G_{A1}},$ with $F_j = 1 + \frac{P_{nj}}{P_{N,m}G_{Aj}}$, $j = 1, 2$
Noise figure of a 2-port amplifier	$F = F_{min} + \frac{r_N}{g_S} \left \frac{y_S - y_{opt}}{y_S} \right ^2$ $F = F_{min} + 4r_N \frac{ \Gamma_S - \Gamma_{opt} ^2}{(1 - \Gamma_S ^2)(1 + \Gamma_{opt} ^2)}$
Constant noise circles	$\underline{C}_F = \frac{\Gamma_{opt}}{1 + N}$ $R_n = \frac{1}{1 + N} \sqrt{N^2 + N(1 - \Gamma_{opt} ^2)}$ $\Delta F_n' = N = (F - F_{min}) \frac{\left 1 + \Gamma_{opt} \right ^2}{4r_n} = \frac{\left \Gamma_S - \Gamma_{opt} \right ^2}{1 - \Gamma_S ^2}$

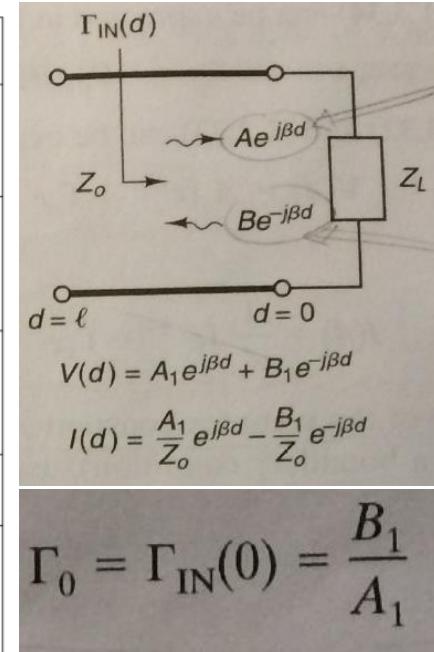

Transmission lines: Problem 1

- Book of Gonzalez: Example 1.13
- Assignment, problem 2

- Calculate the reflection coefficient Γ_{IN} and the VSWR in the $\lambda/4$ line in Fig. 2.
- Calculate the voltage $V(\lambda/4)$, the power available from the source P_{AVS} , and the power delivered to the 100Ω load.


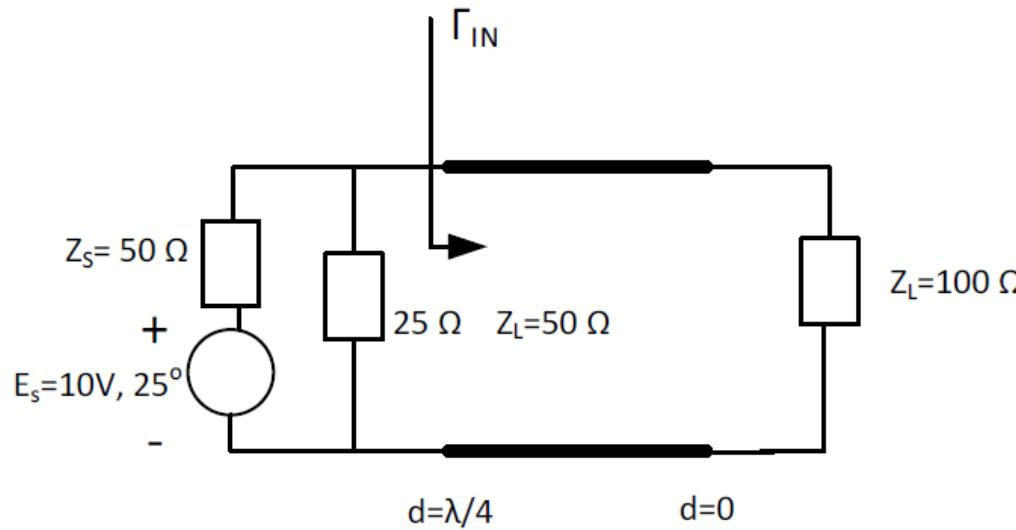


Figure 2 Problem 2.

Transmission lines: Solution for Problem 1a

a) Gonzales, Problem 1.13

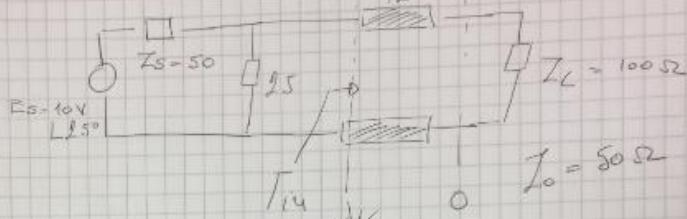

$$V = A_1 e^{j\beta d} + B_1 e^{-j\beta d}$$

$$V = A_1 e^{j\beta d} \left(1 + \frac{B_1}{A_1} e^{-j2\beta d} \right)$$

$$\Gamma_0 = \frac{B_1}{A_1}$$

$$\overline{\Gamma(d)} = \frac{B_1}{A_1} e^{-j2\beta d} = \Gamma_0 e^{-j2\beta d}$$

$$V(d) = A_1 e^{j\beta d} \left(1 + \Gamma_0 e^{-j2\beta d} \right)$$

$$VSWR = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|}$$


$$\text{a) } \Gamma_{in} = \Gamma(\lambda_g) = \Gamma_0 e^{-j2\beta d}$$

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = 0.33$$

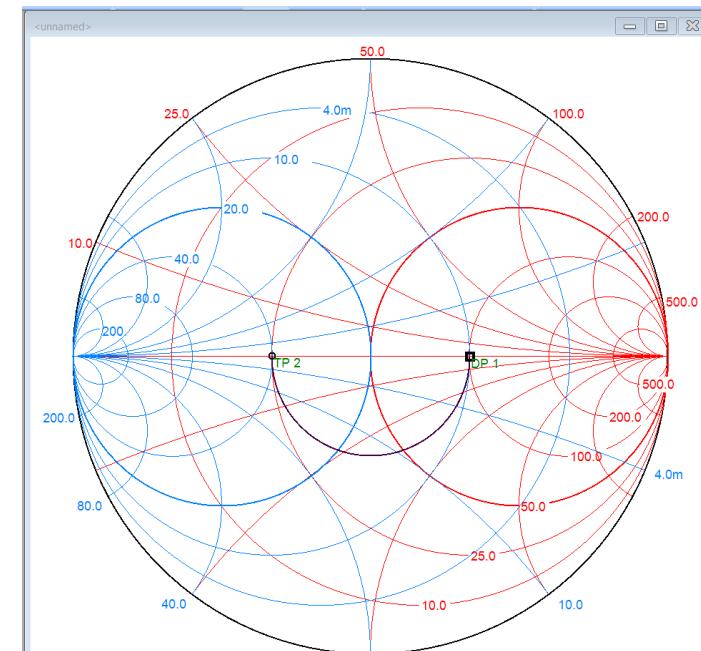(4)

$$\begin{aligned} \Gamma_{in} &= \Gamma\left(\frac{\lambda}{4}\right) = 0.33 e^{j2\frac{2\pi}{\lambda} \frac{\lambda}{4}} \\ \Gamma_{in} &= 0.33 e^{j\frac{\pi}{2}} \\ \boxed{\Gamma_{in} = -0.33} \end{aligned}$$

$$VSWR = \frac{1 + 0.33}{1 - 0.33} = 1.38$$



Transmission lines: Solution for Problem 1 b (1/2)

$$b) \quad V_{in} = I_o \frac{Z_L + j Z_0 \tan \beta d}{Z_0 + j Z_L \tan \beta d}$$

$$d = \frac{\lambda}{4}$$

$$\beta d = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \pi/2$$


$$\tan \pi/2 = \infty$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$Z_{in} = \frac{50^2}{100} = 25 \Omega$$

②

Equivalent circuit:

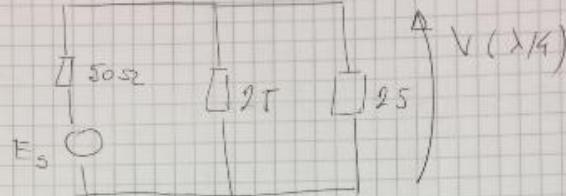

$$V(\frac{\lambda}{4}) = E_s \cdot \frac{12.5}{50 + 12.5}$$

$$V(\frac{\lambda}{4}) = 10 e^{j25} \cdot 0.2$$

$$V(\frac{\lambda}{4}) = 2 e^{j25}$$

$$V(\frac{\lambda}{4}) = A_1 e^{j\beta d} (1 + f_0 e^{-j2\beta d})$$

$$\frac{\lambda}{4} = d \Rightarrow \beta d = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

$$2\beta d = \pi$$

$$2 \cdot e^{j25} = A_1 e^{j\frac{\pi}{2}} (1 + 0.33 e^{-j\pi})$$


$$2 \cdot e^{-j65} = A_1 (1 - 0.33)$$

$$A_1 = 3 e^{-j65}$$

$$e^{j\pi} = \cos(-\pi) + j \sin(-\pi)$$

$$\bar{e}^{j\pi} = -1$$

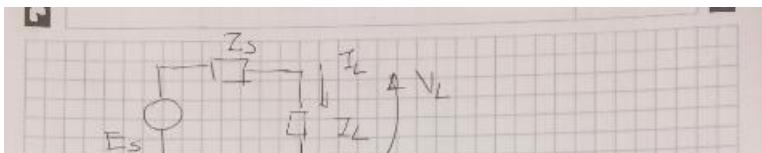Transmission lines: Solution for Problem 1 b (2/2)



$\text{Paus} @ \quad Z_L = Z_s^* = R \Re e \quad | \quad V_L \cdot I_L^*$
 $I_s = R_s + jX_s$
 $I_L = Z_s^* = R_s - jX_s$

$V_L = \frac{E_s}{2}$
 $I_L = \frac{E_s}{2R_s}$

$\boxed{\text{Paus} = \frac{|E_s|^2}{8R_s} = \frac{100}{8 \cdot 50} = 0,25 \text{ W}}$

$N(\omega) = A_f (1 + \Gamma_0)$
 $V(\omega) = 3 e^{-j65^\circ} (1 + 0,33) = \underline{3,33}$
 $\boxed{V(\omega) = 3,33 e^{-j65^\circ}}$

$I(\omega) = \frac{A_f (1 - \Gamma_0)}{Z_0} = \frac{3 e^{-j65^\circ} \cdot 0,67}{50}$
 $I(\omega) = 0,04 e^{-j65^\circ}$

(4)

$P_o = \frac{\Re e}{2} \left| V(\omega) \cdot I(\omega)^* \right|$
 $\Re e = 3,33 e^{-j65^\circ} \cdot 0,04 e^{j65^\circ}$
 $\boxed{P_o = 0,08 \text{ W}}$


Matching: Problem 2

- Assignment, problem 3

Design an LC matching network that transforms impedance $Z=100+j50$ to 50ohm.
Operating frequency is 1GHz.

- A. How many solution are existing?
Draw the solutions in the Smith Chart
- B. Calculate impedance of L and C for all solutions
- C. Calculate values of L and C for all solutions
- D. Take one of the solutions and check solution based on Smith Chart with analytical calculation

Matching: Problem 2 – Solution (1/2)

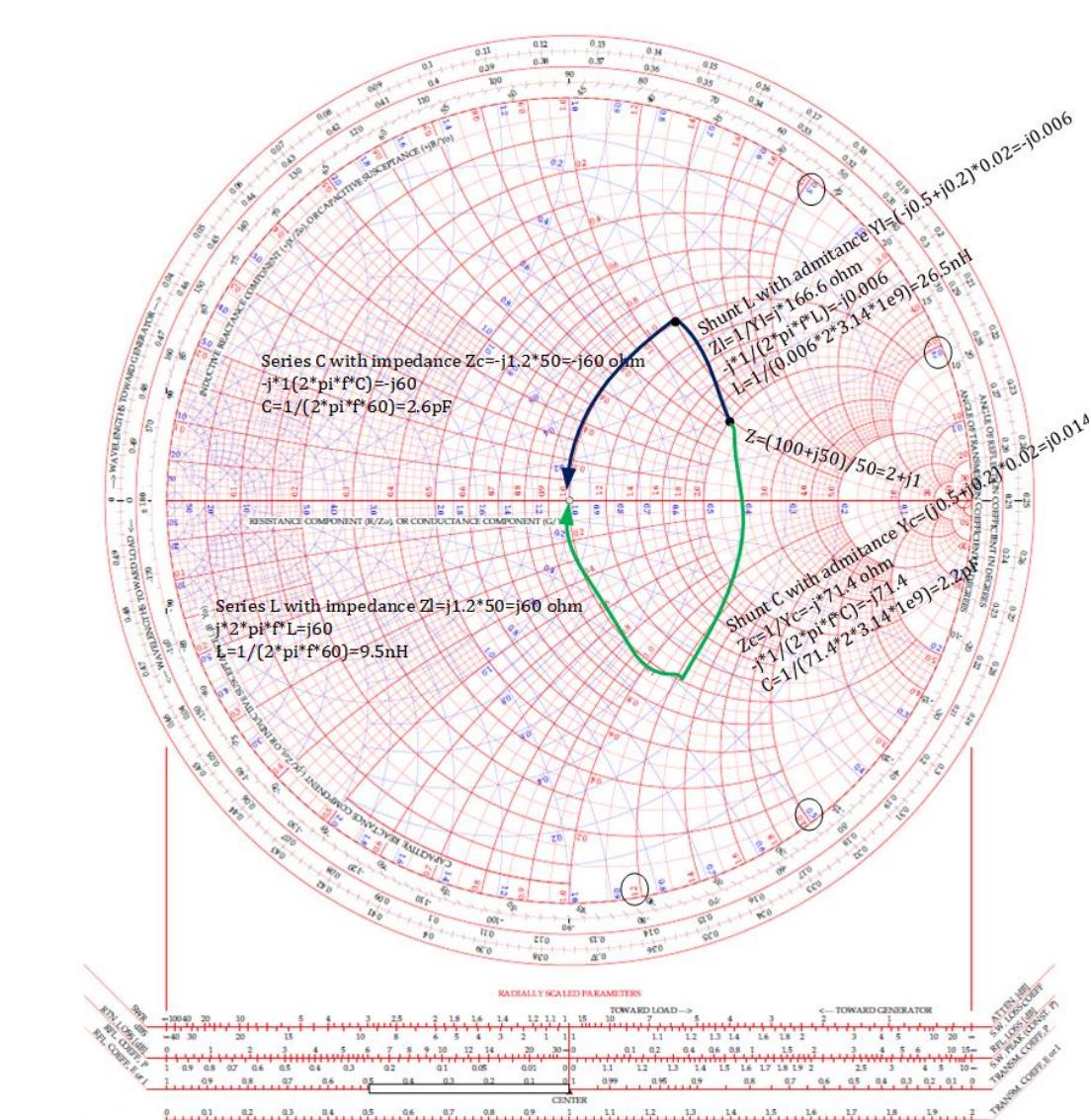

Matching: Problem 2 – Solution (2/2)

$$Z_{1u} = \frac{1}{j\omega C} + \frac{1}{\frac{1}{j\omega L} + \frac{1}{Z}}$$

$$Z_{1u} = -j \frac{1}{\omega C} + \frac{1}{-j \frac{1}{\omega L} + \frac{1}{Z}} \quad \dots (1)$$

$$\frac{1}{\omega C} = A \quad \frac{1}{\omega L} = B$$

$$Z_{1u} = -j \cdot A + \frac{1}{-jB + R + jI_{1u}}$$

$$\frac{1}{Z} = R + jI_{1u} \rightarrow \text{known} \quad \left. \begin{array}{l} Z = 10^{100} + j50 \\ R = 8 \cdot 10^{-3}, I_{1u} = 4 \cdot 10^{-3} \end{array} \right\}$$

$$Z_{1u} = -j \cdot A + \frac{R - j(I_{1u} - B)}{B^2 + (I_{1u} - B)^2}$$

$$Z_{1u} = 50 \rightarrow \text{known}$$

$$S_0 = \frac{R}{R^2 + (I_{1u} - B)^2} \quad \dots (3)$$

$$A + \frac{I_{1u} - B}{R^2 + (I_{1u} - B)^2} = 0 \quad \dots (4)$$

$$(I_{1u} - B)^2 = \frac{R}{S_0} - R^2$$

$$B = \pm \sqrt{\frac{R}{S_0} - R^2} + I_{1u}$$

$$B = 5,8 \cdot 10^{-3} \Rightarrow L = 27,45 \text{ mH}$$

$$\text{From (1)} \Rightarrow L = \frac{1}{2 \cdot \pi \cdot f \cdot B}$$


$$A = \frac{B - I_{1u}}{B^2 + (I_{1u} - B)^2}$$

$$A = 61,23 \Rightarrow C = \frac{1}{2 \cdot \pi \cdot f \cdot A} =$$


$$C = 2,6 \text{ pF}$$

Matching: Problem 3

Using the Smith chart, design a matching network with lumped elements (L and C) as shown below which transforms the load impedance Z_{Load} into the input impedance Z_{IN} .

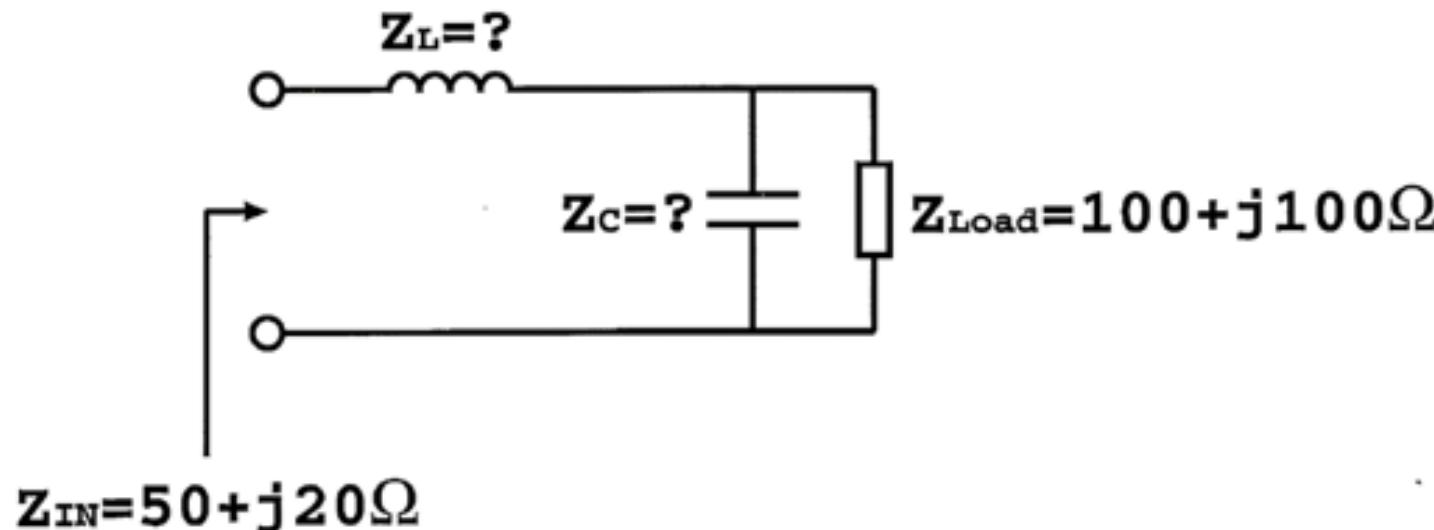

Probklem 3: solution

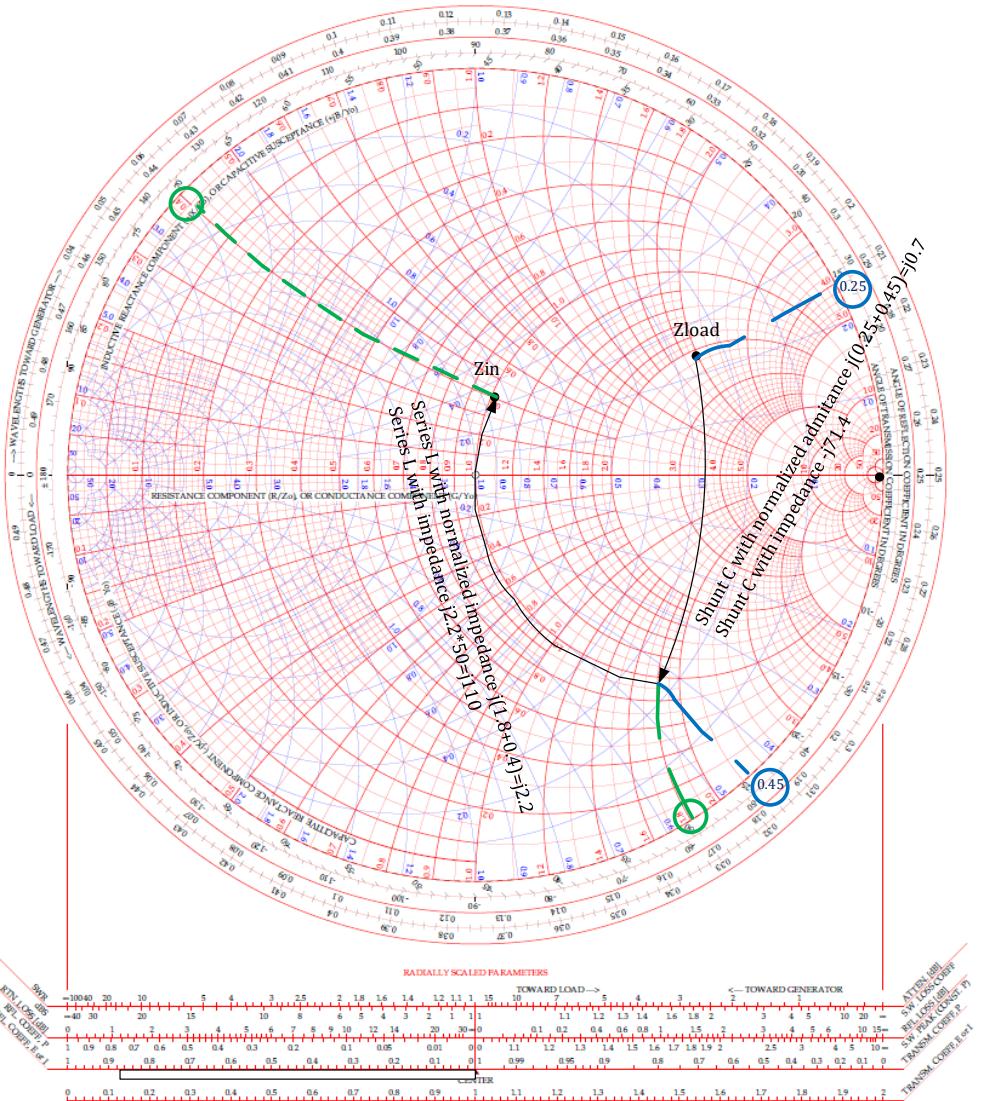

Shunt C with normalized admittance $j(0.25+0.45)=j0.7$

Shunt C with impedance $(1/j0.7)*50=-j71.4$

Series L with normalized impedance $j(1.8+0.4)=j2.2$

Series L with impedance $j2.2*50=j110$

Amplifier design: Similar as example 12.1 book of Pozar

A microwave transistor has the following S parameters at 10 GHz, with a 50Ω reference impedance:

$$S_{11} = 0.45 \angle 150^\circ$$

$$S_{12} = 0.01 \angle -10^\circ$$

$$S_{21} = 2.05 \angle 10^\circ$$

$$S_{22} = 0.40 \angle -150^\circ$$

The source impedance is $Z_S = 20\Omega$ and the load impedance is $Z_L = 30\Omega$. Compute the power gain, the available gain, and the transducer power gain.

Amplifier design

Similar as example 12.1 book of Pozar - Solution

Example 11.1, book of Pozar, page 539

$$S_{11} = 0.45 e^{j180^\circ} = 0.45 e^{j180^\circ}$$

$$S_{12} = 0.01 e^{j10^\circ}$$

$$S_{21} = 2.05 e^{j10^\circ}$$

$$S_{22} = 0.4 e^{-j150^\circ}$$

$$T_S = 20 \Omega$$

$$Z_L = 30 \Omega$$

$$Z_0 = 50 \Omega$$

$$\text{Power gain} = G = |S_{21}|^2 \left(1 - \frac{|T_S|^2}{|1 - S_{11} T_S|^2} \right)$$

$$\text{Available power gain} = G_A = \frac{|S_{21}|^2 (1 - |T_S|^2)}{|1 - S_{11} T_S|^2 (1 - |T_{out}|^2)}$$

~~$$\text{Transducer power gain} = G_T = \frac{|S_{21}|^2 (1 - |T_S|^2) (1 - |T_L|^2)}{|1 - T_S T_M|^2 |1 - S_{22} T_L|^2}$$~~

[S] parameters are known

$$T_L = ? , T_S = ? , T_{out} = ? , T_M = ?$$

$$T_L = \frac{T_S - Z_0}{T_S + Z_0} = -0.250$$

$$T_S = \frac{Z_S - Z_0}{Z_S + Z_0} = -0.429$$

$$T_{out} = S_{22} + \frac{S_{12} S_{21} T_S}{1 - S_{11} T_S} = 0.408 e^{j151^\circ}$$

~~$$T_M = S_{11} + \frac{S_{12} S_{21} T_L}{1 - S_{22} T_L} = 0.408 e^{j151^\circ}$$~~

$$T_{out} = 0.408 e^{-j151^\circ}$$

$$T_M = 0.455 e^{j150^\circ}$$

$$G = 5.39$$

$$G_A = 5.85$$

$$G_T = 5.49$$

Amplifier design: Example 3.4.1 book of Gonzalez

The S parameters of a BJT measured at $V_{CE} = 10$ V, $I_C = 30$ mA, and $f = 1$ GHz, in a $50\text{-}\Omega$ system are

$$S_{11} = 0.73 \angle 175^\circ$$

$$S_{12} = 0$$

$$S_{21} = 4.45 \angle 65^\circ$$

$$S_{22} = 0.21 \angle -80^\circ$$

- (a) Calculate the optimum terminations.
- (b) Calculate $G_{s,\max}$, $G_{L,\max}$, and $G_{TU,\max}$ in decibels.
- (c) Draw several G_s constant-gain circles.
- (d) Design the input matching network for $G_s = 2$ dB.

Example 3.4.1 book of Gonzalez – Solution (1/3)

Example 3.4.1, book of Gonzalez, page 132

$f = 1 \text{ GHz}$

$S_{11} = 0.73 e^{j 175^\circ}$

$S_{12} = 0 \rightarrow \text{unilateral case}$

$S_{21} = 4.45 e^{j 65^\circ}$

$S_{22} = 0.21 e^{j -80^\circ}$

$\Gamma_T = \frac{1 - |\Gamma_S|^2}{1 - |S_{11}\Gamma_L|^2} \quad |S_{11}|^2 \quad \frac{1 - |\Gamma_L|^2}{1 - |S_{22}\Gamma_L|^2}$

Γ_S Γ_L

1) Γ_{max} / conjugate match at input, output
 $\Rightarrow \Gamma_{\text{in}} = \Gamma_S^* \quad \Gamma_{\text{out}} = \Gamma_L^*$

$\Gamma_{S\text{max}} = \frac{1 - |\Gamma_S|}{(1 - |\Gamma_S|^2)^2} = \frac{1}{1 - |\Gamma_S|^2}$


$\Gamma_{T\text{max}} = \frac{1}{1 - |\Gamma_S|^2} \quad |S_{21}|^2 \quad \frac{1 - |\Gamma_L|^2}{1 - |S_{22}\Gamma_L|^2}$

$\Gamma_S^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - |S_{22}\Gamma_L|^2}$

$\Gamma_L^* = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - |S_{11}\Gamma_S|^2}$

$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$

$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$

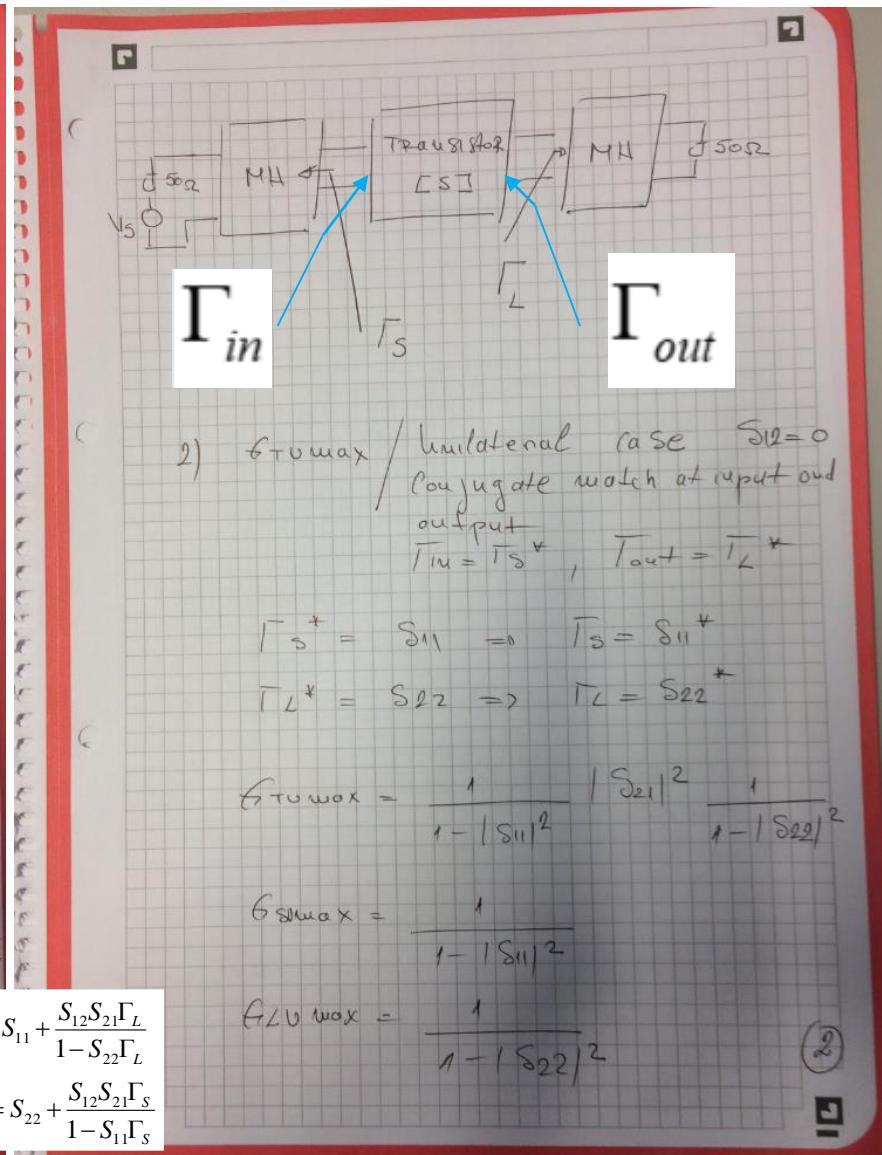

Example 3.4.1 book of Gonzalez – Solution (2/3)

a) optimum terminations \rightarrow
unilateral case $S_{12} = 0 \rightarrow$

$$T_S = S_{11}^* = 0.73 e^{-j175}$$

$$T_L = S_{22}^* = 0.21 e^{+j80}$$

b) $f_{S0\max} = \frac{1}{1 - |S_{11}|^2} = 2.191$

$$f_{S0\max} [dB] = 10 \log f_{S0\max} = 3.31 dB$$

$$f_{G0\max} = \frac{1}{1 - |S_{22}|^2} = 1.046$$

$$f_{G0\max} [dB] = 0.195$$

$$G_0 = |S_{21}|^2 = 13.8$$

$$G_0 [dB] = 12.97 dB$$

$$f_{TU,\max} = 16.47 dB = f_{S0\max} + G_0 +$$

$G_{G0\max} \rightarrow$
all in dB

c) $G_S = 2 dB \rightarrow$ in dB

$$G_S = 1.59$$

$$g_S = \frac{G_S}{G_{S0\max}} = \frac{1.59}{2.191} = 0.73$$

$$C_S = \frac{g_S \cdot S_{11}^*}{1 - (1 - g_S) |S_{11}|^2}$$

$$R_S = \frac{(1 - g_S) (1 - |S_{11}|^2)}{1 - (1 - g_S) |S_{11}|^2}$$

$$C_S = 0.625 e^{j - 175}$$


$$R_S = 0.279$$

Example 3.4.1 book of Gonzalez – Solution (3/3)

$f=1\text{GHz}$

$$\begin{aligned}2\pi f C / 0.02 &= 1.2 \\C = 1.2 * 0.02 / (2\pi f) &\\C &= 3.82 \mu\text{F}\\Z_c = j1 / (2\pi f C) &= -41.7 \Omega\end{aligned}$$
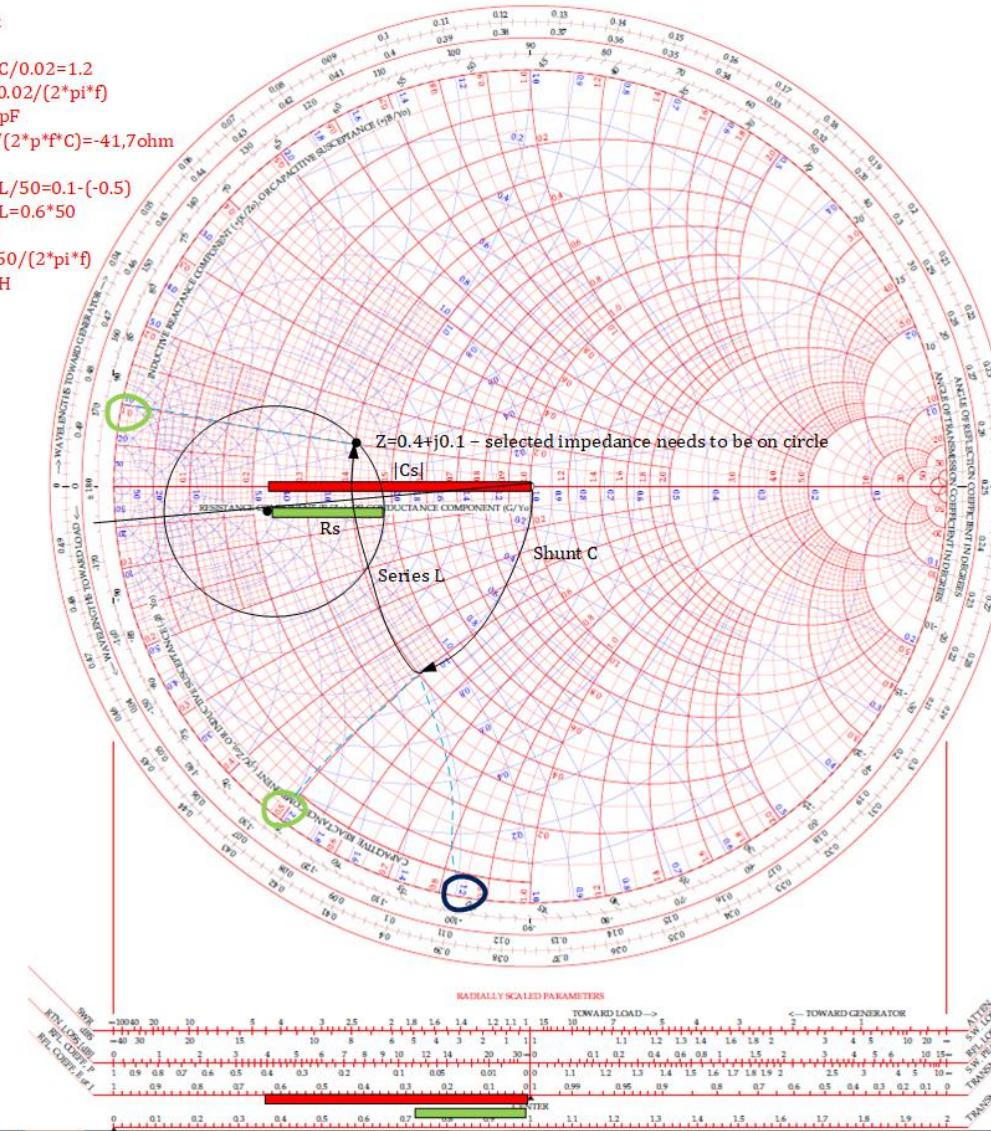
$$\begin{aligned}2\pi f L / 50 &= 0.1 - (-0.5) \\2\pi f L &= 0.6 * 50 \\Z_l &= 30 \\L = 0.6 * 50 / (2\pi f) &\\L &= 4.7 \text{nH}\end{aligned}$$



Amplifier design: problem 4

A microwave amplifier design is to be designed for $G_{TU,\max}$ using a transistor with

$$S_{11}=0.5, \angle 140^\circ$$

$$S_{12} = 0$$

$$S_{21}=5, \angle 45^\circ$$

$$S_{22}=0.6, \angle -95^\circ$$

The S-parameters were measured in a 50Ω system at $f=900 \text{ MHz}$, $V_{CE} = 15 \text{ V}$, and $I_C = 15 \text{ mA}$.

- a) Determine whether this amplifier is unconditionally stable.
- b) Determine $G_{TU,\max}$. Express your answer in dB.
- c) Determine the optimum source impedance and the optimum load impedance for maximum gain. Illustrate your answer in the Smith chart.
- d) Design a 2-element matching network at the input and a 2-element matching network at the output of the amplifier to reach conjugate matching to a 50Ω source and load impedance. Illustrate your answer on the Smith chart.
- e) Calculate the constant gain circle for $G_L=1\text{dB}$ and indicate it in the Smith chart.

Amplifier design: Problem 4 - solution (1/5)

P_{Z_0} case

$$S_{11} = 0.5 e^{j40^\circ}$$

$$S_{12} = 0$$

$$S_{21} = 5 e^{j45^\circ}$$

$$S_{22} = 0.6 e^{j-95^\circ}$$

a) $\Delta = S_{11} S_{22} - S_{12} \cdot S_{21} < 1$

$$K_S = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + \Delta^2}{2 \cdot |S_{12} \cdot S_{21}|} > 1$$

~~For~~ $|S_{11}| < 1$ $|S_{22}| < 1$ $\left| \begin{array}{l} \text{unilateral case} \\ \text{general case} \end{array} \right.$

Conditions for unconditional stability

$S_{12} = 0$, unilateral case

$|S_{11}| = 0.5 < 1$, $|S_{22}| = 0.6 < 1 \rightarrow$ ~~unconditionally stable~~ \rightarrow ~~unconditionally stable~~

b) $f_{TUMAX} = 1/f_{LL}$


f_{TUMAX} / unilateral case $S_{12} = 0$

$$f_{TUMAX} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

$$f_S = S_{11}^*$$


$$f_L = S_{22}^*$$

(1)

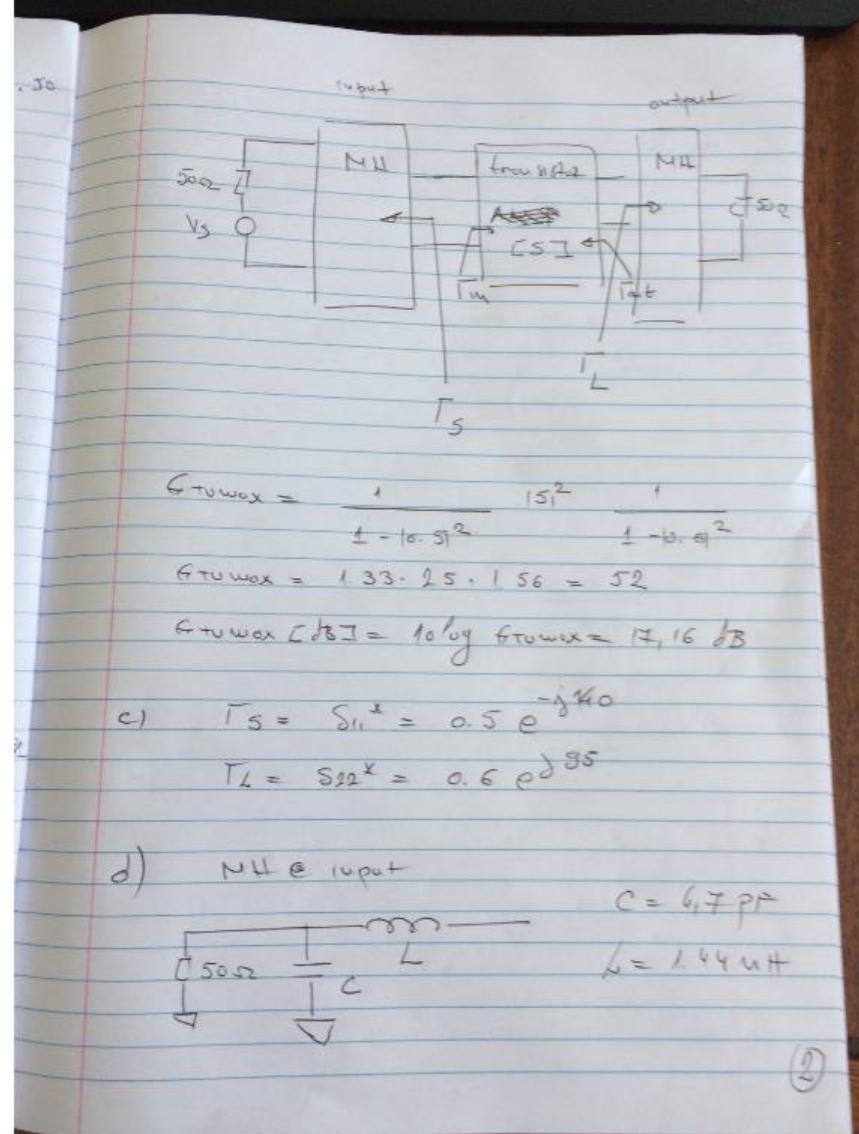

Amplifier design: Problem 4 - solution (2/5)

Matching at output

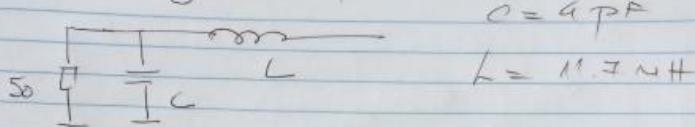

c) $f_L = 1 \text{ dB} \Rightarrow f_L = 126$

$$g_{Lwox} = \frac{1}{1 - |S_{22}|^2} = 1.56$$

$$j\beta = \frac{f_L}{f_{Lwox}} = 0.8$$

$$C_L = \frac{g_L \cdot S_{22}^*}{1 - (1 - j\beta) |S_{22}^*|^2}$$

$$R_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - j\beta) |S_{22}|^2}$$

$$C_L = \frac{0.8 \cdot 0.6 e^{j95}}{1 - (1 - 0.8)(0.6)^2}$$

$$C_L = \frac{0.48 e^{j95}}{0.528}$$


$$\boxed{C_L = 0.52 e^{j95}}$$

$$R_L = \frac{\sqrt{1 - 0.8} (1 - 0.6^2)}{1 - (1 - 0.8)(0.6)^2}$$


$$R_L = \frac{0.286}{0.528}$$

$$\boxed{R_L = 0.31}$$

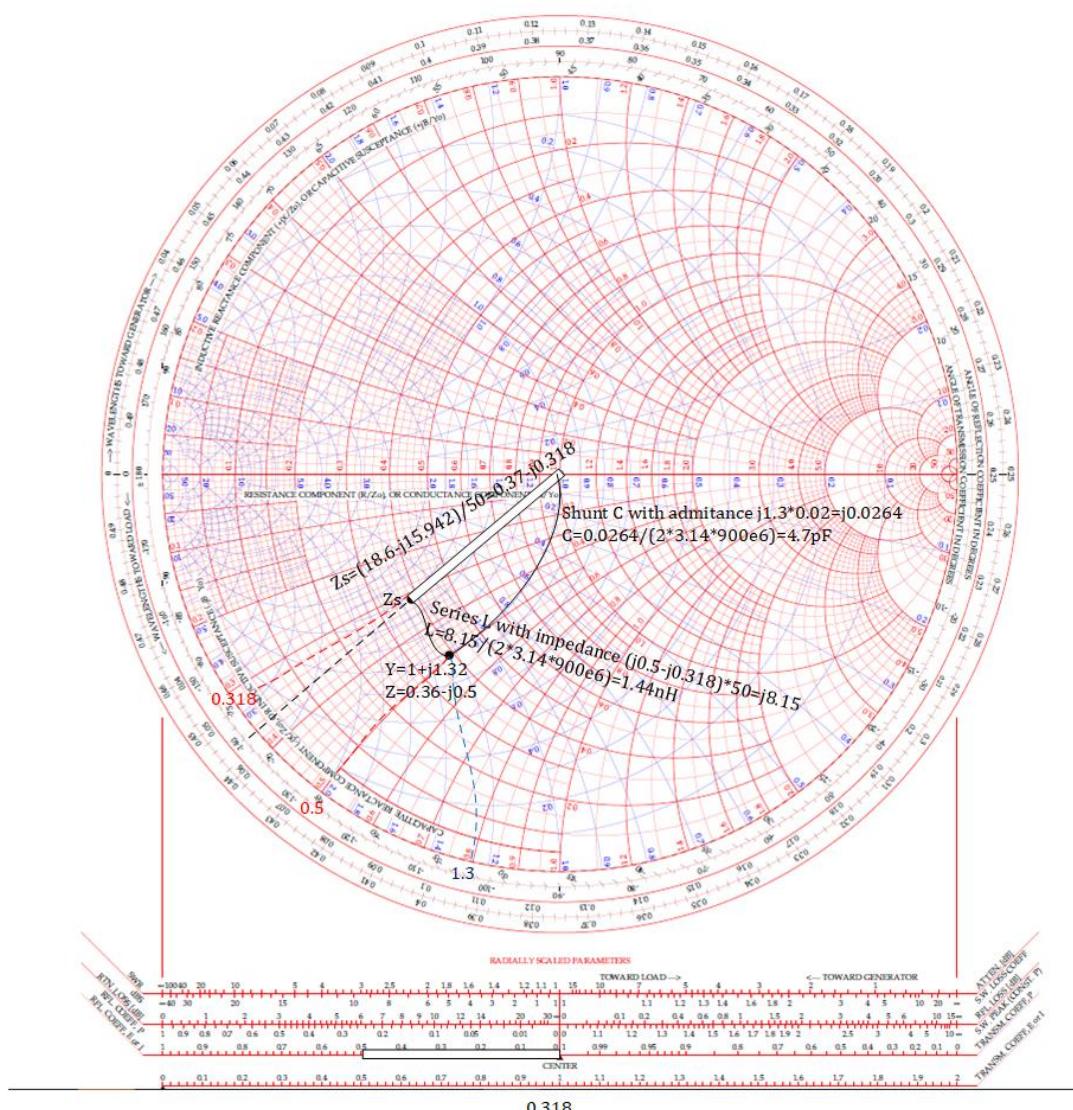
Amplifier design: Problem 4 - solution, input matching (3/5)



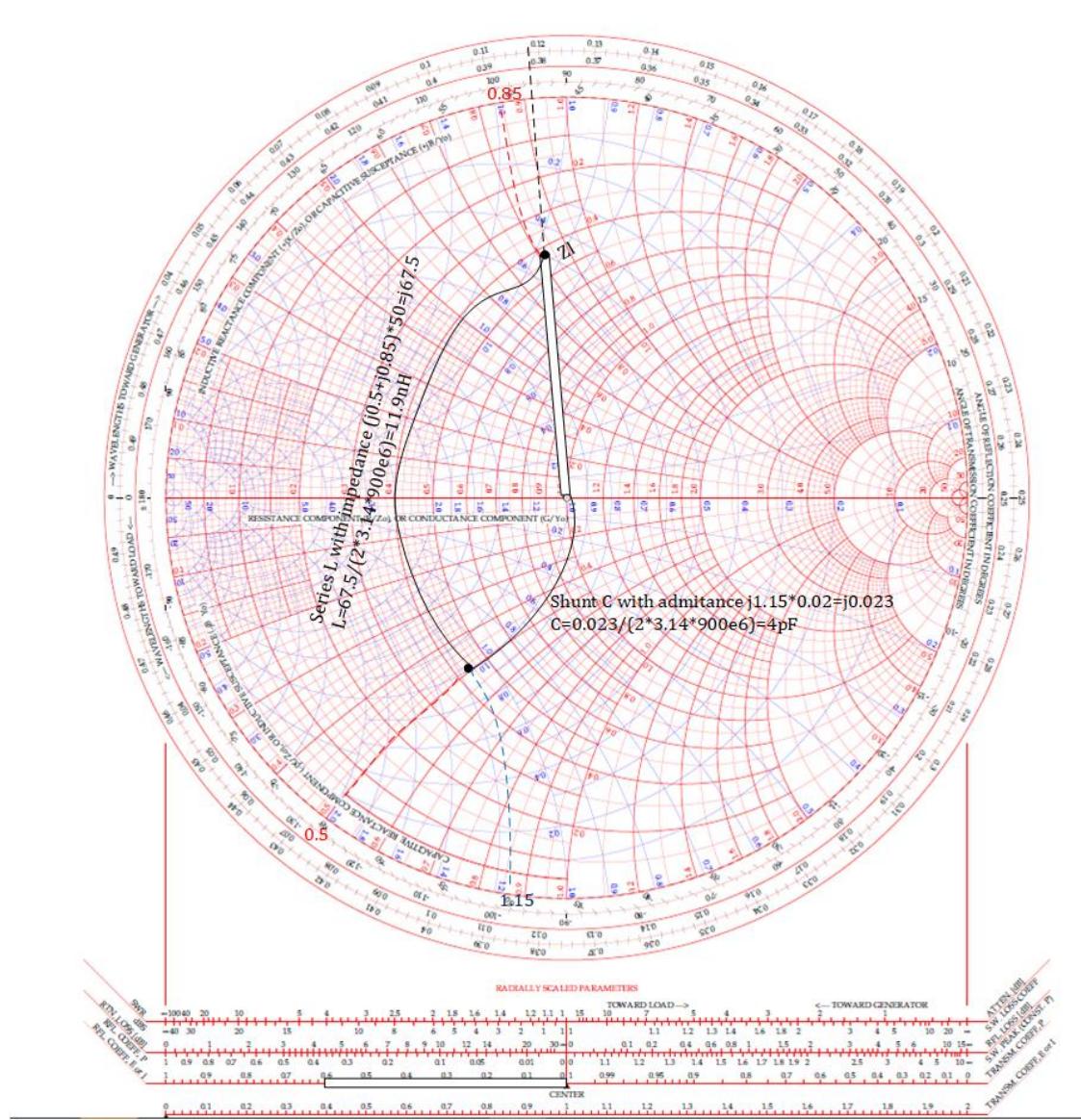Amplifier design: problem 4 - solution, output matching (4/5)



Amplifier design: problem 4 - solution, output matching (5/5)

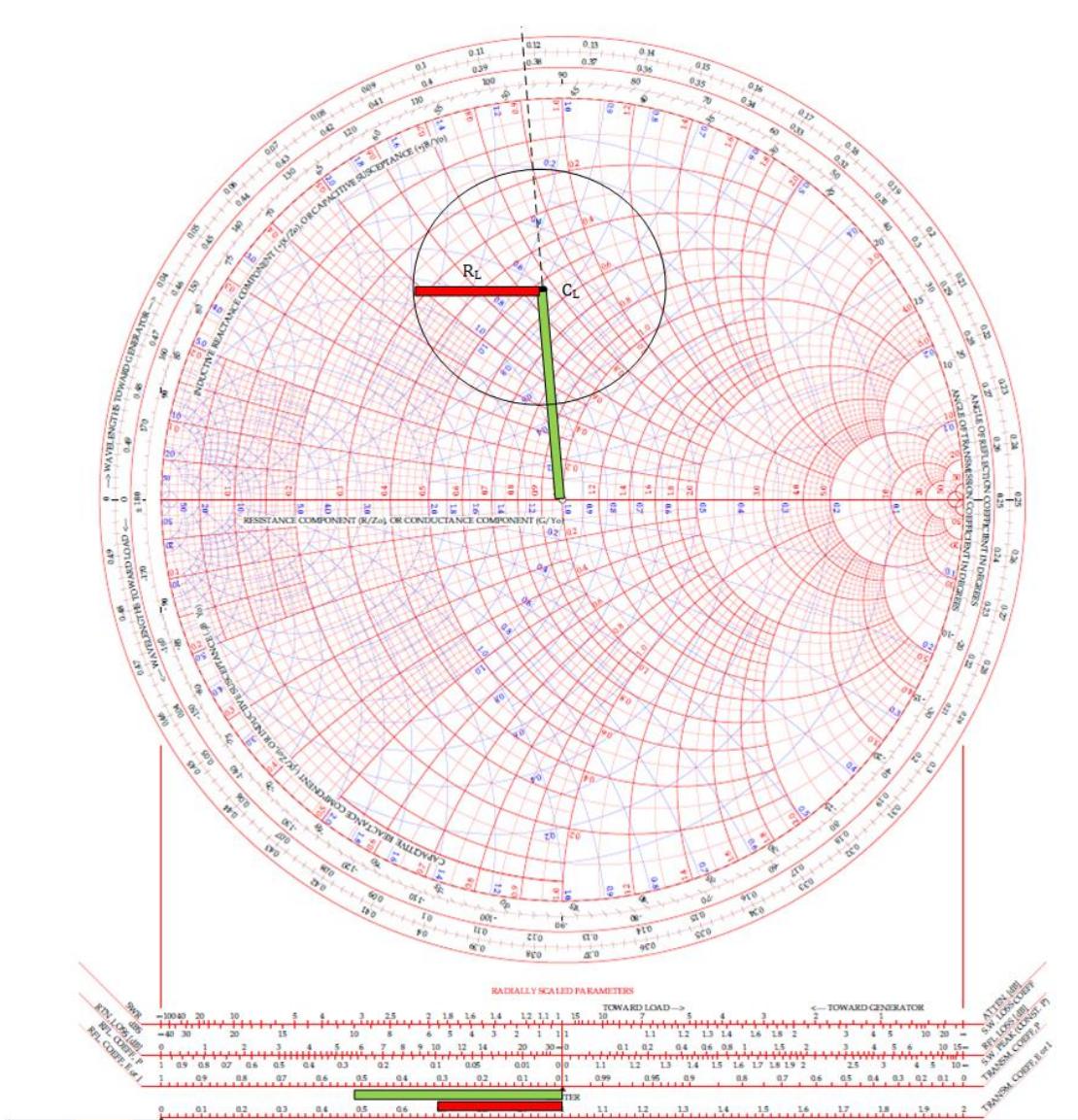

Problem 5 – will be in assignment

A microwave amplifier is to be designed for $G_{TU,\max}$ using a bipolar transistor with:

$$S_{11}=0.4, \angle 130^\circ$$

$$S_{12} = 0$$

$$S_{21}=6, \angle 40^\circ$$

$$S_{22}=0.7, \angle -75^\circ$$

The S-parameters were measured in a 50Ω system at $f=1$ GHz, $V_{CE} = 15$ V, and $I_C = 15$ mA.

- a) Determine whether this amplifier is unconditionally stable.
- b) Determine $G_{TU,\max}$. Express your answer in dB.
- c) Determine the optimum source impedance and the optimum load impedance for maximum gain. Illustrate your answer in the Smith chart.
- d) Design a 2-element matching network at the input and a 2-element matching network at the output of the amplifier to reach conjugate matching to a 50Ω source and load impedance. Illustrate your answer on the Smith chart.
- e) Calculate the constant gain circle for $G_L=1.5$ dB and indicate it in the Smith chart.

Amplifier design

Similar as example 12.2 book of Pozar

The S parameters for the HP HFET-102 GaAs FET at 2 GHz with a bias voltage $V_{gs} = 0$ are given as follows ($Z_0 = 50 \Omega$):

$$S_{11} = 0.894 \angle -60.6^\circ,$$

$$S_{21} = 3.122 \angle 123.6^\circ,$$

$$S_{12} = 0.020 \angle 62.4^\circ,$$

$$S_{22} = 0.781 \angle -27.6^\circ.$$

Determine the stability of this transistor by calculating K and $|\Delta|$, and plot the stability circles.

Amplifier design

Example 11.2 book of Pozar - Solution

From (11.31) and (11.24) we compute K and $|\Delta|$ as

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 0.696 \angle -83^\circ,$$

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2|S_{12}S_{21}|} = 0.607.$$

We have $|\Delta| = 0.696 < 1$, but $K < 1$, so the device is potentially unstable. The centers and radii of the stability circles are given by (11.28) and (11.29);

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} = 1.361 \angle 47^\circ,$$

$$R_L = \frac{|S_{12}S_{21}|}{|S_{22}|^2 - |\Delta|^2} = 0.50,$$

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} = 1.132 \angle 68^\circ,$$


$$R_S = \frac{|S_{12}S_{21}|}{|S_{11}|^2 - |\Delta|^2} = 0.199.$$

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

$\Gamma_{in} = S_{11}$ for $\Gamma_L = 0, |S_{11}| < 1$

$\Gamma_{out} = S_{22}$ for $\Gamma_S = 0, |S_{22}| < 1$

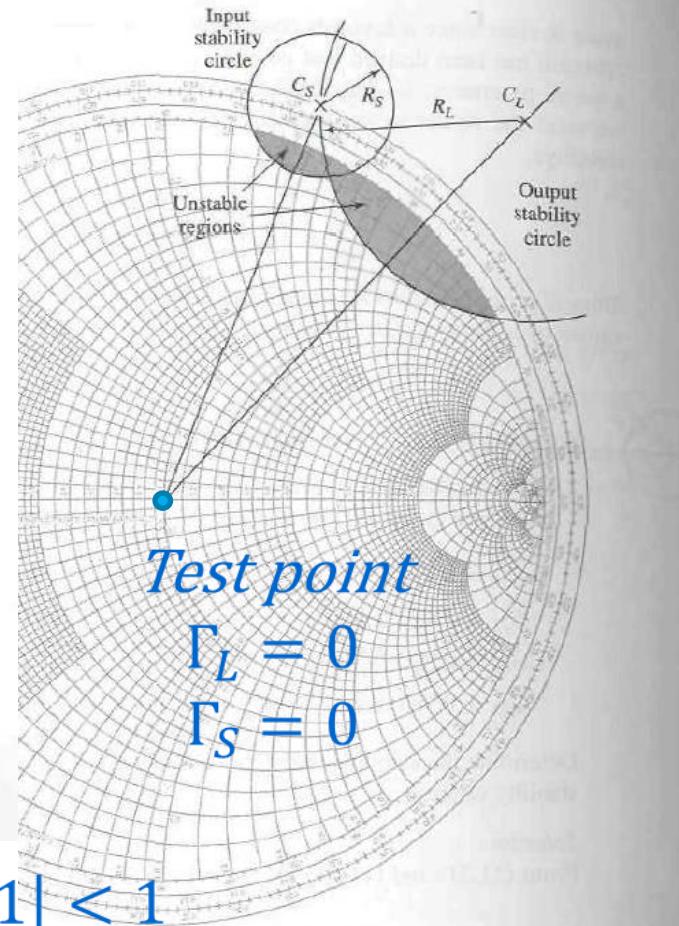

Amplifier design: problem 5

The S-parameters and the noise parameters of a transistor at 1 GHz are

$$S_{11} = 0.76 \angle -160^\circ$$

$$F_{\min} = 2.2 \text{ dB}$$

$$S_{12} = 0$$

$$\Gamma_{\text{opt}} = 0.5 \angle -150^\circ$$

$$S_{21} = 5.01 \angle 85^\circ$$

$$r_n = 6.6 \Omega$$

$$S_{22} = 0.508 \angle -20^\circ$$

- a) Proof that the transistor is unconditionally stable.
- b) How must the source reflection coefficient Γ_S and load reflection coefficient Γ_L be chosen to achieve maximum transducer power gain $G_{\text{TU},\max}$. Calculate the required Γ_S and Γ_L and indicate them on the Smith chart. What are the corresponding values of the source impedance Z_S and the load impedance Z_L ?
- c) For the case of conjugate matching at the input side of the transistor, design an input matching network consisting of an inductor and a capacitor. Calculate the value of the inductance L and the capacitance C required for this network. Illustrate your answer on the Smith chart.
- d) Determine the maximum transducer power gain $G_{\text{TU},\max}$. Give your answer in dB.
- e) For the case that the input matching network is not conjugately matched, calculate the constant gain circle that will lead to a 3 dB lower $G_{\text{TU},\max}$. Draw this constant gain circle on the Smith chart.
- f) Calculate the center and the radius of the 3 dB constant noise figure circle. Draw the 3 dB constant noise figure circle on the Smith chart.

Amplifier design: problem 5 – solution a)

a) $|A| = |\hat{S}_{11} \hat{S}_{22} - \hat{S}_{12} \cdot \hat{S}_{21}| < 1$

$|A| = |0.26 e^{-j160^\circ} \cdot 0.508 e^{-j20^\circ}|$

$|A| = 0.386 < 1 \rightarrow \text{OK}$

$K = \infty > 1 \rightarrow \text{OK}$

$|\hat{S}_{11}| < 1 \Rightarrow 0.76 < 1 \rightarrow \text{OK}$

$|\hat{S}_{22}| < 1 \Rightarrow 0.508 < 1 \rightarrow \text{OK}$

} unilateral case

b) $\epsilon_{TU \max}$ / unilateral case $\hat{S}_{12} = 0$


$$\epsilon_{TU \max} = \frac{1}{1 - |\hat{S}_{11}|^2} \quad |\hat{S}_{21}|^2 \quad \frac{1}{1 - |\hat{S}_{22}|^2}$$

$\Gamma_s = \hat{S}_{11}^* = 0.76 e^{j160^\circ}$

$\Gamma_b = \hat{S}_{22}^* = 0.508 e^{j20^\circ}$

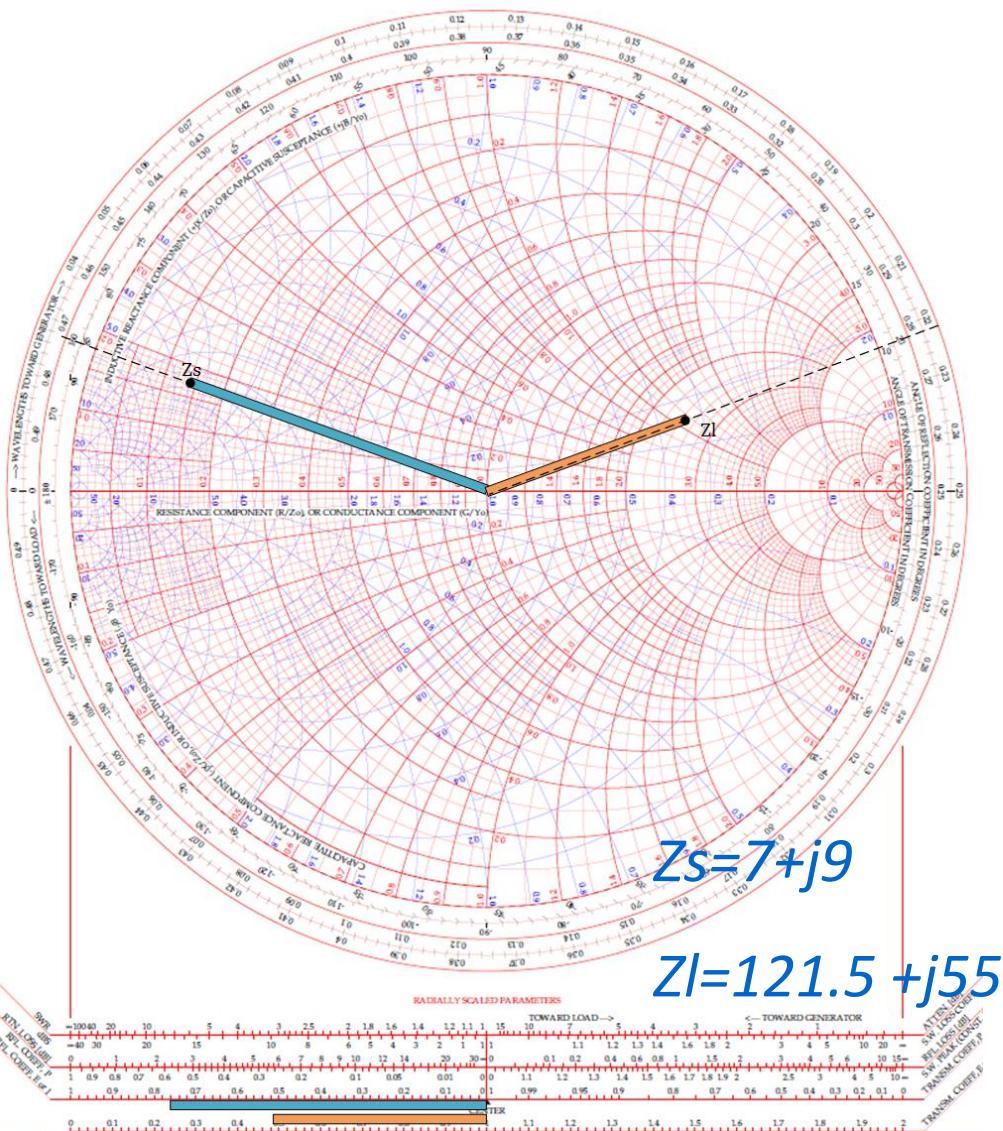(1)

Amplifier design: problem 5 – solution b)



$$\Gamma_s = \frac{Z_s - Z_0}{Z_s + Z_0}$$

$$\Gamma_s (Z_s + Z_0) = Z_s - Z_0$$

$$\Gamma_s Z_s - Z_s = -Z_0 - \Gamma_s Z_0$$

$$Z_s (1 + \Gamma_s) = -Z_0 (1 + \Gamma_s)$$

$$Z_s = Z_0 \cdot \frac{1 + \Gamma_s}{1 - \Gamma_s}$$

$$Z_L = Z_0 \cdot \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

$$Z_s = Z_0 \frac{1 + 0.76 e^{j160^\circ}}{1 - 0.76 e^{j160^\circ}} = Z_0 \frac{1 - 0.76 + j0.26}{1 + 0.76 - j0.26}$$


$$Z_s = Z_0 \frac{0.286 + j0.16}{1.71 - j0.26} = \frac{1.71 + j0.26}{1.71 + j0.26}$$

$$Z_s = Z_0 \frac{0.92 + j0.52}{3} = Z_0 (0.14 + j0.18)$$

$$Z_L = Z_0 \frac{1 + 0.508 e^{j20^\circ}}{1 - 0.508 e^{j20^\circ}} = Z_0 \frac{1.47 + j0.17}{0.52 - j0.17}$$

$$Z_L = Z_0 \frac{0.73 + j0.33}{0.3} = Z_0 \frac{2.43 + j1.12}{0.3}$$

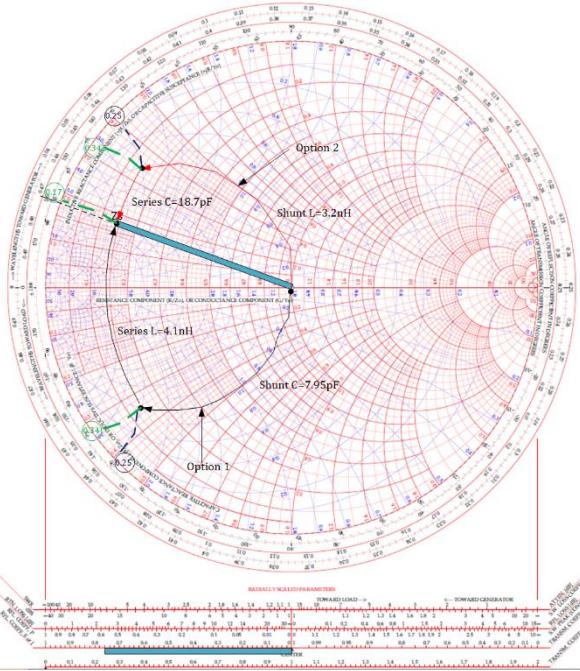Amplifier design: problem 5 – solution c)



c) option 1

Diagram of the circuit:

$$\frac{Z_{in}}{Z_0} = \frac{j \cdot 2.5 - j \frac{2\pi f C}{0.02}}{j \cdot 2.5 + j \frac{2\pi f L}{50}} = \frac{C}{L} = \frac{7.95 \text{ pF}}{4.1 \text{ nH}}$$

$$f = 1 \text{ GHz}$$

$$Z_{in} = j \left(0.34 + j 18 \right) = j \frac{2\pi f L}{50} = 4.1 \text{ nH}$$

c) option 2

Diagram of the circuit:

$$\frac{Z_{in}}{Z_0} = \frac{-j \frac{1}{wL}}{1 + j \frac{1}{wL}} = \frac{-j \frac{1}{0.02 wL}}{1 + j \frac{1}{0.02 wL}}$$
~~$$Z_{in} = -j \frac{1}{0.02 \cdot 2\pi f L} = -j \frac{1}{0.02 \cdot 2\pi \cdot 1 \text{ GHz} \cdot L}$$~~

$$\cancel{Z_{in}} = -j 2.5 = -j \frac{1}{0.02 \cdot 2\pi \cdot f \cdot L}$$

$$L = 3.2 \text{ nH}$$

$$Z_{in} = -j \frac{1}{50 wC} = -j \frac{1}{50 \cdot 2\pi \cdot f \cdot C}$$

$$Z_{in} = +j (0.17 - 0.39) - j \frac{1}{50 \cdot 2\pi \cdot f \cdot C}$$

$$C = 18.7 \text{ pF} \quad 18.7 \text{ pF}$$

35

Amplifier design: problem 5 – solution d)

$$G_{TU \text{ max}} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$
$$G_{TU \text{ max}} = 2,36 \cdot 25,1 \cdot 1,39$$
$$G_{TU \text{ max}} = 79,9$$
$$\boxed{G_{TU \text{ max}} [dB] = 19 dB}$$

Amplifier design: problem 5 – solution e)

$$e) G_{s,max} = \frac{1}{1-|S_{11}|^2} = 2.36$$

$$G_{s,max} = 3.73 \text{ dB}$$

$$G_s \text{ required} = G_{s,max} - 3 \text{ dB}$$

$$G_s \text{ required} = 0.73 \text{ dB}$$

$$G_s \text{ required} = 1.18$$

$$g_s = \frac{1.18}{k_3} = 0.5$$


$$C_S = \frac{0.5 \cdot S_{11}}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_S = \frac{0.5 \cdot 0.73 e^{j160^\circ}}{1 - (1 - 0.5) \cdot 0.73^2} = 0.53 e^{j160^\circ}$$

$$P_S = \frac{|1 - g_s (1 - |S_{11}|^2)|}{1 - (1 - g_s) |S_{11}|^2} = 0.92$$

~~$$P_S = \frac{1}{0.73}$$~~

(16)

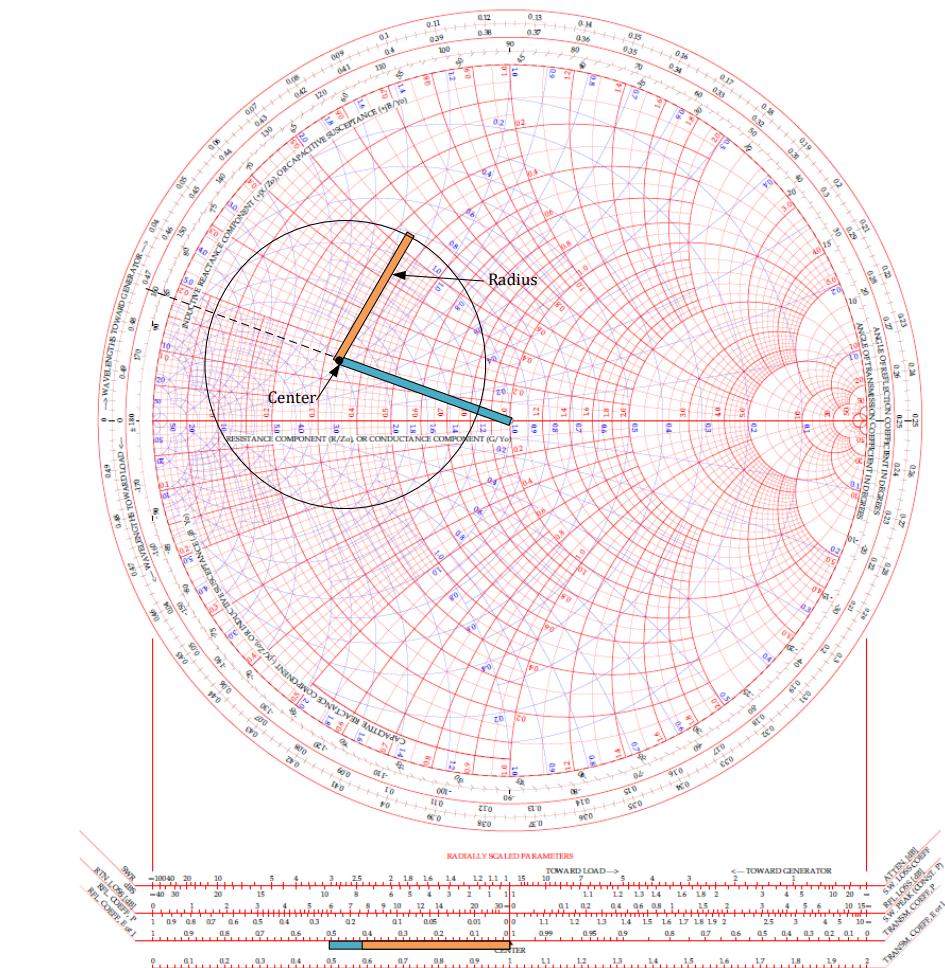

Amplifier design: problem 5 – solution f)

f) $H = \frac{(F - F_{\text{min}})}{4 \pi} \sqrt{1 + T_{\text{opt}}^2}$

$r_o = 6.6$
 $T_{\text{opt}} = 0.5 e^{-j150}$
 $F_{\text{min}} = 2.2 \text{ dB} \Rightarrow F_{\text{min}} = 1.66$
 $F = 3 \text{ dB} \Rightarrow F = 2$

$H = \frac{(2 - 1.66)}{4 \cdot 6.6} \sqrt{1 + 0.5 \cos 150 - j 0.586}$


$H = \frac{0.34 \cdot |0.56 - j 0.25|}{4 \cdot 6.6}$

$H = \frac{0.34 \cdot 0.38}{4 \cdot 6.6} = 4.8 \cdot 10^{-3}$

$C_F = \frac{T_{\text{opt}}}{1+H} = \frac{0.497 e^{-j150}}{1+H}$

$R_F = \frac{1}{H+1} \sqrt{V^2 + V(1 - |T_{\text{opt}}|^2)}$

$R_F = 0.06$

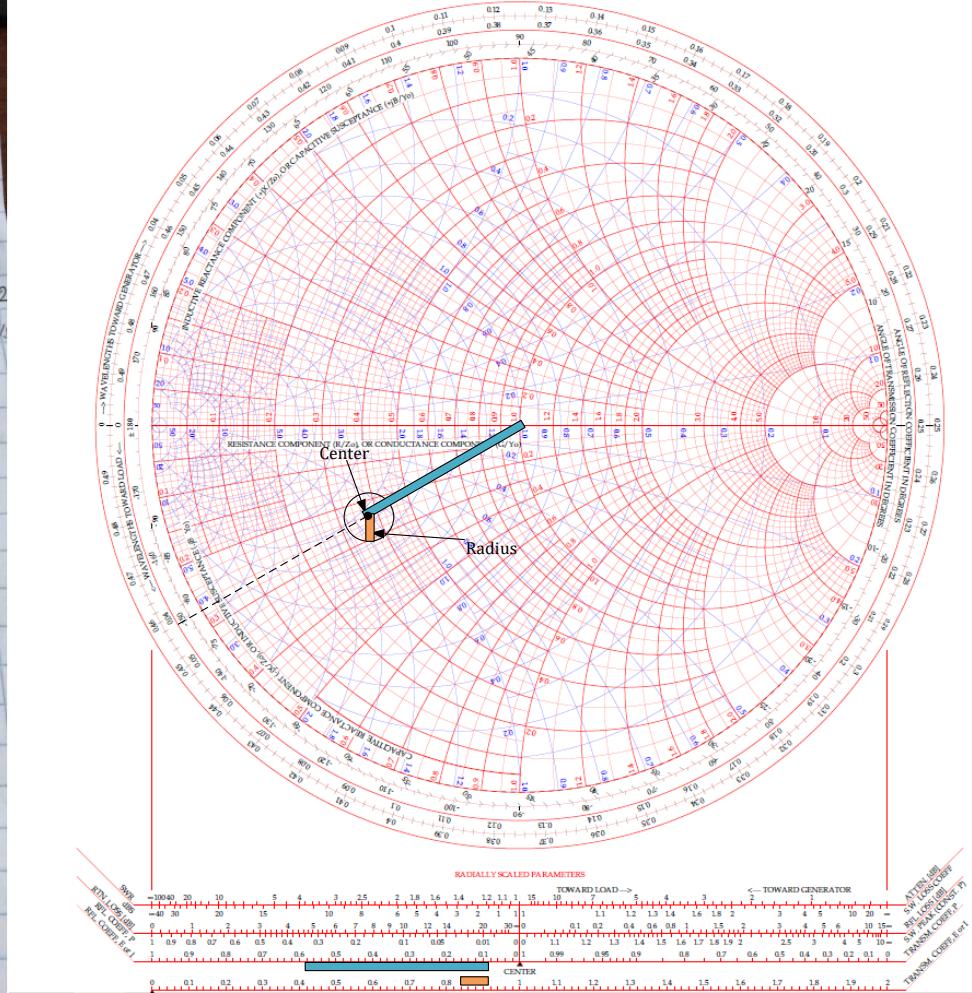

Example 11.5 book of Pozar

A GaAs FET is biased for minimum noise figure, and has the following S parameters and noise parameters at 4 GHz ($Z_0 = 50 \Omega$): $S_{11} = 0.6/-60^\circ$, $S_{21} = 1.9/81^\circ$, $S_{12} = 0.05/26^\circ$, $S_{22} = 0.5/-60^\circ$; $F_{\min} = 1.6 \text{ dB}$, $\Gamma_{\text{opt}} = 0.62/100^\circ$, $R_N = 20 \Omega$. For design purposes, assume the device is unilateral, and calculate the maximum error in G_T resulting from this assumption. Then design an amplifier having a 2.0 dB noise figure with the maximum gain that is compatible with this noise figure.

Example 11.4 book of Pozar – solution (1/2)

Next, we use (11.59) and (11.61) to compute the center and radius of the 2 dB noise figure circle:

$$N = \frac{F - F_{\min}}{4R_N/Z_0} |1 + \Gamma_{\text{opt}}|^2 = \frac{1.58 - 1.445}{4(20/50)} |1 + 0.62 \angle 100^\circ|^2 \\ = 0.0986,$$

$$C_F = \frac{\Gamma_{\text{opt}}}{N + 1} = 0.56 \angle 100^\circ$$

$$R_F = \frac{\sqrt{N(N + 1 - |\Gamma_{\text{opt}}|^2)}}{N + 1} \approx 0.24.$$

This noise figure circle is plotted in Figure 11.15a. Minimum noise figure ($F_{\min} = 1.6$ dB) occurs for $\Gamma_S = \Gamma_{\text{opt}} = 0.62 \angle 100^\circ$.

Next we calculate data for several input section constant gain circles. From (11.52),

G_S (dB)	g_s	C_S	R_S
1.0	0.805	$0.52 \angle 60^\circ$	0.300
1.5	0.904	$0.56 \angle 60^\circ$	0.205
1.7	0.946	$0.58 \angle 60^\circ$	0.150

These circles are also plotted in Figure 11.15a. We see that the $G_S = 1.7$ dB gain circle just intersects the $F = 2$ dB noise figure circle, and that any higher gain will result in a worse noise figure. From the Smith chart the optimum solution is then $\Gamma_S = 0.53 \angle 75^\circ$, yielding $G_S = 1.7$ dB and $F = 2.0$ dB.

For the output section we choose $\Gamma_L = S_{22}^* = 0.5 \angle 60^\circ$ for a maximum G_L of

$$G_L = \frac{1}{1 - |S_{22}|^2} = 1.33 \approx 1.25 \text{ dB.}$$

The transistor gain is

$$G_0 = |S_{21}|^2 = 3.61 = 5.58 \text{ dB,}$$

