

Em2 - Part - 1 - Transmission lines - Scatter/transfer Matrices +
 (Matching and radio telescopes) - Slab waveguide - Antenna stub - Time-harmonic 1D waves

- Power Splitting/Matrices

$$\epsilon_0 = 8.85 \cdot 10^{-12}$$

$$\mu_0 = 4\pi \cdot 10^{-7}$$

characteristic impedance

- propagation speed: $v = \frac{1}{\sqrt{\epsilon_0 \mu}} = \frac{1}{\sqrt{LC}}$; • impedance: $z_0 = \sqrt{\frac{\epsilon_0}{\mu}} \sqrt{\frac{L}{C}} = 50 \Omega$ usm
- matched impedance: $z_L = 50 \Omega$; load impedance: z_L .
- $\Gamma = V^-/V^+ = \frac{z_L - z_0}{z_L + z_0}$ • matched: $z_L = z_0 \rightarrow \Gamma = 0$.
- open circuit: $z_L = \infty \rightarrow \Gamma = 1$ • short circuit: $z_L = 0 \rightarrow \Gamma = -1$.
- $T = 1 + \Gamma$

Circuit analysis of $t=0$, t , $t \geq \infty$

- z_g : source/generator impedance \rightarrow starts forward wave \rightarrow no reflection if $z_g = z_0$.
 \rightarrow at start of TL.
- z_0 : characteristic impedance \rightarrow wave prop \rightarrow intrinsic \rightarrow along TL.
- z_L : load/output impedance \rightarrow wave terminating \rightarrow no reflection if $z_L = z_0$
 \rightarrow end of TL.
- before $t=0$: no signal; $V=0$; $I=0$. $\rightarrow I^+ = \frac{Vg}{z_0 + z_g}$
- immediate after ON: V_g launch wave: $V^+ = \frac{z_0}{z_0 + z_g} V_g$ forward propagation
- after reflection occurs: $\Gamma = \frac{z_L - z_0}{z_L + z_0} \rightarrow$ backward propagation: $V^- = \frac{z_L}{z_L + z_0} V^+$ $\rightarrow V = \Gamma V^+$
- $V = V^+ + V^-$; $I = I^+ - I^- = \frac{V^+}{z_0} - \frac{V^-}{z_0} \rightarrow$ traveling V, I.
- $t \rightarrow \infty \rightarrow$ steady state \rightarrow no traveling wave $\rightarrow V_{\text{steady}} = \frac{z_L}{z_L + z_g} V_g$; I_{steady}
- Summary: $V(z, t) \rightarrow$ total field from wave V^+ , V^- superposition.

V^+ \rightarrow traveling wave components.

V_g \rightarrow generator/supply voltage.

V_{steady} \rightarrow final circuit value

• Standing wave ratio: $V_{\text{SWR}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$.

• during the stage of reflections if we know V , I can count to decompose:

$$V^+ = \frac{1}{2}(V + z_0 I); V^- = \frac{1}{2}(V - z_0 I)$$

↳ no need to memorize it's just derived from V, I eqs.

$$V = V^+ + V^-; I = \frac{1}{z_0}(V^+ - V^-) \rightarrow V + z_0 I = (V^+ + V^-) + (V^+ - V^-) = 2V^+$$

$$\rightarrow \frac{1}{2}(V + z_0 I) = V^+ //$$

• note: Steady State V_{st} can be decomposed into V^+ and V^- .

• when there is multiple transmission lines means there is $V_1^+, V_1^-; V_2^+, V_2^-$

$$\boxed{V_{\text{steady}} = \frac{V_g}{z_0 + z_g}}$$


Bounce diagrams and time voltage plots

1. • time period of bounce propagation: $t = \frac{1}{c}$

2. * reflection/transmission → calculated.

Plot:

e.g. 2TL [ms]

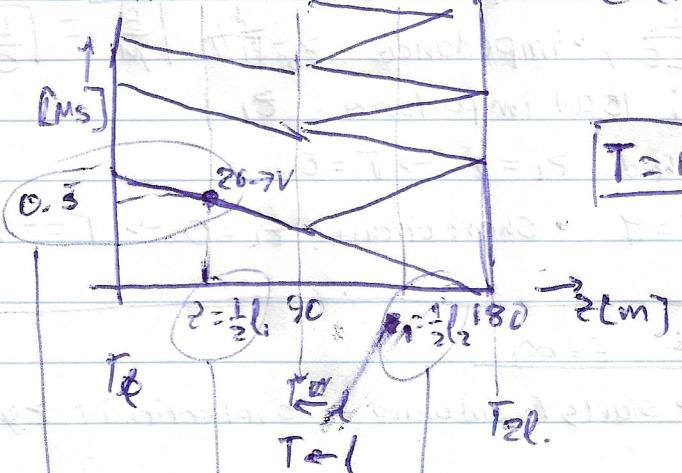

$T_d, \Gamma_{zL}, \Gamma_{dd}, \Gamma_{T_1}, \Gamma_{T_2}$

$$T = t + T$$

\downarrow

T_{T_1}

T_{T_2}

V

26.7V

$t + c$

0.5ms

$\rightarrow t [ns]$

voltage of half way plots.

Plot same

1. Plot per TL,

remember bounce diagram starts from where switch closes.

~~10% for power~~

~~10% for power losses~~

$$P_{loss} = |I|^2 \cdot 100\%$$

$$P_{gain} = |1 - |I|^2| \cdot 100\%$$

bounce diagram
start with V_{comp} .

↓ between drawing graph



you start with what's before

e.g. 4V before → $V_{comp} = 16V$

$$\text{so: } \begin{array}{c} 4V \xrightarrow{20\%} 4 + 25\mu s \\ \xrightarrow{25\mu s} 4 + 25\mu s \end{array} \rightarrow \boxed{6V}$$

• compensating voltage is afteroggle there is new voltage → V_{comp} is $V_{before} + V_{comp} = V_{after}$.

$$\text{eg: } V_{before} = 4V \rightarrow V_{after} = 20V \quad V_{comp} = +16V$$

Part 1

Scatter and Transfer Matrices - Matching

- Impedance matching (quarter-wave transformer).

$$- z_2 = \sqrt{z_1 z_3} \quad l = \frac{\lambda}{4} \rightarrow C = \lambda \cdot f \rightarrow l = \frac{\lambda}{f}$$

Z match of
Stub. z_{generator} z_{load} Only quarter wave stubs.

$$A\text{-matrix} \rightarrow A = D_1 T C_2 = \frac{1}{2} \begin{pmatrix} 1 & z_1 \\ 1 & -z_1 \end{pmatrix} \begin{pmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{pmatrix} \begin{pmatrix} 1 & -Y_2 \\ Y_2 & -1 \end{pmatrix}$$

can be multiple

↳ * Start with decomposition matrix

$$A = \begin{pmatrix} V_+ \\ V_- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & z_1 \\ 1 & -z_1 \end{pmatrix} \begin{pmatrix} V_+ \\ I_+ \end{pmatrix}$$

* decomposition matrix

$$\begin{pmatrix} V_+ \\ I_+ \end{pmatrix} = T_2 T_3 \begin{pmatrix} V_+ \\ I_+ \end{pmatrix} \rightarrow \text{e.g.}$$

$$\hookrightarrow A = \begin{pmatrix} V_+ \\ V_- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & z_1 \\ 1 & -z_1 \end{pmatrix} T_2 T_3 \begin{pmatrix} V_+ \\ I_+ \end{pmatrix}$$

* composition matrix

$$\begin{pmatrix} V_+ \\ I_+ \end{pmatrix} = \begin{pmatrix} 1 & -Y_2 \\ Y_2 & -1 \end{pmatrix} \begin{pmatrix} V_+ \\ I_+ \end{pmatrix}$$

$$\hookrightarrow A = \begin{pmatrix} V_+ \\ V_- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & z_1 \\ 1 & -z_1 \end{pmatrix} T_2 T_3 \begin{pmatrix} 1 & -Y_2 \\ Y_2 & -1 \end{pmatrix} \begin{pmatrix} V_+ \\ I_+ \end{pmatrix}$$


↳ so now we described 1 part of propagating waves using the other.

$$* T = \begin{pmatrix} \cos(kl) & jY \sin(kl) \\ jY \sin(kl) & \cos(kl) \end{pmatrix} \rightarrow k = \frac{2\pi}{\lambda}$$

$\ell = \text{length or } \frac{\lambda}{4}$
for quarter stub.

- * how is matching achieved \rightarrow even though diff impedances
- \rightarrow it's not 1 wave it's multiple waves \rightarrow add em up \rightarrow matches

Resist Aug 2022 $Z_0, Z_1 = 50\Omega$

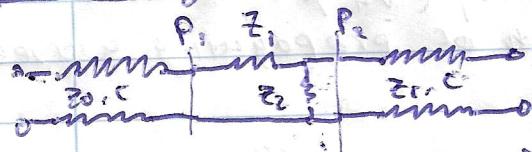

$$T_{\text{series}} \cdot T_{\text{shunt}} = \begin{pmatrix} 1 & Z_1 \\ \frac{1}{Z_2} & 1 \end{pmatrix}$$

$$T = \begin{pmatrix} 1.5 & 100 \\ 0.005 & 1 \end{pmatrix}. \text{ Find } Z_1, Z_2$$

$$\text{Toenes: } \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$T_{\text{shunt}}: \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ \frac{1}{Z_2} & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\Rightarrow Z_1 = 100\Omega, Z_2 = 200\Omega$$