

5XTCO - June 2020

Q1

a) $Z_L = (15 + j39) \Omega$

$Z_1 = 150 \Omega$

$$\frac{Z_L}{Z_1} = \frac{15}{150} + j \frac{39}{150} = 0.1 + j 0.26 \rightarrow \text{Find in SC}$$

$$\underline{\underline{\frac{|P_L| = 0.83}{\angle = 131^\circ}}}$$

b)

$$l_1 = 0.321 \text{ m}, \lambda = \frac{C}{f} = \frac{3 \cdot 10^8 \text{ m/s}}{400 \cdot 10^6 \text{ Hz}} = 0.75 \text{ m}$$

$$\frac{l_1}{\lambda} = 0.428 \Leftrightarrow l_1 = 0.428\lambda \rightarrow \text{Turn } 0.428\lambda \text{ towards generator}$$

$$\underline{\underline{\frac{Z_L'}{Z_1} = 0.1 - j 0.2}}$$

$$\underline{\underline{Z_L' = (15 - j30) \Omega}}$$

c)


$$\underline{\underline{\frac{Z_L'}{Z_0} = \frac{15}{75} - j \frac{30}{75}}} = 0.2 - j 0.4 \rightarrow \text{Find in SC}$$

$$\text{From SC: } \underline{\underline{\frac{Y_L'}{Y_0} = 1 + j 2}} \Rightarrow \underline{\underline{Z_S = 0 \Omega}}$$

$$Y_P = (-j2)Y_0 = -j \frac{2}{75} \frac{1}{\Omega}$$

$$\underline{\underline{Z_P = j 27.5 \Omega}}$$

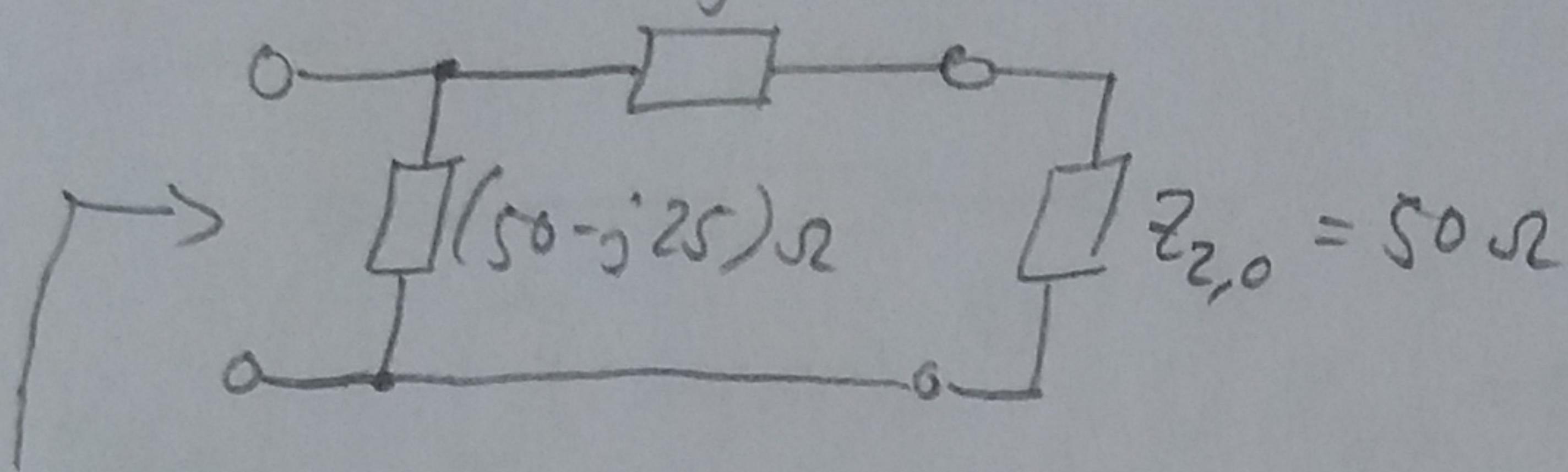d) S_{11} : Ref. impedance $\underline{Z_0 = 50\Omega}$



$$\Gamma_1 = S_{11}$$

$$Z_{in,1} = \frac{(50-j25)\Omega}{\text{find in SC}} \parallel \frac{(50+j100)\Omega}{\text{find in SC}} \rightarrow \underline{\underline{Z_2 = \frac{50}{50} + j \frac{100}{50} = 1+j2}}$$

$\frac{Z_1}{Z_0} = \frac{50}{50} - j \frac{25}{50}$

$\frac{Z_2}{Z_0} = 1 - j 0.5$

$\frac{Y_1}{Y_0} = 0.8 + j 0.4$


$\frac{Y_2}{Y_0} = 0.2 - j 0.4$

$\boxed{\frac{Y_1 + Y_2}{Y_0} = 1} \quad \text{center of SC!}$

$\Rightarrow Z_{in,1} = 50\Omega$

$\Rightarrow \underline{\underline{S_{11} = 0}}$

S_{22}'

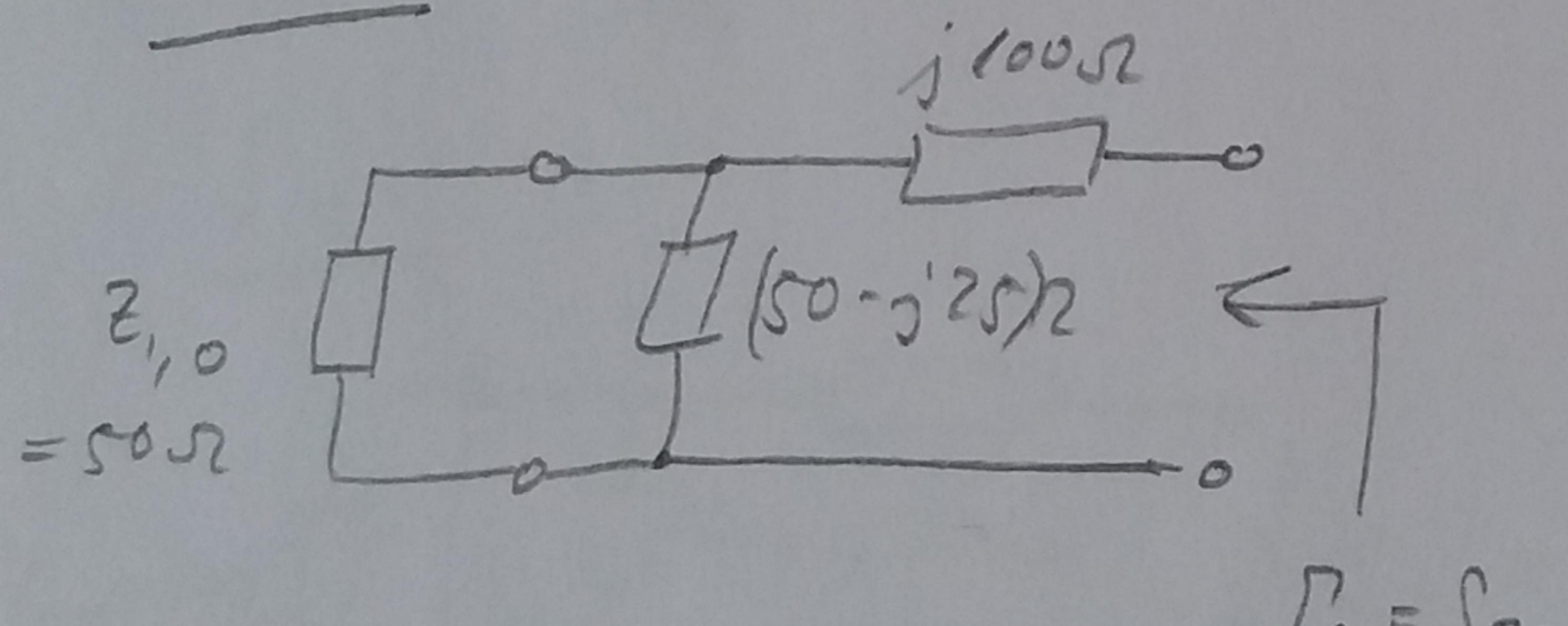

$$Z_{in,2} = j100\Omega + \left\{ \frac{50\Omega}{(50-j25)\Omega} \right\}$$

$$\frac{Y_1}{Y_0} = 1 + 0.8 + j 0.4$$

$$\frac{Y_2}{Y_0} = 1.8 + j 0.4$$

$$\frac{Z_1}{Z_0} = 0.53 - j 0.12$$


$$\cancel{j100\Omega} \rightarrow Z_0 = 26.5 - j 6$$

$$Z_{in,2} = (26.5 - j 9k)\Omega$$

$$\underline{\underline{S_{22} = \frac{Z_{in,2} - Z_0}{Z_{in,2} + Z_0} = 0.48 + j 0.64}}$$

d) cont'd

S_{21} :

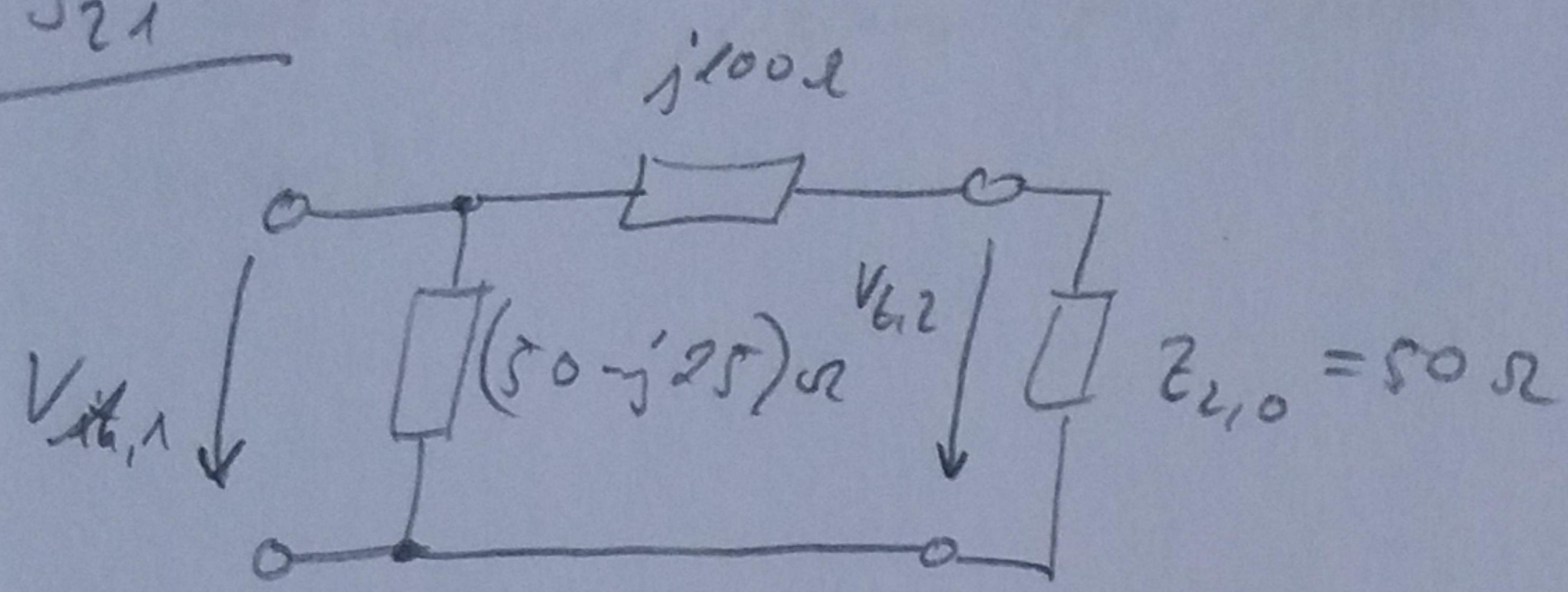

$V_{t,1} = (1 + S_{11}) V_{in,1}$; $V_{in,1}$: incident voltage wave on port 1 (from the left)

$$V_{t,2} = \frac{Z_{L,0}}{Z_{L,0} + j100\omega} V_{in,1} \quad V_{t,1} = \frac{Z_{L,0}}{Z_{L,0} + j100\omega} (1 + S_{11}) V_{in,1}; \quad \underline{V_{t,2}}: \text{accepted/dissipated power in } Z_{L,0} \text{ (i.e. port 2)}$$


$$= \frac{50\Omega}{(50 + j100)\Omega} (1+0) V_{in,1}$$

$$= \frac{1}{1+j2} V_{in,1} = \frac{1-j2}{5} V_{in,1} = (0.2 - j0.4) V_{in,1}$$

$$\underline{S_{21}} = \frac{\underline{V_{t,2}}}{\underline{\sqrt{Z_0}}} \cdot \frac{\sqrt{Z_0}}{\underline{V_{in,1}}} = \frac{\underline{V_{t,2}}}{\underline{V_{in,1}}} = \underline{0.2 - j0.4}$$

$$b_2 \quad \frac{1}{a_1}$$

S_{12} :

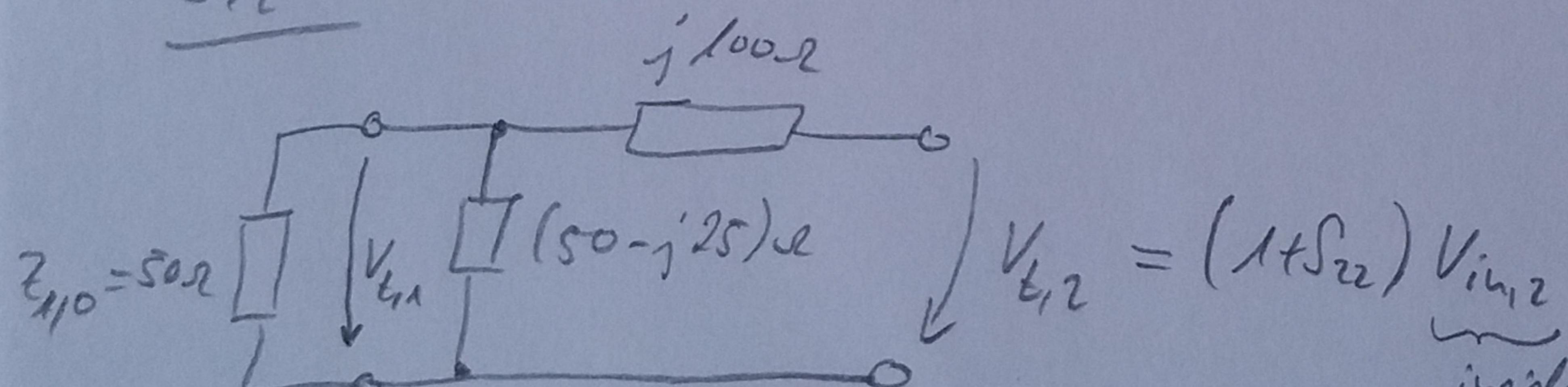

$V_{t,1}$: accepted/dissipated power in $Z_{L,0}$ (i.e. port 1)

$$V_{t,1} = \frac{\overbrace{50\Omega / ((50 - j25)\omega)}^j100 + \overbrace{(50\Omega / ((50 - j25)\omega)}}^{50\Omega / ((50 - j25)\omega)}}{j100 + \overbrace{(50\Omega / ((50 - j25)\omega)}}^{50\Omega / ((50 - j25)\omega)}} (1 + S_{22}) V_{in,2}$$

$$= 26.5 - j6 \quad = 0.48 + j0.64$$

$$\underline{S_{12}} = \frac{\underline{V_{t,1}}}{\underline{V_{in,2}}} = \underline{0.2 - j0.4} = \underline{S_{21}} \quad ! \rightarrow \text{This result could have been known without calculations. The network is passive and must be reciprocal} \Rightarrow S\text{-matrix must be symmetrical!}$$

c) The scattering matrix of the setup shown in Fig. 2 is not unitary, because the network contains lossy components (resistors).