

## Question 2. Transfer & scatter matrices

(1)

2A. Although the  $\frac{1}{4}\lambda$  transformer matches the load to the transmission line, it is only for 1 frequency only. So, this limits the usage, e.g. very limited bandwidth.

2B.  $T(l, l) = \begin{pmatrix} \cos(kl) & jZ_1 \sin(kl) \\ jY \sin(kl) & \cos(kl) \end{pmatrix}$

now:  $l = \frac{1}{4}\lambda$        $k = \frac{2\pi}{\lambda} \Rightarrow kl = \frac{1}{4}\lambda \frac{2\pi}{\lambda} = \frac{\pi}{2}$

$\Rightarrow T(l, \frac{1}{4}\lambda) = \begin{pmatrix} 0 & jZ_1 \\ jY & 0 \end{pmatrix}$


2C. So, we have the transfer matrix and we need to find the scatter matrix.

From theory:

\* scatter matrix

$$\begin{pmatrix} V_1^- \\ V_2^+ \end{pmatrix} = \bar{S} \begin{pmatrix} V_1^+ \\ V_2^- \end{pmatrix}$$

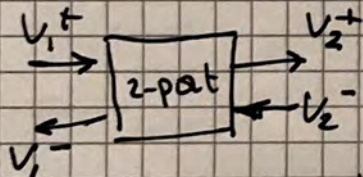↑                      ↑  
outgoing            incoming



\* transfer matrix

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \bar{T} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

In this case it is handy to use the  $\bar{A}$ -matrix

$$\bar{A} = D_1 T C_2$$

$$\Rightarrow \begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \bar{A} \begin{pmatrix} V_2^+ \\ V_2^- \end{pmatrix}$$

with  $D = \frac{1}{2} \begin{pmatrix} 1 & Z_1 \\ 1 & -Z_1 \end{pmatrix}$  and  $C = \begin{pmatrix} 1 & 1 \\ Y_0 & -Y_0 \end{pmatrix}$

So, first calculate the  $\bar{A}$ -matrix and then rearrange to get the  $\bar{S}$ -matrix



(2)

$$\begin{aligned} \vec{A} = \vec{D}_1 \cdot T \cdot \vec{C}_2 &= \begin{pmatrix} \frac{1}{2} & \frac{1}{2}Z_1 \\ \frac{1}{2} & -\frac{1}{2}Z_1 \end{pmatrix} \begin{pmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{pmatrix} \begin{pmatrix} 1 & 1 \\ Y_0 & -Y_0 \end{pmatrix} \\ &= \begin{pmatrix} \frac{1}{2}j & \frac{1}{2}jZ_1 \\ -\frac{1}{2}j & \frac{1}{2}jZ_1 \end{pmatrix} \\ &= \begin{pmatrix} \frac{1}{2}j + \frac{1}{2}j & \frac{1}{2}j - \frac{1}{2}j \\ -\frac{1}{2}j + \frac{1}{2}j & -\frac{1}{2}j - \frac{1}{2}j \end{pmatrix} = \begin{pmatrix} j & 0 \\ 0 & -j \end{pmatrix} \end{aligned}$$


$$\Rightarrow \begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \begin{pmatrix} j & 0 \\ 0 & -j \end{pmatrix} \begin{pmatrix} V_2^+ \\ V_2^- \end{pmatrix}$$

$$\Rightarrow \begin{cases} V_1^+ = j V_2^+ \\ V_1^- = -j V_2^- \end{cases} \Rightarrow V_2^+ = -j V_1^+$$

$$\Rightarrow \begin{pmatrix} V_1^- \\ V_2^+ \end{pmatrix} = \underline{\underline{\vec{S}}} \begin{pmatrix} V_1^+ \\ V_2^- \end{pmatrix} = \underline{\underline{\begin{pmatrix} 0 & -j \\ -j & 0 \end{pmatrix}}} \begin{pmatrix} V_1^+ \\ V_2^- \end{pmatrix}$$

2d.  $Z_1 = \sqrt{Z_0 Z_L}$  → although some students might know this answer, the question is to deduce the answer.

situation:

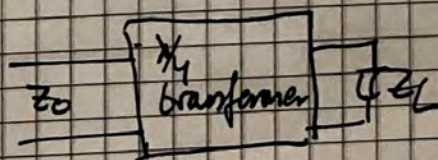

$$\uparrow$$

$$T\text{-matrix} = \begin{pmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{pmatrix}$$

idea → use T-matrix to get an expression of  $V_1^+$  and  $V_1^-$  (input 2-port =  $X_1$  transformer)  
 $V_1^-$  should be zero (= matched)



Decomposition matrix:

3

$$\begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \bar{D} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}$$

$$\longrightarrow = \frac{1}{2} \begin{pmatrix} 1 & Z_0 \\ 1 & -Z_0 \end{pmatrix}$$

now

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = T \cdot \begin{pmatrix} V_2 \\ I_2 \end{pmatrix} = \begin{pmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{pmatrix} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \begin{pmatrix} V_1^+ \\ \Gamma \cdot V_1^+ \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & Z_0 \\ 1 & -Z_0 \end{pmatrix} \begin{pmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{pmatrix} \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

$$\longrightarrow = \begin{pmatrix} T \cdot V_1^+ \\ T \cdot V_1^+ \cdot \Gamma \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} 1 \\ \Gamma \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & Z_0 \\ 1 & -Z_0 \end{pmatrix} \begin{pmatrix} 0 & jZ_1 \\ jY_1 & 0 \end{pmatrix} \begin{pmatrix} 1 \\ Y_L \end{pmatrix}$$

$$\Rightarrow \begin{pmatrix} 1 \\ \Gamma \end{pmatrix} = \frac{1}{2} \begin{pmatrix} jY_1 Z_0 & jZ_1 \\ -jY_1 Z_0 & jZ_1 \end{pmatrix} \begin{pmatrix} 1 \\ Y_L \end{pmatrix} = \frac{j}{2} \begin{pmatrix} Y_1 Z_0 + Z_1 Y_L \\ Y_L Z_1 - Y_1 Z_0 \end{pmatrix}$$

now, we know  $\Gamma$  should be 0 ( $Z_L$  is matched to the transmission line, so no reflection)

$$\Rightarrow Y_L Z_1 - Y_1 Z_0 = 0$$

$$\Rightarrow Y_L Z_1 = Y_1 Z_0 \Rightarrow \frac{Z_1}{Z_L} = \frac{Z_0}{Z_1}$$


$$\Rightarrow Z_1 = \sqrt{Z_0 Z_L}$$



22.

4

Situation:  $Z_0$   $Z_1$   $Z_L$

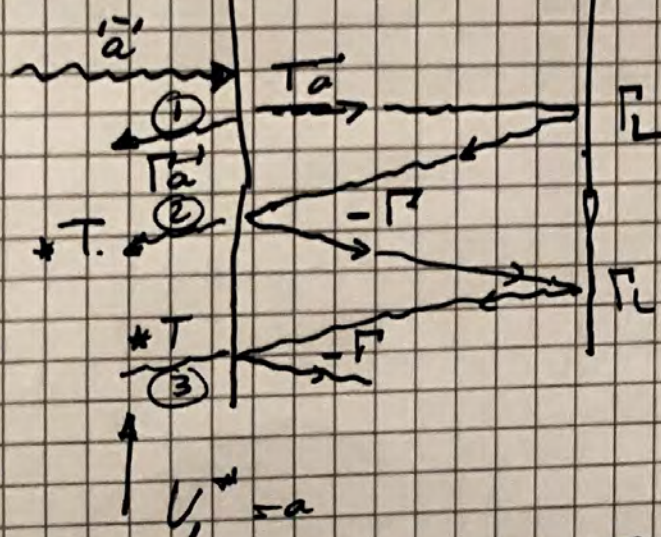

$$V_1 = T \cdot a + \textcircled{2} + \textcircled{3} + \textcircled{4} + \dots$$

and should be zero of course

So, task here is to identify all the waves and make this equal to zero --- this should give the same answer as in 2d:

$$Z_1 = \sqrt{Z_0 Z_L}$$

(A) First one is  $\Gamma \cdot a$  with  $\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0}$


(B) second one



$$\frac{1}{4} \lambda \rightarrow \text{total} = \frac{1}{2} \lambda = -\text{sign}$$

$$\Rightarrow -T^2 \cdot \Gamma_L \cdot a$$

(C) third one

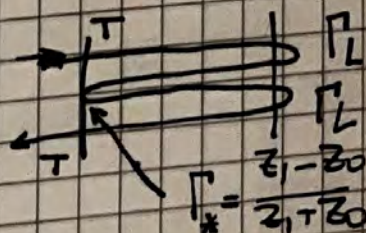

$$\frac{1}{4} \lambda \rightarrow \text{total} = 4 \cdot \frac{1}{4} \lambda = \lambda = +\text{sign}$$

$$\Rightarrow -T^2 \Gamma_L^2 \Gamma \cdot a$$

(D) fourth one =  $-T^2 \Gamma_L^3 \Gamma \cdot a$

etc. etc.



So, the complete  $V_1^-$  wave is:

$$\begin{aligned} & \Gamma - T^2 \Gamma_L - T^2 \Gamma_L^2 \Gamma - T^2 \Gamma_L^3 \Gamma^2 - \dots \\ \Rightarrow & \Gamma - T^2 \Gamma_L (\Gamma_L \Gamma)^0 - T^2 \Gamma_L (\Gamma_L \Gamma)^1 - T^2 \Gamma_L (\Gamma_L \Gamma)^2 - \dots \\ \Rightarrow & \Gamma - T^2 \Gamma_L \left( \sum_{n=0}^{\infty} (\Gamma_L \Gamma)^n \right) \end{aligned}$$

$$\downarrow \sum_{n=0}^{\infty} r^n = \frac{1}{1-r} \quad \text{if } r < 1$$

$$\begin{aligned} \Rightarrow & \Gamma - T^2 \Gamma_L \left( \frac{1}{1 - \Gamma_L \Gamma} \right) \\ \Rightarrow & \frac{\Gamma(1 - \Gamma_L \Gamma)}{1 - \Gamma_L \Gamma} - \frac{T^2 \Gamma_L}{1 - \Gamma_L \Gamma} = \underline{\underline{\frac{\Gamma - \Gamma_L \Gamma^2 - T^2 \Gamma_L}{1 - \Gamma_L \Gamma}}} \end{aligned}$$

So, what we have:

$$V_1^- = \left( \frac{\Gamma - \Gamma_L \Gamma^2 - T^2 \Gamma_L}{1 - \Gamma_L \Gamma} \right) V_1^+$$

and -- as mentioned before -- should be  $\phi$   
that means:

$$\Gamma - \Gamma_L \Gamma^2 - T^2 \Gamma_L = \phi$$

we know:

$$\Gamma = \frac{z_1 - z_0}{z_1 + z_0}$$

$$\Gamma_L = \frac{z_L - z_1}{z_L + z_1}$$

$$T = 1 + \Gamma = 1 + \frac{z_1 - z_0}{z_1 + z_0} = \frac{2z_1}{z_1 + z_0}$$

now we fill this in the equation:



(6)

$$\Gamma - \Gamma_L \Gamma^2 - T^2 \Gamma_L$$

$$\Rightarrow \Gamma - \Gamma_L \Gamma^2 - (1 - \Gamma^2) \Gamma_L$$

$$\Rightarrow \Gamma - \Gamma_L$$

$$\boxed{T^2 = 1 - \Gamma^2}$$

$$= \frac{z_1 - z_0}{z_1 + z_0} - \frac{z_L - z_1}{z_L + z_1}$$

$$\Rightarrow \frac{(z_1 - z_0)(z_L + z_1) - (z_L - z_1)(z_1 + z_0)}{(z_1 + z_0)(z_L + z_1)}$$

$$\Rightarrow \frac{z_1 z_L - z_0 z_L + z_1^2 - z_0 z_1 - (z_L^2 + z_L z_0 + z_1 z_0 - z_1 z_0)}{(z_1 + z_0)(z_L + z_1)}$$

$$\Rightarrow \frac{2z_1^2 - 2z_0 z_L}{(z_1 + z_0)(z_L + z_1)} = \frac{2(z_1^2 - z_0 z_L)}{(z_1 + z_0)(z_L + z_1)}$$

this means

$$z_1^2 = z_0 z_L$$

$$\rightarrow z_1 = \sqrt{z_0 z_L}$$

indeed the same as before.