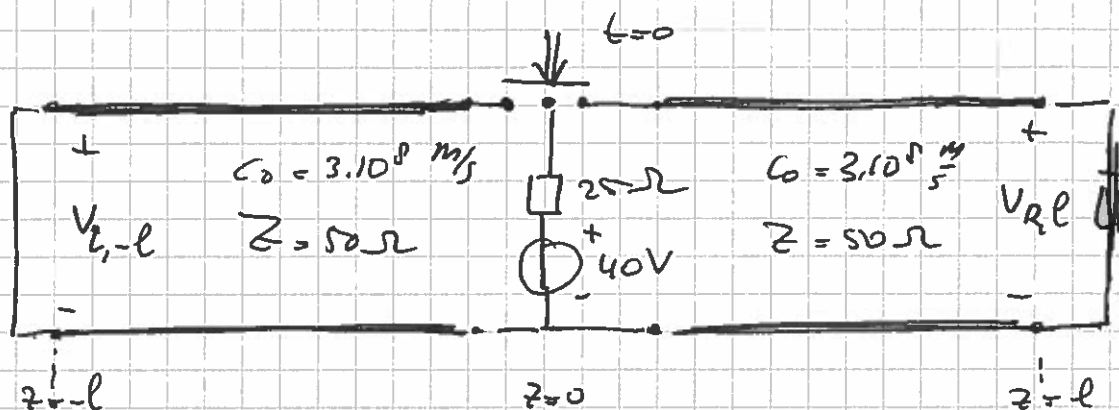


Solutions exam question made in class

①

situation




length $l = 0.7 \text{ m}$

④ for $t \rightarrow \infty \Rightarrow$ steady state, so... no time varying voltage?

$V_{L, \text{steady}}(z, t)$?
 $I_{L, \text{steady}}(z, t)$?

\rightarrow TL is steady state

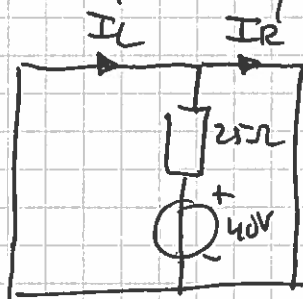So, we get the following circuit representation:



note the directions
 (it is a choice!)

total current = $\frac{40}{25} = 1.6 \text{ A}$
 will flow in both branches, therefore

$$I_{L, \text{steady}}(z, t) = -0.8 \text{ A} \quad (\text{direction?})$$

$$I_{R, \text{steady}}(z, t) = +0.8 \text{ A}$$

$$V_{L, \text{steady}}(z, t) = 0 \text{ V} \quad (\text{short circuit})$$

$$V_{R, \text{steady}}(z, t) = 0 \text{ V}$$

next step is the progressive and regressive waves

(2)

This is called wave-decomposition

$$\text{So } \begin{matrix} V_{L, \text{steady}} \\ I_{L, \text{steady}} \end{matrix} \Rightarrow \begin{matrix} V_{L, \text{steady}}^+ \\ I_{L, \text{steady}}^+ \end{matrix} + \begin{matrix} V_{L, \text{steady}}^- \\ I_{L, \text{steady}}^- \end{matrix}$$

now we have

$$\begin{aligned} V_{L, \text{steady}}^+ + V_{L, \text{steady}}^- &= V_{L, \text{steady}} = 0 \text{ [V]} \\ I_{L, \text{steady}}^+ + I_{L, \text{steady}}^- &= I_{L, \text{steady}} = -0.8 \text{ [A]} \end{aligned}$$

$$I_{L, \text{st.}}^+ = V_{L, \text{steady}}^+ / Z \quad \text{and} \quad I_{L, \text{steady}}^- = -V_{L, \text{steady}}^- / Z$$

So 4 equations, 4 unknowns --- must be possible

$$\frac{V_{L, \text{steady}}^+}{Z} - \frac{V_{L, \text{steady}}^-}{Z} = -0.8$$

$$\frac{V_{L, \text{steady}}^+}{Z} - \frac{-V_{L, \text{steady}}^-}{Z} = -0.8$$

$$\Rightarrow 2 \cdot V_{L, \text{steady}}^+ = -0.8 \cdot Z = -40$$

$$\Rightarrow V_{L, \text{steady}}^+ = -20 \text{ [V]}$$

$$\Rightarrow V_{L, \text{steady}}^- = 20 \text{ [V]}$$

(check $\Sigma = 0$ \checkmark)

and therefore

$$I_{L, \text{steady}}^+ = \frac{V_{L, \text{steady}}^+}{Z} = -0.4 \text{ [A]}$$

$$I_{L, \text{steady}}^- = \frac{-V_{L, \text{steady}}^-}{Z} = -0.4 \text{ [A]}$$

(check $\Sigma = -0.8 \text{ A}$ \checkmark)


(B) Reflection coefficients

(3)

$$\Gamma_{L,L} = -1 \quad (\text{short})$$

$$\Gamma_{R,R} = -1 \quad (\text{short})$$

situation is

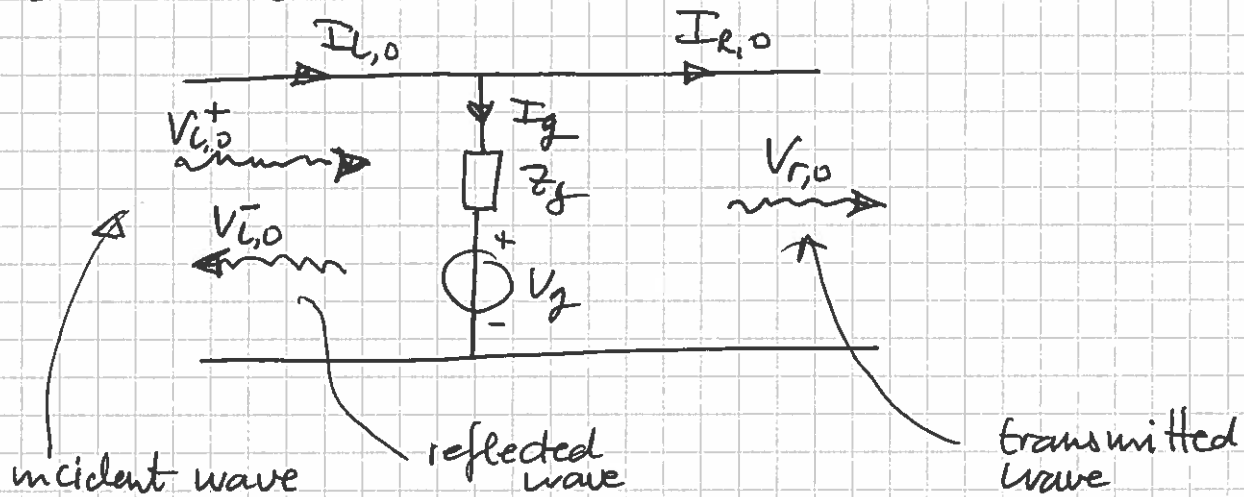

we know: $V_{L,0}^- = \Gamma V_{L,0}^+$

and $V_{R,0} = T V_{L,0}^+$

at this $z=0$:

left side: $V_{L,0} = V_{L,0}^+ + V_{L,0}^- = V_{L,0}^+ (1 + \Gamma)$
 and $I_{L,0} = \frac{V_{L,0}}{50} (1 - \Gamma)$

right side: $V_{R,0} = T V_{L,0}^+$
 $I_{R,0} = T \cdot \frac{V_{L,0}^+}{50}$

now

KVL: $V_{L,0} = V_{R,0} \Rightarrow V_{L,0}^+ (1 + \Gamma) = V_{L,0}^+ (T)$
 $\Rightarrow T = 1 + \Gamma$

KCL: $I_{L,0} = I_{R,0} + I_g$

$$\frac{V_{L,0}^+}{50} (1 - \Gamma) = \frac{V_{L,0}^+}{50} \cdot T + \frac{I_g}{\frac{V_{L,0}^+ T}{25}}$$

④

$$\begin{aligned} \underline{S_0} \quad \frac{V_{L0}^+}{50} (1 - \Gamma) &= \frac{V_{L0}^+}{50} T + \frac{V_{L0}^+}{25} \cdot T \\ &= \frac{V_{L0}^+}{50} (1 - \Gamma) = \frac{V_{L0}^+}{50} (T + 2T) \end{aligned}$$

$$\Rightarrow 1 - \Gamma = 3T$$

now


$$\frac{T = \frac{1 + \Gamma}{3T} = \frac{1 - \Gamma}{1 - \Gamma}}{4T = 2}$$

$$\rightarrow \boxed{T = \frac{1}{2}}$$

$$\Rightarrow \boxed{\Gamma = -\frac{1}{2}}$$

Alternative solution

@ $t \approx 0$

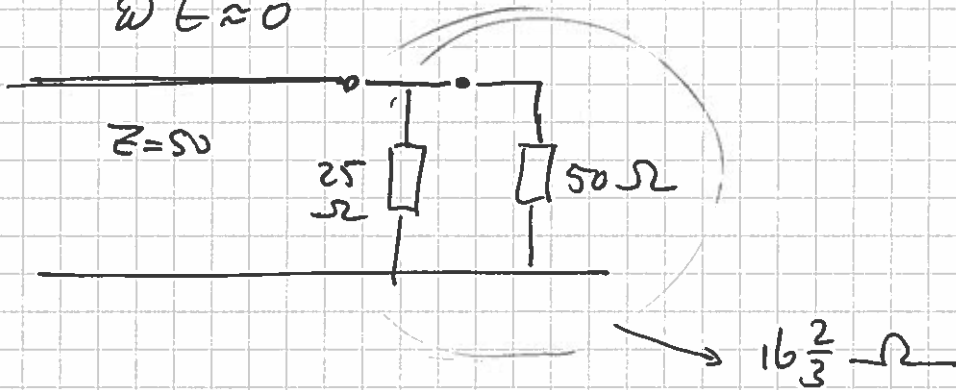

that means

$$\Gamma = \frac{Z_L - Z}{Z_L + Z} = \frac{-50 + 16 \frac{2}{3}}{50 + 16 \frac{2}{3}} = -\frac{1}{2}$$

$$T = 1 + \Gamma \Rightarrow \underline{\underline{T = \frac{1}{2}}}$$

(5)

last part of the question

-- the other way around.

\Rightarrow same answers

$$\Gamma = -\frac{1}{2} \quad T = \frac{1}{2}$$

(C) Now we need to sketch the bounce diagram of the total voltage at $z=0.6$ m for $t \in [0, 18 \text{ ns}]$


So, what happens is.



same situation at both sides!

$$\text{length} = 0.9 \text{ m} \rightarrow c = 3 \cdot 10^8 \text{ m/s} \rightarrow \text{single trip} = \underline{3 \text{ ns}}$$

at $t=0 \rightarrow$ voltage divider:

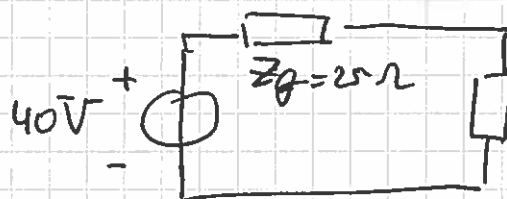

two transmission lines in parallel


$$Z_L = 50 \Omega // 50 \Omega = 25 \Omega$$

$$\text{that means } V_0 = \underline{20 \text{ V}}$$

$$\text{we also know } \Gamma_{L,L} = \Gamma_{L,R} = -1$$


So, let's sketch the beginning of the bounce diagram.

6

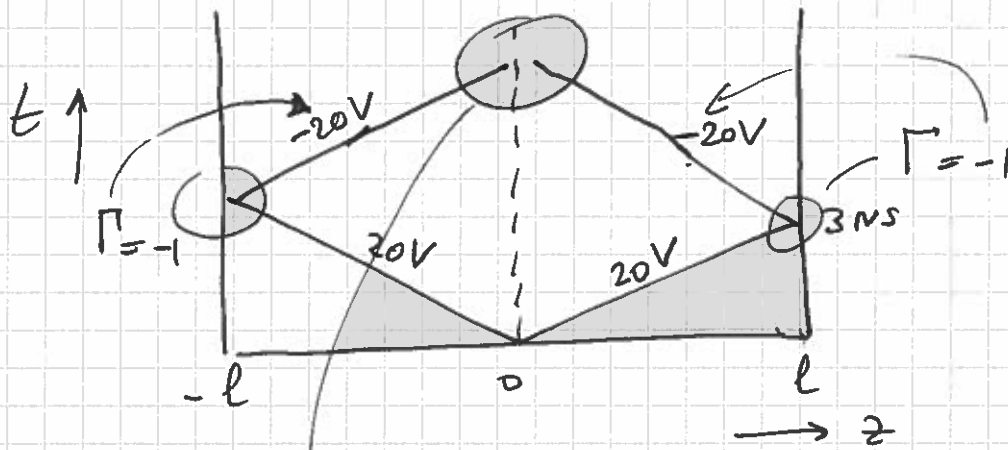


Here it becomes interesting!
 we first have to determine the reflection coefficients.
 $\Gamma = \frac{Z_l - Z_0}{Z_l + Z_0} = \dots$ see before $\Gamma = -\frac{1}{2}, T = \frac{1}{2}$


We have

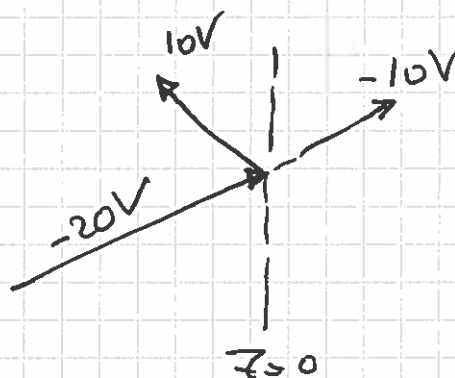

and at the same time
 ($t = 6ns$)

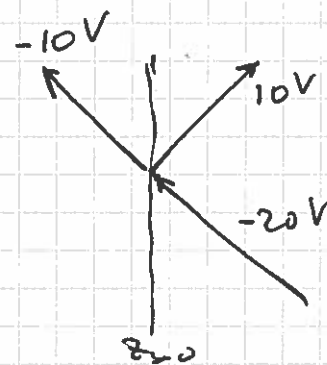


Superposition gives

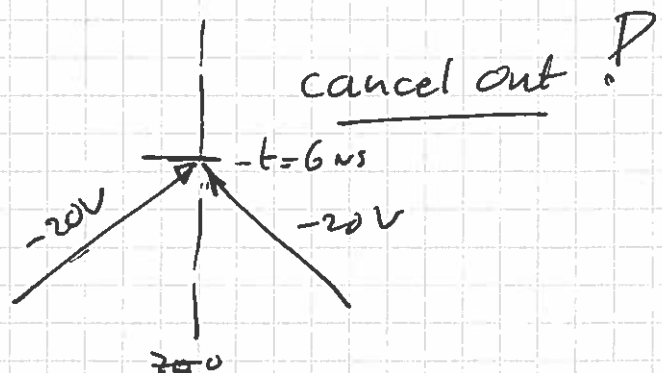

7


S_0 , total bounce diagram

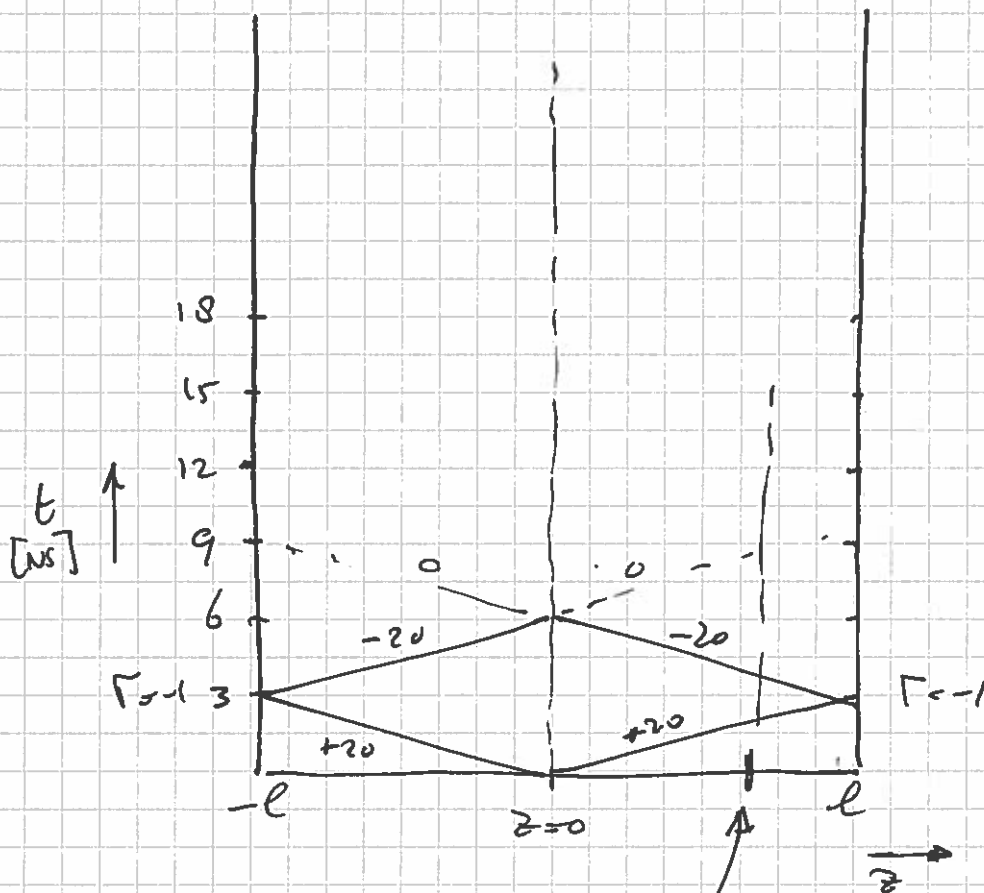

now at $z = 0.6$

ob meter $\rightarrow c = 3 \cdot 10^8 \text{ m/s} \rightarrow t = 2 \text{ ns}$

regressive wave at $t = 4 \text{ ns}$

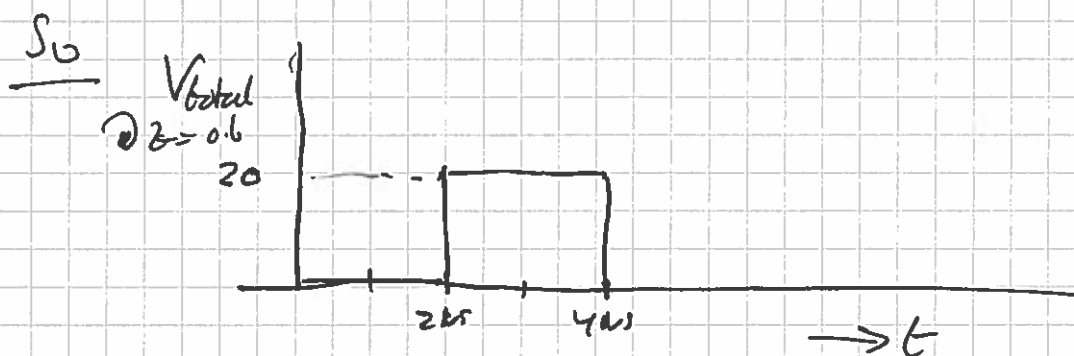


④ Now we make an "open" at the right ⑧
branche.

Q: What is $V_{R, \text{steady}}(z, t)$ and $I_{R, \text{steady}}(z, t)$
+ with wave decomposition

$$V_{R, \text{steady}}^{+-}(z, t) \text{ and } I_{R, \text{steady}}^{+-}(z, t)$$

now situation is

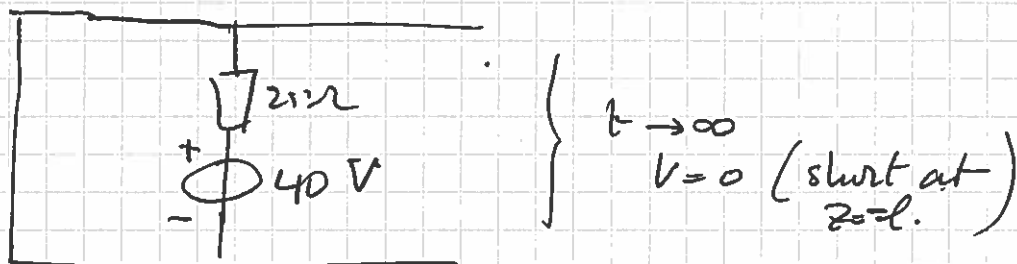

$$V_{R, \text{steady}}(z, t) = 0 \text{ [V]}$$

Since it is open at the right side $\Rightarrow I_{R, \text{steady}}(z, t) = 0 \text{ [A]}$
no current at an open end.

Same situation for the progressive and regressive wave in the $t \rightarrow \infty$ situation

$$\text{So } V_{R, \text{steady}}^{+-}(z, t) = 0$$

$$I_{R, \text{steady}}^{+-}(z, t) = 0$$

⑤ What is the total voltage at $z = 0.6$ for $t \in [0, 18] \text{ ns}$



At the beginning: $V_0 = 40 \cdot \frac{25}{25+25} = \underline{20 \text{ [V]}}$

is $\frac{25}{25+25} \Omega$ in parallel.


same situation as before.

So:

(16)

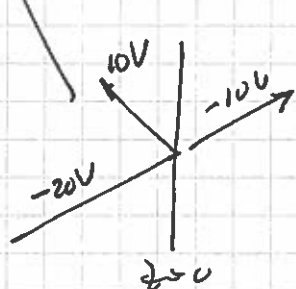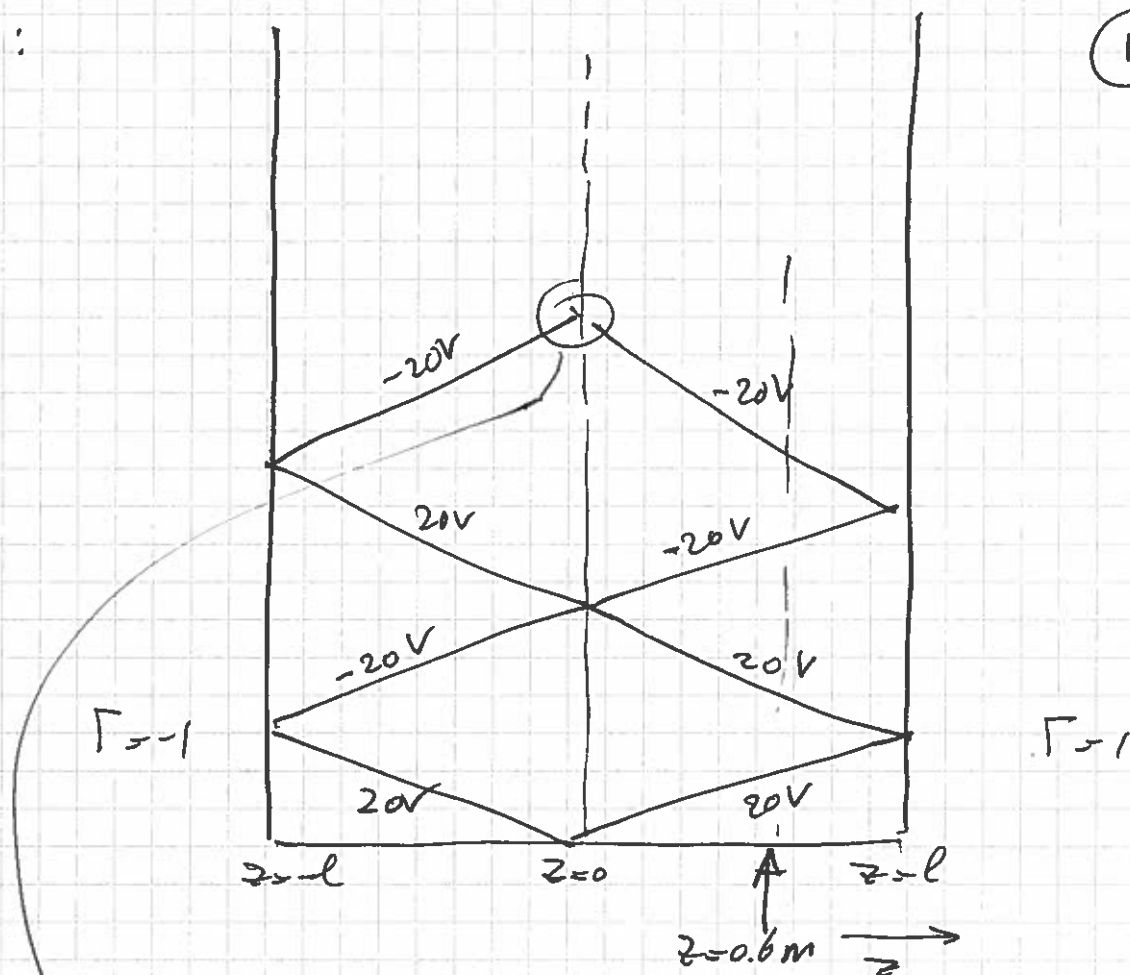

+

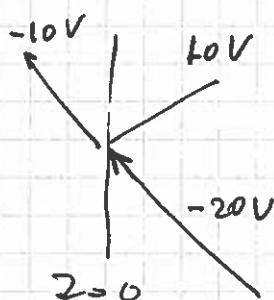

= cancel out again!

So, now at $z=0.6$ m

