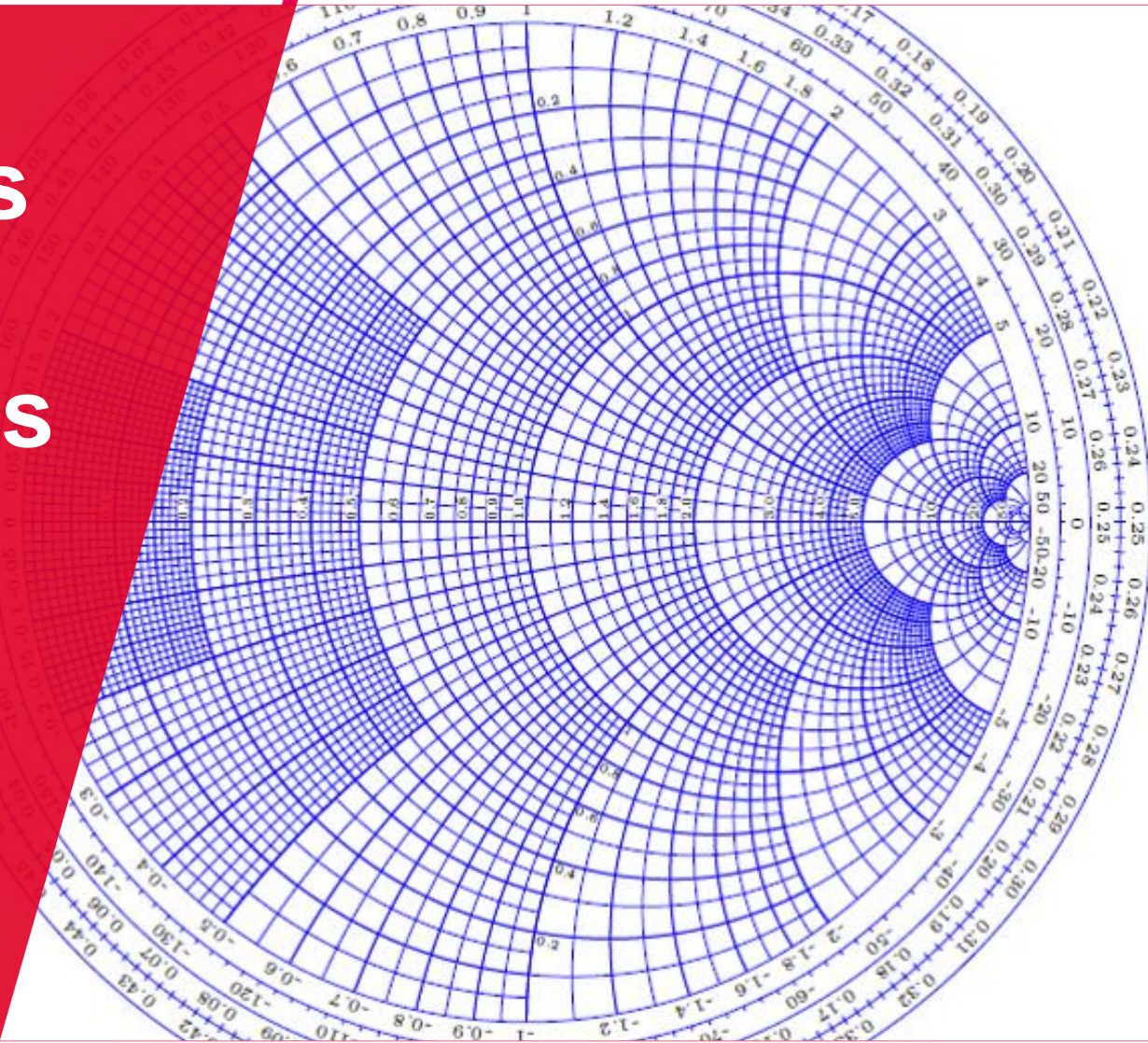



Components in Wireless Technologies

Module 1: Transmission Line Theory

Sander Bronckers



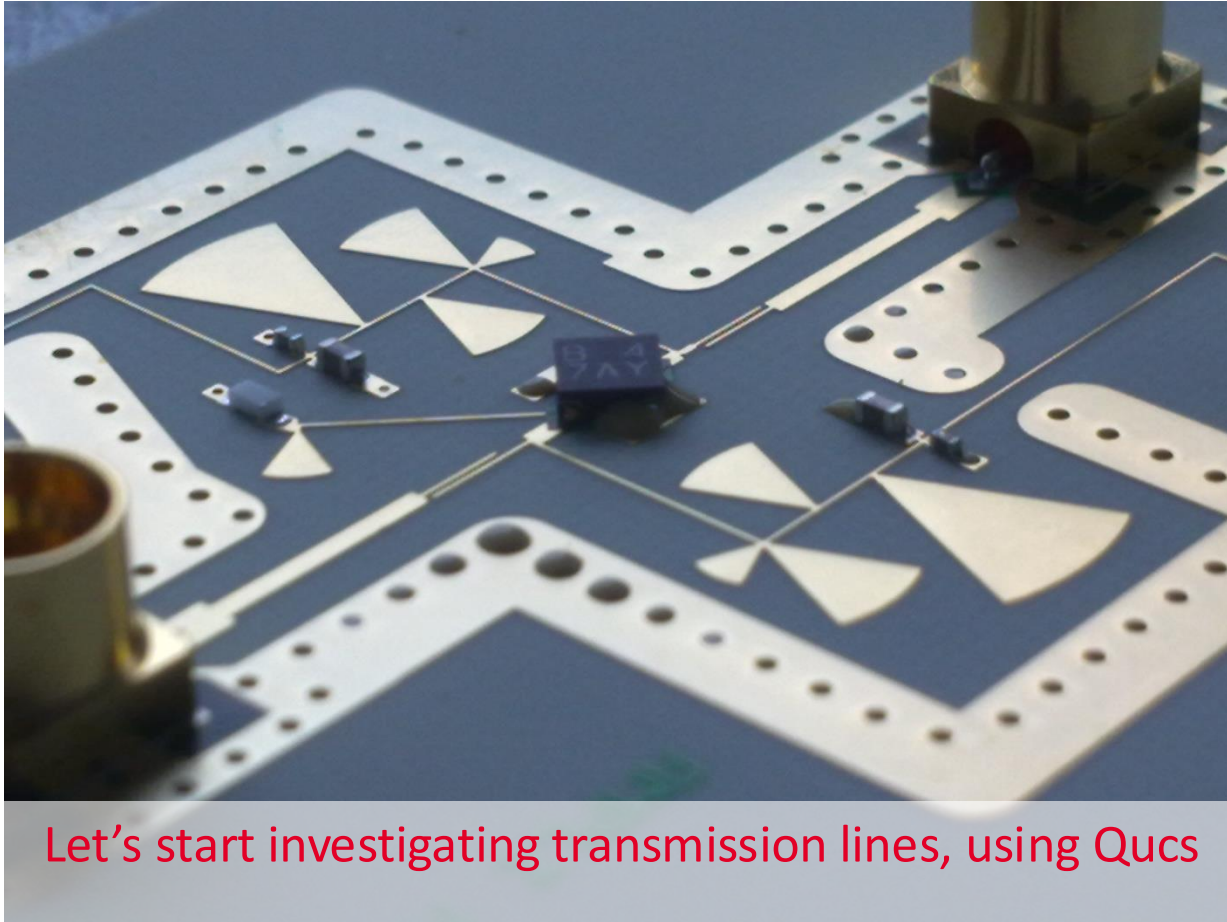
Transmission Lines of a 24 GHz Low-Noise Amplifier



Let's start investigating transmission lines, using Qucs

Free online book:

<https://arxiv.org/abs/1911.08484>

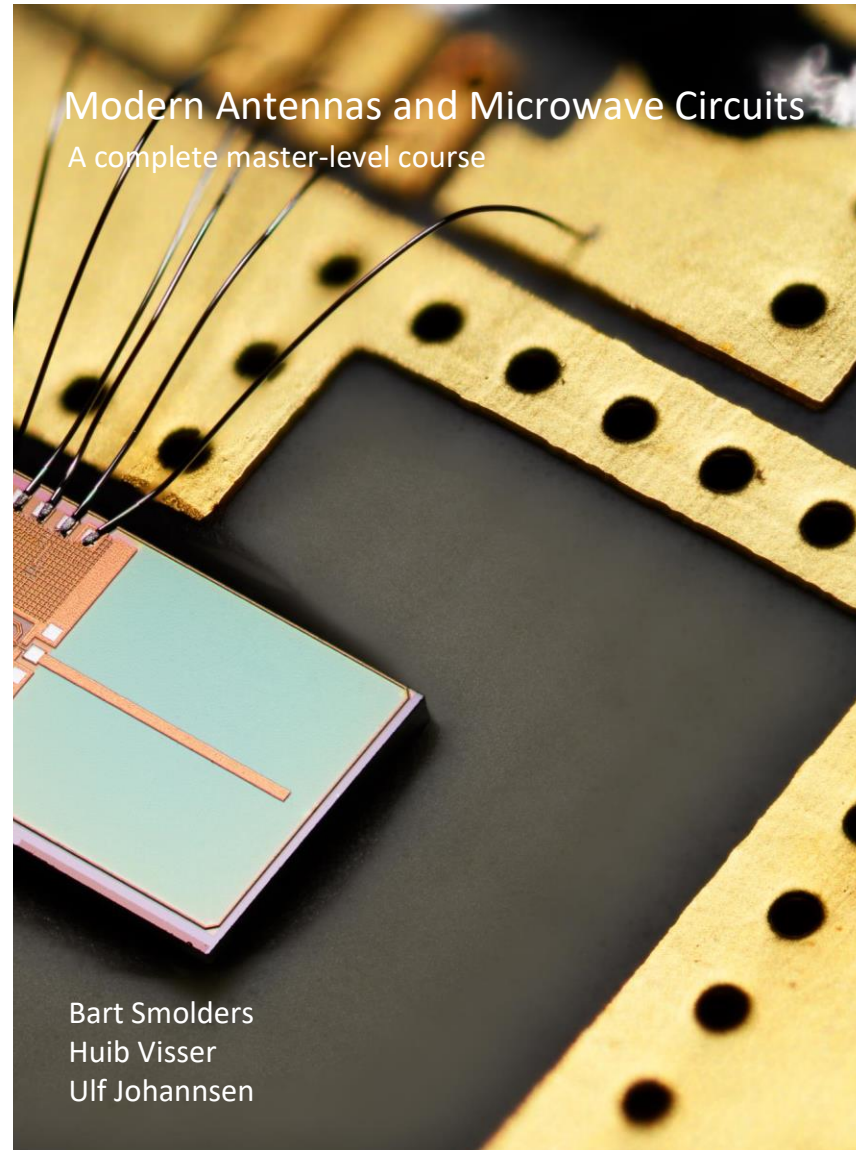


Modern Antennas and Microwave Circuits

A complete master-level course

Bart Smolders
Huib Visser
Ulf Johannsen




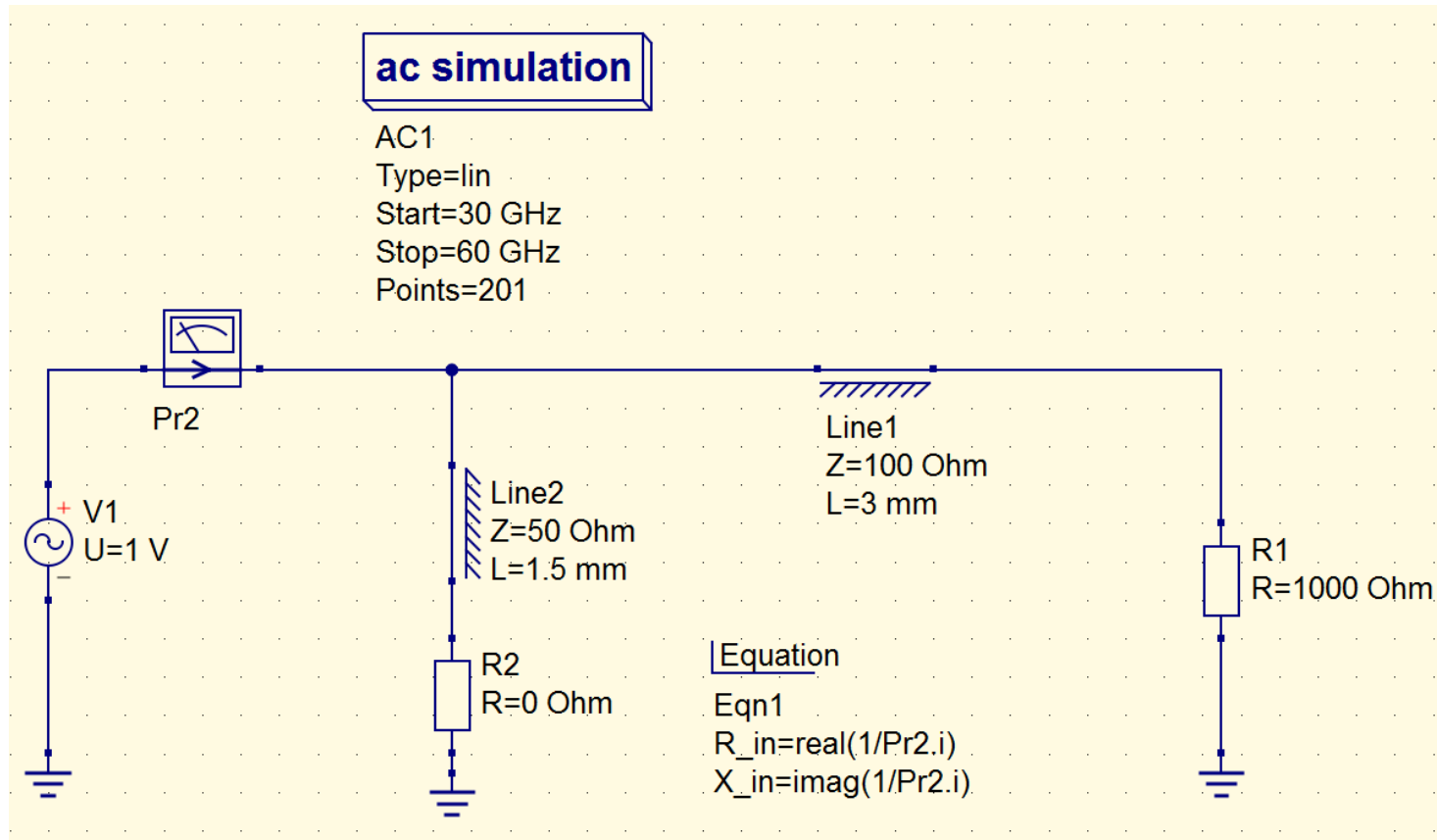
One of the goals of today is to understand this!




Transmission Line Theory

Content


- Telegrapher Equations
- Wave Propagation on a Transmission Line
- The Lossless Transmission Line

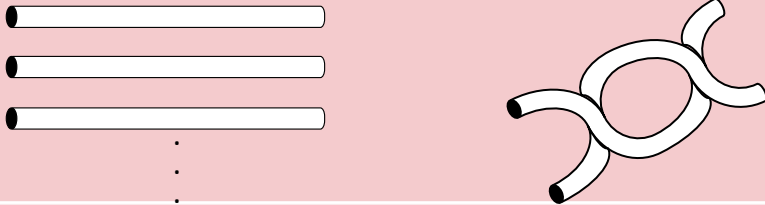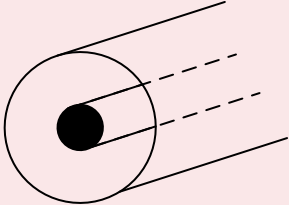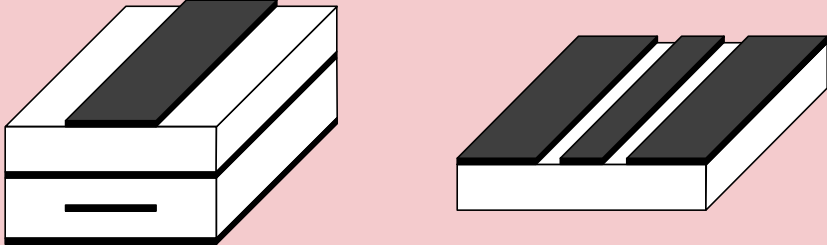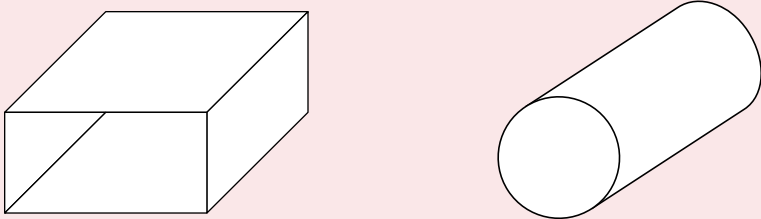Examples of transmission line	Schematic view	Field mode
Parallel wires and twisted pair		TEM
Coaxial		TEM
Micro-/Strip and coplanar waveguide		Quasi-TEM
Hollow waveguides		Non-TEM

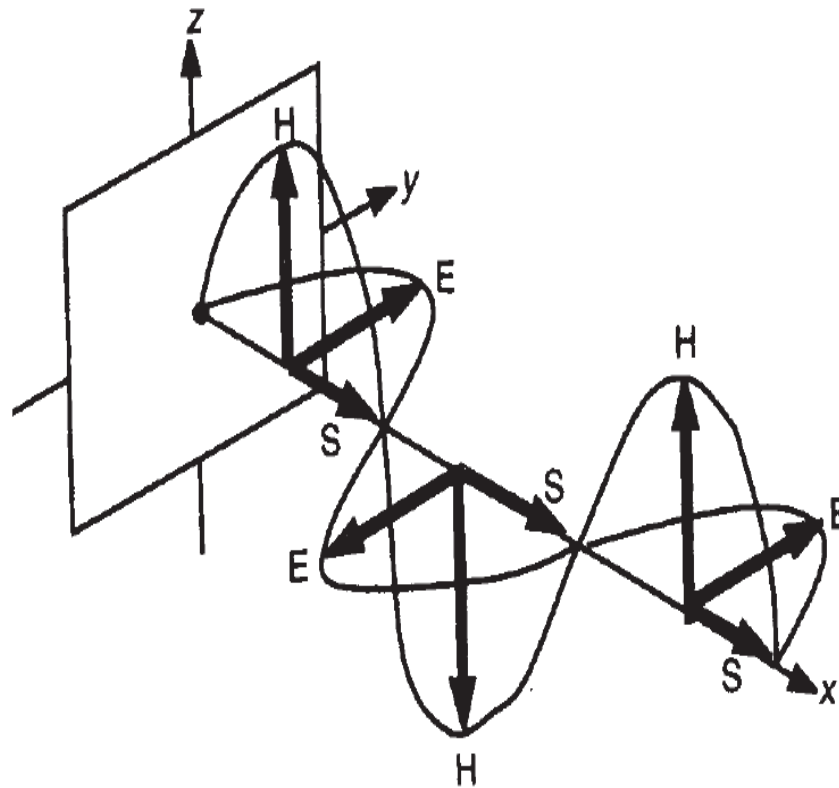- Following theory is derived for transmission lines with TEM field modes!




Basic Transmission line along z-axis

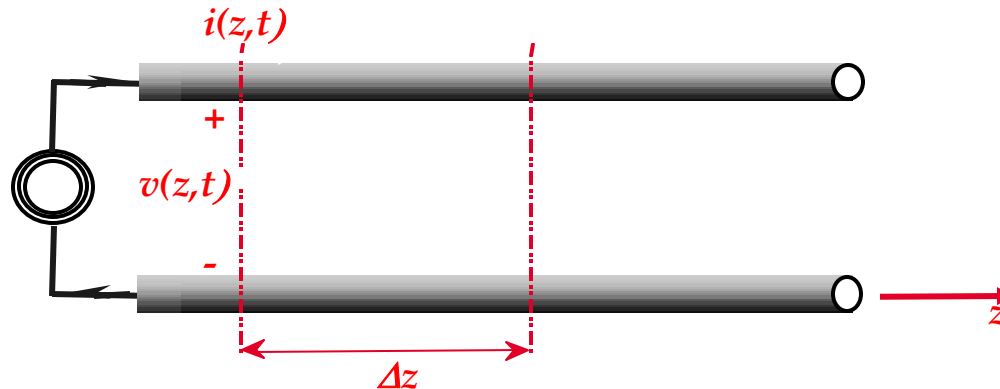

- Two-wire line representation
- Tline with TEM wave propagation has at least two conductors
- A short piece of length is Δz ($\ll \lambda$) and can be modelled as a lumped-element circuit
- Question: How???

Lumped-element circuit model

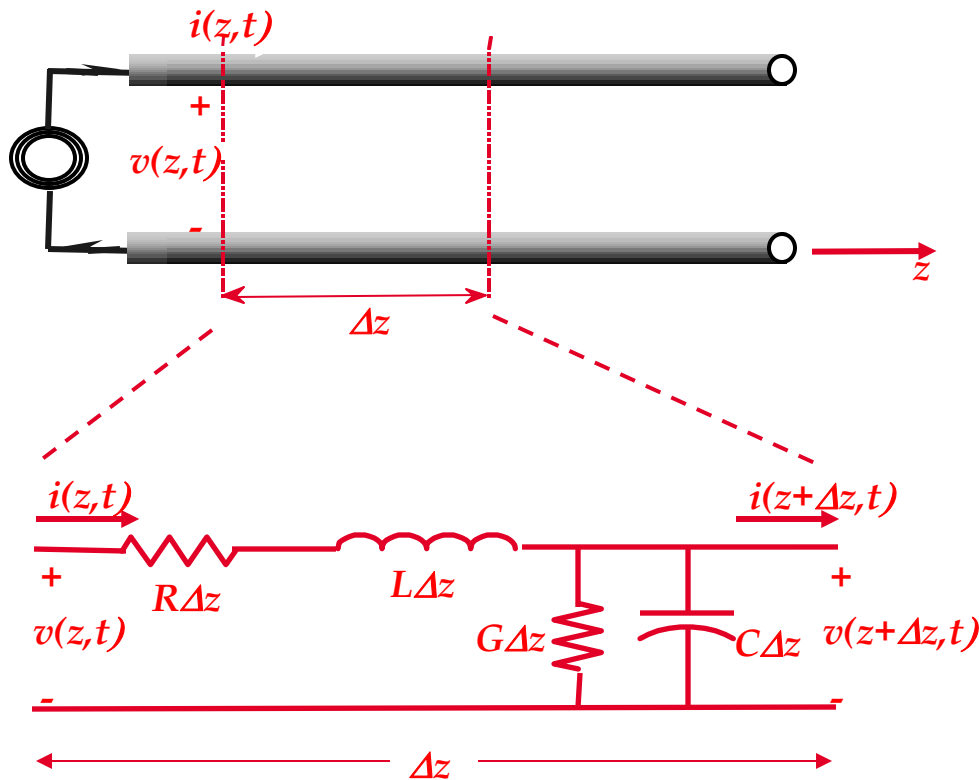

R: series resistance per unit length (Ohm/m)



L: series inductance per unit length (H/m)

G: shunt conductance per unit length (S/m)

C: shunt capacitance per unit length (F/m)

Physical interpretation

“Simplified view”

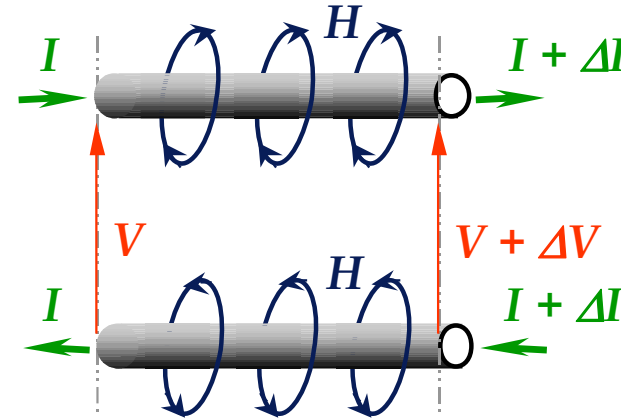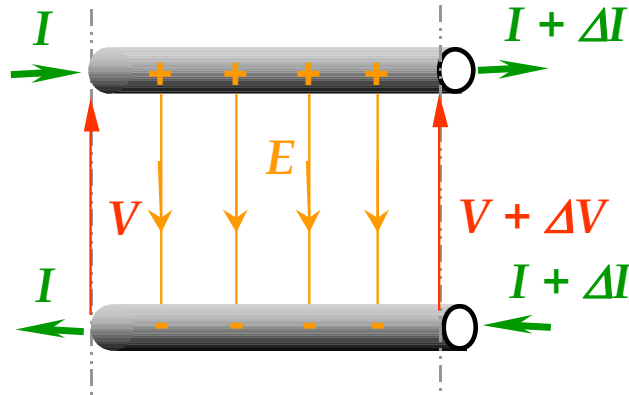

Both Electric and Magnetic fields are present in the transmission lines

- These fields are perpendicular to each other and to the direction of wave propagation for TEM mode waves


Electric field is established by a potential difference between two conductors.

- Implies equivalent circuit model must contain capacitor.

Magnetic field induced by current flowing on the line

- Implies equivalent circuit model must contain inductor.

Telegrapher Equations (Time Domain)

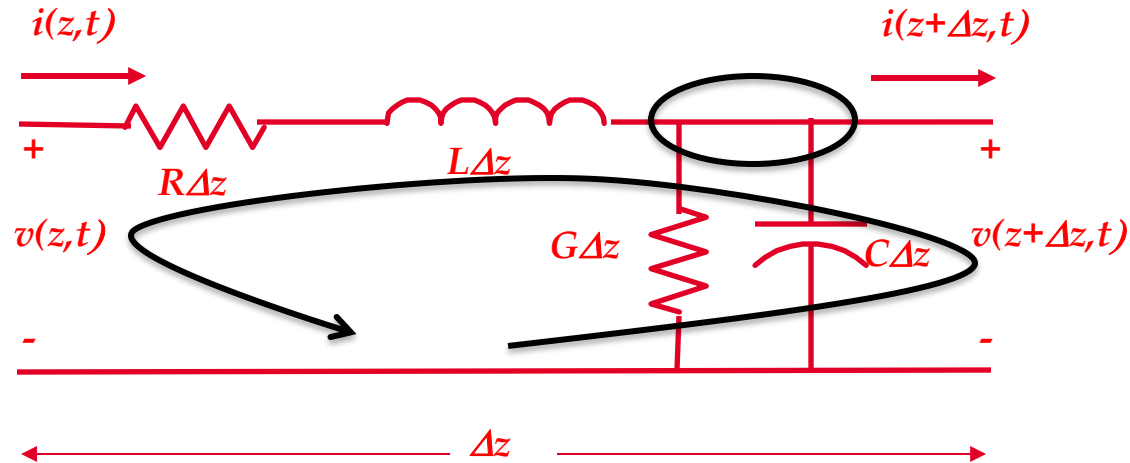


Apply Kirchhoff's voltage and current laws:

$$v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0$$

$$i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

Telegrapher Equations (Time Domain)

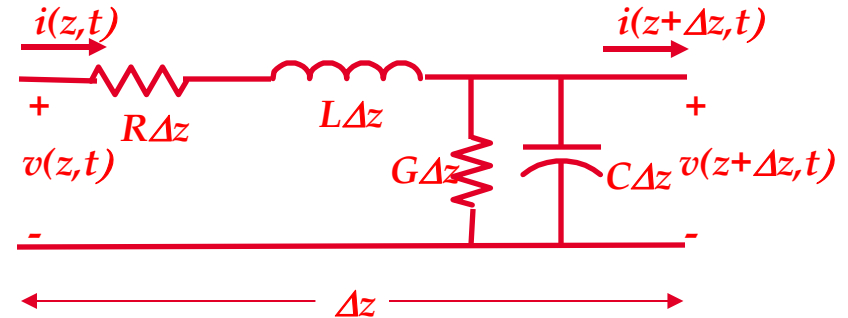

$$v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0$$


$$i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

Divide by Δz and take limit $\Delta z \rightarrow 0$:

$$\frac{\partial v(z, t)}{\partial z} = -Ri(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\frac{\partial i(z, t)}{\partial z} = -Gv(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

Telegrapher equations (Frequency Domain)

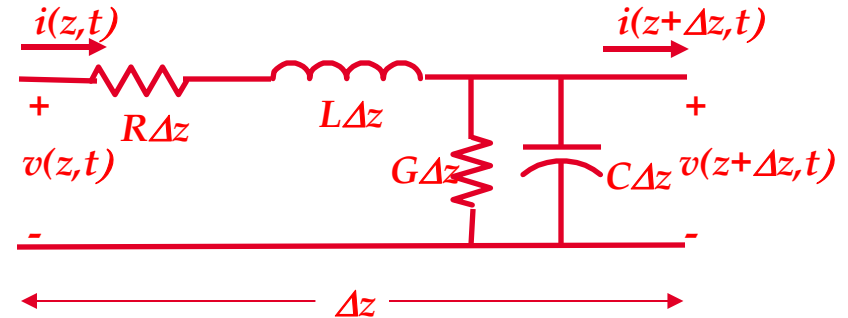

$$\frac{\partial v(z, t)}{\partial z} = -Ri(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\frac{\partial i(z, t)}{\partial z} = -Gv(z, t) - C \frac{\partial v(z, t)}{\partial t}$$



$$\frac{\partial v(z, t)}{\partial t} \leftrightarrow j\omega V(z)$$

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L)I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C)V(z)$$

- Telegrapher Equations
- Wave Propagation on a Transmission Line
 - Propagation constant
 - Characteristic impedance
- The Lossless Transmission Line

Wave propagation on a transmission line

Solving the Telegrapher equations:

$$I. \quad \frac{\partial V(z)}{\partial z} = -(R + j\omega L)I(z)$$

Telegrapher equations (see previous slide)

$$II. \quad \frac{\partial I(z)}{\partial z} = -(G + j\omega C)V(z)$$

$$\Leftrightarrow V(z) = -\frac{1}{(G + j\omega C)} \frac{\partial I(z)}{\partial z}$$

$$\xrightarrow{I.} \frac{\partial V(z)}{\partial z} = -\frac{1}{(G + j\omega C)} \frac{\partial^2 I(z)}{\partial z^2} = -(R + j\omega L)I(z)$$

$$\frac{\partial^2 I(z)}{\partial z^2} = (R + j\omega L)(G + j\omega C)I(z) = \gamma^2 I(z)$$

Wave propagation on a transmission line

Solving the Telegrapher equations gives:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

Where γ is the **complex propagation constant**:

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

Wave propagation on a Tline

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

The relation between Voltage and Current amplitudes is:

$$I_0^+ = \frac{\gamma}{R + j\omega L} V_0^+, I_0^- = \frac{-\gamma}{R + j\omega L} V_0^-$$

$$Z_0 = \frac{R + j\omega L}{\gamma}$$

**Why...?
(next slide)**


Z_0 is the **characteristic impedance** of the Tline.


Wave propagation on a Tline

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$$\begin{aligned} \textcircled{I.} \quad \frac{\partial V(z)}{\partial z} &= -\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z} = -(R + j\omega L)I(z) \\ &= -(R + j\omega L)I_0^+ e^{-\gamma z} - (R + j\omega L)I_0^- e^{\gamma z} \end{aligned}$$

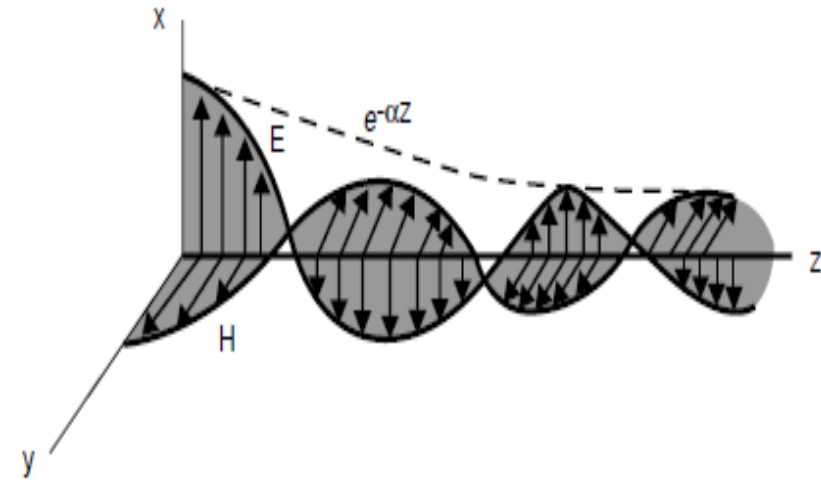

$$I_0^+ = \frac{\gamma}{R + j\omega L} V_0^+$$


$$I_0^- = \frac{-\gamma}{R + j\omega L} V_0^-$$

$$Z_0 = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-} = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}}$$

Z_0 is the **characteristic impedance** of the Tline.

Complex propagation constant




$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

α is called **attenuation constant**.

β is called **phase constant**.


- Telegrapher Equations
- Wave Propagation on a Transmission Line
- The Lossless Transmission Line
 - Reflection coefficient
 - Impedance transformation

The lossless line

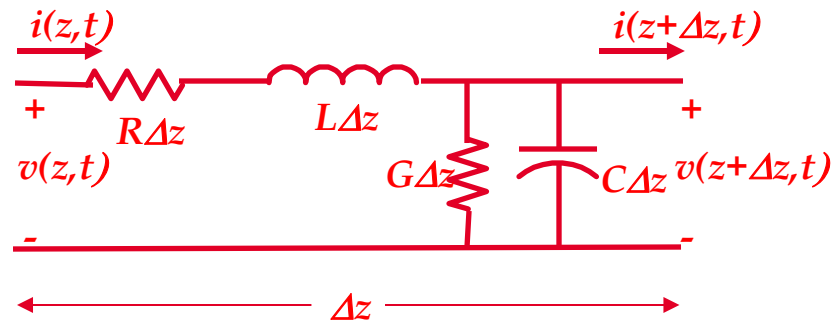

$$R = 0$$

$$G = 0$$

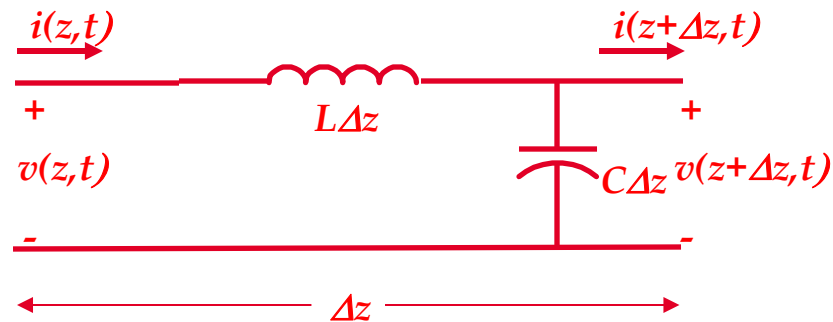

The lossless line

Since $R = 0$ and $G = 0$:

$$\gamma = \alpha + j\beta = j\beta = j\omega\sqrt{LC},$$

$$\beta = \omega\sqrt{LC},$$

$$\alpha = 0,$$

$$Z_0 = \sqrt{\frac{L}{C}},$$


$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}},$$

Wavelength

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

Phase velocity

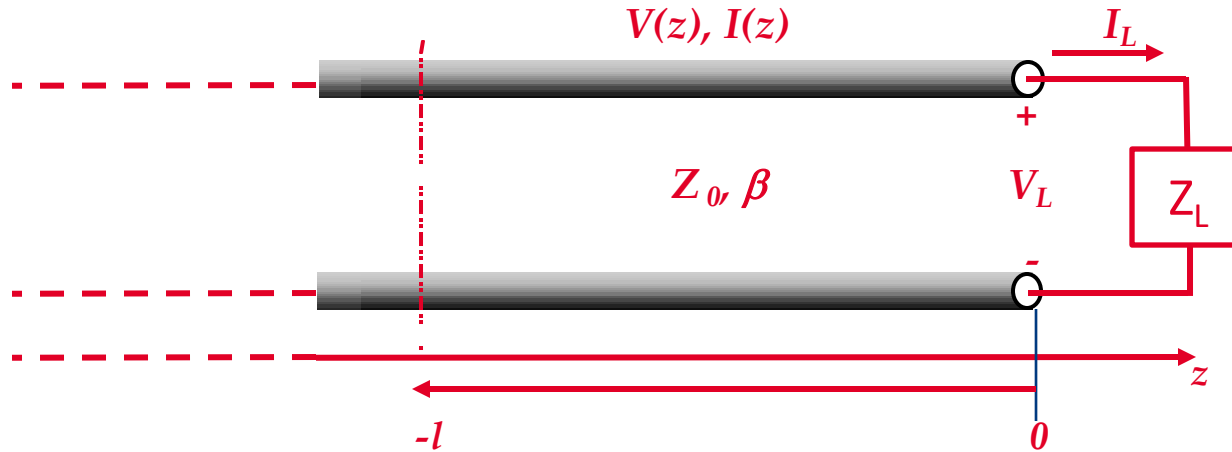
The terminated lossless Transmission Line



Total voltage and current are now:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{j\beta z}$$
$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{j\beta z}$$

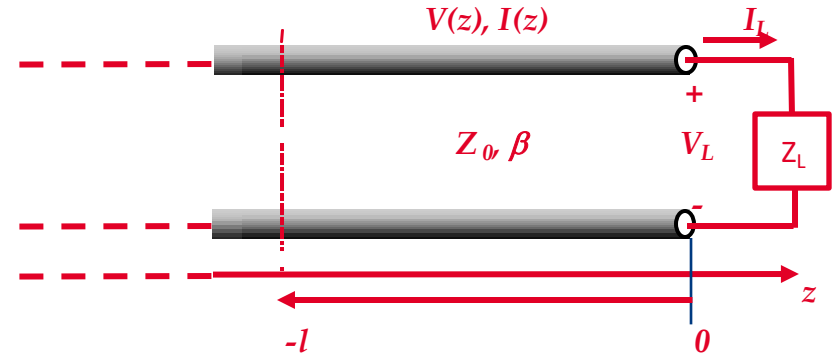The terminated lossless Transmission Line



Total voltage and current at the load at $z=0$:

$$Z_L = \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} Z_0$$


Rewriting gives:

$$V_0^- = \frac{Z_L - Z_0}{Z_L + Z_0} V_0^+$$

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Reflection coefficient

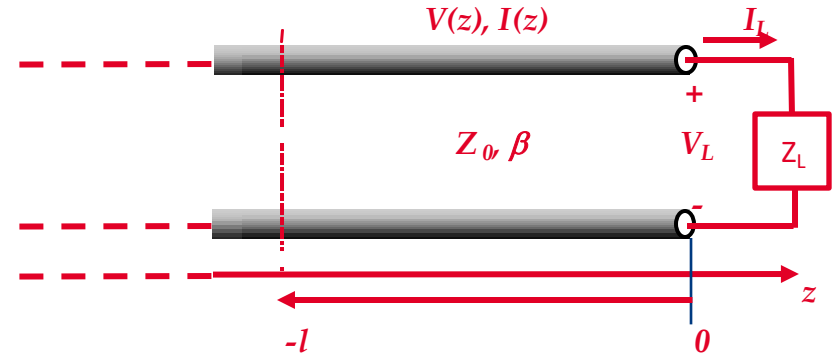The terminated lossless Transmission Line




Special cases:

$$Z_L = Z_0 \Rightarrow \Gamma = 0,$$

$$Z_L = 0 \Rightarrow \Gamma = -1,$$

$$Z_L = \infty \Rightarrow \Gamma = 1.$$

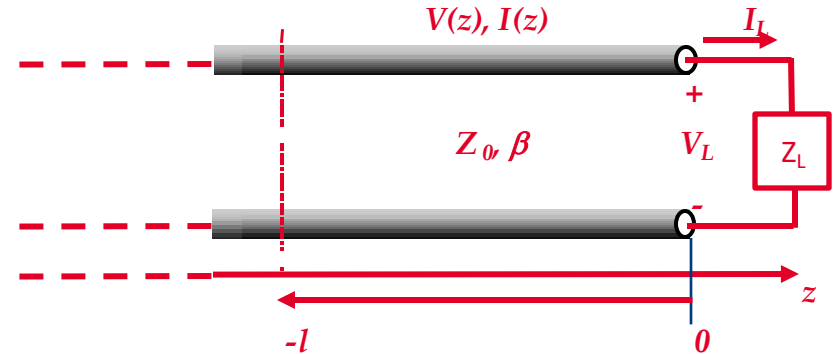The terminated lossless Transmission Line



Γ can be generalised to any point l on the transmission line:

$$\Gamma(z = -l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \Gamma e^{-2j\beta l},$$

$$\Gamma = \Gamma(z = 0).$$

The **impedance** Z_{in} at $z = -l$ is now:

$$Z_{in} = \frac{V(z = -l)}{I(z = -l)} = \frac{V_0^+ \left[e^{j\beta l} + \Gamma e^{-j\beta l} \right]}{V_0^+ \left[e^{j\beta l} - \Gamma e^{-j\beta l} \right]} Z_0 = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

Insertion Loss

Consider two transmission lines connected to each other.

Transmitted wave for $z > 0$:

$$V(z) = V_0^+ T e^{-j\beta z}$$


T is the transmission coefficient:

$$T = 1 + \Gamma = 1 + \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{2Z_1}{Z_1 + Z_0}$$

The insertion loss (IL) is now:


$$\begin{aligned} IL &= -10 \log \left(\frac{P_1}{P_0} \right) = -10 \log \left(\frac{|V_1|^2 / Z_1}{|V_0|^2 / Z_0} \right) \\ &= -20 \log |T| + 10 \log (Z_1 / Z_0) \end{aligned}$$

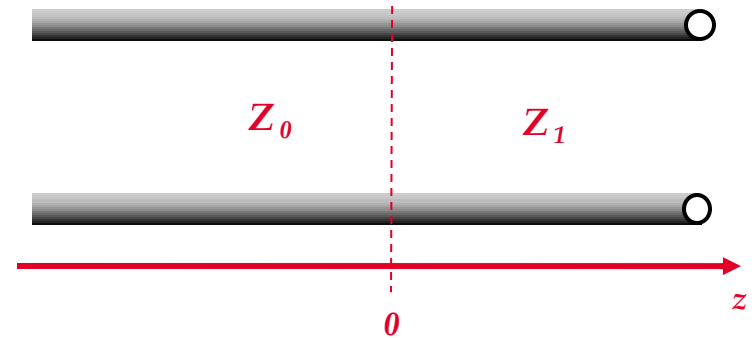Minus sign because we are calculating the loss



Quarter-wave transformer

“The impedance viewpoint”

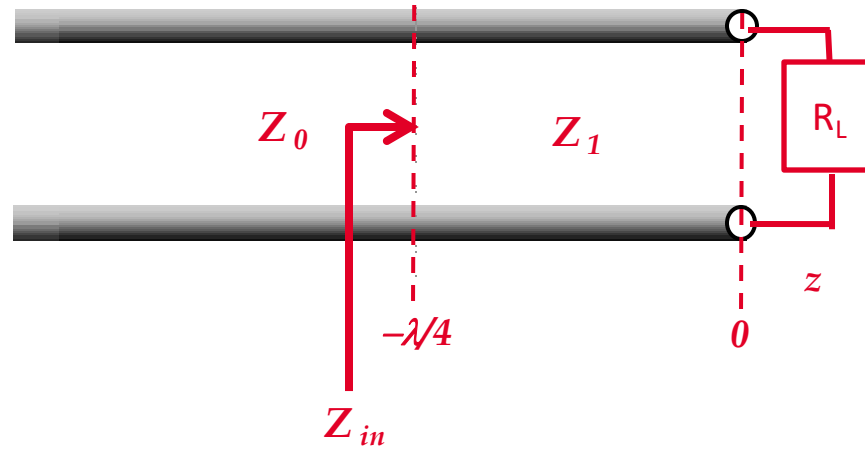

Input impedance at $z=-\lambda/4$:

$$Z_{in} = Z_1 \frac{R_L + jZ_1 \tan \beta l}{Z_1 + jR_L \tan \beta l}$$

Now

$$\beta l = (2\pi / \lambda)(\lambda / 4) = \pi / 2$$

$$Z_{in} = \frac{Z_1^2}{R_L}$$



$$\Gamma = 0$$


if

$$Z_1 = \sqrt{Z_0 R_L}$$

Can we now understand this?


ac simulation

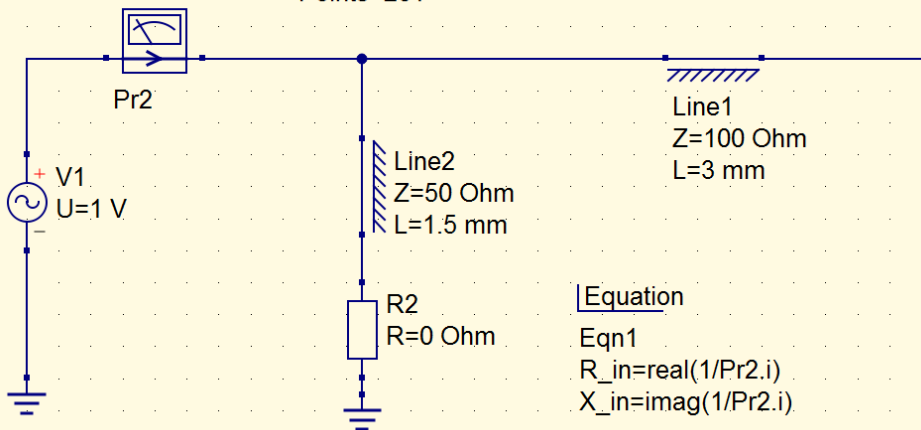AC1
Type=lin
Start=30 GHz
Stop=60 GHz
Points=201



Equation

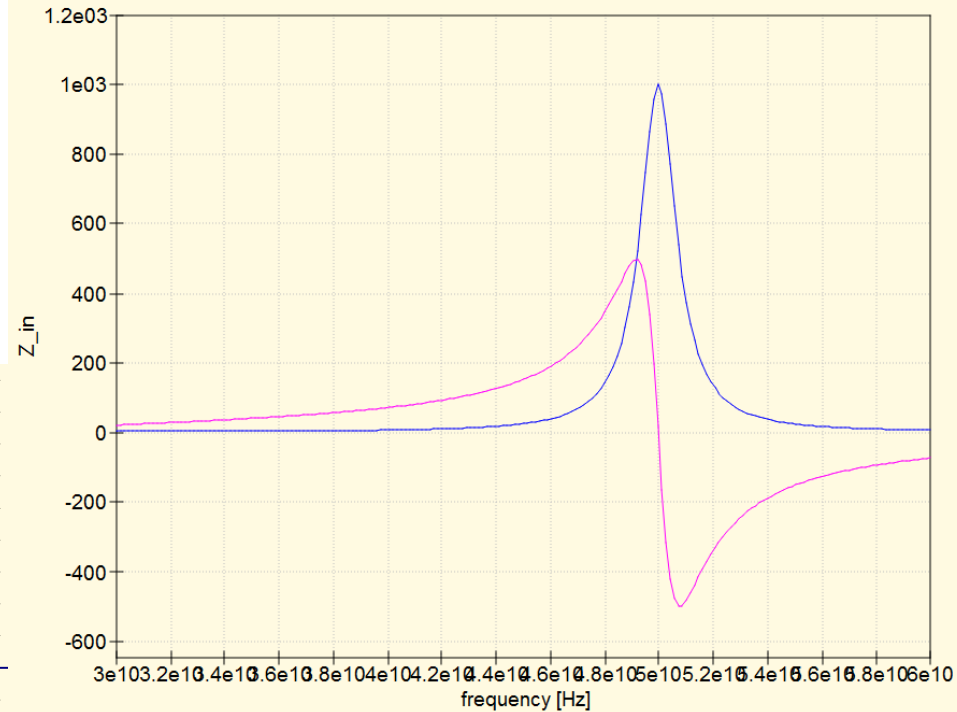Eqn1
 $R_{in} = \text{real}(1/\text{Pr2.i})$
 $X_{in} = \text{imag}(1/\text{Pr2.i})$




The Smith Chart

Smith Chart



Phillip H. Smith (1905-1987)

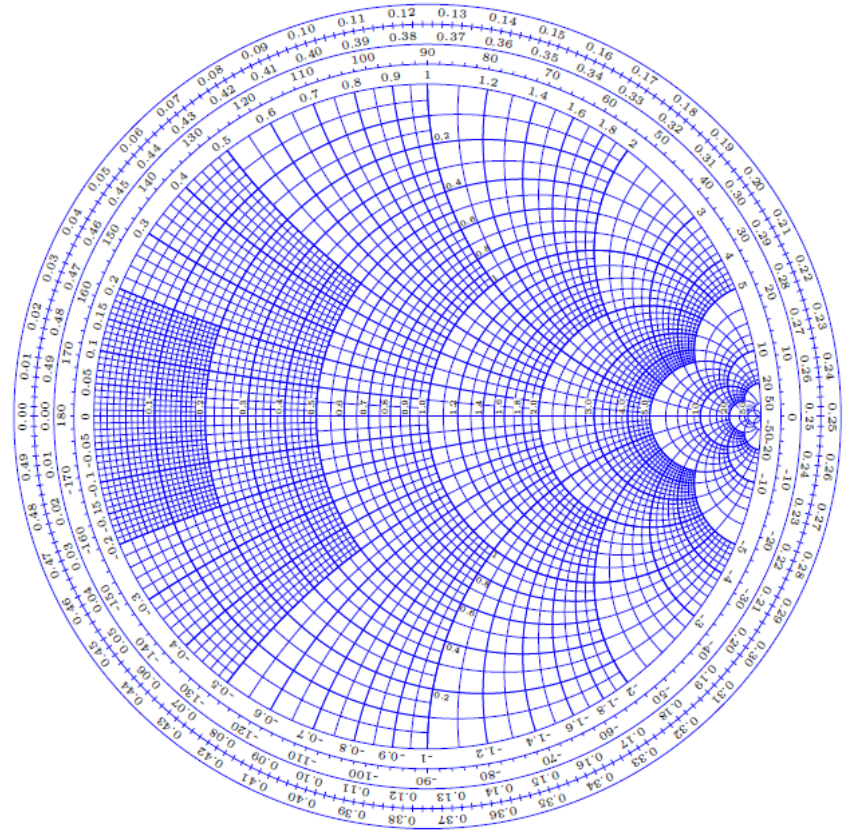


- Invented by Phillip H. Smith in 1939
- Easily usable graphical representation of the complex reflection coefficient Γ
- Easily reading the associated complex terminating impedance


“Derivation” of the Smith Chart

$$\text{Re}\{Z\} = \text{const.}$$

Z domain

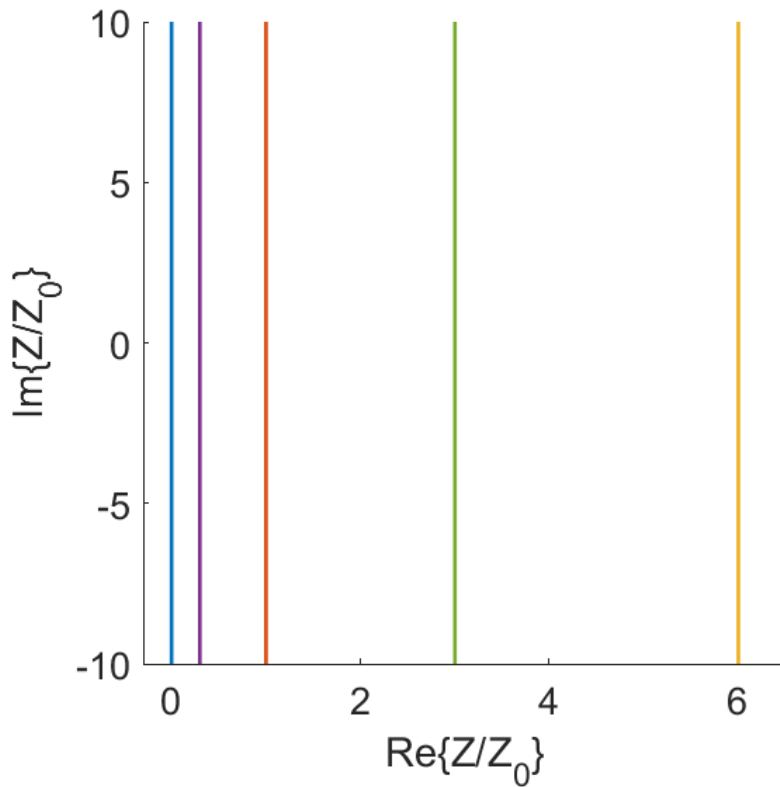


Γ domain

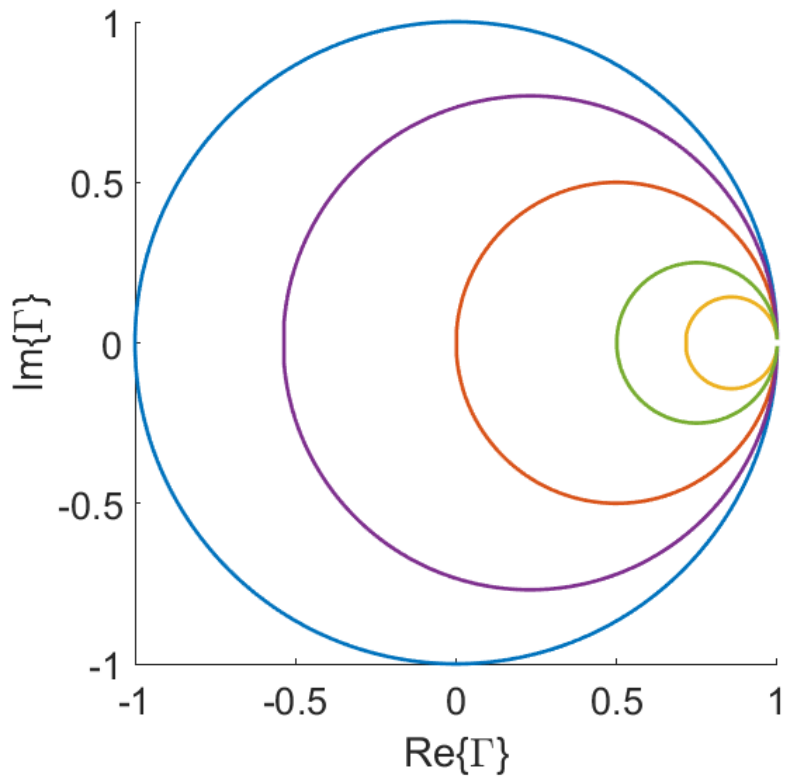


“Derivation” of the Smith Chart

$$\text{Im}\{Z\} = \text{const.}$$

Z domain

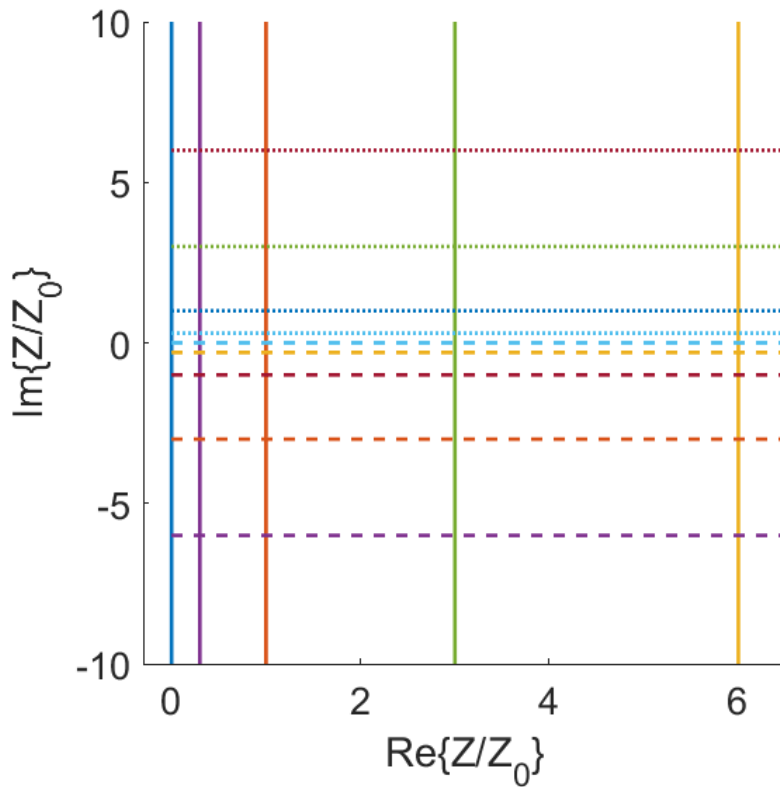


Γ domain

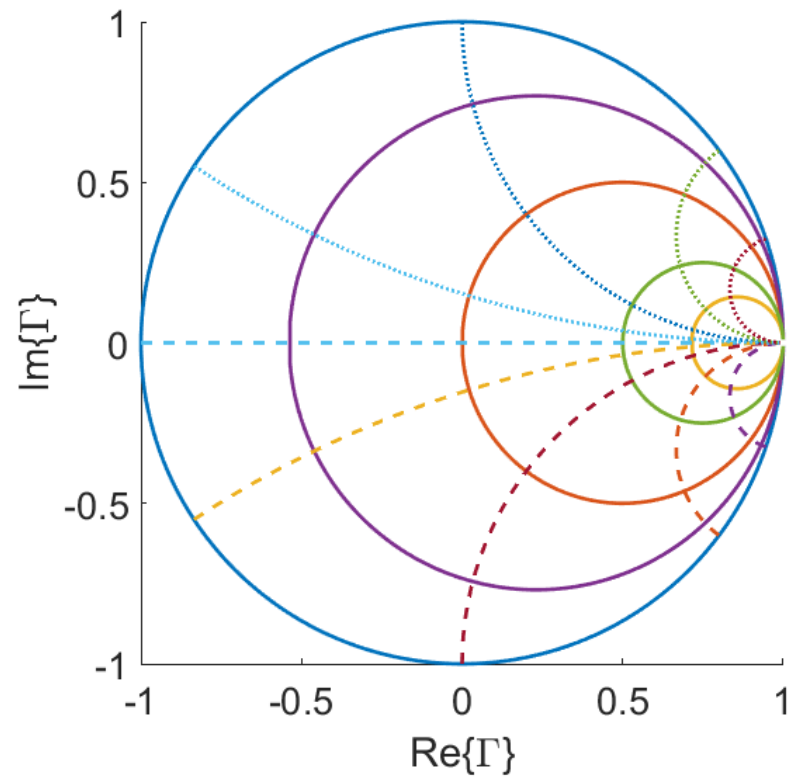


“Derivation” of the Smith Chart

$$\text{Im}\{Z\} = \text{const.}$$

Z domain

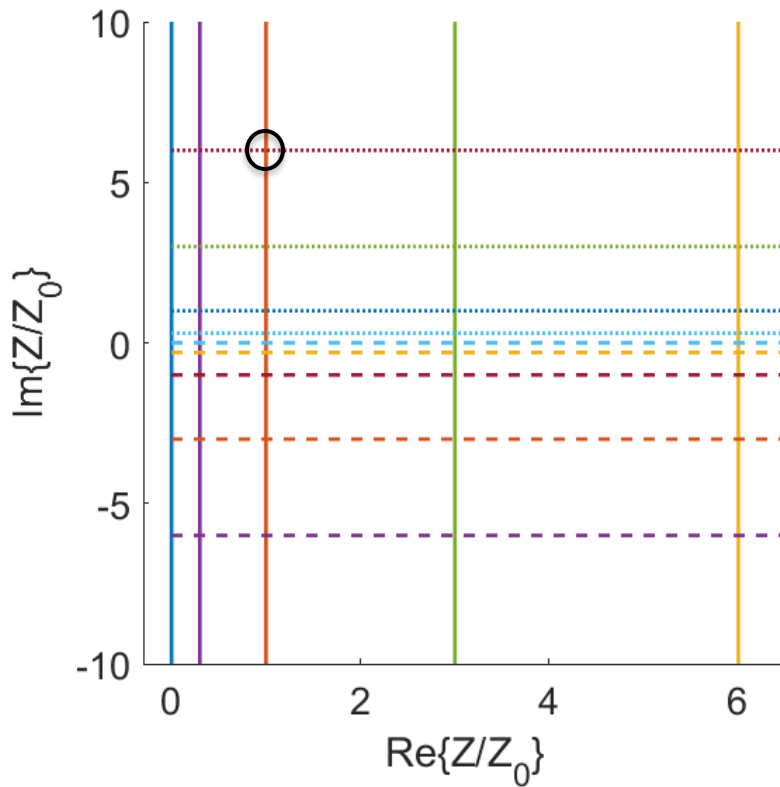


Γ domain

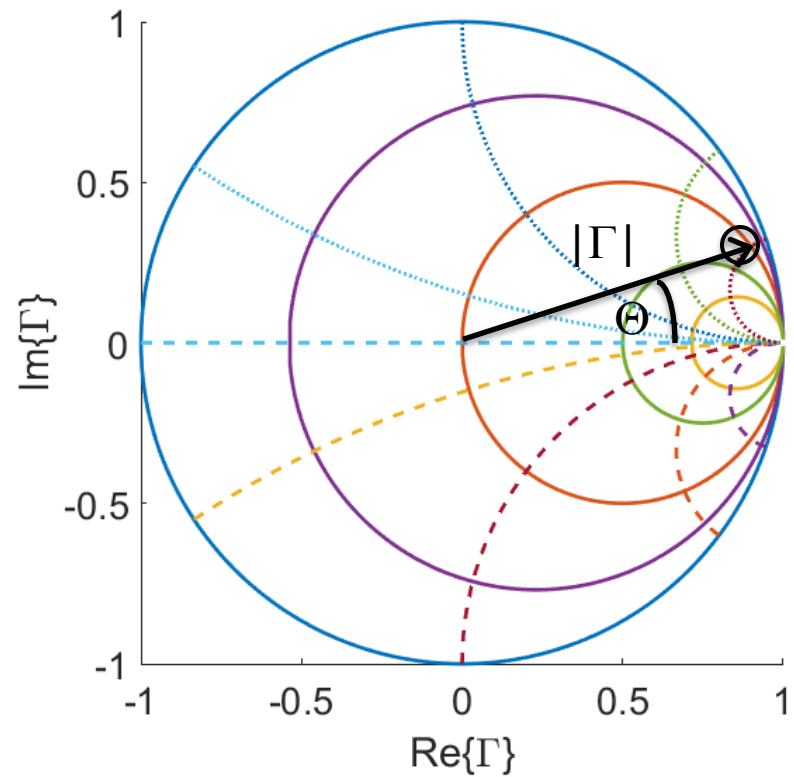

“Derivation” of the Smith Chart

The same can be done for admittances!

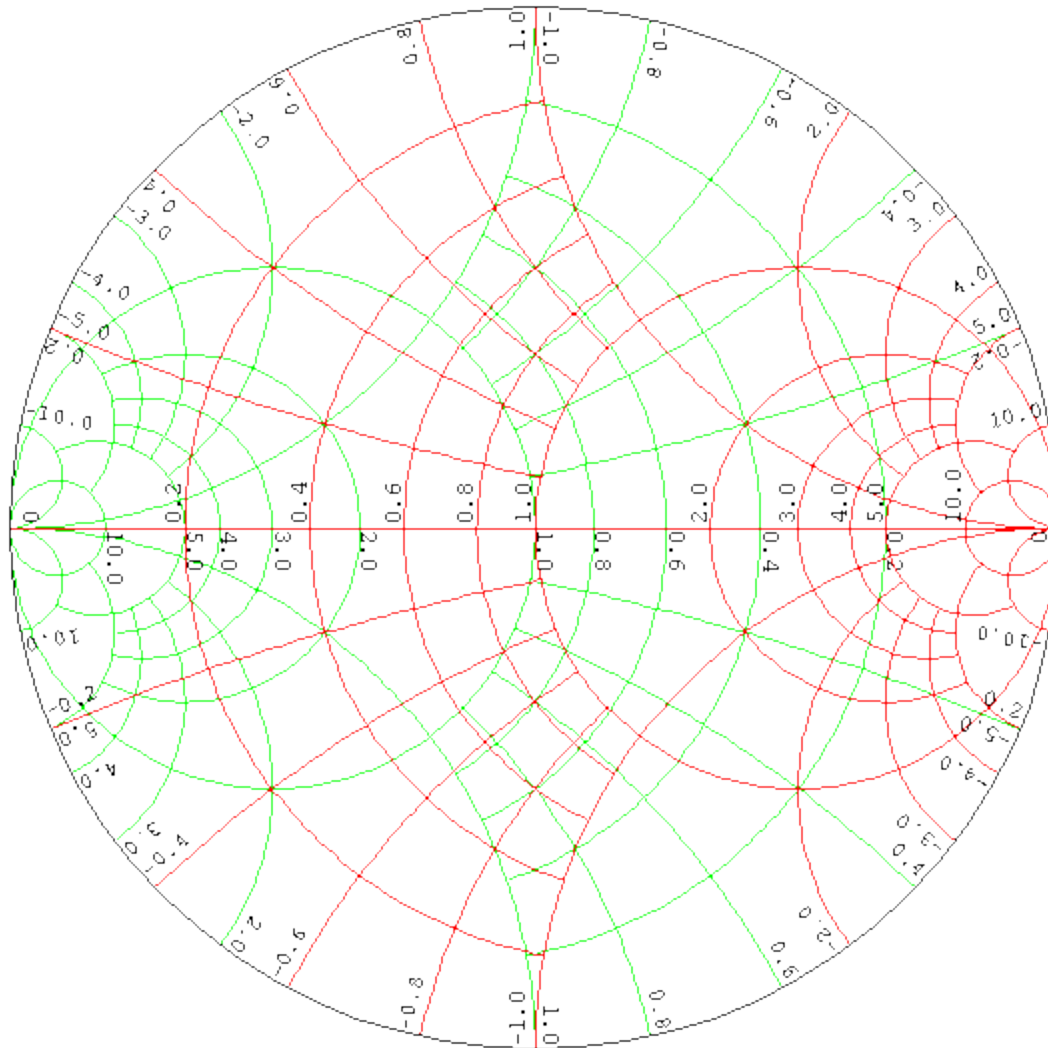


$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z - Z_0}{Z + Z_0}$$

$$\Gamma = \frac{\frac{Z}{Z_0} - 1}{\frac{Z}{Z_0} + 1} = \frac{1 - \frac{Y}{Y_0}}{1 + \frac{Y}{Y_0}}$$

Red lines: $\frac{Z}{Z_0}$
Green lines: $\frac{Y}{Y_0}$

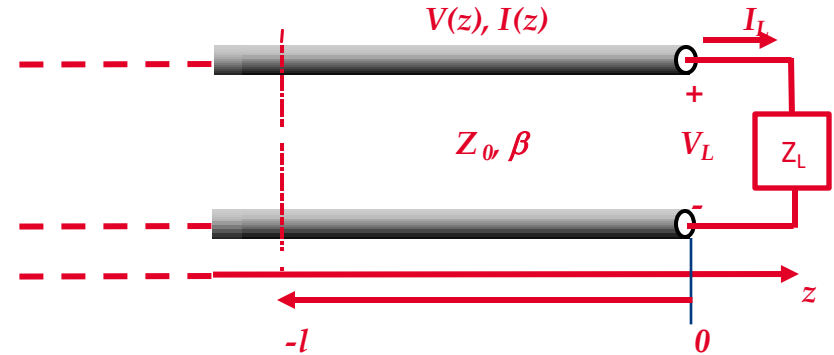The terminated lossless Transmission Line




From previously:

Γ at any point l on the transmission line:

$$\Gamma(z = -l) = \frac{V_0^- e^{-j\beta l}}{V_0^+ e^{j\beta l}} = \Gamma e^{-2j\beta l}$$

$$\beta = \frac{2\pi}{\lambda}$$
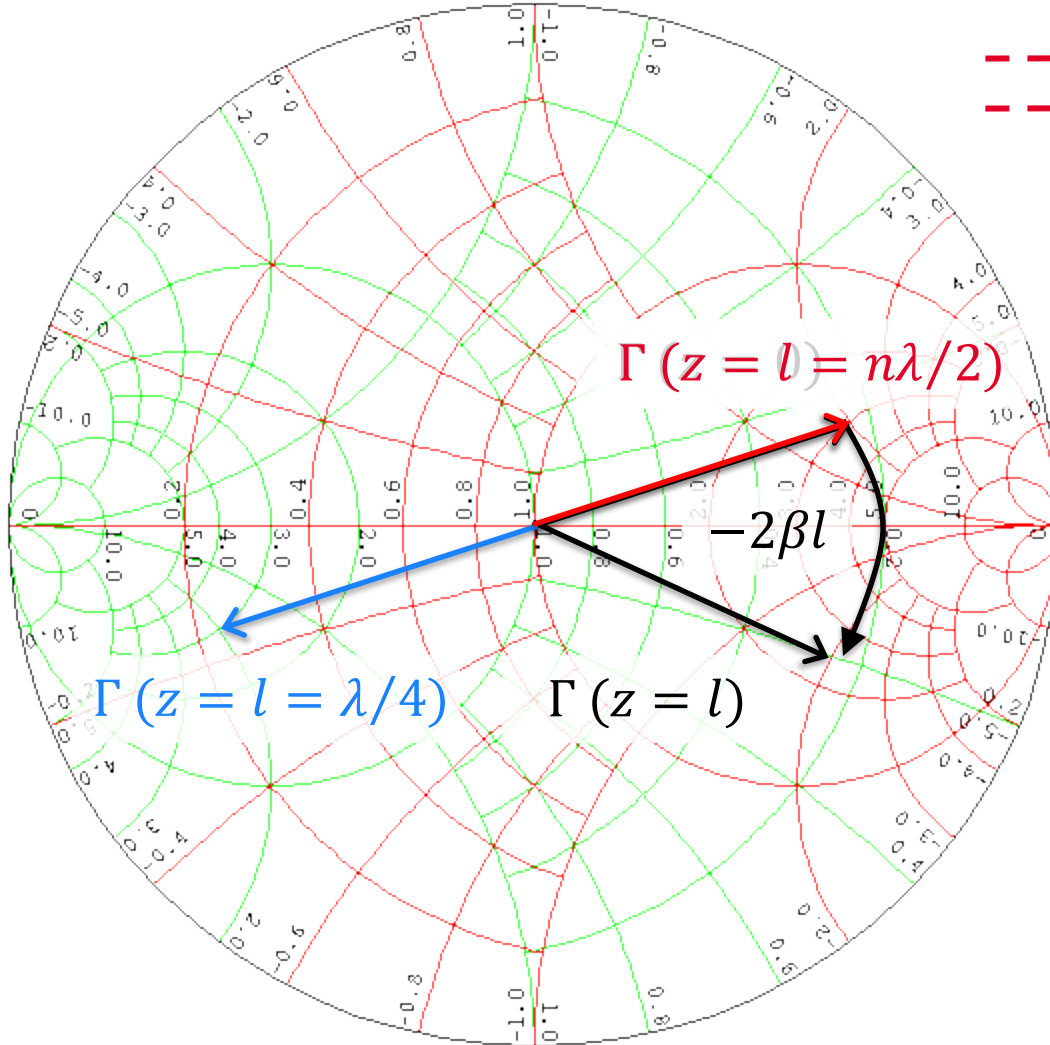
$$\Rightarrow -2\beta l = -2\pi \text{ for } l = \frac{\lambda}{2}$$



Smith Chart - Summary

- The Smith Chart contains
 - Magnitude, $|\Gamma|$, of the reflection coefficient
 - Phase, Θ , of the reflection coefficient
 - Real and imaginary part of the reflection coefficient
 - Real and imaginary part of the load impedance and admittance (normalised to the reference impedance Z_0 and admittance Y_0 , respectively)