

Components in wireless technology, 5XTC0

Module 5

Lecture: Low-Noise Amplifier design

Vojkan Vidojkovic



Technische Universiteit
Eindhoven
University of Technology

Where innovation starts

Outline

- Recap
 - S parameters
 - Power gain definitions
 - Transducer gain
 - Gain circles
 - Stability circles
- Noise
- Characterization of noise in amplifiers
- Noise in multi-stage amplifiers
- Noise circles


Learning Objectives

- Recap
 - Understand S-parameters definition
 - Understand the different gains of an amplifier
 - Understand gain circles and stability circles
- Understand thermal noise
- Understand how to characterize noise in amplifiers
- Noise in multi-stage amplifiers
- Understand noise circles

Outline

- **Recap**
 - S parameters
 - Power gain definitions
 - Transducer gain
 - Gain circles
 - Stability circles
- Noise
- Characterization of noise in amplifiers
- Noise in multi-stage amplifiers
- Noise circles


2-port network description: S parameters

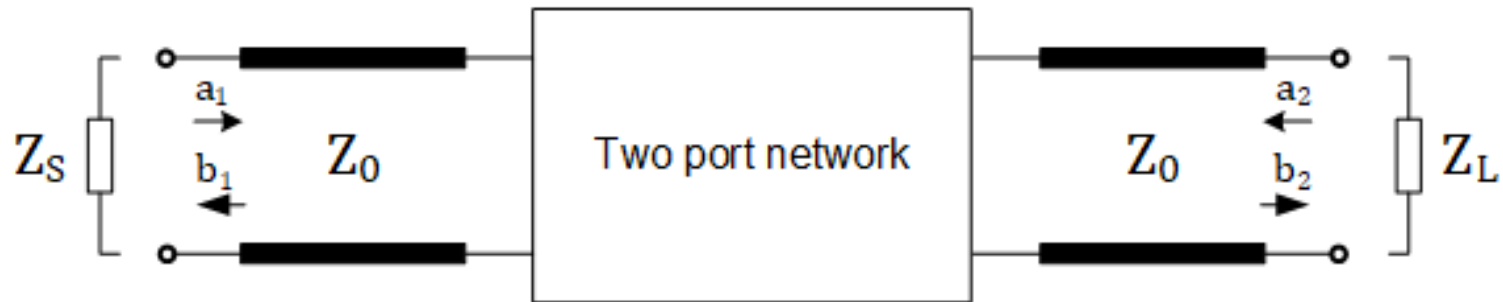

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad (\text{input reflection coefficient with output properly terminated})$$
$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad (\text{forward transmission coefficient with output properly terminated})$$
$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \quad (\text{output reflection coefficient with input properly terminated})$$
$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \quad (\text{reverse transmission coefficient with input properly terminated})$$

- To measure S parameters matched terminations are required: $Z_L = Z_0$ and $Z_S = Z_0$
- At high frequencies matched terminations could be realized much easier compared to short and open terminations

Gain definitions

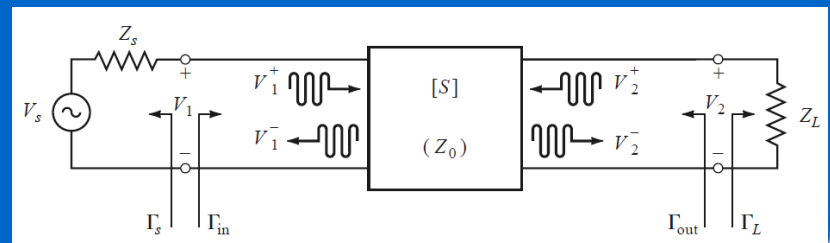

Power gain G : Ratio of the power dissipated in the load Z_L to the power delivered to the input of the two-port network

Available power gain G_A : Ratio of the power available from the two-port network to the power available from the source. Assumes conjugate matching of source and load impedance.

Transducer power gain G_T : Ratio of the power delivered to the load to the power available from the source. Assumes a matched source impedance.

Unilateral transducer power gain G_{TU} :

Transducer power gain for a device with $S_{12}=0$

Amplifier gains: Equations

Power gain:

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22}\Gamma_L|^2}$$

Available power gain:

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{out}|^2)}$$

Transducer power gain:


$$G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_S\Gamma_{in}|^2 |1 - S_{22}\Gamma_L|^2}$$

Unilateral transducer
power gain:

$$G_{TU} = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11}$$

General transistor amplifier circuit

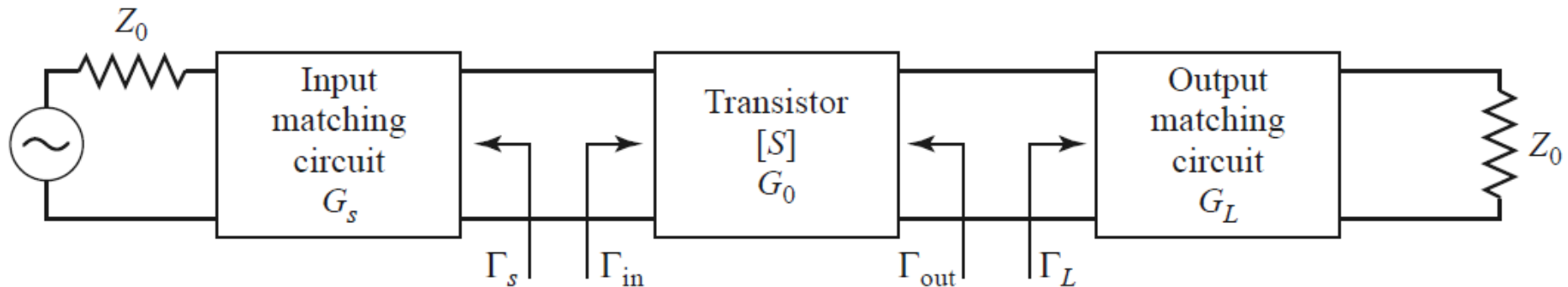

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2}$$

$$G_0 = |S_{21}|^2$$

Unilateral case

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$G_T = G_S G_0 G_L$$

$$G_{T,dB} = G_{S,dB} + G_{0,dB} + G_{L,dB}$$

Remark: If $S_{12}=0$ then: $\Gamma_{out} = S_{22}$ and $\Gamma_{in} = S_{11}$

Circles of constant power gain

Unilateral transducer power gain G_{TU} :

$$\begin{aligned}
 G_{TU} &= \left. \frac{P_L}{P_{AVS}} \right|_{\underline{S}_{12}=0} \\
 &= \frac{1 - |\underline{\Gamma}_S|^2}{|1 - \underline{\Gamma}_S \underline{S}_{11}|^2} \underbrace{|\underline{S}_{21}|^2}_{\downarrow G_0} \frac{1 - |\underline{\Gamma}_L|^2}{|1 - \underline{\Gamma}_L \underline{S}_{22}|^2} \\
 &= \underbrace{G_S}_{\downarrow \text{Impact of the input matching network on the gain}} \cdot \underbrace{G_0}_{\downarrow \text{Transistor gain}} \cdot \underbrace{G_L}_{\downarrow \text{Impact of the output matching network on the gain}}
 \end{aligned}$$

For which values of Γ_S do we achieve the desired value of G_S ?


For which values of Γ_L do we achieve the desired value of G_L ?

The values of Γ_S that lead to a constant G_S are situated on circles in the complex Γ plane.

The values of Γ_L that lead to a constant G_L are situated on circles in the complex Γ plane.

These circles are called:
Constant gain circles

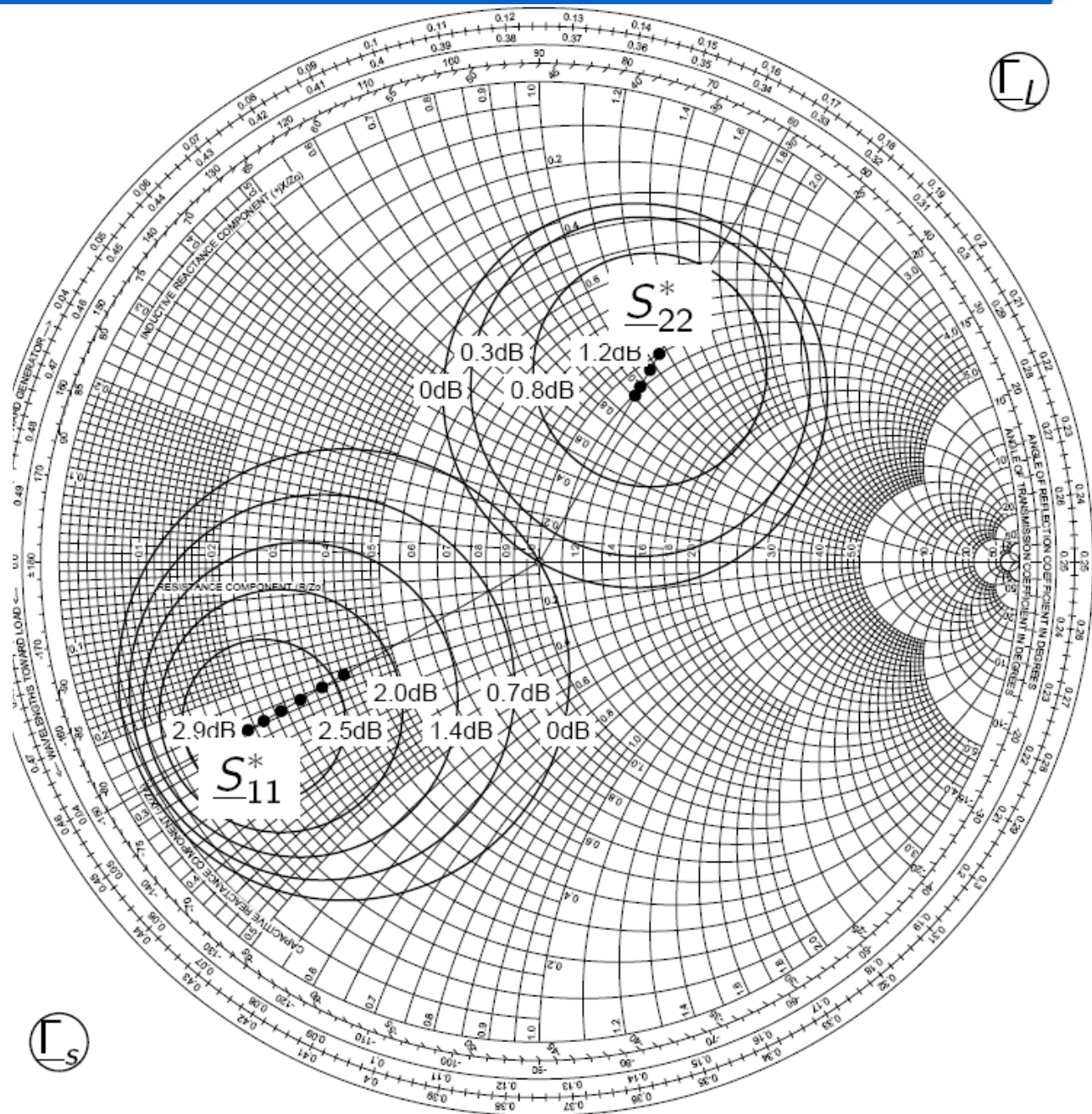For $\Gamma_S = S_{11}^*$
maximum G_S is obtained.
For $\Gamma_L = S_{22}^*$
maximum G_L is obtained.



Circles of constant power gain

Maximum gain of the input and output matching networks

$$G_{S_{\max}} = \frac{1}{1 - |S_{11}|^2}, \quad \text{for } \Gamma_S = S_{11}^*$$

$$G_{L_{\max}} = \frac{1}{1 - |S_{22}|^2}, \quad \text{for } \Gamma_L = S_{22}^*$$

Normalized gain factors g_S and g_L

$$g_S = \frac{G_S}{G_{S_{\max}}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} (1 - |S_{11}|^2),$$

$$g_L = \frac{G_L}{G_{L_{\max}}} = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} (1 - |S_{22}|^2).$$

Center and radius of the constant gain circle for the input and output matching network

$$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S)|S_{11}|^2},$$


$$R_S = \frac{\sqrt{1 - g_S} (1 - |S_{11}|^2)}{1 - (1 - g_S)|S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L)|S_{22}|^2},$$

$$R_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L)|S_{22}|^2}$$

More info: book of Pozar, page 624, book of Gonzalez, page 103

Stability discussion of 2-port circuits

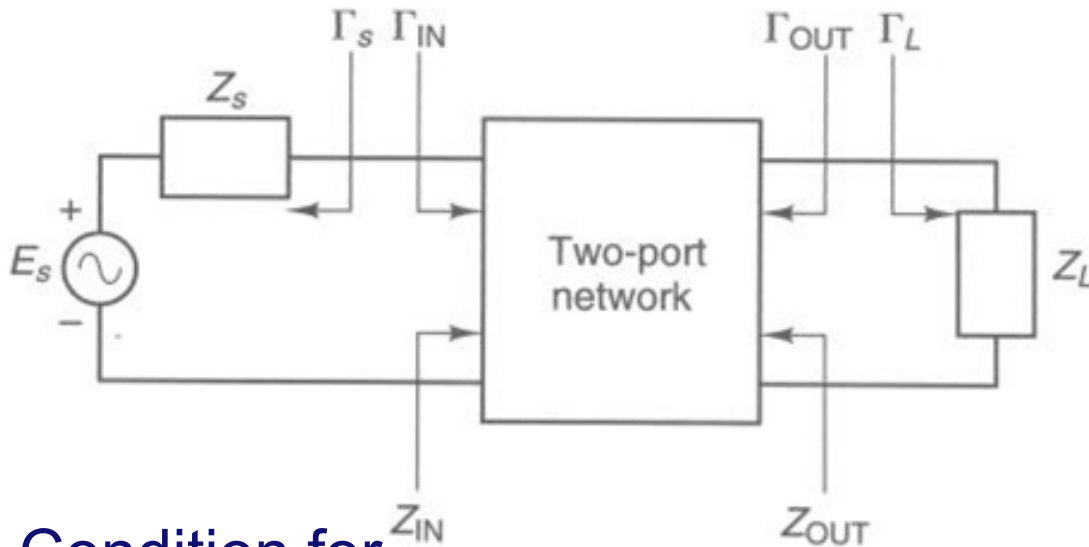

Stability analysis
of an amplifier means:
Investigation whether
there can be oscillations

Condition for
“**unconditionally stable**” device:

for all $|\Gamma_L| < 1$ and $|\Gamma_S| < 1$

$$\Rightarrow \begin{cases} |\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| < 1 \\ |\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right| < 1 \end{cases}$$

If at a given frequency
there are source and load
reflection coefficients, for which
this condition does not hold
the device is called
“**potentially unstable**”.

Input stability circles

Boundary between stability and instability is given by:

$$|\Gamma_{\text{OUT}}| = 1$$

$$|\Gamma_{\text{OUT}}| = \left| S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} \right| = 1$$

$$\left| \Gamma_s - \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

Circle equation
in the complex Γ -plane

$$r_s = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \quad (\text{radius})$$

$$C_s = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad (\text{center})$$

This circle is called the **output stability circle**. It is the boundary between the region Γ_s that lead to a stable or an unstable reflection amplifier.

$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

An equivalent derivation of the output reflection coefficient leads to the **input stability circle**.

Output stability circles

Boundary between stability and instability is given by:

$$|\underline{\Gamma}_{in}| = 1$$

$$\Leftrightarrow \left| \underline{S}_{11} + \frac{\underline{S}_{12}\underline{S}_{21}\underline{\Gamma}_L}{1 - \underline{S}_{22}\underline{\Gamma}_L} \right| = 1$$

$$\left| \underline{\Gamma}_L - \frac{\underline{S}_{22}^* - \underline{\Delta}^* \underline{S}_{11}}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \right|^2 = \left| \frac{\underline{S}_{12}\underline{S}_{21}}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \right|^2$$

← Circle equation
in the complex Γ -plane

$$|\underline{\Gamma}_L - \underline{C}_L|^2 = |\underline{R}_L|^2$$



This circle is called the **output stability circle**. It is the boundary between the region Γ_L that lead to a stable or an unstable reflection amplifier.

$$\underline{C}_L = \frac{(\underline{S}_{22} - \underline{\Delta}\underline{S}_{11}^*)^*}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \quad (\text{center}),$$

$$\underline{R}_L = \left| \frac{\underline{S}_{12}\underline{S}_{21}}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \right| \quad (\text{radius}).$$


$$\underline{\Delta} = \underline{S}_{11}\underline{S}_{22} - \underline{S}_{12}\underline{S}_{21}$$

An equivalent derivation of the output reflection coefficient leads to the **input stability circle**.

Construction Of the Output Stability circle

$$\left| \Gamma_{in} \right| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right|$$

$$\left| \Gamma_{out} \right| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right|$$

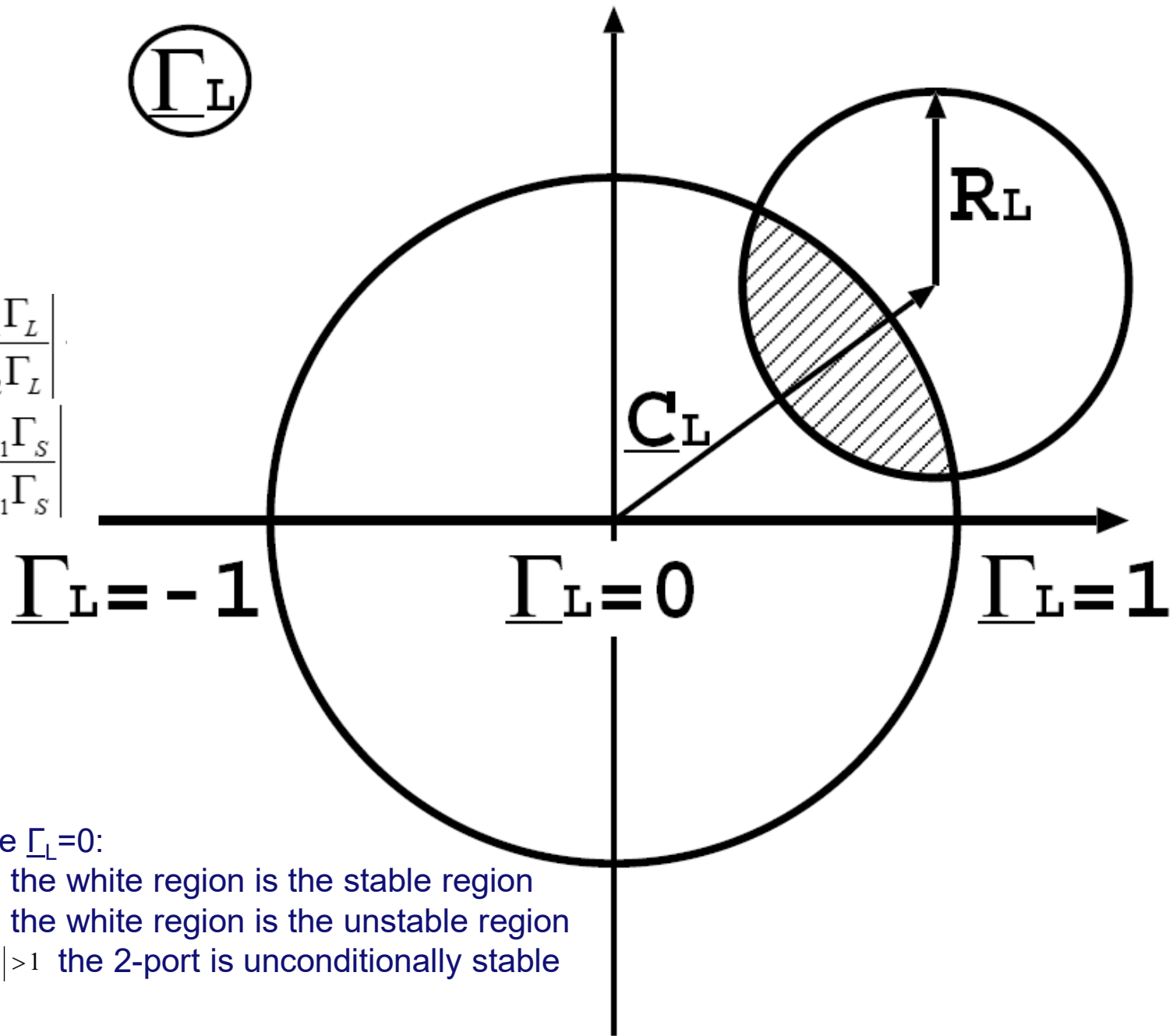

1) Consider the case $\Gamma_L = 0$:

if $|\Gamma_{in}| = |S_{11}| < 1$, then the white region is the stable region

if $|\Gamma_{in}| = |S_{11}| > 1$, then the white region is the unstable region

2) If $|S_{11}| < 1$ and $|C_L - R_L| > 1$ the 2-port is unconditionally stable

Tests for unconditional stability

If $|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1$

Rollet stability factor K

and $K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + \Delta^2}{2|S_{12}S_{21}|} > 1$

than the 2-port is unconditionally stable.

Unilateral case: $S_{12}=0$

Conditions for
unconditional
stability:

$$|S_{11}| < 1$$

$$|S_{22}| < 1$$

Outline

- Recap
 - S parameters
 - Power gain definitions
 - Transducer gain
 - Gain circles
 - Stability circles
- **Noise**
- Characterization of noise in amplifiers
- Noise in multi-stage amplifiers
- Noise circles

Why do we need to analyze noise?

- Link budget allows to calculate received signal power S across a wireless link
- To transmit information across a wireless link, the received signal power must be significantly larger than the noise power N .
- The ratio between the signal power and the noise power is called “Signal-to-noise ratio” SNR:

$$SNR = \frac{S}{N}$$

- If we cannot distinguish the signal from the noise we cannot extract the information!

Origin of the noise power

All electronic devices:


1. **Thermal noise:** Thermal agitation of electrons
2. **Shot noise:** Fluctuation of current due to number of discrete charges

Semiconductor devices have additionally:

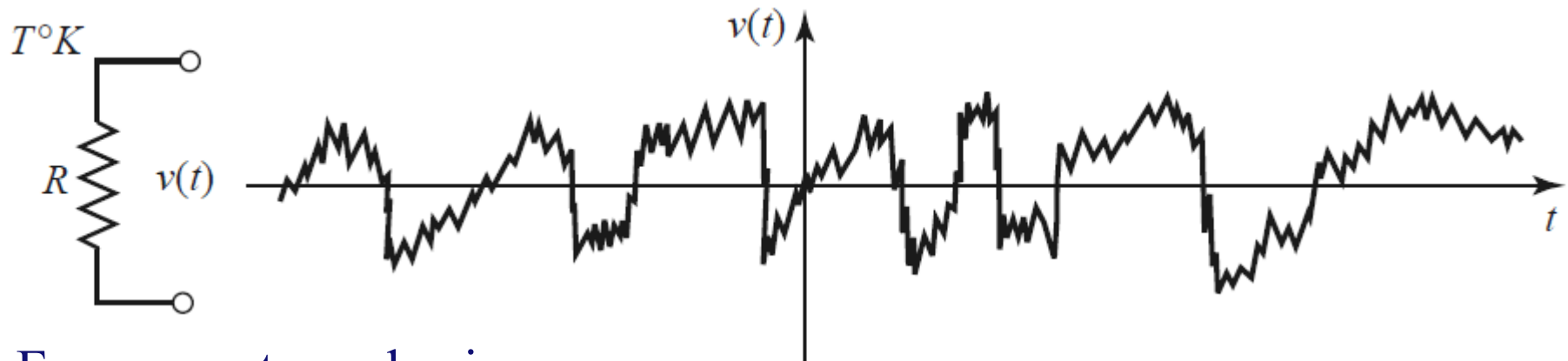3. **Flicker noise:** $1/f$ noise caused by impurities in the channel region, recombination and generation of charges, ...
4. **Burst noise:** Charge trapping at semiconductor interfaces
e.g. FET channel bias that is randomly changed
5. **Avalanche noise:** Free carrier generation in strong electric fields due to carrier acceleration (also this is a statistic process)

Thermal noise

- Electrons at a temperature T have thermal energy
- They move randomly inside the material and generate random voltage drops
- Example: Resistor at temperature T :



From quantum physics:

$$P_n = k_B \cdot T \cdot B$$

Average voltage is zero.

But: Non-zero average power!

k_B : Boltzmann constant


T : temperature in Kelvin

B : Bandwidth of the system

White noise: Representation of a resistor as a noiseless resistor and a noise voltage source

Noiseless
resistor

Noise
source

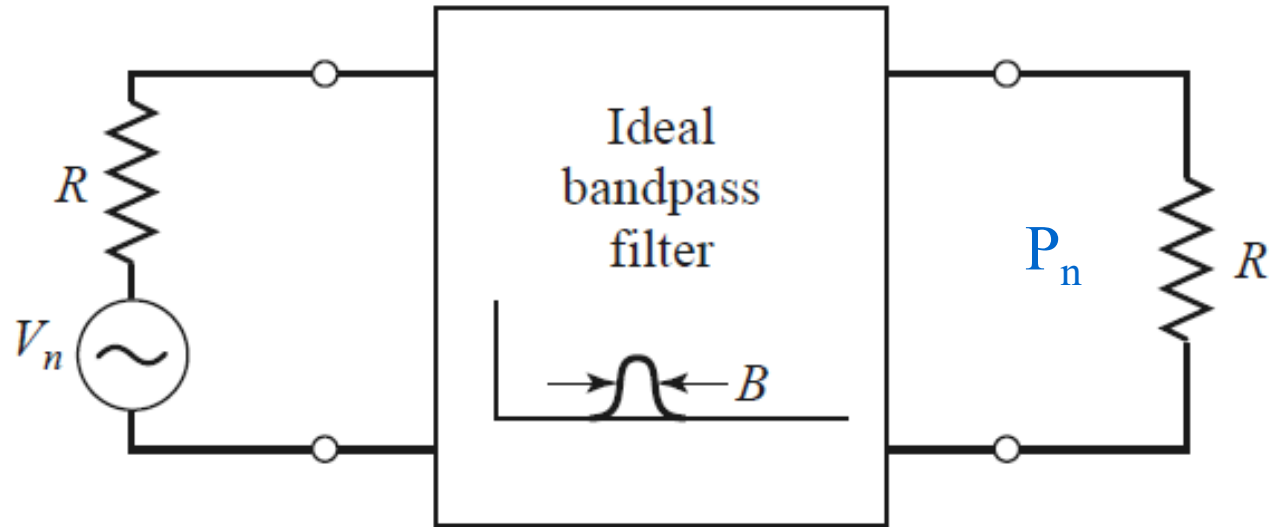

Available noise power:


$$P_n = \frac{V_N^2}{4R_N} = k_B TB$$

What is the noise power at room temperature (300 K)
for a bandwidth of 1Hz? Calculate it in W as well as in dBm.

$$k_B = 1,38 \cdot 10^{-23} \frac{\text{kgm}^2}{\text{s}^2 \text{K}}$$

$$T(K) = T(^{\circ}\text{C}) + 273$$

Noise of an arbitrary source

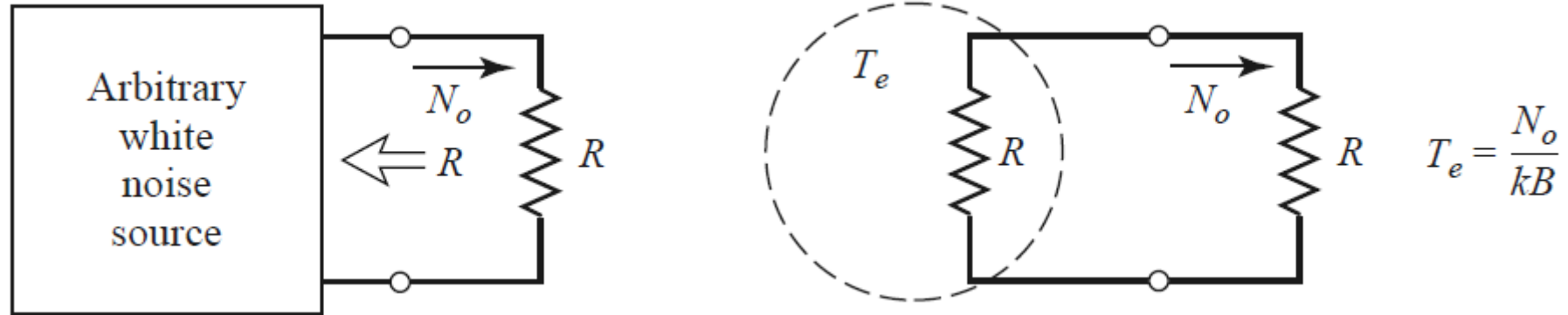

Measure the noise power N_o and input resistance R .

Define the equivalent noise temperature as:
$$T_e = \frac{N_o}{k_B B}$$

For a noise analysis: use a resistor of temperature T_e .


This resistor produces the same noise power as the original source.

Noise analysis is always aiming at noise power.


Outline

- Recap
 - S parameters
 - Power gain definitions
 - Transducer gain
 - Gain circles
 - Stability circles
- Noise
- **Characterization of noise in amplifiers**
- Noise in multi-stage amplifiers
- Noise circles

Noise temperature of an amplifier

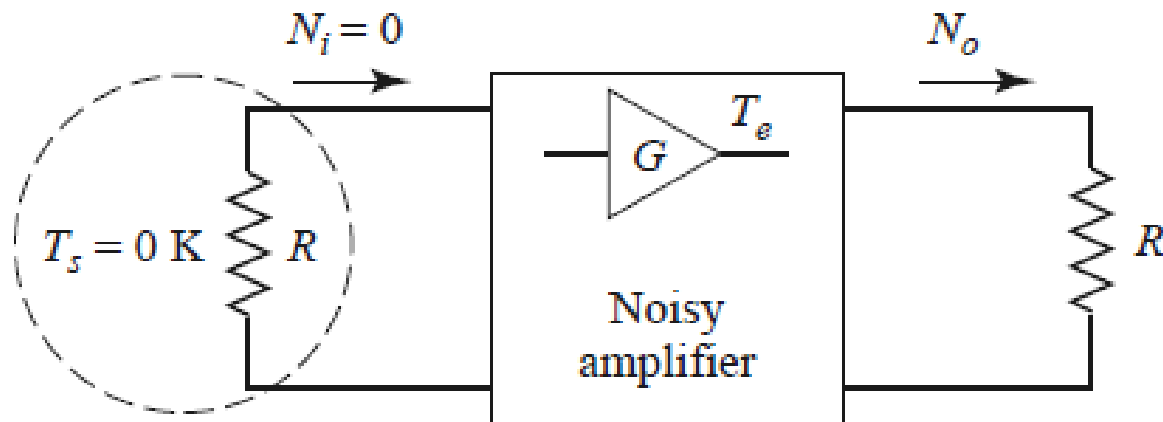

(a)

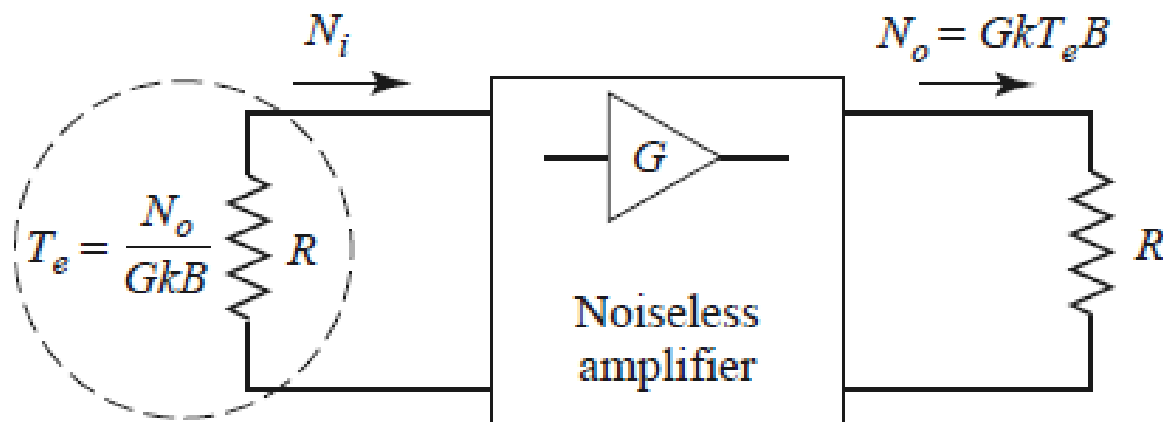


(b)

Remark:
The equivalent
noise source
is at the input of the
amplifier

Definition: Noise figure

For room temperature input noise level!

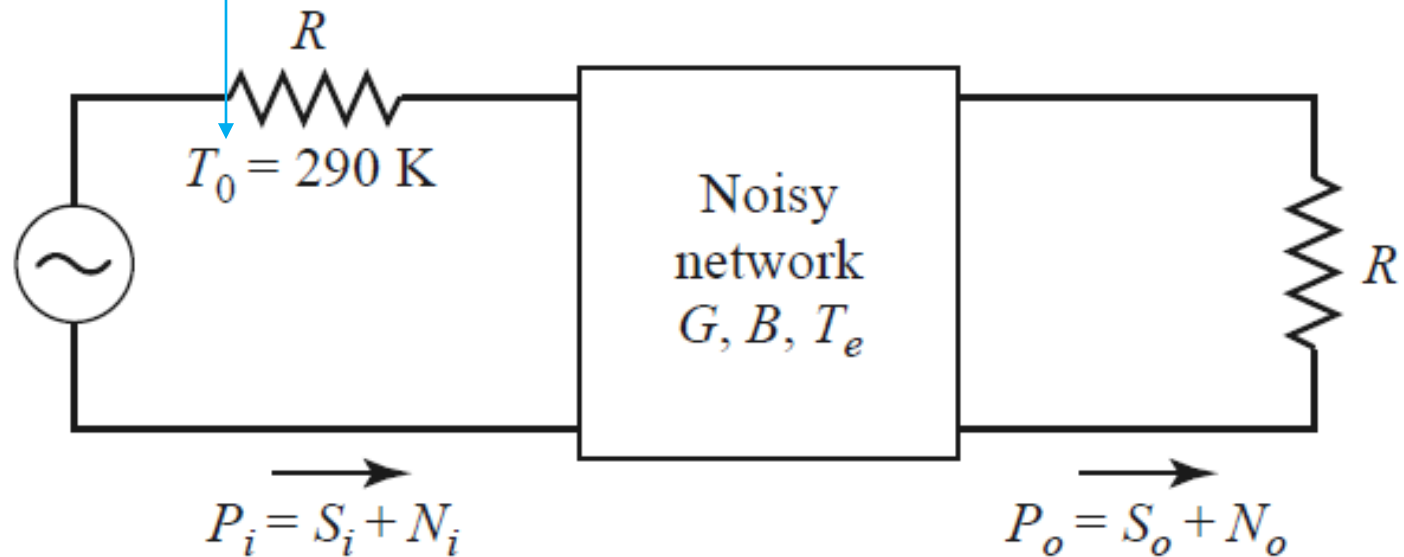

$$F = \frac{S_i / N_i}{S_o / N_o} = \frac{S_i}{S_o} \frac{N_o}{N_i} = \frac{1}{G} \frac{G k_B (T_0 + T_e) B}{k_B T_0 B} = 1 + \frac{T_e}{T_0} > 1$$


$NF = 10 \text{ Log } (F)$

- $\left\{ \begin{array}{l} NF \rightarrow \text{noise figure (dB)} \\ F \rightarrow \text{noise factor} \end{array} \right.$

Outline

- Recap
 - S parameters
 - Power gain definitions
 - Transducer gain
 - Gain circles
 - Stability circles
- Noise
- Characterization of noise in amplifiers
- **Noise in multi-stage amplifiers**
- Noise circles

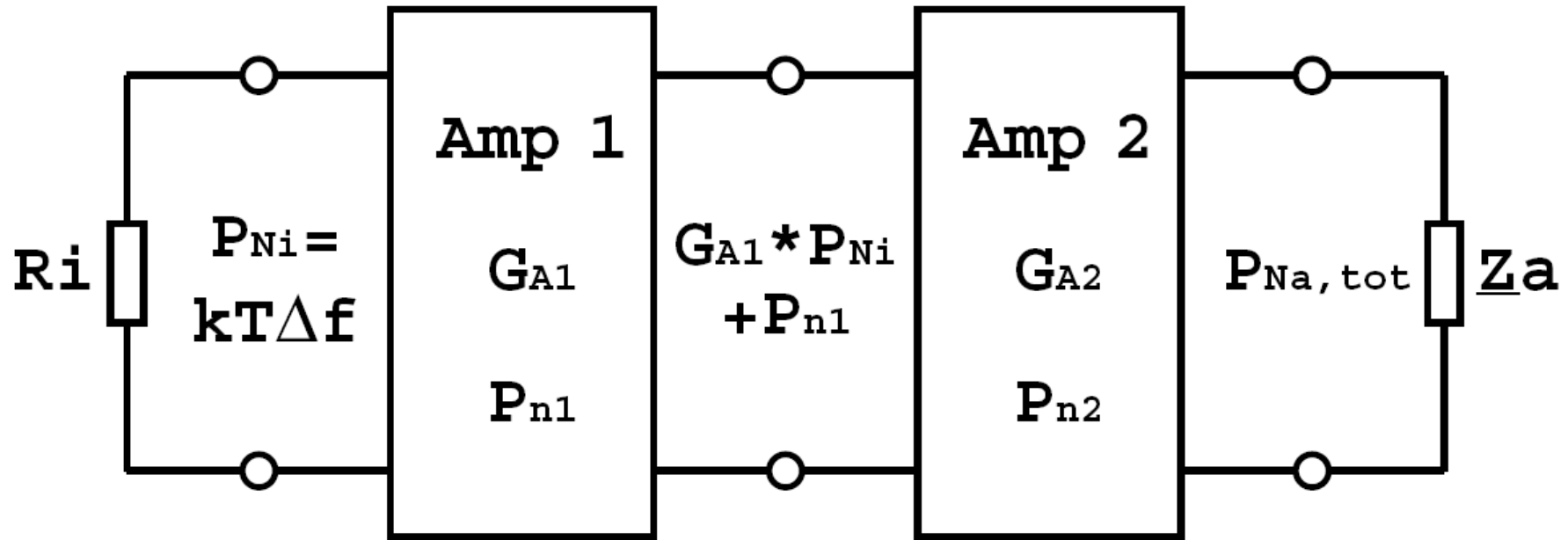Determination of the noise figure of a two-stage amplifier



$$P_{N,total} = G_{A2}(G_{A1}P_{N,in} + P_{n1}) + P_{n2}$$


$$\Rightarrow F_{total} = \frac{P_{N,total}}{P_{N,in} G_{A1} G_{A2}} = 1 + \frac{P_{n1}}{P_{N,in} G_{A1}} + \frac{P_{n2}}{P_{N,in} G_{A1} G_{A2}}$$

$$\text{with } F_j = 1 + \frac{P_{nj}}{P_{N,in} G_{Aj}}, \quad j=1,2$$


$$F_{total} = F_1 + \frac{F_2 - 1}{G_{A1}}$$

F_1 has the strongest impact on the overall noise figure!

Gain, F and T_e of a cascaded system

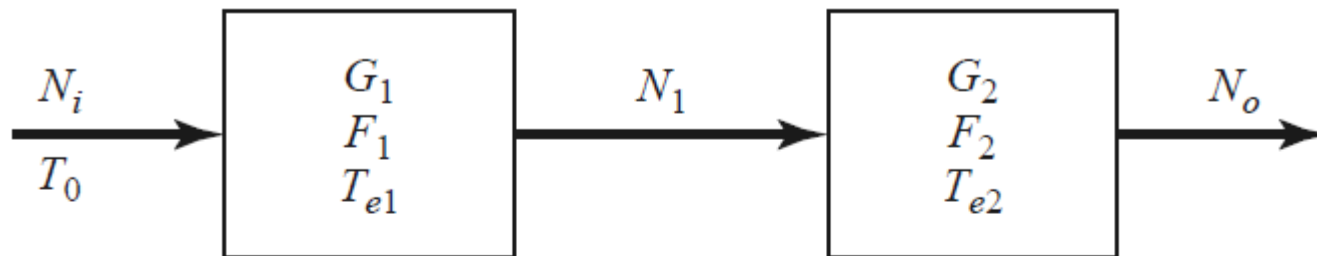


(a)

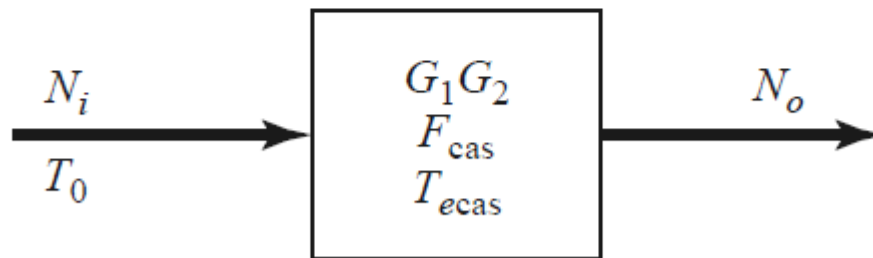

(b)

$$G_{cas} = G_1 G_2 \quad T_{cas} = T_{e1} + \frac{1}{G_1} T_{e2} \quad F_{cas} = F_1 + \frac{1}{G_1} (F_2 - 1)$$

Cascaded NF: Friis' formula

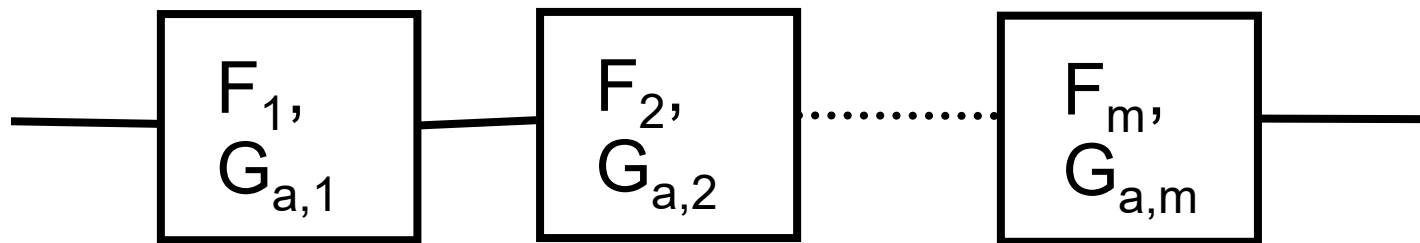

System with cascaded sub-systems with noise figure F_m and available gain $G_{a,m}$

$$F_{total} = 1 + (F_1 - 1) + \frac{F_2 - 1}{G_{a,1}} + \dots + \frac{F_m - 1}{G_{a,1} G_{a,2} \dots G_{a,(m-1)}}$$

Outline

- Recap
 - S parameters
 - Power gain definitions
 - Transducer gain
 - Gain circles
 - Stability circles
- Noise
- Characterization of noise in amplifiers
- Noise in multi-stage amplifiers
- **Noise circles**

Noise figure of an amplifier (1)

- Noise figure of a 2-port amplifier: Normalized equivalent noise resistor: $r_n = \frac{R_n}{Z_0}$
 - Source admittance: $\underline{Y}_S = g_S + jb_S$
 - Minimum noise figure for the chosen bias point: $F_{\min} = \min(F)$
- $$F = F_{\min} + \frac{r_N}{g_S} \left| \underline{y}_S - \underline{y}_{opt} \right|^2$$

- Expression with the reflection coefficients Γ_S and Γ_{opt}

Scaling factor
"sensitivity to offset"

↓

$$F = F_{\min} + 4r_N \frac{|\underline{\Gamma}_S - \underline{\Gamma}_{opt}|^2}{\underbrace{(1 - |\underline{\Gamma}_S|^2) \cdot |1 + \underline{\Gamma}_{opt}|^2}_{\text{Offset to optimum value}}}$$

Noise figure of an amplifier (2)

$$F = F_{\min} + 4r_N \frac{|\underline{\Gamma}_S - \underline{\Gamma}_{opt}|^2}{(1 - |\underline{\Gamma}_S|^2) \cdot |1 + \underline{\Gamma}_{opt}|^2}$$

Which values of $\underline{\Gamma}_S$ lead to a constant value of F ?

The values are on circles and we can calculate the center and the radius. The circles are called constant noise circles.

Constant noise circles


Centers: $\underline{C}_F = \frac{\Gamma_{opt}}{1+N}$

Radii: $R_F = \frac{1}{1+N} \sqrt{N^2 + N(1-|\Gamma_{opt}|^2)}$

With the “Noise figure parameter N” defined as:

$$\Delta F_n' = N = (F - F_{\min}) \frac{|1 + \underline{\Gamma}_{opt}|^2}{4r_n} = \frac{|\underline{\Gamma}_S - \underline{\Gamma}_{opt}|^2}{1 - |\underline{\Gamma}_S|^2}$$

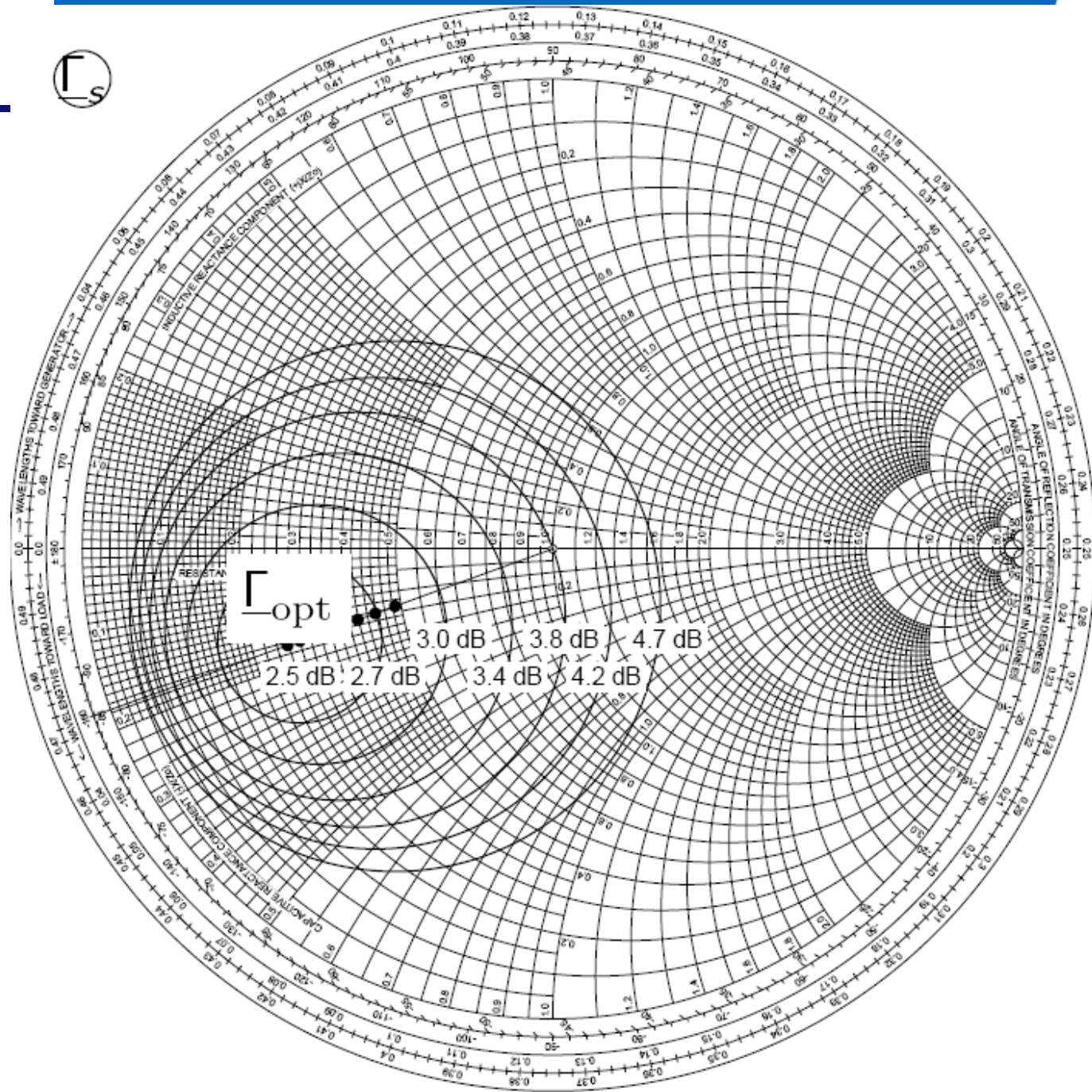Constant noise-circles in the source-reflection-coefficient Smith Chart



Design for specific noise figure

Typically the values of Γ_{opt} , r_n and F_{min} are known for the transistor.

The amplifier specification requires a noise figure F and a gain G .

Procedure:

1. Calculate N
2. Calculate C_F and R_F
3. Draw the constant noise circle for the required F in the Smith chart as well as the input section constant gain circle for several G_S
4. Choose a value for Γ_S that is on the desired noise circle and a certain gain circle
5. The remaining gain must come from the transistor and the output matching stage

Study guide amplifier design

- Study the slides
- Pozar: Read Paragraphs 12.1, 12.2, 12.3
- Be able to calculate the exercises from the book of Pozar:
Example 12.1, 12.2, 12.3, 12.4 and 12.5
- Extra training:
Book: G. Gonzalez, Microwave transistor amplifiers
Various exercises in Chapter 2, 3, 4