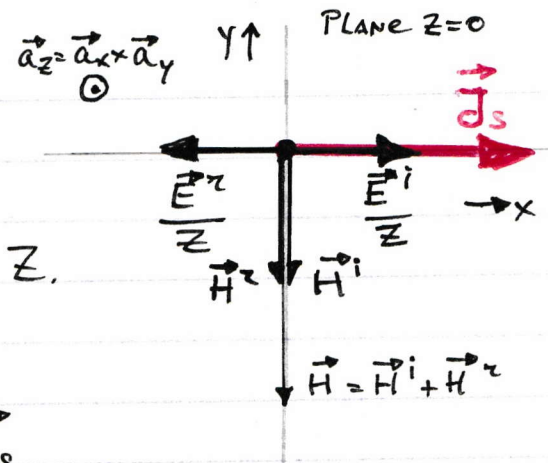


# EM II Chapter 1

## Question 1.1


Plane wave  $\vec{E}^i = V^i(z, t) \vec{a}_x$ , travelling in the negative  $z$ -direction towards a PEC plate at  $z=0$ . Wave impedance  $Z$ . Reflected wave  $\vec{E}^r = V^r(z, t) \vec{a}_x$



$$\vec{v} \times \vec{H}_t = -\vec{J}_s \Rightarrow -\vec{a}_z \times (\vec{H}^i + \vec{H}^r) = -\vec{J}_s$$
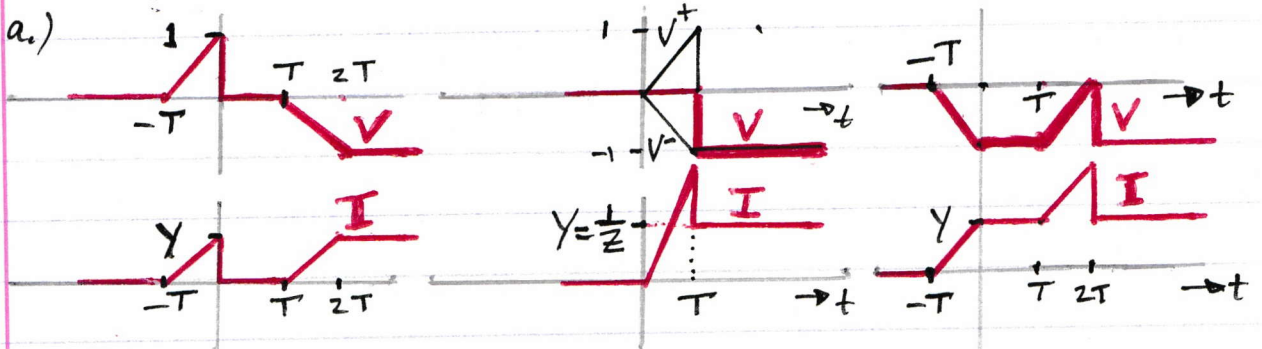
## Question 1.2

$$V^+(t) = [u(t) - u(t-T)] \frac{t}{T} [V], \quad V^-(t) = -u(t) \frac{t}{T} + u(t-T) \left( \frac{t}{T} - 1 \right) [V]$$




$$z = -cT$$

$$z = 0$$


$$z = cT$$
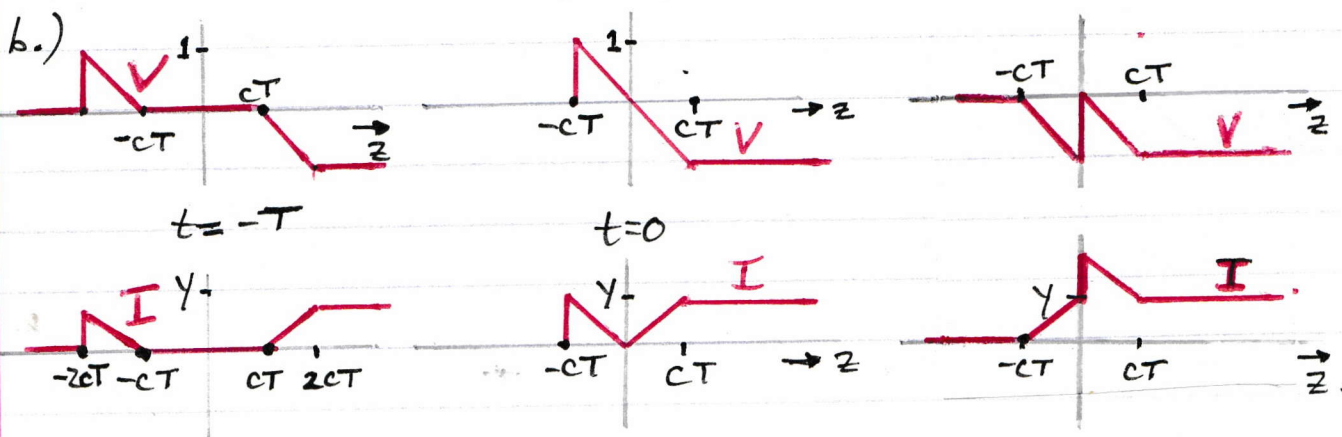
$$I^\pm(t \mp \frac{z}{c}) = \pm Y V^\pm(t \mp \frac{z}{c}) \quad Y = Z^{-1}$$



$$t = -T$$

$$t = 0$$

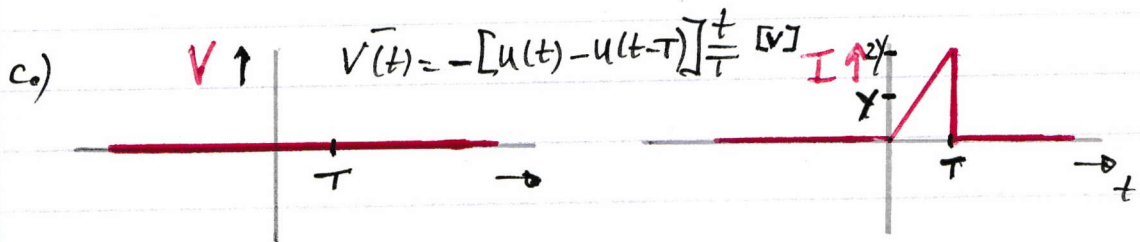

$$d.) \quad Z|_{z=0} = \frac{V}{I}|_{z=0} = 0 \, \Omega$$

The voltage constituents  $V^+$  and  $V^-$  cancel at  $z=0$ , indicative of a perfect electric conductor at  $z=0$

## EM II Chapter 1



### Question 1.3

$$a.) -\frac{\partial V}{\partial z} = L \frac{\partial I}{\partial t} \Rightarrow \frac{V(z,t) - V(z+\Delta z,t)}{\Delta z} = L \frac{\partial I}{\partial t}$$

$$\Rightarrow V(z,t) - V(z+\Delta z,t) = L \Delta z \frac{\partial I}{\partial t}(z,t)$$

Likewise:
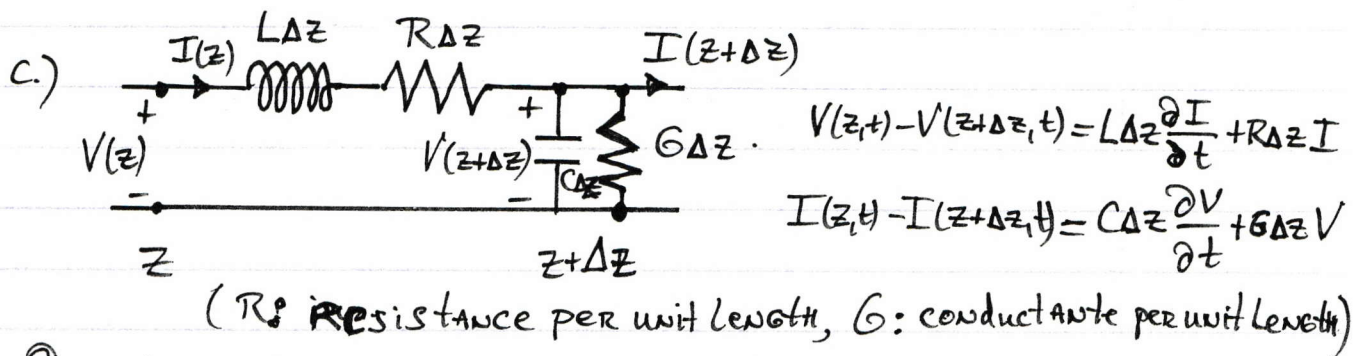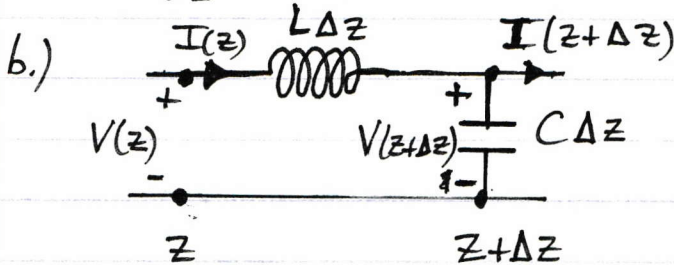
$$-\frac{\partial I}{\partial z} = C \frac{\partial V}{\partial t} \Rightarrow I(z,t) - I(z+\Delta z,t) = C \Delta z \frac{\partial V}{\partial t}(z,t)$$



### Question 1.4

$$a.) V^-(t) = \Gamma V^+(t-T) \Rightarrow V^-(t + \frac{l}{c}) = \Gamma V^+(t + \frac{l}{c} - T)$$

$$= \Gamma V^+(t - \frac{cT-l}{c})$$

$$\Rightarrow \frac{V}{I} = Z \frac{V^+(t - \frac{l}{c}) + \Gamma V^+(t - \frac{cT-l}{c})}{V^+(t - \frac{l}{c}) - \Gamma V^+(t - \frac{cT-l}{c})} = Z \frac{1+\Gamma}{1-\Gamma} = Z_L$$

if  $\frac{l}{c} = \frac{cT-l}{c} \Rightarrow l = \frac{1}{2}cT$

b.  $|\Gamma| > 1$  Firstly, let us assume that  $V^+$  is the incident wave, and that  $V^- = \Gamma V^+$  at  $z = l = \frac{1}{2}cT$

$$\Rightarrow Z_L = Z \frac{1+\Gamma}{1-\Gamma} < 0 \text{ if } |\Gamma| > 1 \Rightarrow \text{Negative (Active) Load}$$

Secondly, let us assume that  $V^-$  is the incident wave, and that  $V^- = \Gamma V^+$  at  $z = l = \frac{1}{2}cT \Rightarrow V^+ = \frac{1}{\Gamma} V^-$  at  $z = l = \frac{1}{2}cT$

$$\Rightarrow Z_L = Z \frac{1+\Gamma^{-1}}{1-\Gamma^{-1}} = -Z \frac{1+\Gamma}{1-\Gamma} > 0 \text{ if } |\Gamma| > 1 \Rightarrow \text{positive impedance}$$

( $\Rightarrow$  passive Load)



# EM II Chapter 1

## Question 1.5

a.)  $I = I^+ + I^-$ ,  $V = V^+ + V^-$ ,  $I^\pm = \pm \frac{1}{Z} V^\pm$

b.) At  $z=0$ , where the load is located, we have

$$I = I_G + I_C = GV + C \frac{dV}{dt}$$

$$= (I^+ + I^-)|_{z=0} = \frac{1}{Z} (V^+ - V^-) = (C \frac{d}{dt} + G) V^- + (C \frac{d}{dt} + G) V^+$$

Multiply by  $Z \Rightarrow$

$$(CZ \frac{d}{dt} + GZ + 1) V^- = - (CZ \frac{d}{dt} + GZ - 1) \underbrace{V^+}_{u(t): \text{known}}$$

c.) A Homogeneous, first-order differential equation for a function  $f(t)$  can always be cast in the form  $\frac{-t}{\tau}$

$$(\tau \frac{d}{dt} + 1) f(t) = 0, \quad f(0) = f_0 \Rightarrow f(t) = f_0 e^{-\frac{t}{\tau}}$$

$\Rightarrow$  divide the equation for  $V^-$  found above by  $(GZ + 1) \Rightarrow$

$$(\tau \frac{d}{dt} + 1) V^- = - \left( \tau \frac{d}{dt} + \frac{GZ - 1}{GZ + 1} \right) u(t) = -\tau \delta(t) + \frac{1 - GZ}{1 + GZ} u(t)$$

$\Rightarrow \tau = \frac{CZ}{1 + GZ}$  is the time constant.

$$\begin{aligned} d.) \quad \tau = \frac{CZ}{1 + GZ} &\Rightarrow (\tau \frac{d}{dt} + 1) V^- = (\tau \frac{d}{dt} + 1) \left[ (A + B e^{-\frac{t}{\tau}}) u(t) \right] \\ &= \tau (A + B e^{-\frac{t}{\tau}}) \delta(t) - B e^{-\frac{t}{\tau}} u(t) + A u(t) + B e^{-\frac{t}{\tau}} u(t) \\ &\quad \downarrow \text{for } t=0 \\ &= -\tau \delta(t) + \frac{1 - GZ}{1 + GZ} u(t) \Rightarrow A + B = -1 \quad \& \quad A = \frac{1 - GZ}{1 + GZ} \\ &\quad \Rightarrow B = \frac{-2}{1 + GZ} \end{aligned}$$

$$e.) \quad \lim_{t \rightarrow 0} V(t) = \lim_{t \rightarrow 0} (V^+(t) + V^-(t)) = 1 + A + B = 0$$

$$\lim_{t \rightarrow 0} I(t) = \frac{1}{Z} (1 - A - B) = \frac{2}{Z} \quad \text{For } t \rightarrow 0, \text{ the empty capacitor acts as a short circuit}$$

$$f.) \quad \lim_{t \rightarrow \infty} V(t) = 1 + A = -B = \frac{2}{1 + GZ}; \quad \lim_{t \rightarrow \infty} I(t) = \frac{1}{Z} (1 - A) = \frac{2GZ}{1 + GZ}$$

$\Rightarrow \lim_{t \rightarrow \infty} \frac{V}{I} = \frac{1}{G}$  For  $t \rightarrow \infty$ , the charged capacitor acts as an open circuit

g.) Time shift:  $V^-(t + \frac{Z}{c}) = (A + B e^{-\frac{t}{\tau} - \frac{Z}{c\tau}}) u(t + \frac{Z}{c})$  for  $Z < 0$ .