





# Components in wireless technologies (5XTC0)

## Module 5, Lab QUCS RF Amplifier design/simulation

Rainier van Dommele

# Introduction

- Current 5XTC0\_V2 Amplifier board:

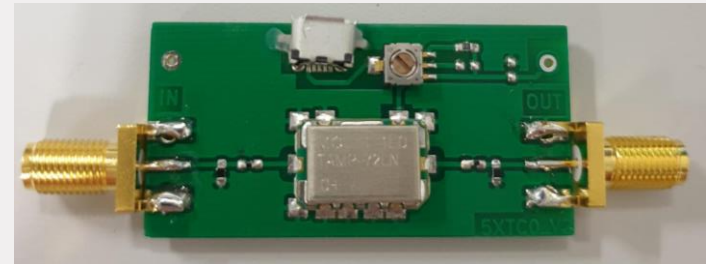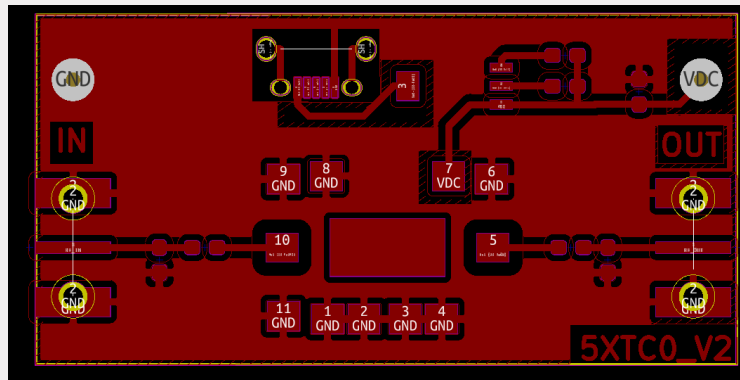

Includes the [Mini-Circuits TAMP-72LN+](#) amplifier.


- Assignments for today:
  - simulate the stand-alone amplifier and amplifier board.
  - redesign amplifier board input and output matching circuits using LC components.

# Stand-alone amplifier: S parameters simulation

Link to S parameter file of the amplifier:


[https://www.minicircuits.com/pages/s-params/TAMP-72LN+\\_S2P.zip](https://www.minicircuits.com/pages/s-params/TAMP-72LN+_S2P.zip) OR  
[https://canvas.tue.nl/files/3712855/download?download\\_frd=1](https://canvas.tue.nl/files/3712855/download?download_frd=1)

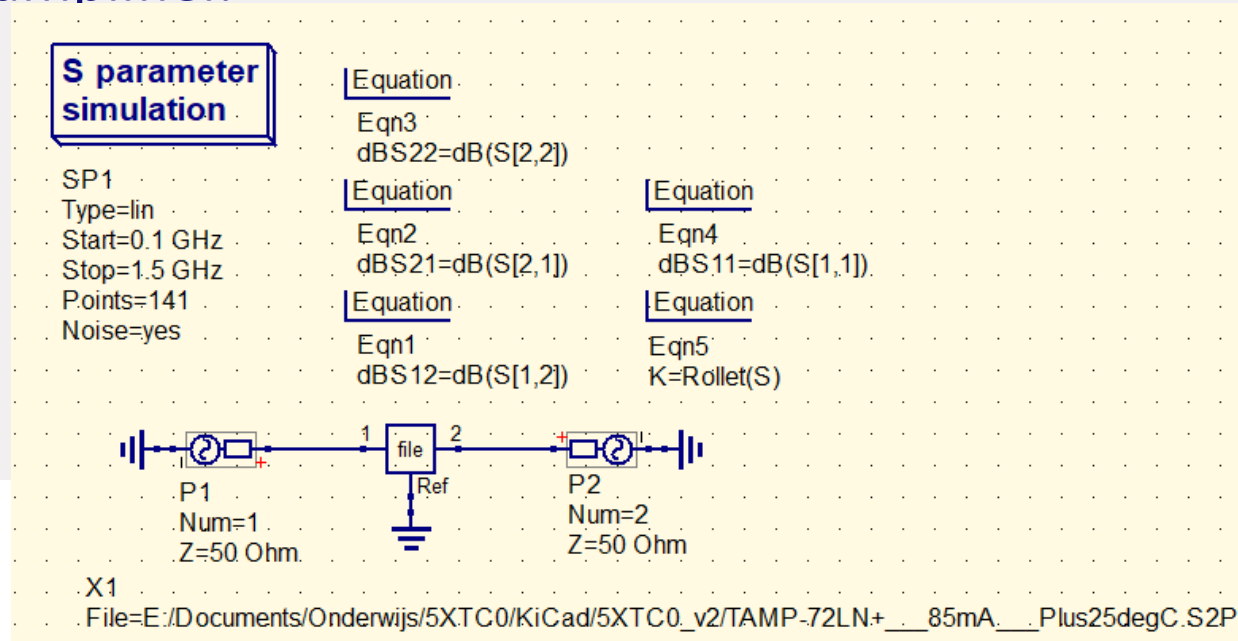**Task:** generate test-bench in QUCS for simulating S parameters of the stand-alone amplifier as shown in figure below.  
Use 2-port s-parameter file component to include the S parameters of the amplifier.


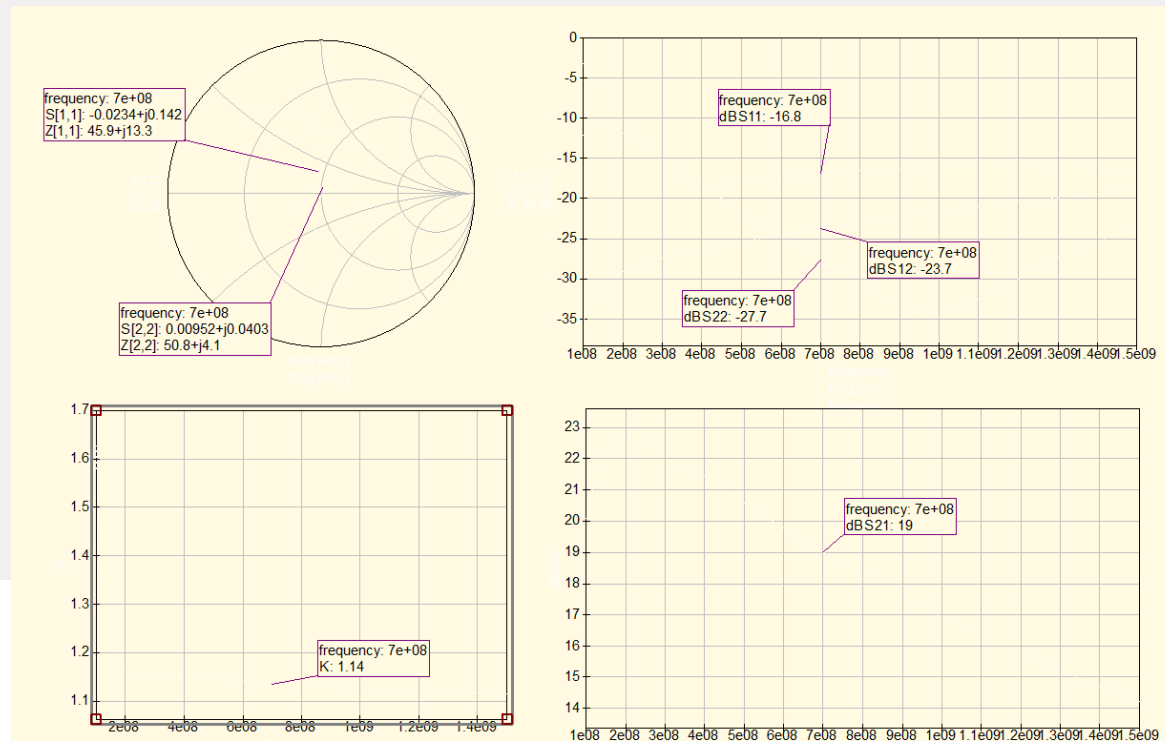
# Stand-alone amplifier: simulated results

- **Assignment task**
  - Simulate and plot S11, S12, S21, S22 and K factor
  - Provide these results in the **answer template**
- Results should look as in the figure below



# Comparison: simulated data versus amplifier data sheet

Assignment questions, use the [answer template](#).

1. Explain meaning of:
  - $S_{11}$ ,  $S_{12}$ ,  $S_{21}$ ,  $S_{22}$
  - K factor
2. What is frequency range where amplifier can be used?
3. You did not need to provide biasing, why?


[Link to data sheet of amplifier](#)

Compare simulated S parameters and stability factor with information parameters provided in datasheet.

4. Are there any differences?


# Amplifier board: S parameter simulations

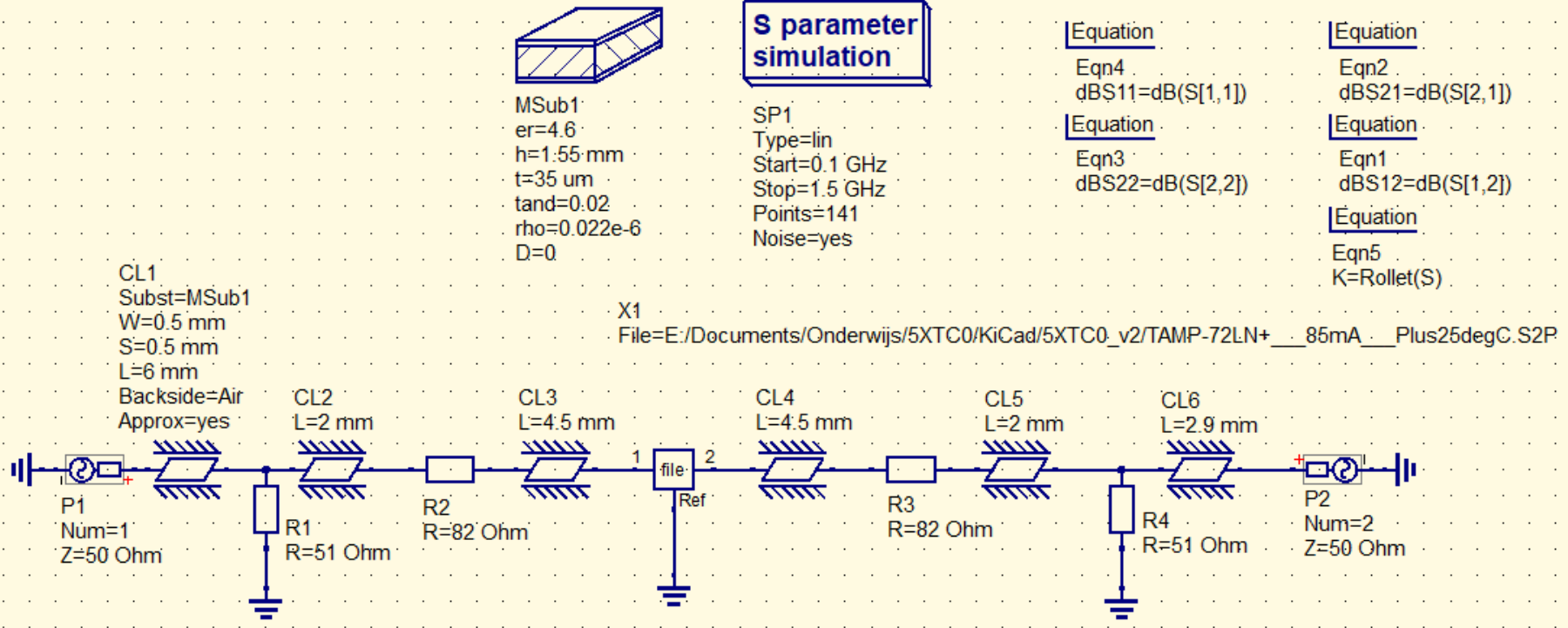**Task:** generate test-bench in QUCS for simulating the S parameters of the amplifier board as shown in figure below.


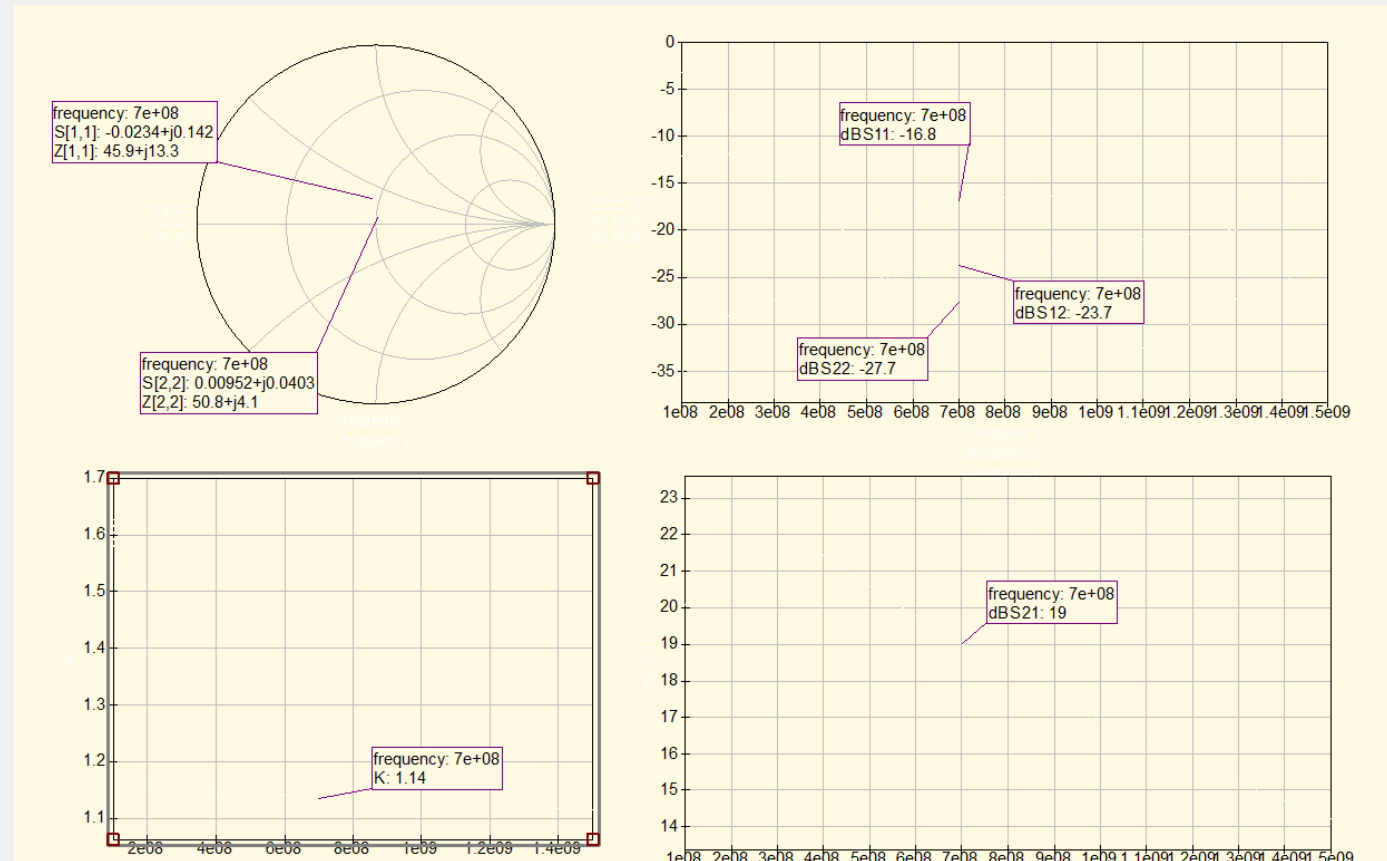
# Amplifier board: simulation results

Plot the results in the answer template as shown below.



# Difference between stand-alone and amplifier board simulations

We observed differences between simulations of stand-alone amplifier and amplifier board. Explain the differences.

Assignment questions, use [the answer template](#) to note your answers.

5. Why do the  $S_{11}$  &  $S_{22}$  change when you have resistors on the amplifier board (compared to the situation where there are only transmission lines and the amplifier)?
6. Why is the  $S_{21}$  (gain) much lower?
7. Why is the stability factor higher?

*Assume the frequency of interest is 700 MHz.*

8. What is the impedance of the transmission lines (at this frequency)?
9. What should have been “S” (space between transmission line and ground plane) in order to make the transmission line 50 Ohm at this frequency, keeping the width of the transmission line 0.5 mm?



# Redesign of Amplifier board

The resistors R1, R2, R3, R4 are to reduce the gain so the NanoVNA can measure this board.

If we now assume this board would not be used with the NanoVNA, but as an amplifier in a transceiver, we would remove the resistors.


**Task:** Remove the resistors from the schematic and match the amplifier board in such a way that the gain is maximized at 700MHz.

You can use LC matching on the locations of the resistors. To make the assignment simpler, remove CL1, CL2, CL5 & CL6. See next slides.

# Capacitor values to use during redesign

Capacitors: 0603 inch size (1608 metric) and E12 series. See screenshot below which values to take. So only realistic values.

You can use the ideal C component.

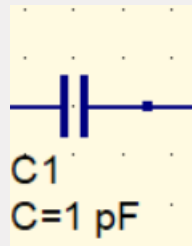

0603

| NP0, 50V |           | NP0, 25V |           | X7R, 16V |           |
|----------|-----------|----------|-----------|----------|-----------|
| Value    | Tolerance | Value    | Tolerance | Value    | Tolerance |
| 0.47 pF  | ± 0.25 pF | 1.0 nF   | ± 5 %     | 33 nF    | ± 10 %    |
| 0.68 pF  | ± 0.25 pF | 1.5 nF   | ± 5 %     | 47 nF    | ± 10 %    |
| 1.0 pF   | ± 0.25 pF | X7R, 50V |           | 68 nF    | ± 10 %    |
| 1.5 pF   | ± 0.25 pF | Value    | Tolerance | 100 nF   | ± 10 %    |
| 2.2 pF   | ± 0.25 pF | 100 pF   | ± 10 %    | Y5V, 50V |           |
| 3.3 pF   | ± 0.25 pF | 150 pF   | ± 10 %    | Value    | Tolerance |
| 4.7 pF   | ± 0.25 pF | 220 pF   | ± 10 %    | 10 nF    | ± 20 %    |
| 6.8 pF   | ± 0.5 pF  | 330 pF   | ± 10 %    | 15 nF    | ± 20 %    |
| 10 pF    | ± 5 %     | 470 pF   | ± 10 %    | 22 nF    | ± 20 %    |
| 15 pF    | ± 5 %     | 680 pF   | ± 10 %    | 33 nF    | ± 20 %    |
| 22 pF    | ± 5 %     | 1.0 nF   | ± 10 %    | 47 nF    | ± 20 %    |
| 33 pF    | ± 5 %     | 1.5 nF   | ± 10 %    | 68 nF    | ± 20 %    |
| 47 pF    | ± 5 %     | 2.2 nF   | ± 10 %    | 100 nF   | ± 20 %    |
| 68 pF    | ± 5 %     | 3.3 nF   | ± 10 %    | Y5V, 16V |           |
| 100 pF   | ± 5 %     | 4.7 nF   | ± 10 %    | Value    | Tolerance |
| 150 pF   | ± 5 %     | 6.8 nF   | ± 10 %    | 150 nF   | ± 20 %    |
| 220 pF   | ± 5 %     | 10 nF    | ± 10 %    | 220 nF   | ± 20 %    |
| 330 pF   | ± 5 %     | X7R, 25V |           | 330 nF   | ± 20 %    |
| 470 pF   | ± 5 %     | Value    | Tolerance | 470 nF   | ± 20 %    |
| 680 pF   | ± 5 %     | 15 nF    | ± 10 %    |          |           |
|          |           | 22 nF    | ± 10 %    |          |           |

# Inductor values to use (1/2)

Inductors: 0603 inch size (1608 metric).

Use real inductors: [Murata LQW18AN series \(link\)](#).

| No. | Part Name     |             |
|-----|---------------|-------------|
| 1   | LQW18AN2N2D00 | 2.2nH±0.5nH |
| 2   | LQW18AN3N6C00 | 3.6nH±0.2nH |
| 3   | LQW18AN3N9C00 | 3.9nH±0.2nH |
| 4   | LQW18AN4N3C00 | 4.3nH±0.2nH |
| 5   | LQW18AN4N7D00 | 4.7nH±0.5nH |
| 6   | LQW18AN5N6C00 | 5.6nH±0.2nH |
| 7   | LQW18AN6N2C00 | 6.2nH±0.2nH |
| 8   | LQW18AN6N8C00 | 6.8nH±0.2nH |
| 9   | LQW18AN7N5C00 | 7.5nH±0.2nH |
| 10  | LQW18AN8N2C00 | 8.2nH±0.2nH |
| 11  | LQW18AN8N7C00 | 8.7nH±0.2nH |
| 12  | LQW18AN9N1C00 | 9.1nH±0.2nH |
| 13  | LQW18AN9N5D00 | 9.5nH±0.5nH |
| 14  | LQW18AN10NG00 | 10nH±2%     |
| 15  | LQW18AN11NG00 | 11nH±2%     |
| 16  | LQW18AN12NG00 | 12nH±2%     |
| 17  | LQW18AN13NG00 | 13nH±2%     |
| 18  | LQW18AN15NG00 | 15nH±2%     |
| 19  | LQW18AN16NG00 | 16nH±2%     |
| 20  | LQW18AN18NG00 | 18nH±2%     |
| 21  | LQW18AN20NG00 | 20nH±2%     |
| 22  | LQW18AN22NG00 | 22nH±2%     |
| 23  | LQW18AN24NG00 | 24nH±2%     |
| 24  | LQW18AN27NG00 | 27nH±2%     |
| 25  | LQW18AN30NG00 | 30nH±2%     |
| 26  | LQW18AN33NG00 | 33nH±2%     |
| 27  | LQW18AN36NG00 | 36nH±2%     |
| 28  | LQW18AN39NG00 | 39nH±2%     |
| 29  | LQW18AN43NG00 | 43nH±2%     |
| 30  | LQW18AN47NG00 | 47nH±2%     |
| 31  | LQW18AN51NG00 | 51nH±2%     |
| 32  | LQW18AN56NG00 | 56nH±2%     |
| 33  | LQW18AN62NG00 | 62nH±2%     |
| 34  | LQW18AN68NG00 | 68nH±2%     |
| 35  | LQW18AN72NG00 | 72nH±2%     |
| 36  | LQW18AN75NG00 | 75nH±2%     |

These are samples for evaluation purpose.  
Please do not ship out your completed product with the sample



| No. | Part Name     |             |
|-----|---------------|-------------|
| 37  | LQW18AN82NG00 | 82nH±2%     |
| 38  | LQW18AN91NG00 | 91nH±2%     |
| 39  | LQW18ANR10G00 | 100nH±2%    |
| 40  | LQW18ANR11G00 | 110nH±2%    |
| 41  | LQW18ANR12G00 | 120nH±2%    |
| 42  | LQW18ANR13G00 | 130nH±2%    |
| 43  | LQW18ANR15G00 | 150nH±2%    |
| 44  | LQW18ANR16G00 | 160nH±2%    |
| 45  | LQW18ANR18G00 | 180nH±2%    |
| 46  | LQW18ANR20G00 | 200nH±2%    |
| 47  | LQW18ANR22G00 | 220nH±2%    |
| 48  | LQW18ANR27G00 | 270nH±2%    |
| 49  | LQW18ANR33G00 | 330nH±2%    |
| 50  | LQW18ANR39G00 | 390nH±2%    |
| 51  | LQW18ANR47G00 | 470nH±2%    |
| 52  | LQW18AN2N2D10 | 2.2nH±0.5nH |
| 53  | LQW18AN3N9C10 | 3.9nH±0.2nH |
| 54  | LQW18AN5N6D10 | 5.6nH±0.5nH |
| 55  | LQW18AN6N8C10 | 6.8nH±0.2nH |
| 56  | LQW18AN8N2D10 | 8.2nH±0.5nH |
| 57  | LQW18AN10NG10 | 10nH±2%     |
| 58  | LQW18AN12NG10 | 12nH±2%     |
| 59  | LQW18AN15NJ10 | 15nH±5%     |
| 60  | LQW18AN18NG10 | 18nH±2%     |
| 61  | LQW18AN22NG10 | 22nH±2%     |
| 62  | LQW18AN27NG10 | 27nH±2%     |
| 63  | LQW18AN33NJ10 | 33nH±5%     |

These are samples for evaluation purpose.  
Please do not ship out your completed product with the sample

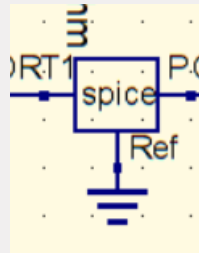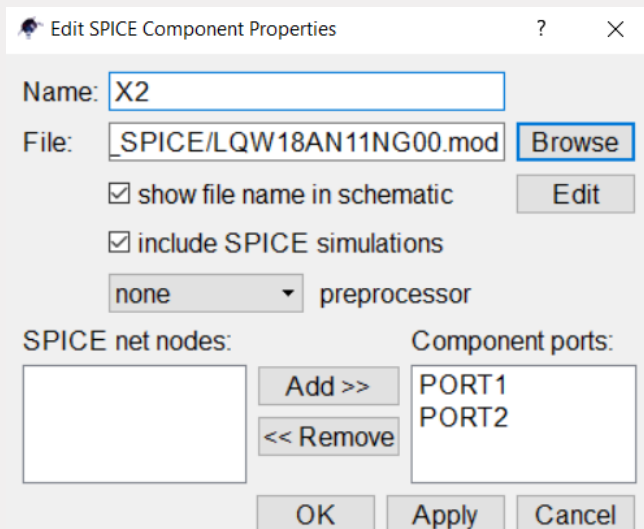
# Inductor values to use (2/2)

First calculate which ideal inductor value you would use. Then download the spice model of the inductor which has a value closest to the calculated value from [Murata LQW18AN series \(link\)](#).


Place a “file components” -> “spice netlist” item and double click it. Browse to the .mod file and add the ports:



Ignore this error:

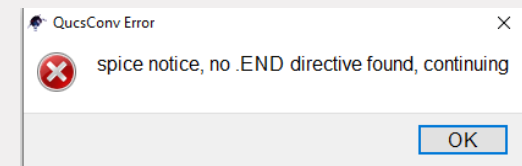
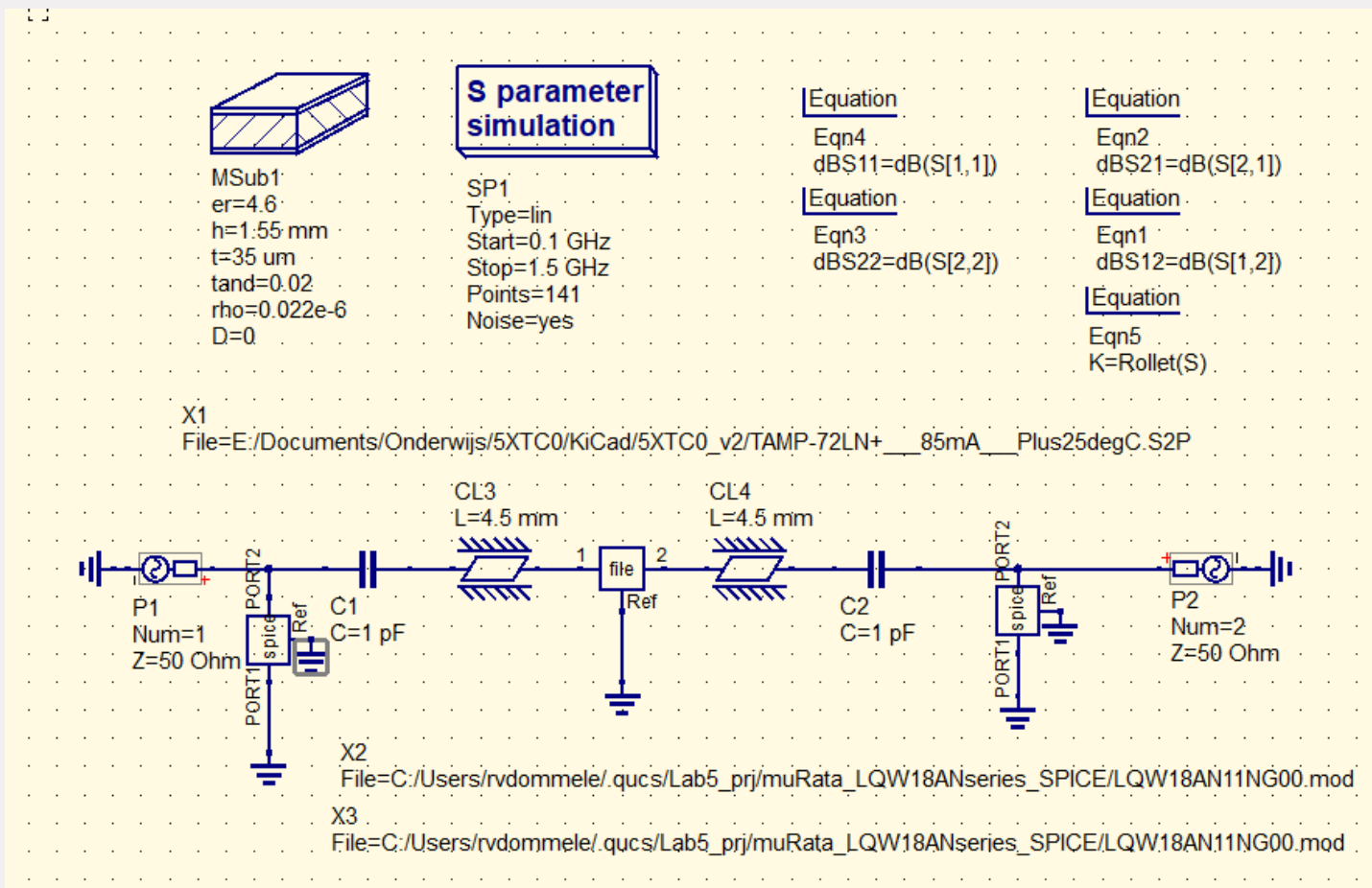
# Redesign example with LC matching and transmission lines CL1,2,5,6 removed



## Assignments after redesign task

We observe differences between the 5XTC0\_V2 amplifier board and your redesigned matching amplifier board. Explain the differences.

Assignment questions, use [the answer template](#).

10. How high was the gain of the 5XTC0\_V2 board originally?
11. And how high is the gain if we remove R1&R4 and short R2&R3 (board without resistors, unmatched)?
12. And how high is the gain with your redesign matched board?
13. What do you notice in the S11 / S22 curves of your redesigned matched board?

# Reporting

Upload a small report with your answers of Lab 5 and 6 to Canvas before Friday March 28, 23:59. Use the answer template for this. And please note your name in the file, as well as in the filename. During the oral exam you'll get questions about the labs.