



# Components in wireless technology, 5XTC0

## Module 4 Lecture: Amplifier design

Vojkan Vidojkovic

**TU/e**

Technische Universiteit  
Eindhoven  
University of Technology

Where innovation starts

# Outline


- Design methods
- Two-port network descriptions
- Introduction of S-parameters
- Definitions
  - Reflection coefficient
  - Power
  - Power gain
- Gain circles
- Stability
- Stability circles

# Learning Objectives

- Understand design methods at low and high frequency
- Understand S-parameters definition
- Calculate and understand the different gains of an amplifier
- Know the basic amplifier architecture
- Understand gain circles
- Understand the concept of stability
- Be able to evaluate whether an amplifier is unconditionally stable
- Be able to evaluate the stability of an amplifier by calculating the stability circles

# Design methods: low versus high frequency

- Example: single MOS transistor

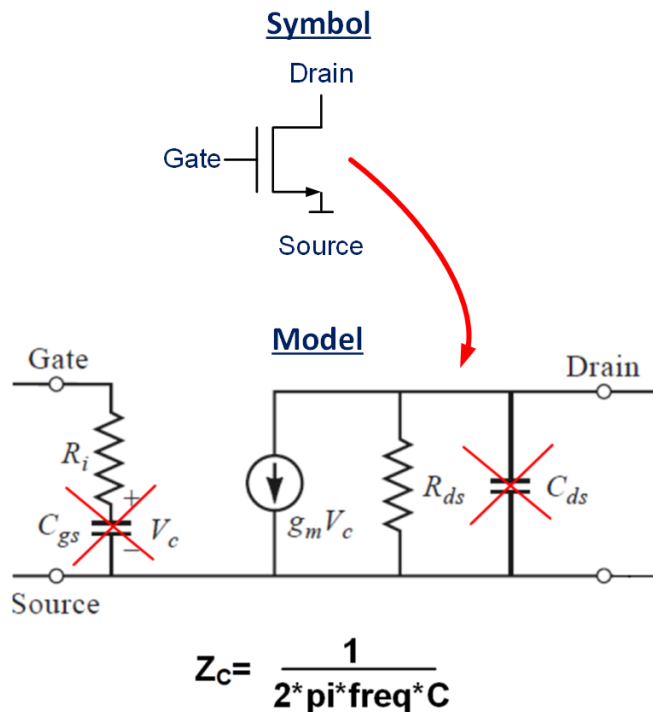

Most analog circuit have more than one transistor !!!


- **Low frequency method**

- Capacitors can be neglected
- Circuit complexity reduced
- Working with  $g_m$  and  $R_{ds}$  is sufficient
- Complexity is manageable

- **High frequency method**

- Capacitors must be included
- Circuit complexity increases
- Black box approach
- In general, every circuit can be described with N-port element
- Most of circuits have 2 ports
- Z, Y, S parameters used for N- port description


# Design methods: large vs small signal

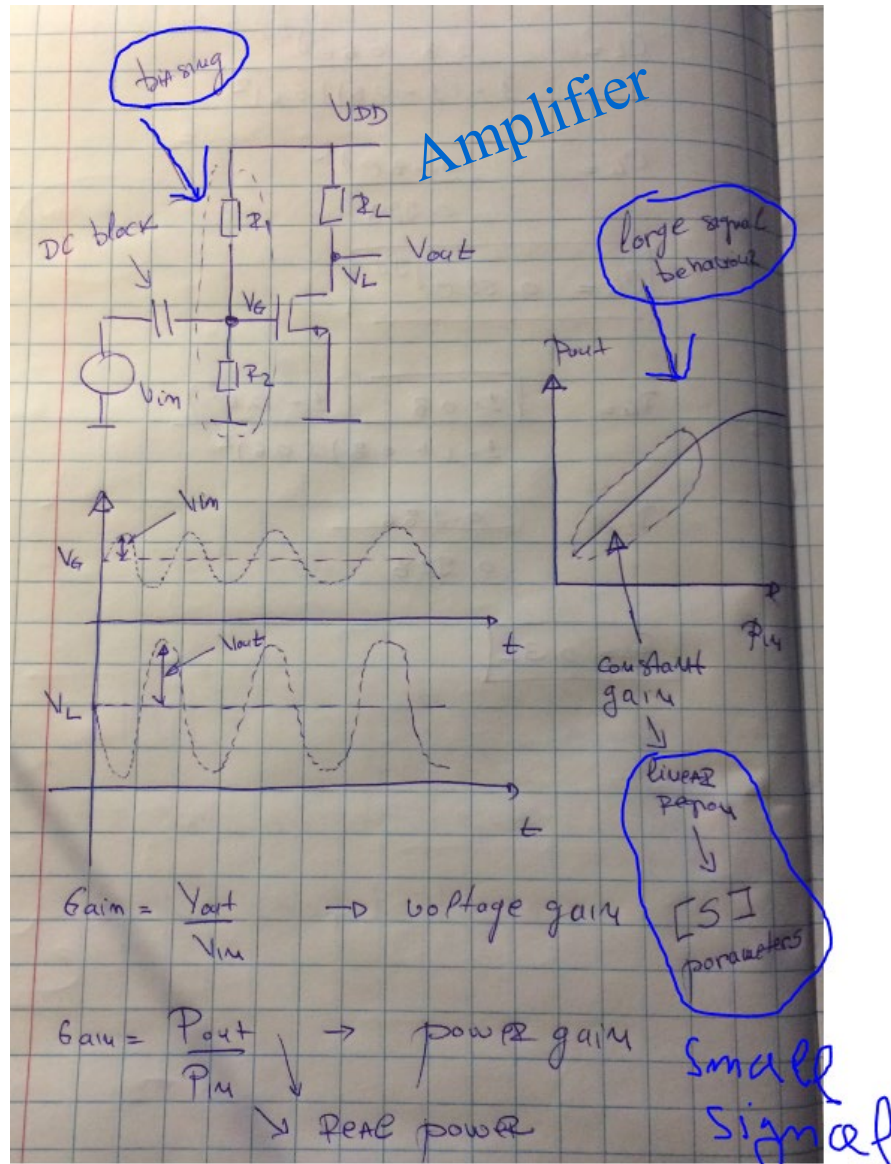
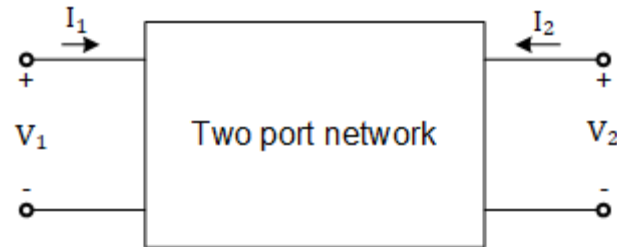
# 2-port network description: Z,Y parameters

- Z parameters

$$\begin{aligned} V_1 &= Z_{11}I_1 + Z_{21}I_2 \\ V_2 &= Z_{12}I_1 + Z_{22}I_2 \end{aligned}$$



- Y parameters

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2 = 0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1 = 0}$$

$$\left. \frac{I_1}{V_1} \right|_{V_2 = 0} = Y_{11}$$

$$\left. \frac{I_1}{V_2} \right|_{V_1 = 0} = Y_{12}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2 = 0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1 = 0}$$


$$\left. \frac{I_2}{V_1} \right|_{V_2 = 0} = Y_{21}$$

$$\left. \frac{I_2}{V_2} \right|_{V_1 = 0} = Y_{22}$$

- I=0 means open, V=0 means short**
- To measure Z and Y parameters open and short terminations are required
- At high frequencies there are no perfect open and short terminations



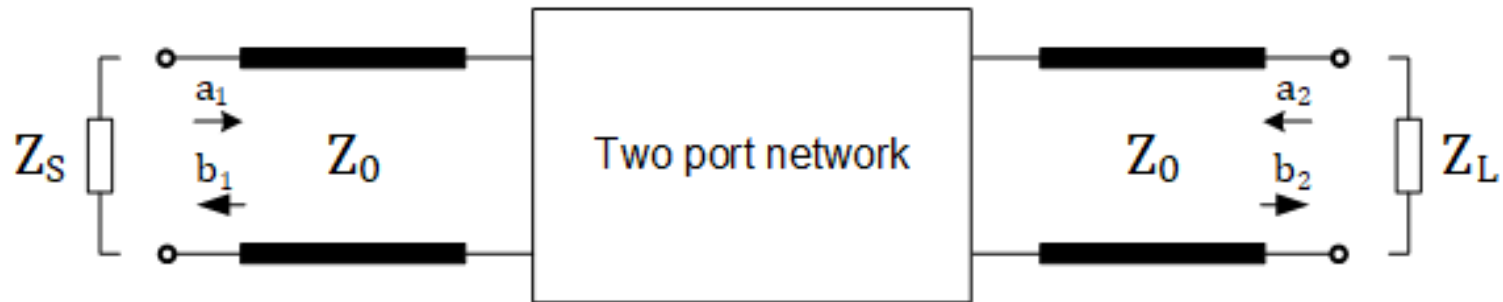
# 2-port network description: S parameters



$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad (\text{input reflection coefficient with output properly terminated})$$
$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad (\text{forward transmission coefficient with output properly terminated})$$
$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} \quad (\text{output reflection coefficient with input properly terminated})$$
$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} \quad (\text{reverse transmission coefficient with input properly terminated})$$

- To measure S parameters matched terminations are required:  $Z_L = Z_0$  and  $Z_S = Z_0$
- At high frequencies matched terminations could be realized much easier compared to short and open terminations

# 2-port network with source and load

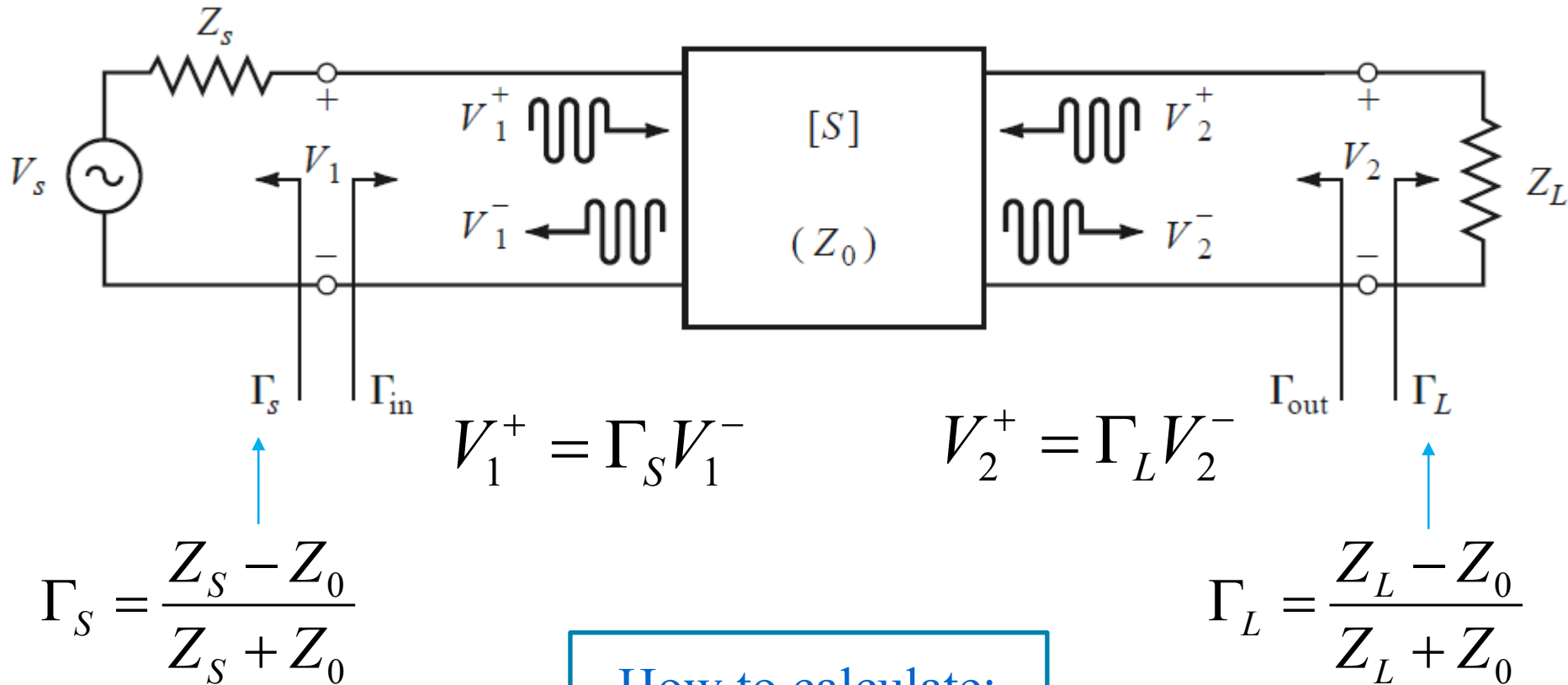


How to calculate:

$\Gamma_{in}$  and  $\Gamma_{out}$


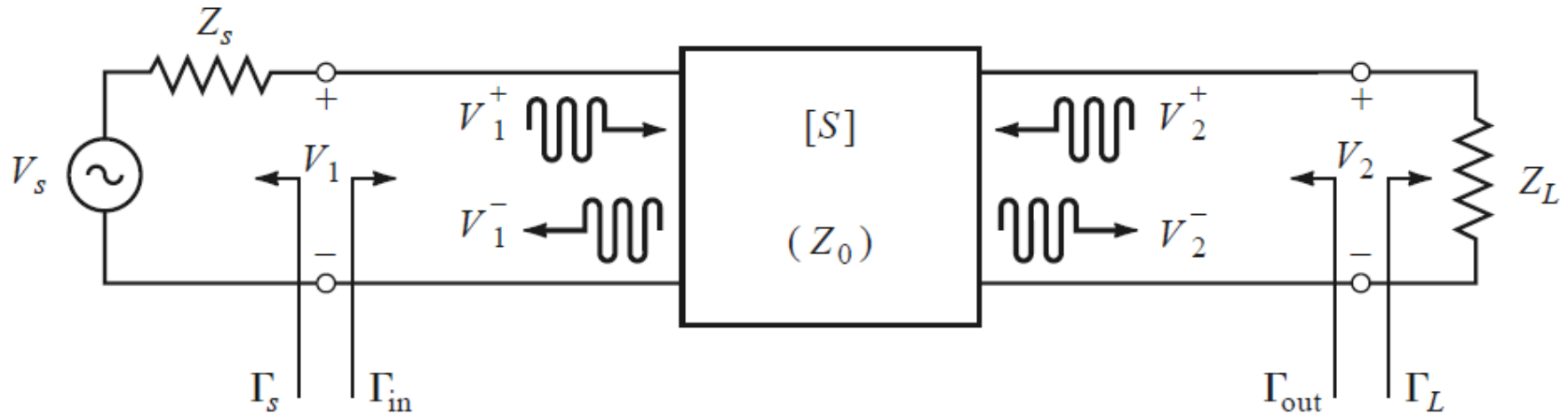
# Derivation of the input/output reflection coefficient



$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

Unilateral case:  $S_{12} = 0$

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22}$$

More info: book of Pozar, page 607

# Derivation of the input reflection coefficient – guidelines

• Derivation for  $S_{11}$  and  $T_{in}$

$$V_1^- = S_{11} V_1^+ + S_{12} V_2^+ \quad \dots (1)$$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+ \quad \dots (2)$$

$$T_L = \frac{V_2^+}{V_2^-} \quad \dots (3)$$


$$\Gamma_{in} = \frac{V_1^-}{V_1^+} \quad \leftarrow \text{Definition}$$

Let's use (1) to express  $V_1^-$

$$\Gamma_{in} = \frac{S_{11} V_1^+ + S_{12} V_2^+}{V_1^+}$$

$$\Gamma_{in} = S_{11} + S_{12} \left( \frac{V_2^+}{V_1^+} \right) \quad \dots (4)$$

Needs better expression

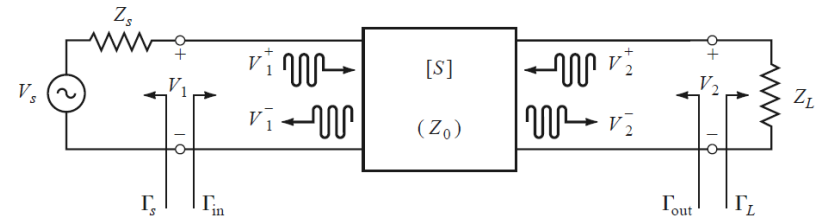

Let's combine (2) and (3)

$$\frac{V_2^+}{T_L} = S_{21} V_1^+ + S_{22} V_2^+$$


$$V_2^+ \left( \frac{1}{T_L} - S_{22} \right) = S_{21} V_1^+$$

$$\frac{V_2^+}{V_1^+} = \frac{S_{21} T_L}{1 - S_{22} T_L} \quad \dots (5)$$

Let's combine (4) and (5)

$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} T_L}{1 - S_{22} T_L}$$

# Power definitions

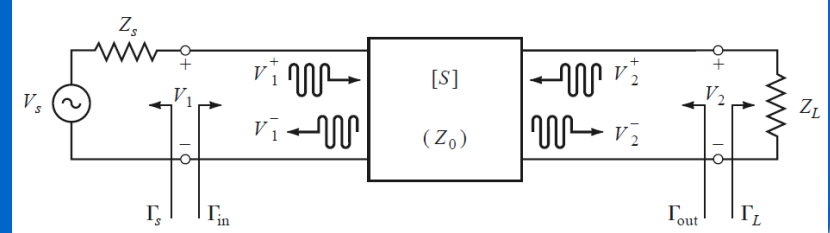

- **Power delivered to the load:**

$$P_L = \frac{|V_2^-|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

- **Input power to the network:**

$$P_{in} = \frac{|V_1^+|^2}{2Z_0} (1 - |\Gamma_{in}|^2)$$

- **Power available from the source:**  $P_{avs}$   
 $P_{in}$  when the source impedance is **conjugately**  
 matched to the input impedance

$$Z_{in} = Z_S^*$$

- **Power available from the network:**  $P_{avn}$   
 $P_L$  when the load impedance is **conjugately** matched  
 to the output impedance


$$Z_{out} = Z_{load}^*$$

# Power definitions – derivation guidelines (1/2)

Derivation of power delivered to network

$$V_1 = V_1^+ + V_1^-$$
$$I_1 = \frac{V_1^+ - V_1^-}{Z_0}$$

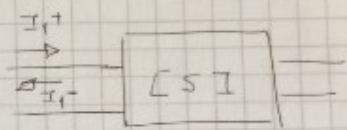
$\rightarrow$  Gonzalez chapters 1.3, 1.4



The diagram shows a rectangular box labeled [S] representing a network. To the left of the box, there are two horizontal arrows: the top one points right and is labeled  $I_1^+$ , and the bottom one points left and is labeled  $I_1^-$ . To the right of the box, there are two horizontal lines representing output ports.

$$P_{in} = \frac{V_1 \cdot I_1^+}{2}$$
$$P_{in} = \frac{(V_1^+ + V_1^-) \cdot (V_1^+ - V_1^-)}{2 \cdot Z_0}$$
$$P_{in} = \frac{|V_1^+|^2 - |V_1^-|^2}{2 \cdot Z_0}$$
$$P_{in} = \frac{|V_1^+|^2 \cdot (1 - |\Gamma_{in}|^2)}{2 \cdot Z_0} \quad \dots (1)$$
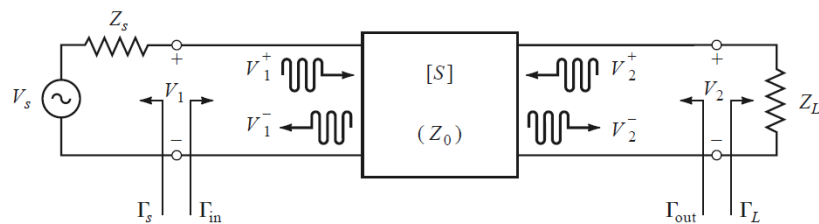
# Power definitions – derivation guidelines (2/2)



$$V_1 = V_s \cdot \frac{Z_{in}}{Z_s + Z_{in}} \quad \dots (2)$$

$$V_1 = V_1^+ + V_1^- = V_1^+ \cdot (1 + \Gamma_{in}) \quad \dots (3)$$

After ~~combining~~ combination (2) and (3)

$$V_1^+ = V_s \cdot \frac{Z_{in}}{Z_s + Z_{in}} \cdot \frac{1}{1 + \Gamma_{in}} \quad \dots (4)$$

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \Rightarrow Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \quad (5)$$

$$\bar{\Gamma}_s = \frac{Z_s - Z_0}{Z_s + Z_0} \Rightarrow Z_s = Z_0 \frac{1 + \bar{\Gamma}_s}{1 - \bar{\Gamma}_s} \quad (6)$$

After combination (1), (5), (6)

$$V_1^+ = \frac{V_s}{2} \cdot \frac{1 - \bar{\Gamma}_s}{1 - \bar{\Gamma}_s \Gamma_{in}} \quad \dots (7)$$


After combination (1) and (7)

$$P_{in} = \frac{|V_s|^2}{8 Z_0} \cdot \frac{|1 - \bar{\Gamma}_s|^2}{|1 - \bar{\Gamma}_s \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2)$$

# Meaning of the word gain

- **Requires additional specifications:**
  - *What is the load / source impedance*
  - *Voltage, current or power gain*
  - *Which power gain?*
- **Analog designers often use voltage gain.**
- **RF / microwave designers often use power gain.**

# Gain definitions

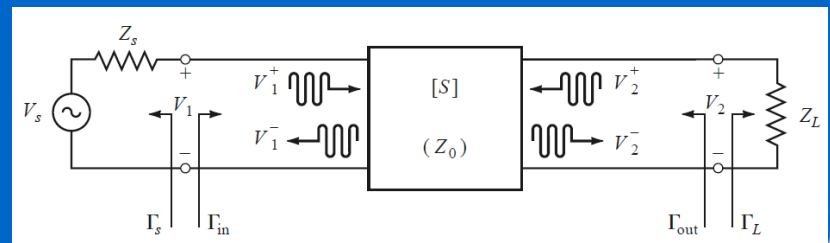

**Power gain  $G$ :** Ratio of the power dissipated in the load  $Z_L$  to the power delivered to the input of the two-port network

**Available power gain  $G_A$ :** Ratio of the power available from the two-port network to the power available from the source. Assumes conjugate matching of source and load impedance.


**Transducer power gain  $G_T$ :** Ratio of the power delivered to the load to the power available from the source. Assumes a matched source impedance.

**Unilateral transducer power gain  $G_{TU}$ :**

Transducer power gain for a device with  $S_{12}=0$



# Load condition for max real power

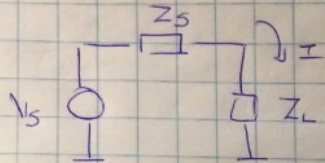

$$I = \frac{V_s}{Z_s + Z_L}$$

$$V_L = \frac{Z_L}{Z_L + Z_s} \cdot V_s$$

$$P_{re} = \operatorname{Re} \left\{ V_L \cdot I^* \right\} \quad \leftarrow \text{We are interested in Real power}$$

$$P_{re} = \operatorname{Re} \left\{ \frac{Z_L}{Z_L + Z_s} \cdot \frac{1}{(Z_s + Z_L)^*} \cdot V_s^2 \right\}$$

$$P_{re} = \operatorname{Re} \left\{ \frac{Z_L}{|Z_L + Z_s|^2} V_s^2 \right\}$$

$$P_{re} = \operatorname{Re} \left\{ Z_L \right\} \frac{V_s^2}{|Z_L + Z_s|^2}$$

$$P_{re} = \frac{R_L}{(R_L + R_s)^2 + (X_L + X_s)^2} \cdot V_s^2$$

$$\max P_{re} \Rightarrow \textcircled{1} \boxed{X_L = -X_s}$$

$$\textcircled{2} \left( \frac{R_L}{(R_L + R_s)^2} \right)' = 0$$

$$(R_L + R_s)^2 - R_L \cdot 2 \cdot (R_L + R_s) = 0$$

$$R_L + R_s - 2R_L = 0$$

$$\boxed{R_s = R_L}$$

$$\boxed{Z_L = Z_s^*}$$

conjugate match  
leads to max  
REAL power on  
load.

# Amplifier gains: Equations

Power gain:

$$G = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2) |1 - S_{22}\Gamma_L|^2}$$

Available power gain:

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{out}|^2)}$$

Transducer power gain:


$$G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2) (1 - |\Gamma_L|^2)}{|1 - \Gamma_S\Gamma_{in}|^2 |1 - S_{22}\Gamma_L|^2}$$

Unilateral transducer  
power gain:

$$G_{TU} = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11}$$

# General transistor amplifier circuit

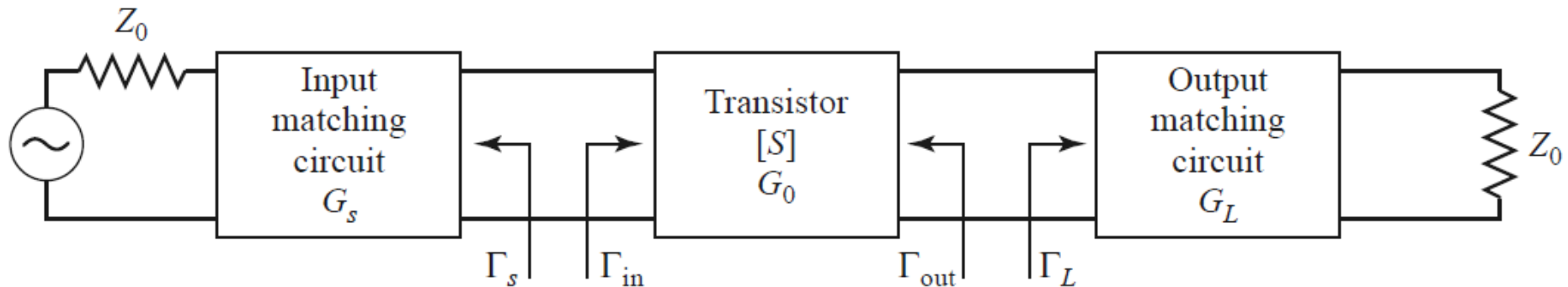

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2}$$

$$G_0 = |S_{21}|^2$$

Unilateral case

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$G_T = G_S G_0 G_L$$

$$G_{T,dB} = G_{S,dB} + G_{0,dB} + G_{L,dB}$$

Remark: If  $S_{12}=0$  then:  $\Gamma_{out} = S_{22}$  and  $\Gamma_{in} = S_{11}$

# Circles of constant power gain

Unilateral transducer power gain  $G_{TU}$  :

$$\begin{aligned}
 G_{TU} &= \left. \frac{P_L}{P_{AVS}} \right|_{\underline{S}_{12}=0} \\
 &= \frac{1 - |\underline{\Gamma}_S|^2}{|1 - \underline{\Gamma}_S \underline{S}_{11}|^2} \underbrace{|\underline{S}_{21}|^2}_{\downarrow G_0} \frac{1 - |\underline{\Gamma}_L|^2}{|1 - \underline{\Gamma}_L \underline{S}_{22}|^2} \\
 &= \underbrace{G_S}_{\downarrow \text{Impact of the input matching network on the gain}} \cdot \underbrace{G_0}_{\downarrow \text{Transistor gain}} \cdot \underbrace{G_L}_{\downarrow \text{Impact of the output matching network on the gain}}
 \end{aligned}$$

For which values of  $\Gamma_S$  do we achieve the desired value of  $G_S$ ?

For which values of  $\Gamma_L$  do we achieve the desired value of  $G_L$ ?




The values of  $\Gamma_S$  that lead to a constant  $G_S$  are situated on circles in the complex  $\Gamma$  plane.

The values of  $\Gamma_L$  that lead to a constant  $G_L$  are situated on circles in the complex  $\Gamma$  plane.

These circles are called:  
**Constant gain circles**

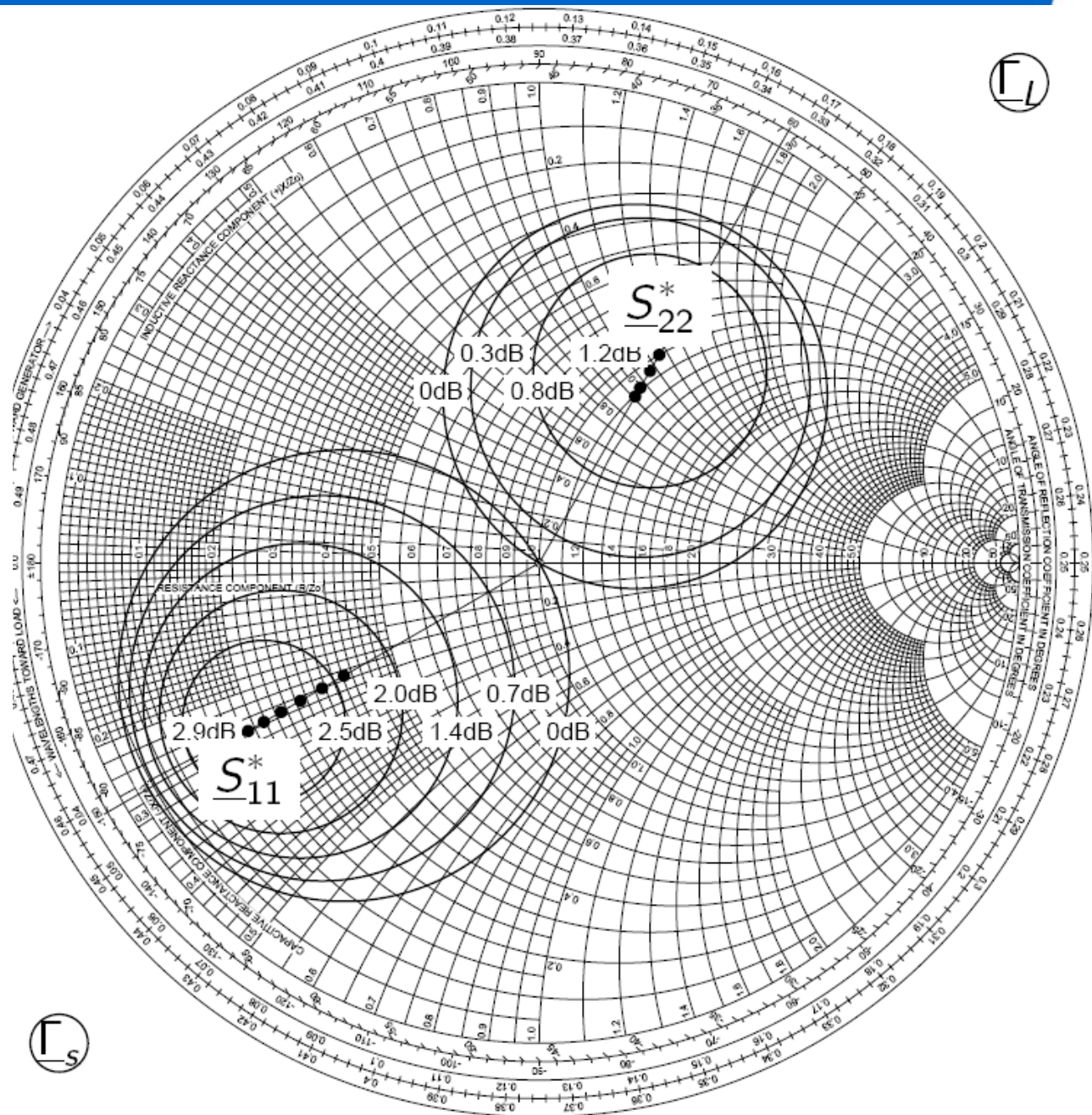For  $\Gamma_S = S_{11}^*$   
maximum  $G_S$  is obtained.  
For  $\Gamma_L = S_{22}^*$   
maximum  $G_L$  is obtained.



# Circles of constant power gain

Maximum gain of the input and output matching networks

$$G_{S_{\max}} = \frac{1}{1 - |S_{11}|^2}, \quad \text{for } \Gamma_S = S_{11}^*$$

$$G_{L_{\max}} = \frac{1}{1 - |S_{22}|^2}, \quad \text{for } \Gamma_L = S_{22}^*$$

Normalized gain factors  $g_S$  and  $g_L$

$$g_S = \frac{G_S}{G_{S_{\max}}} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} (1 - |S_{11}|^2),$$

$$g_L = \frac{G_L}{G_{L_{\max}}} = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} (1 - |S_{22}|^2).$$

Center and radius of the constant gain circle for the input and output matching network

$$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S)|S_{11}|^2},$$


$$R_S = \frac{\sqrt{1 - g_S} (1 - |S_{11}|^2)}{1 - (1 - g_S)|S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L)|S_{22}|^2},$$

$$R_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L)|S_{22}|^2}$$

More info: book of Pozar, page 624, book of Gonzalez, page 103
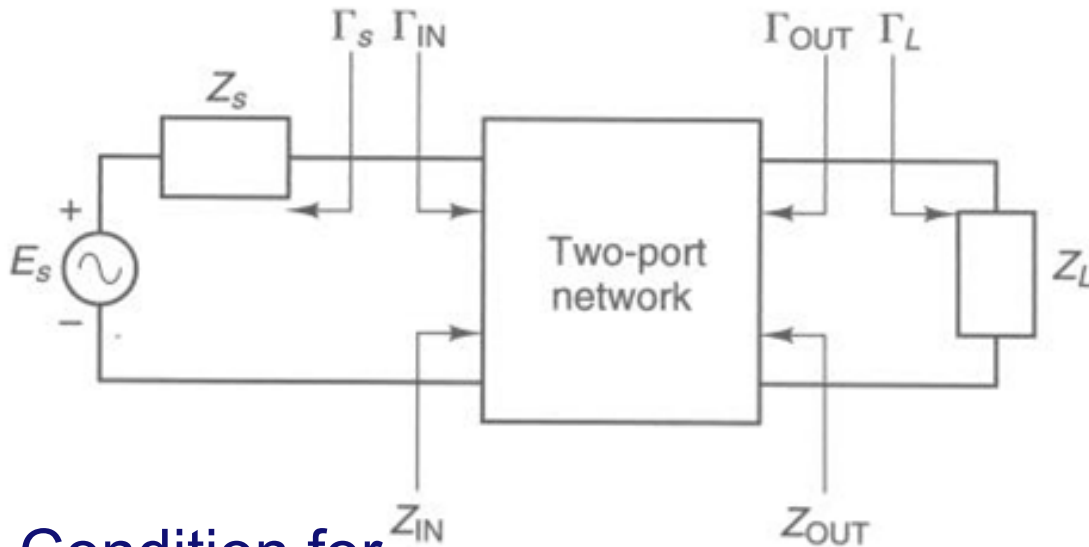
# Stability discussion of 2-port circuits



Stability analysis  
of an amplifier means:  
Investigation whether  
there can be oscillations

Condition for  
“**unconditionally stable**” device:

for all  $|\Gamma_L| < 1$  and  $|\Gamma_s| < 1$

$$\Rightarrow \begin{cases} |\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| < 1 \\ |\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \right| < 1 \end{cases}$$

If at a given frequency  
there are source and load  
reflection coefficients, for which  
this condition does not hold  
the device is called  
“**potentially unstable**”.



# Simplification: Unilateral case

for all  $|\underline{\Gamma}_L| < 1$  and  $|\underline{\Gamma}_S| < 1$

General case:

$$S_{12} \neq 0$$

$$\Rightarrow \begin{cases} |\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| < 1 \\ |\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} \right| < 1 \end{cases}$$

Unilateral case:

$$S_{12} = 0$$

$$\Rightarrow \begin{cases} |\Gamma_{in}| = |S_{11}| < 1 \\ |\Gamma_{out}| = |S_{22}| < 1 \end{cases}$$

# Stability - background

$$\Gamma = \frac{Z - Z_0}{Z + Z_0}$$

$$Z = R + jX$$


---


$$\Gamma = \frac{R + jX - Z_0}{R + jX + Z_0}$$


$$Z_0 = 50 \Omega = R_0$$


---


$$\Gamma = \frac{R - R_0 + jX}{R + R_0 + jX}$$

$$|\Gamma|^2 = \frac{(R - R_0)^2 + X^2}{(R + R_0)^2 + X^2}$$

$R > 0 \Rightarrow |\Gamma| < 1$   
 $R < 0 \Rightarrow |\Gamma| > 1$

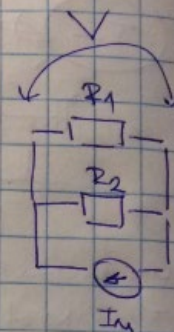

$$R_e = R_1 || R_2$$

$$R_e = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$R_1 = -R_2 \Rightarrow R_e = \infty$$

$$V = R_e \cdot I_n$$

$R_1 = -R_2 \Rightarrow V = \infty$

↑     ↑  
oscillations

# Input stability circles

Boundary between stability and instability is given by:

$$|\Gamma_{\text{OUT}}| = 1$$

$$|\Gamma_{\text{OUT}}| = \left| S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} \right| = 1$$

$$\left| \Gamma_s - \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

Circle equation  
in the complex  $\Gamma$ -plane

$$r_s = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \quad (\text{radius})$$

$$C_s = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad (\text{center})$$

This circle is called the **output stability circle**. It is the boundary between the region  $\Gamma_s$  that lead to a stable or an unstable reflection amplifier.

$$\Delta = S_{11} S_{22} - S_{12} S_{21}$$

An equivalent derivation of the output reflection coefficient leads to the **input stability circle**.

# Output stability circles

Boundary between stability and instability is given by:

$$|\underline{\Gamma}_{in}| = 1$$

$$\Leftrightarrow \left| \underline{S}_{11} + \frac{\underline{S}_{12}\underline{S}_{21}\underline{\Gamma}_L}{1 - \underline{S}_{22}\underline{\Gamma}_L} \right| = 1$$

$$\left| \underline{\Gamma}_L - \frac{\underline{S}_{22}^* - \underline{\Delta}^* \underline{S}_{11}}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \right|^2 = \left| \frac{\underline{S}_{12}\underline{S}_{21}}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \right|^2$$

← Circle equation  
in the complex  $\Gamma$ -plane

$$|\underline{\Gamma}_L - \underline{C}_L|^2 = |\underline{R}_L|^2$$



This circle is called the **output stability circle**. It is the boundary between the region  $\Gamma_L$  that lead to a stable or an unstable reflection amplifier.

$$\underline{C}_L = \frac{(\underline{S}_{22} - \underline{\Delta}\underline{S}_{11}^*)^*}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \quad (\text{center}),$$

$$\underline{R}_L = \left| \frac{\underline{S}_{12}\underline{S}_{21}}{|\underline{S}_{22}|^2 - |\underline{\Delta}|^2} \right| \quad (\text{radius}).$$


$$\underline{\Delta} = \underline{S}_{11}\underline{S}_{22} - \underline{S}_{12}\underline{S}_{21}$$

An equivalent derivation of the output reflection coefficient leads to the **input stability circle**.

# Construction Of the Output Stability circle

$$\left| \Gamma_{in} \right| = \left| S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right|$$

$$\left| \Gamma_{out} \right| = \left| S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S} \right|$$

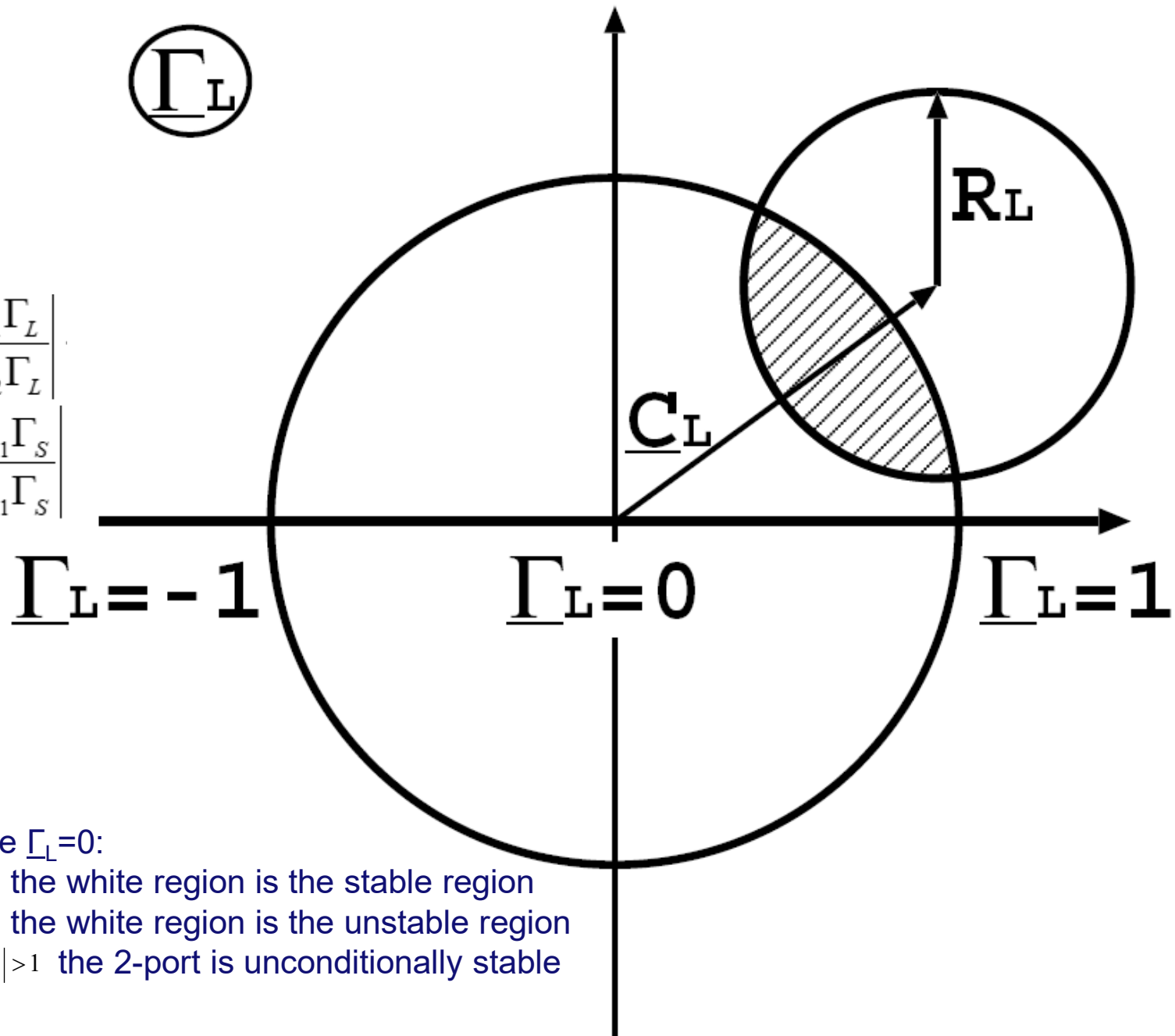

1) Consider the case  $\Gamma_L = 0$ :

if  $|\Gamma_{in}| = |S_{11}| < 1$ , then the white region is the stable region

if  $|\Gamma_{in}| = |S_{11}| > 1$ , then the white region is the unstable region

2) If  $|S_{11}| < 1$  and  $|C_L - R_L| > 1$  the 2-port is unconditionally stable

# Tests for unconditional stability

If  $|\Delta| = |S_{11}S_{22} - S_{12}S_{21}| < 1$

Rollet stability factor K

and  $K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + \Delta^2}{2|S_{12}S_{21}|} > 1$

than the 2-port is unconditionally stable.

**Unilateral case:**  $S_{12}=0$

Conditions for  
unconditional  
stability:

$$|S_{11}| < 1$$

$$|S_{22}| < 1$$