


# Power splitter problem

①

Q: Find the S-matrix of an (ideal) power splitter

The question is, of course, what is the circuit behind a power splitter. There are 4 (!) (and perhaps even more) different versions of a power splitter/divider.

## ① The perfect case

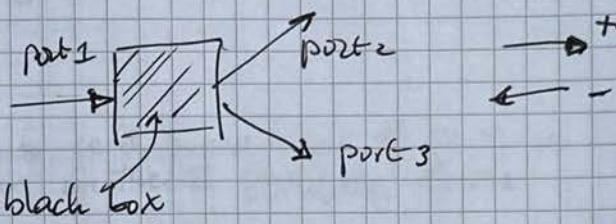

if port 1 is the input of the black box, and port 2 and 3 are the outputs, you want  $\frac{1}{2}$  the power in port 2 and the other half in port 3.

→ since  $P \propto V^2 \Rightarrow$  voltage in port 2 and 3 is  $\frac{1}{\sqrt{2}} (= \frac{1}{2} V_2)$  that of port 1

no reflection


So

$$\begin{pmatrix} V_1^- \\ V_2^+ \\ V_3^+ \end{pmatrix} = \begin{pmatrix} 0 & 0 & 0 \\ \frac{1}{\sqrt{2}} & 0 & 0 \\ \frac{1}{\sqrt{2}} & 0 & 0 \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^- \\ V_3^- \end{pmatrix}$$

However, how to make this? No reflections, perfect matching

... little bit difficult.

## ② The very simple splitter:

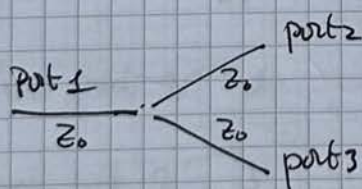

suppose  $Z_0 = 50 \Omega$  (why not?)

Now... we do have lots of reflections

For instance at port 1

$$\Gamma_{11} = \frac{Z_{01}/Z_0 - Z_0}{Z_{01}/Z_0 + Z_0} = \frac{-0.5 Z_0}{1.5 Z_0} = -\frac{1}{3}$$

system is symmetrical  $\Rightarrow \Gamma_{22} = \Gamma_{33} = -\frac{1}{3}$




(2)

That also means that the Transmission is equal

$$T = 1 + \Gamma = 1 - \frac{1}{3} = \frac{2}{3}$$

$$\Rightarrow \begin{pmatrix} V_1^- \\ V_2^+ \\ V_3^+ \end{pmatrix} = \begin{pmatrix} -\frac{1}{3} & \frac{2}{3} & \frac{2}{3} \\ \frac{2}{3} & -\frac{1}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{2}{3} & -\frac{1}{3} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^- \\ V_3^- \end{pmatrix} = \frac{1}{3} \begin{pmatrix} -1 & 2 & 2 \\ 2 & -1 & 2 \\ 2 & 2 & -1 \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^- \\ V_3^- \end{pmatrix}$$

### (3) The power splitter.

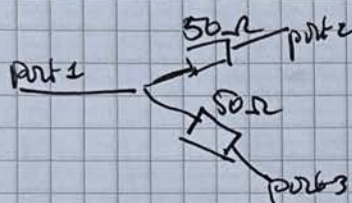

So, two real impedances of  $50 \Omega$  in series in the 2 out going lines

again we have to look at the progressive and regressive voltages.

$$\Gamma_{11} = \frac{(50 \parallel 50) / (50 + 50) - 50}{(50 + 50) / (50 + 50) + 50} = 0 \Rightarrow \text{no input reflection}$$

↑  
series Z + characteristic impedance !!

Let's have a look on the reflection at port 2 (= reflection at port 3)  
looking in port 2, we 'see':

$$50 \parallel \left( 50 + \frac{50 \parallel 50}{2} \right) = 50 + 33\frac{1}{3} = 83\frac{1}{3} \Omega$$

$$\text{So: } \Gamma_{22} = \frac{83\frac{1}{3} - 50}{83\frac{1}{3} + 50} = \frac{33\frac{1}{3}}{133\frac{1}{3}} = \frac{1}{4}$$

$$\text{So: } \Gamma_{33} = \frac{1}{4}$$

$$\text{From port 2} \rightarrow 1 : V_1^- = \frac{50}{50+50} = \frac{1}{2} V_2^- \quad \text{same for port 3} \rightarrow 1$$


$$\text{From port 2} \rightarrow 3 : \frac{1}{2} \times \frac{1}{2} = \frac{1}{4} \quad (\text{two times voltage divider})$$

$$\Rightarrow \begin{pmatrix} V_1^- \\ V_2^+ \\ V_3^+ \end{pmatrix} = \begin{pmatrix} 0 & \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{4} & \frac{1}{4} \\ \frac{1}{2} & \frac{1}{4} & \frac{1}{4} \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^- \\ V_3^- \end{pmatrix}$$



#### 4 The power divider (port symmetric)

(3)

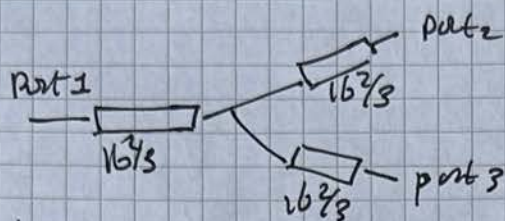


Looks symmetrical :)

First

$$\begin{aligned}\Gamma_{11} &= \frac{[(16\frac{2}{3} + 50) \parallel (16\frac{2}{3} + 50) + 16\frac{2}{3}] - 50}{[(16\frac{2}{3} + 50) \parallel (16\frac{2}{3} + 50) + 16\frac{2}{3}] + 50} \\ &= \frac{66\frac{2}{3} \parallel 66\frac{2}{3} + 16\frac{2}{3} - 50}{66\frac{2}{3} \parallel 66\frac{2}{3} + 16\frac{2}{3} + 50} \\ &= \frac{33\frac{1}{3} + 16\frac{2}{3} - 50}{33\frac{1}{3} + 16\frac{2}{3} + 50} = \phi \quad \text{jipie... no reflection}\end{aligned}$$

$$\Rightarrow \Gamma_{22} = \Gamma_{33} = \phi$$

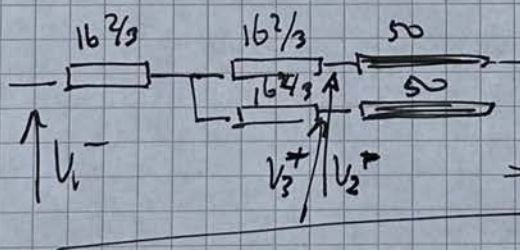now the relation between, for instance  $V_1^-$  and  $V_2^+$



$\Rightarrow$  just a division of the  $16\frac{2}{3}$  impedance in one branch and a  $16\frac{2}{3}$  impedance in the other branch.  
 $\Rightarrow \frac{1}{2}$

So,

$$\begin{pmatrix} V_1^- \\ V_2^+ \\ V_3^+ \end{pmatrix} = \begin{pmatrix} 0 & \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & 0 & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} & 0 \end{pmatrix} \begin{pmatrix} V_1^+ \\ V_2^- \\ V_3^- \end{pmatrix}$$