

EM II Chapter 2

Question 2.1

a.) $H_Y^{(2)} = H_Y^{(1)}$

b.) $\mu_2 H_Y^{(3)} = \mu_1 H_Y^{(1)}$
 $\Rightarrow H_Y^{(3)} = \frac{\mu_1}{\mu_2} H_Y^{(1)}$

c.) $H_Y^{(4)} = H_Y^{(2)} = H_Y^{(1)}$

d.) $H_Y^{(4)} = H_Y^{(3)} = \frac{\mu_1}{\mu_2} H_Y^{(1)}$ contradiction

D_1 ϵ_1, μ_1	D_2 ϵ_1, μ_1
D_3 ϵ_2, μ_2	D_4 ϵ_1, μ_1

$\rightarrow x$

At the right angle where the two line segments meet, ^(A corner) the interface is NOT SMOOTH. The field has singular components at A CORNER, and the piecewise constant approximation fails.

Question 2.2

a.) $V_{\text{steady}} = \frac{450}{450+50} \times 120 \text{ V} = 108 \text{ V}$, $I_{\text{steady}} = \frac{120}{450+50} = 0.24 \text{ A}$

b.) $V_{\text{steady}}^+ = \frac{1}{2} (V_{\text{steady}}^+ + Z I_{\text{steady}}) = \frac{1}{2} (108 + 36) = 72 \text{ V}$
 $V_{\text{steady}}^+ / Z = I_{\text{steady}}^+ = 0.48 \text{ A}$

$V_{\text{steady}}^- = \frac{1}{2} (V_{\text{steady}}^- - Z I_{\text{steady}}) = \frac{1}{2} (108 - 36) = 36 \text{ V}$

$-V_{\text{steady}}^- / Z = I_{\text{steady}}^- = -0.24 \text{ A}$



c.) At $z=0$, after $t=0$, the ^{total} current must be 0, because of the open switch.

d.) $I_{\text{total}}|_{z=0, t>0} = 0 \Rightarrow \frac{V_{\text{comp}}}{Z} + I_{\text{steady}} = 0 \Rightarrow V_{\text{comp}} = -36 \text{ V}$

e.) $\frac{Z_L - Z}{Z_L + Z} = \Gamma_L = \frac{1}{2}$, $\Gamma_g = \frac{\infty - Z}{\infty + Z} = 1$ (open switch).

f.) $\begin{cases} V_{2n}^+ = (\Gamma_L \Gamma_g)^n V_{\text{comp}} = 2^{-n} V_{\text{comp}} = -36 \times 2^{-n} \text{ V} \\ I_{2n}^+ = Y V_{2n}^+ = -0.24 \times 2^{-n} \text{ A} \end{cases}$

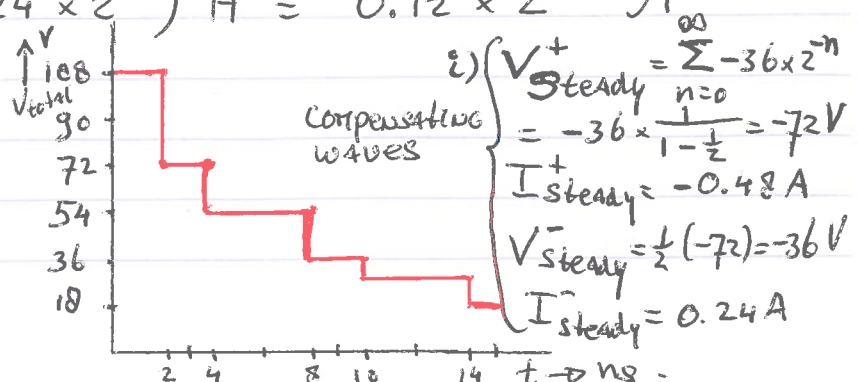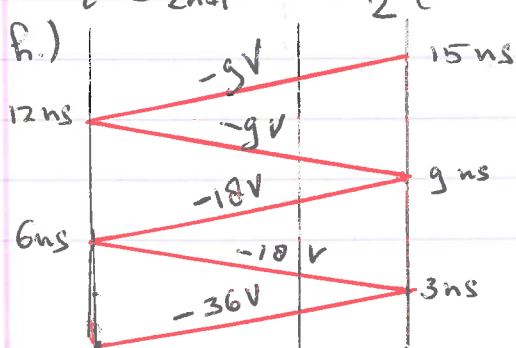g.) $\begin{cases} V_{2n+1}^- = \Gamma_L (\Gamma_L \Gamma_g)^n V_{\text{comp}} = -18 \times 2^{-n} \text{ V} \\ I_{2n+1}^- = -\frac{1}{2} (-0.24 \times 2^{-n}) \text{ A} = 0.12 \times 2^{-n} \text{ A} \end{cases}$



EM II Chapter 2

Question 2.3

a.) Because of the circular symmetry of the configuration, the scalar potential Φ must be independent of φ

$$\Rightarrow \frac{\partial^2}{\partial \varphi^2} \Phi = 0$$

$$b.) \frac{1}{\rho} \frac{d}{d\rho} \left(\rho \frac{d\Phi}{d\rho} \right) = 0 \Rightarrow \frac{d}{d\rho} \left(\rho \frac{d\Phi}{d\rho} \right) = 0 \Rightarrow \rho \frac{d\Phi}{d\rho} = A \text{ (constant)}$$

$$c.) \frac{d\Phi}{d\rho} = \frac{A}{\rho} \Rightarrow \Phi(\rho) = \int_{\rho'=a}^{\rho} \frac{A}{\rho'} d\rho' = A(\underbrace{\log \rho - \log a}_{\text{LN}}) = A \log \frac{\rho}{a} + \Phi(a)$$

$$d.) \Phi(a) = 1 \quad \Phi(b) = \Phi(a) + A \log \frac{b}{a} = 1 + A \log \frac{b}{a} = 0.$$

$$\Rightarrow A = \frac{-1}{\log \frac{b}{a}} \Rightarrow \Phi(\rho) = 1 - \frac{\log \frac{\rho}{a}}{\log \frac{b}{a}} = \frac{\log \frac{b}{\rho}}{\log \frac{b}{a}}$$


$$e.) C = \epsilon \oint_{C_R} \underbrace{-\underline{v} \cdot \nabla_{\perp} \Phi}_{-\frac{d\Phi}{d\rho}} dl = \frac{\epsilon}{\log \frac{b}{a}} \oint_{C_R} \frac{1}{\rho} dl = \frac{2\pi\epsilon}{\log \frac{b}{a}}$$

$$CL = \epsilon \mu \Rightarrow L = \frac{\mu}{\epsilon} \log \frac{b}{a}.$$


$$f.) Z = \sqrt{L/C} = \sqrt{\frac{\mu}{\epsilon}} \cdot \frac{1}{2\pi} \log \frac{b}{a}.$$

note: \log is a more common notation for LN

Question 2.4

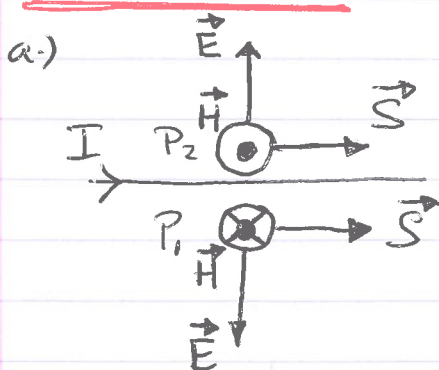

b.)

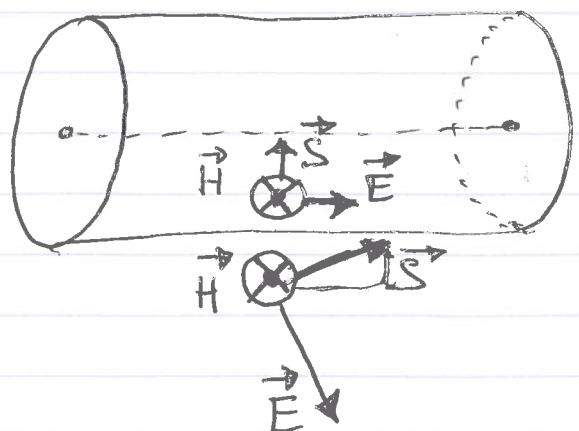

The Poynting vector still points mostly from the battery ~~area~~ to the light bulb. But ~~it~~ it HAS A small component into the wire, where power is dissipated.

1a) $V_{L, \text{steady}}(z, t)|_{z=0} = 0$ (due to short circuit at $z=0$)


$I_{L, \text{steady}}(z, t)|_{z=0} = -\frac{1}{2} \frac{40}{25} \text{ A} = -0.8 \text{ A}$

direction of current
Symmetry of configuration

$V_{L, \text{steady}}^{\pm}|_{z=0} = \frac{1}{2} (V_{L, \text{steady}} \pm \frac{Z}{50\Omega} I_{L, \text{steady}})|_{z=0} = \mp 20 \text{ V}$

$I_{L, \text{steady}}^{\pm}|_{z=0} = \pm \frac{V_{L, \text{steady}}^{\pm}}{Z} = \mp 0.4 \text{ A}$

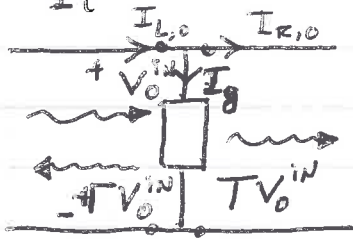1b) $\Gamma_{\pm l} = -1$ (short circuit)



$V_0^{in} + \Gamma V_0^{in} = T V_0^{in}$ (voltage amplitude continuity)


$\frac{V_0^{in}}{Z} - \frac{\Gamma V_0^{in}}{Z} = \frac{(1+\Gamma)V_0^{in}}{25 (=Z_0)} + \frac{T V_0^{in}}{Z}$

$\Rightarrow 1+\Gamma = T$
 $\frac{1-\Gamma}{50} = (1+\Gamma) \left(\frac{1}{25} + \frac{1}{50} \right)$
 $1-\Gamma = 3(1+\Gamma) \Rightarrow \Gamma = -\frac{1}{2}$
 $T = \frac{1}{2}$



Equivalent to

$\Gamma = \frac{\frac{50}{3} - 50}{\frac{50}{3} + 50} = -\frac{1}{2}$

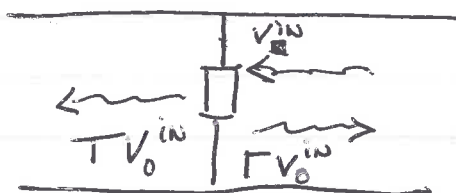$25\Omega \parallel 50\Omega = \frac{50}{3}\Omega$



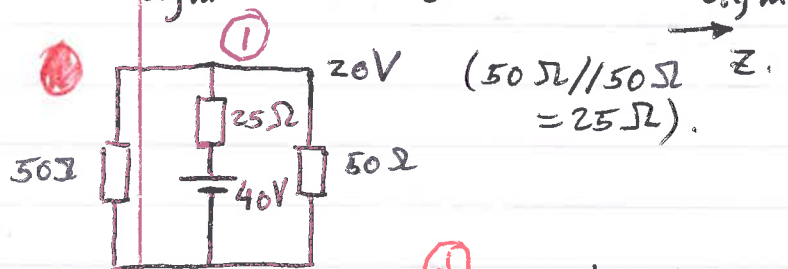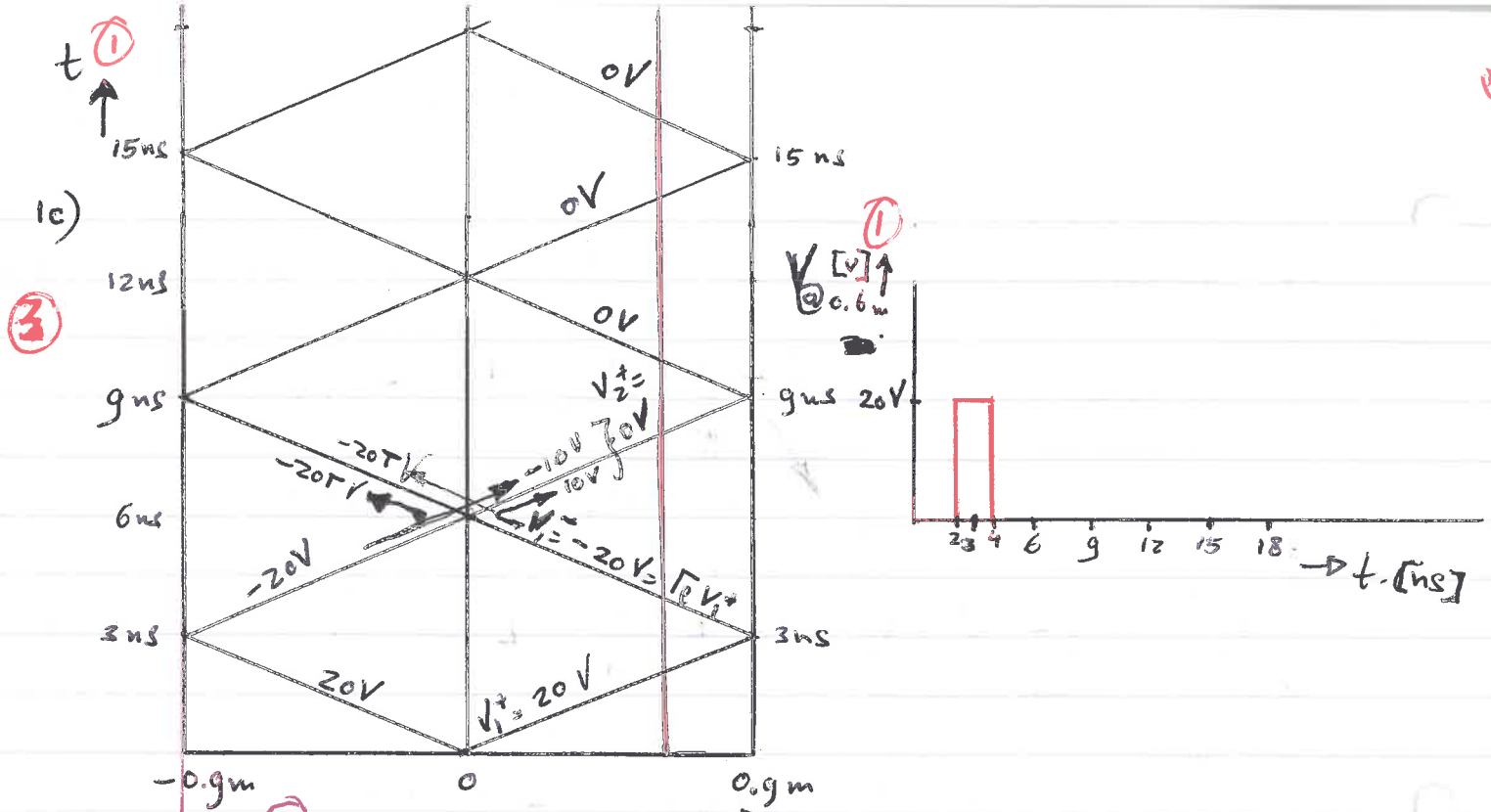$\Rightarrow \Gamma = -\frac{1}{2} \quad T = \frac{1}{2}$ (the same of course)



1d)

$$\left. \begin{aligned} V_{R, \text{steady}}|_{z > 0} &= 0 \quad \left(\begin{array}{l} \text{due to} \\ \text{short circuit at } z = -l \end{array} \right) \\ I_{R, \text{steady}}|_{z > 0} &= 0 \quad \left(\text{due to open end at } z = l \right) \end{aligned} \right\} \begin{aligned} V_{R, \text{steady}} &= 0 \text{ V} \\ I_{R, \text{steady}} &= 0 \text{ A} \end{aligned}$$

(Note: The boundary conditions are labeled with circled 1/2.)

