
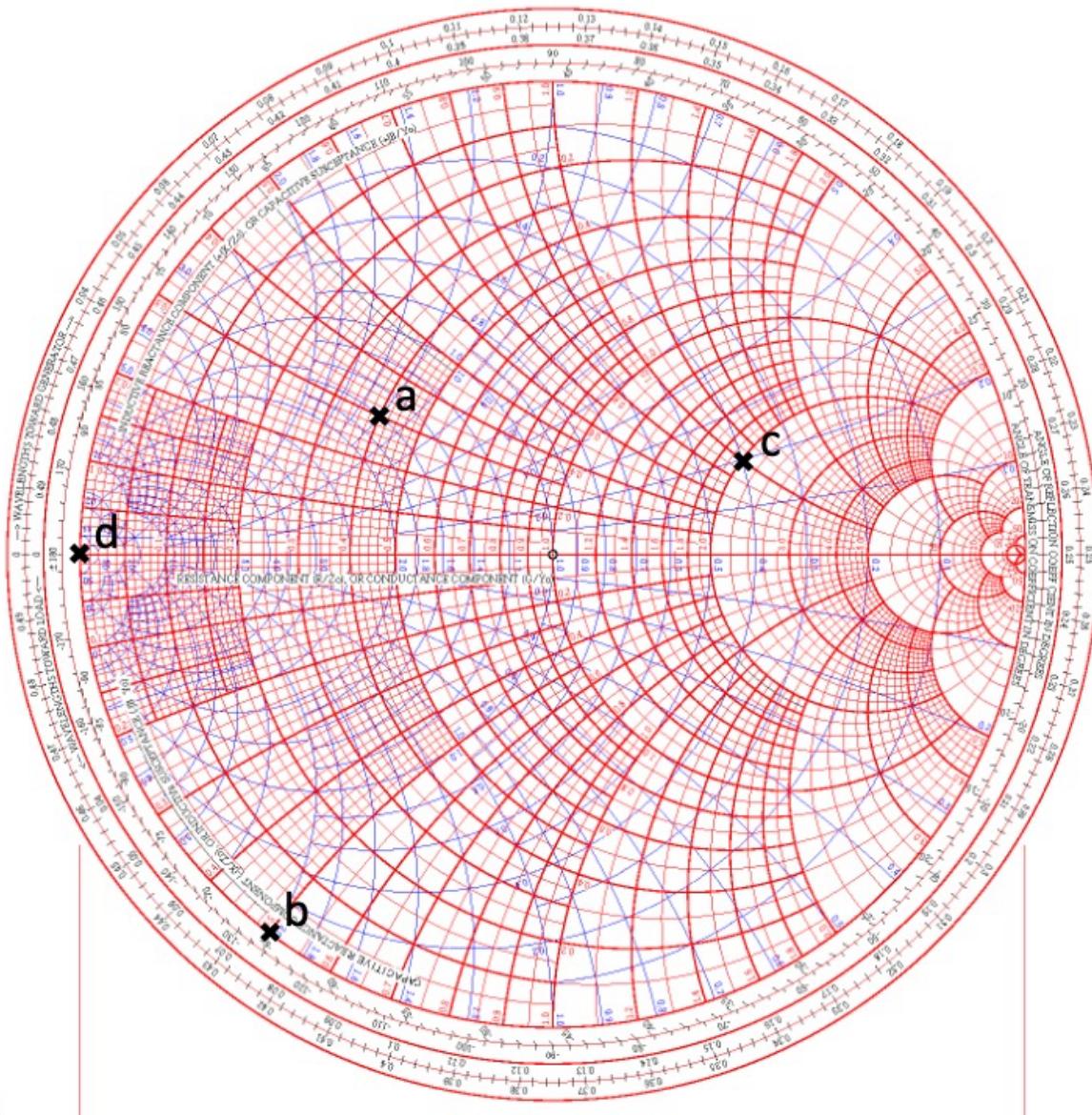


Problem 1 (from old intermediate test)

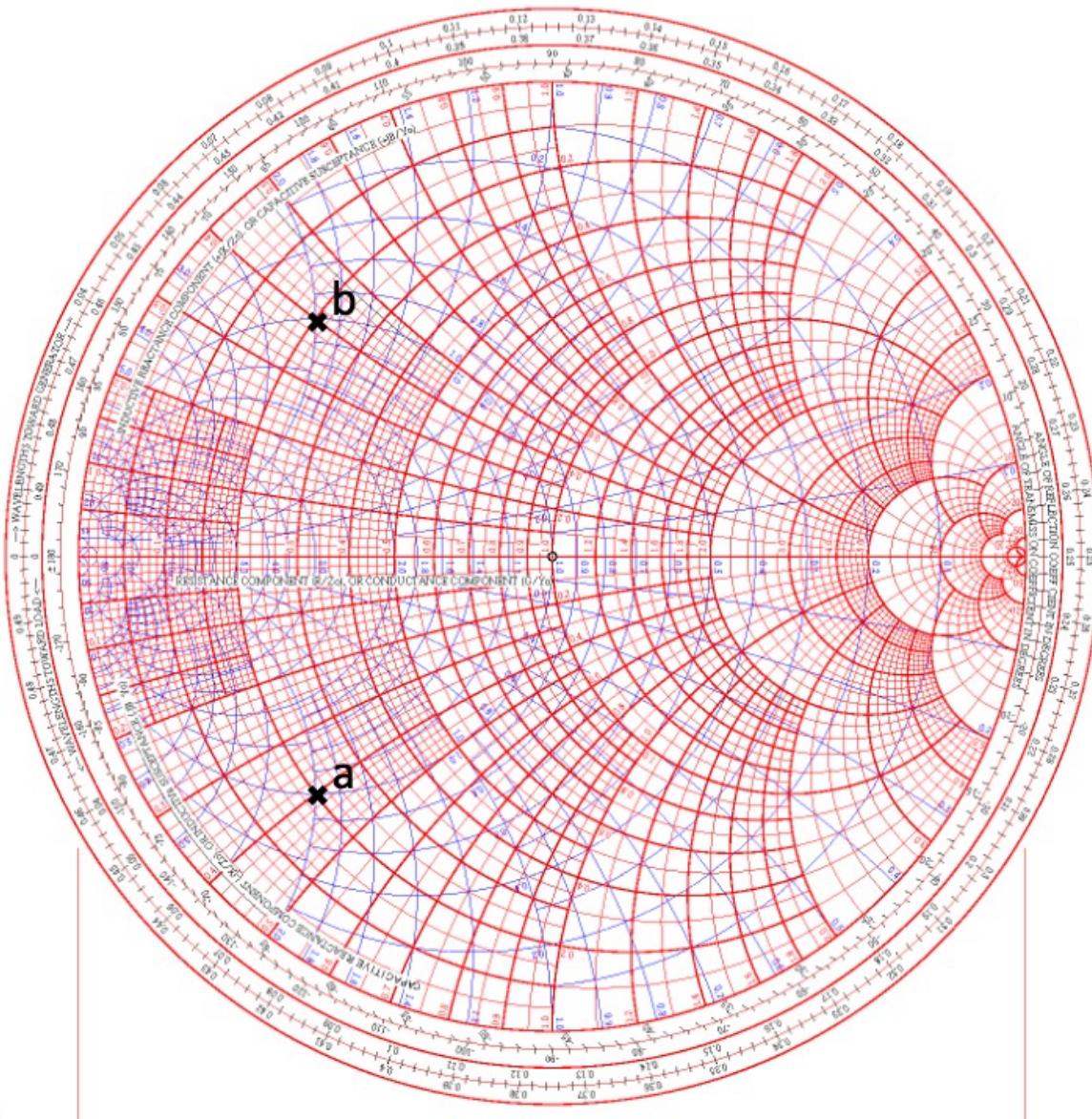

Problem 2 (a-d from old intermediate test)



- (a) $Z'_L = 0.2 - j0.4$ – see Smith. Normalize first: $Z'_L = \frac{10-j20}{50} = 0.2 - j0.4$.
- (b) You should rotate in the Smith chart to get to the point marked b.
- (c) Read the normalized value from the smith chart using (b), and un-normalize it: $Z'_{in} = 0.2 + j0.4 \rightarrow Z_{in} = 50 \cdot Z'_{in} = 10 + j20$.
- (d) Your answer should mention that you will use a capacitor in shunt (only), and that the value needed for it can be found by turning over the admittance.

Problem 3: Transmission lines and microwave networks (old exam question)

5XTCO - June 2020

Q1

a) $Z_L = (15 + j79) \Omega$

$Z_1 = 150 \Omega$

$$\frac{Z_L}{Z_1} = \frac{15}{150} + j \frac{79}{150} = 0.1 + j 0.26 \rightarrow \text{Find in SC}$$

$$\begin{aligned} |P_L| &= 0.89 \\ \underline{\underline{\phi}} &= 131^\circ \end{aligned}$$

b)

$$l_1 = 0.321 \text{ m}, \lambda = \frac{c}{f} = \frac{3 \cdot 10^8 \text{ m/s}}{400 \cdot 10^6 \text{ Hz}} = 0.75 \text{ m}$$

$$\frac{l_1}{\lambda} = 0.428 \Leftrightarrow l_1 = 0.428\lambda \rightarrow \text{Turn } 0.428\lambda \text{ towards generator}$$

$$\frac{Z_L'}{Z_1} = 0.1 - j 0.2 \leftarrow \text{in SC}$$

$$\underline{\underline{Z_L'}} = (15 - j70) \Omega$$

c)


$$\frac{Z_L'}{Z_0} = \frac{15}{45} - j \frac{70}{45} = 0.2 - j 0.4 \rightarrow \text{Find in SC}$$

$$\text{From SC: } \frac{Y_L'}{Y_0} = 1 + j 2 \Rightarrow \underline{\underline{Z_P}} = 0 \Omega$$

$$Y_P = (-j2) Y_0 = -j \frac{2}{45} \frac{1}{\Omega}$$

$$\underline{\underline{Z_P}} = j 27.5 \Omega$$

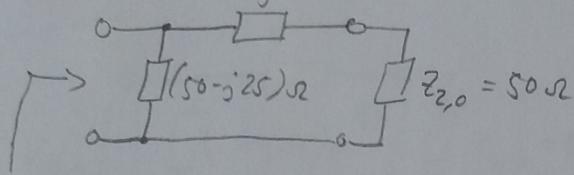d) $S_{11}:$ Ref. impedance $Z_0 = 50 \Omega$



$$\Gamma_1 = S_{11}$$

$$Z_{in,1} = \underbrace{(50-j25)\Omega}_{\text{from } \Delta \text{ SC}} \parallel \underbrace{(50+j100)\Omega}_{\text{from } \Delta \text{ SC}} \rightarrow \frac{Z_2}{Z_0} = \frac{50}{50} + j \frac{100}{50} = \underbrace{1+j2}_{\text{from } \Delta \text{ SC}}$$

$$\underline{Z_1} = \frac{50}{50} - j \frac{25}{50}$$

$$\underline{Z_2} = \frac{1-j0.5}{Y_0}$$


$$\underline{Y_1} = \frac{0.8+j0.4}{Y_0}$$

$$\boxed{\frac{Y_1+Y_2}{Y_0} = 1} \quad \text{center of SC!}$$

$$\Rightarrow Z_{in,1} = 50 \Omega$$

$$\Rightarrow \underline{S_{11}} = 0$$

$S_{22}:$

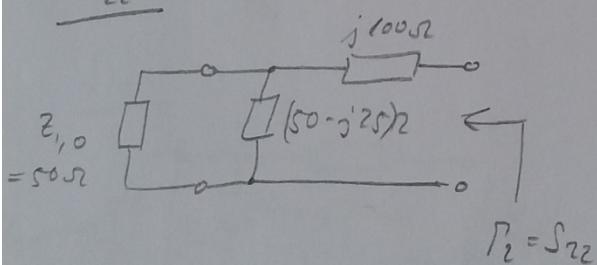

$$\Gamma_2 = S_{22}$$

$$Z_{in,2} = j100\Omega + \left\{ \underbrace{50\Omega \parallel (50-j25)\Omega}_{\text{from } \Delta \text{ SC}} \right\}$$

$$\underline{Y_1} = 1 + 0.8 + j0.4$$

$$\underline{Y_2} = 1.8 + j0.4$$


$$\underline{Z_1} = \frac{0.53-j0.12}{Y_0}$$

$$\cancel{j100\Omega} + Z_2 = 26.5 - j6$$

$$Z_{in,2} = (26.5 - j9\Omega) \Omega$$

$$\underline{\underline{S_{22}}} = \frac{Z_{in,2} - Z_0}{Z_{in,2} + Z_0} = \underline{\underline{0.48 + j0.64}}$$


d) cont'd

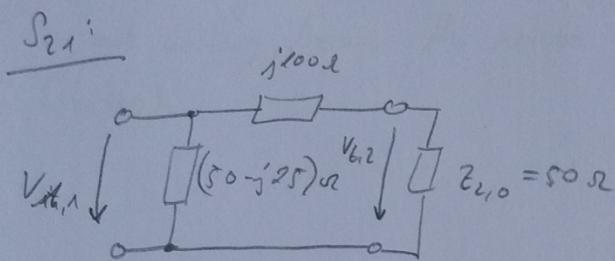

$$V_{t,1} = (1 + S_{11}) V_{in,1}; \quad V_{in,1}: \text{incident voltage wave on port 1 (from the left)}$$

$$\begin{aligned} V_{t,2} &= \frac{Z_{L,0}}{Z_{L,0} + j100} V_{t,1} = \frac{Z_{L,0}}{Z_{L,0} + j100} (1 + S_{11}) V_{in,1}; \quad V_{t,2}: \text{accepted/dissipated} \\ &\quad \text{power in } Z_{L,0} \quad (\text{i.e. port 2}) \\ &= \frac{50\Omega}{(50 + j100)\Omega} (1+0) V_{in,1} \\ &= \frac{1}{1+j2} V_{in,1} = \frac{1-j2}{5} V_{in,1} = (0.2 - j0.4) V_{in,1} \end{aligned}$$
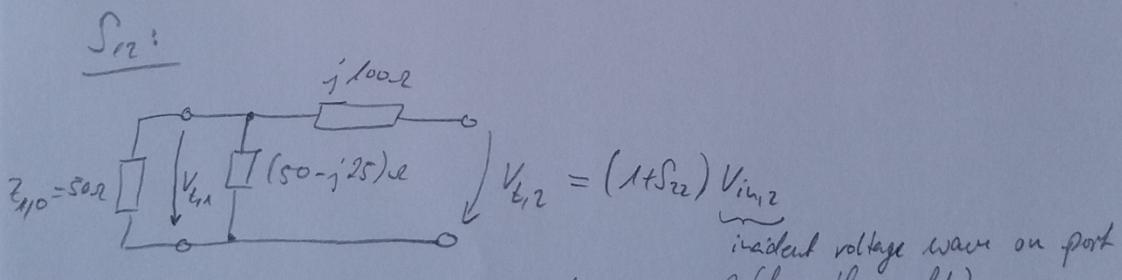
$$\begin{aligned} S_{21} &= \frac{V_{t,2}}{\sqrt{Z_0}} \cdot \frac{\sqrt{Z_0}}{V_{in,1}} = \frac{V_{t,2}}{V_{in,1}} = \underline{0.2 - j0.4} \\ &= \frac{b_2}{a_1} \end{aligned}$$



$$V_{t,2} = (1 + S_{22}) V_{in,2} \quad \text{incident voltage wave on port 2 (from the right)}$$

$V_{t,1}$: accepted/dissipated power in $Z_{L,0}$ (i.e. port 1)

$$\begin{aligned} V_{t,1} &= \frac{\overbrace{50\Omega / ((50 - j25)\Omega)}^{\underline{=21}}}{j100 + \overbrace{\{50\Omega / ((50 - j25)\Omega)\}}^{\underline{=22}}} (1 + \underbrace{S_{22}}_{=0.48 + j0.64}) V_{in,2} \\ &= 26.5 - j6 \end{aligned}$$

$$\begin{aligned} S_{12} &= \frac{V_{t,1}}{V_{in,2}} = \frac{0.2 - j0.4}{V_{in,2}} = S_{21} \quad ! \rightarrow \text{This result could have been known without} \\ &\quad \text{calculations. The network is passive and must be reciprocal} \Rightarrow S\text{-matrix must be symmetrical!} \end{aligned}$$

c) The scattering matrix of the setup shown in Fig. 2
is not unitary, because the network contains lossy components
(resistors).