

Components in wireless technology, 5XTC0

**Module 4
Exercise: Amplifier design**

Vojkan Vidojkovic



Technische Universiteit
Eindhoven
University of Technology


Where innovation starts

Outline

- Introduction to Smith Chart tool
- Introduction to formula list that can be used during exam
- Exercise:
 - Smith Chart
 - Transmission lines
 - Matching networks
 - Amplifier design

Smith Chart Tool

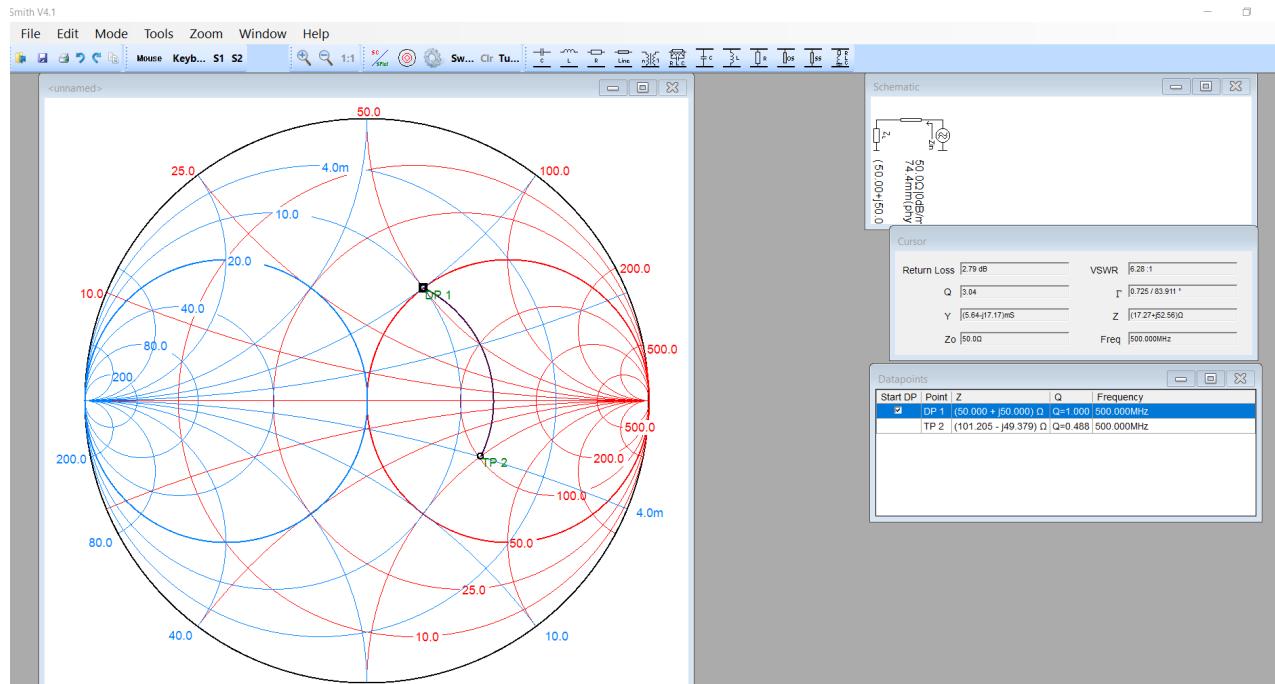- Very good to practice and check analytical expressions
- Link to download the tool:
<https://www.fritz.dellsperger.net.smith.html>
- Smith 4.1




- Link to download Smith Chart: https://leleivre.com/rf_smith.html

Formula list available for exam


Power delivered to the load	$P_L = \frac{ V_2^+ ^2}{2Z_0} (1 - \Gamma_L ^2)$
Input power to the network	$P_m = \frac{ V_1^+ ^2}{2Z_0} (1 - \Gamma_m ^2)$
Input and output reflection coefficients of a transistor with a source and load: general case	$\Gamma_m = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$ $\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$
Input and output reflection coefficients of a transistor with a source and load: unilateral case	$\Gamma_m = \frac{V_1^-}{V_1^+} = S_{11}$ $\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22}$
Gain of the input matching network	$G_S = \frac{1 - \Gamma_S ^2}{ 1 - \Gamma_{in}G_S ^2}$
Gain of the output matching network	$G_L = \frac{1 - \Gamma_L ^2}{ 1 - S_{22}\Gamma_L ^2}$
Gain of the transistor (unilateral case)	$G_0 = S_{21} ^2$
Transducer gain of the basic amplifier circuit (input matching, unilateral transistor, output matching)	$G_T = G_S G_0 G_L$ $G_{T,dB} = G_{S,dB} + G_{0,dB} + G_{L,dB}$
Maximum gain of the input and output matching networks	$G_{S_{max}} = \frac{1}{1 - S_{11} ^2},$ $G_{L_{max}} = \frac{1}{1 - S_{22} ^2}.$
Maximum transducer power gain, unilateral case	$G_{TU_{max}} = \frac{1}{1 - S_{11} ^2} S_{21} ^2 \frac{1}{1 - S_{22} ^2}$
Normalized gain factors g_s and g_L	$g_S = \frac{G_S}{G_{S_{max}}} = \frac{1 - \Gamma_S ^2}{ 1 - S_{11}\Gamma_S ^2} (1 - S_{11} ^2),$ $g_L = \frac{G_L}{G_{L_{max}}} = \frac{1 - \Gamma_L ^2}{ 1 - S_{22}\Gamma_L ^2} (1 - S_{22} ^2).$
Center and radius of the constant gain circle for the input matching network	$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S) S_{11} ^2},$ $R_S = \frac{\sqrt{1 - g_S}(1 - S_{11} ^2)}{1 - (1 - g_S) S_{11} ^2}$
Center and radius of the constant gain circle for the output matching network	$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) S_{22} ^2},$ $R_L = \frac{\sqrt{1 - g_L}(1 - S_{22} ^2)}{1 - (1 - g_L) S_{22} ^2}$
Condition for "unconditionally stable" device, general case	for all $ \Gamma_L < 1$ and $ \Gamma_S < 1$ $\Rightarrow \begin{cases} \Gamma_m = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} < 1 \\ \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} < 1 \end{cases}$

Conditions for "unconditionally stable" device, unilateral case	$ \Gamma_m = S_{11} < 1$ $ \Gamma_{out} = S_{22} < 1$
Center and radius of the stability circles, load side	$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{ S_{22} ^2 - \Delta ^2}$ (center), $R_L = \left \frac{S_{12}S_{21}}{ S_{22} ^2 - \Delta ^2} \right $ (radius). $\Delta = S_{11}S_{22} - S_{12}S_{21}$
Center and radius of the stability circles, source side	$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{ S_{11} ^2 - \Delta ^2}$ (center), $R_S = \left \frac{S_{12}S_{21}}{ S_{11} ^2 - \Delta ^2} \right $ (radius) $\Delta = S_{11}S_{22} - S_{12}S_{21}$
Test for unconditional stability, general case	$ \Delta = S_{11}S_{22} - S_{12}S_{21} < 1$ and $K = \frac{1 - S_{11} ^2 - S_{22} ^2 + \Delta^2}{2 S_{12}S_{21} } > 1$
Test for unconditional stability, unilateral case	$ S_{11} < 1$ $ S_{22} < 1$
Two-stage amplifier: Output noise and noise figure	$P_{N_{total}} = G_{A2}(G_{A1}P_{N,m} + P_{n1}) + P_{n2}$ $\Rightarrow F_{total} = \frac{P_{N_{total}}}{P_{N,m}G_{A1}G_{A2}} = 1 + \frac{P_{n1}}{P_{N,m}G_{A1}} + \frac{P_{n2}}{P_{N,m}G_{A1}G_{A2}}$ $F_{total} = F_1 + \frac{F_2 - 1}{G_{A1}},$ with $F_j = 1 + \frac{P_{nj}}{P_{N,m}G_{Aj}}$, $j = 1, 2$
Noise figure of a 2-port amplifier	$F = F_{min} + \frac{r_N}{g_S} \left \frac{y_S - y_{opt}}{y_S} \right ^2$ $F = F_{min} + 4r_N \frac{\left \Gamma_S - \Gamma_{opt} \right ^2}{\left(1 - \left \Gamma_S \right ^2 \right) \left(1 + \left \Gamma_{opt} \right ^2 \right)}$
Constant noise circles	$\underline{C}_F = \frac{\Gamma_{opt}}{1+N}$ $R_n = \frac{1}{1+N} \sqrt{N^2 + N(1 - \Gamma_{opt} ^2)}$ $\Delta F_n' = N = (F - F_{min}) \frac{\left 1 + \Gamma_{opt} \right ^2}{4r_n} = \frac{\left \Gamma_S - \Gamma_{opt} \right ^2}{1 - \left \Gamma_S \right ^2}$

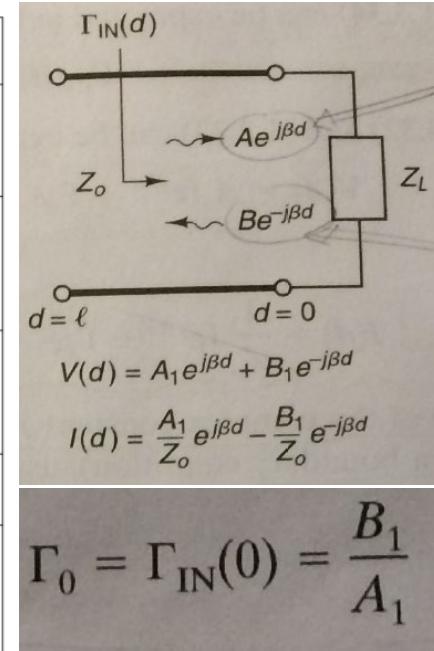

$$\Gamma_0 = \Gamma_{IN}(0) = \frac{B_1}{A_1}$$

Smith Chart Explanation

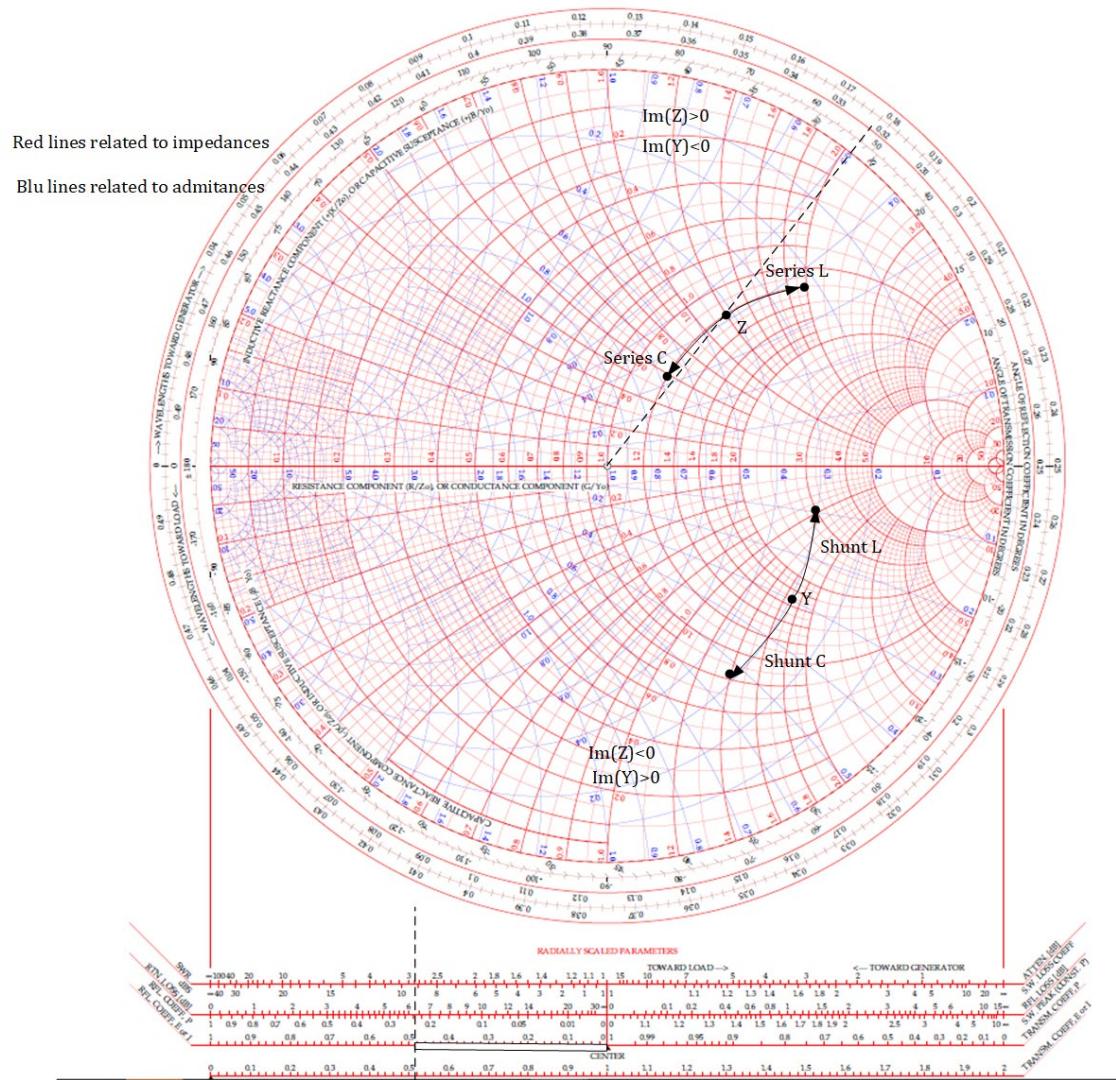

Smith Chart: Problem 1

Problem 1: Locating impedances and admittances in the Smith chart, reading of reflection coefficients

- a) Find the following impedances in the Smith chart (normalized to 50Ω) and determine the corresponding reflection coefficient:

$Z_1 = 50 \Omega$ (matched load)	$Z_2 = 0 \Omega$ (short circuit)	$Z_3 = \infty$ (open circuit)
$Z_4 = 20\Omega + j 25\Omega$	$Z_5 = 20\Omega - j 30\Omega$	$Z_6 = 150\Omega - j 150\Omega$

- b) Find the following admittances in the Smith chart (normalized to $0.02 S$) and determine the corresponding reflection coefficient:

$Y_1 = 0.02 S$ (matched load)	$Y_2 = \infty$ (short circuit)	$Y_3 = 0$ (open circuit)
$Y_4 = 0.02 + j 0.02 S$	$Y_5 = 0.05 - j 0.1 S$	$Y_6 = 0.01 + j 0.05 S$

Smith Chart: Solution for Problem 1a (1/2)

$Z_1 = 50 \Omega$ (matched load)



$Z_4 = 20\Omega + j 25\Omega$

$Z_2 = 0 \Omega$ (short circuit)

$Z_5 = 20\Omega - j 30\Omega$

$Z_3 = \infty$ (open circuit)

$Z_6 = 150\Omega - j 150\Omega$

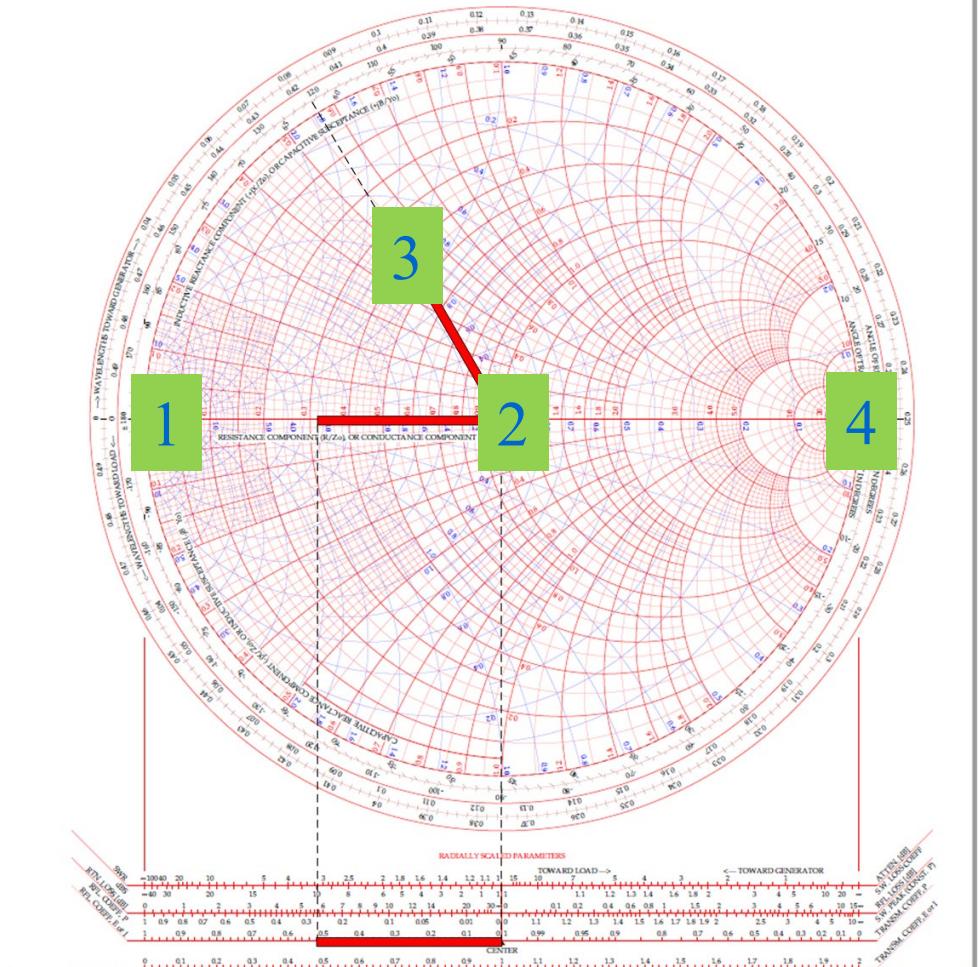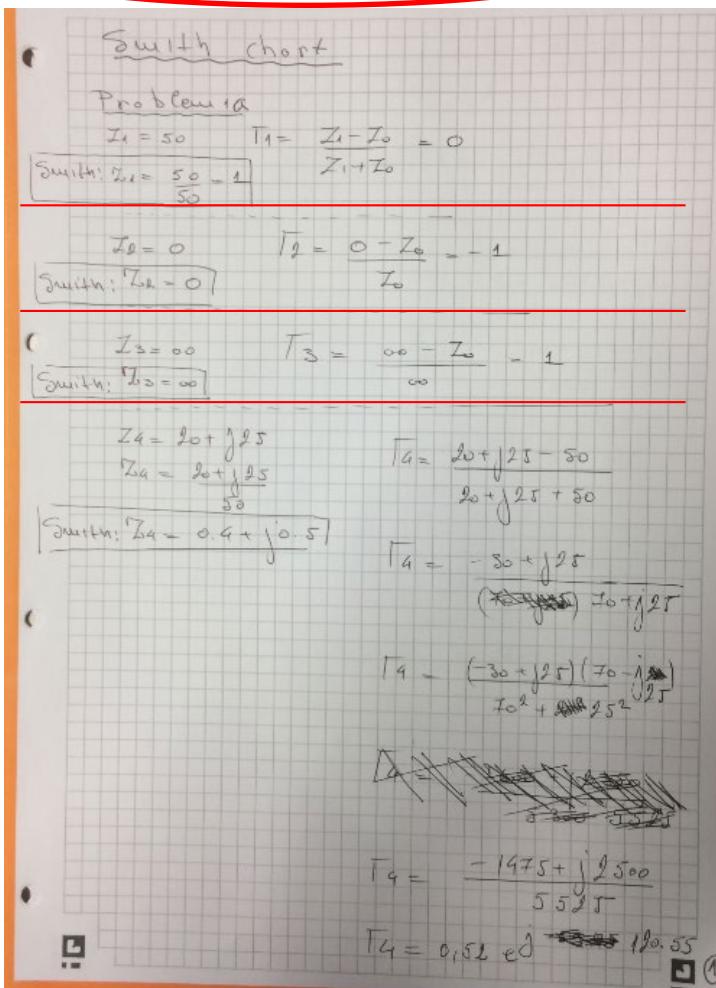

Smith Chart: Solution for Problem 1a (2/2)

$Z_1 = 50 \Omega$ (matched load)



$Z_4 = 20\Omega + j 25\Omega$

$Z_2 = 0 \Omega$ (short circuit)

$Z_5 = 20\Omega - j 30\Omega$

$Z_3 = \infty$ (open circuit)

$Z_6 = 150\Omega - j 150\Omega$

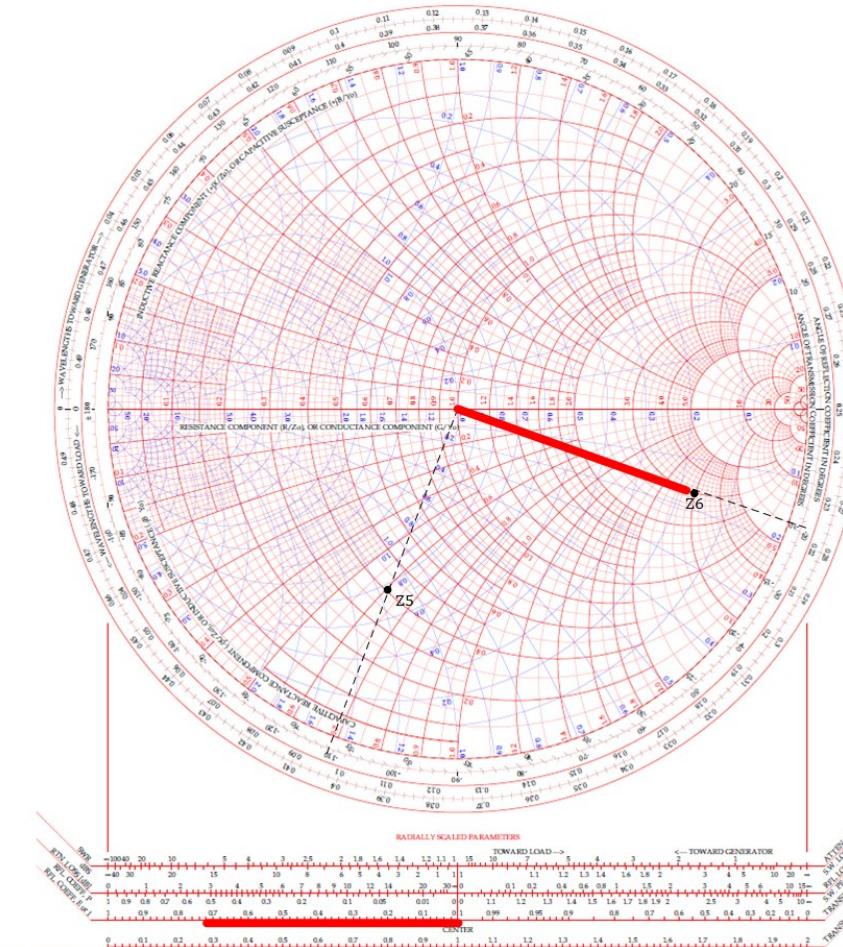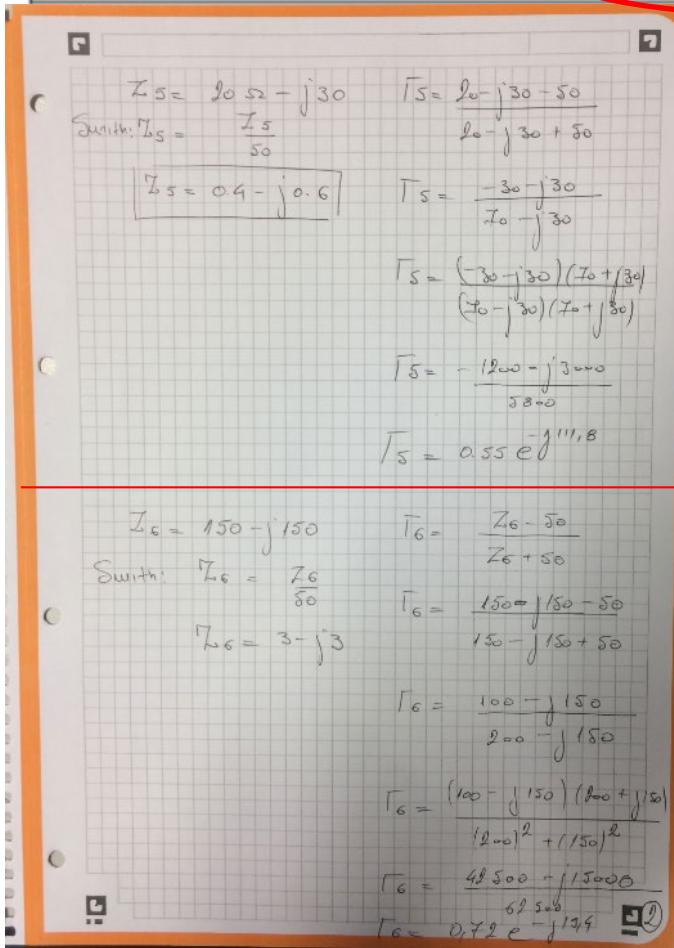

Smith Chart: Solution for Problem 1b (1/3)

$$Y_1 = 0.02 \text{ S} \text{ (matched load)}$$



$$Y_4 = 0.02 + j 0.02 \text{ S}$$

$$Y_2 = \infty \text{ (short circuit)}$$

$$Y_5 = 0.05 - j 0.1 \text{ S}$$

$$Y_3 = 0 \text{ (open circuit)}$$

$$Y_6 = 0.01 + j 0.05 \text{ S}$$

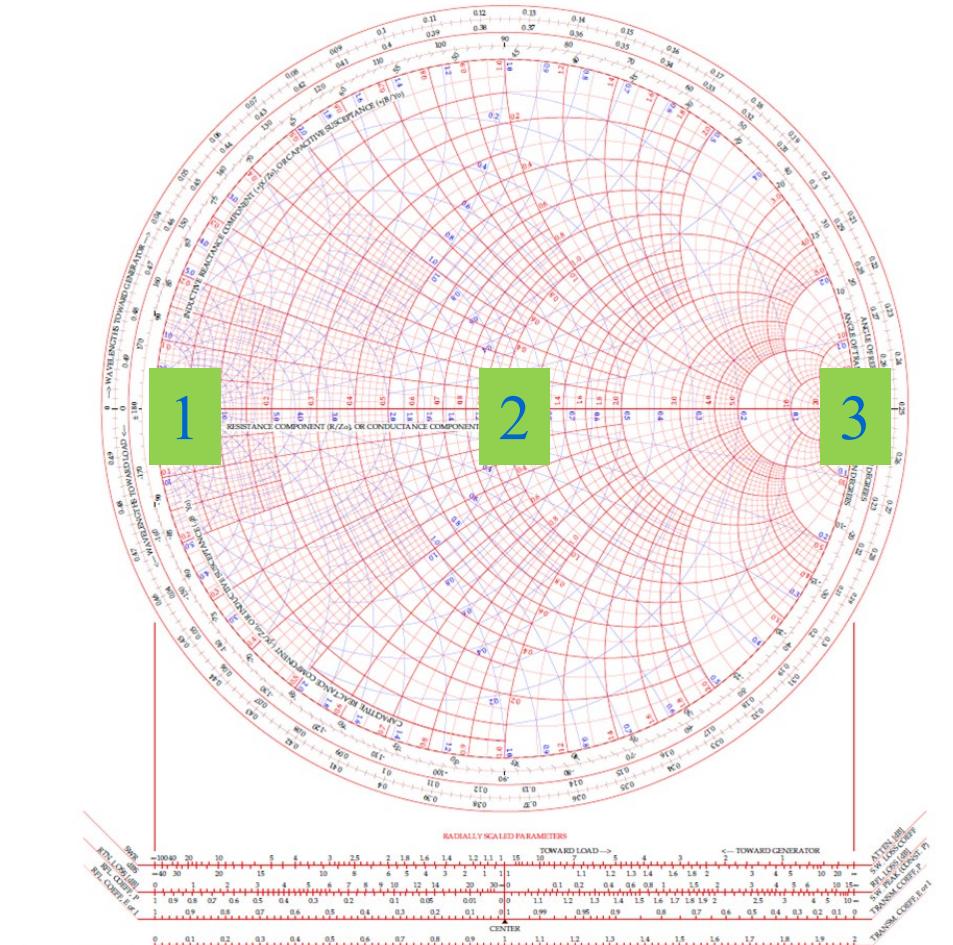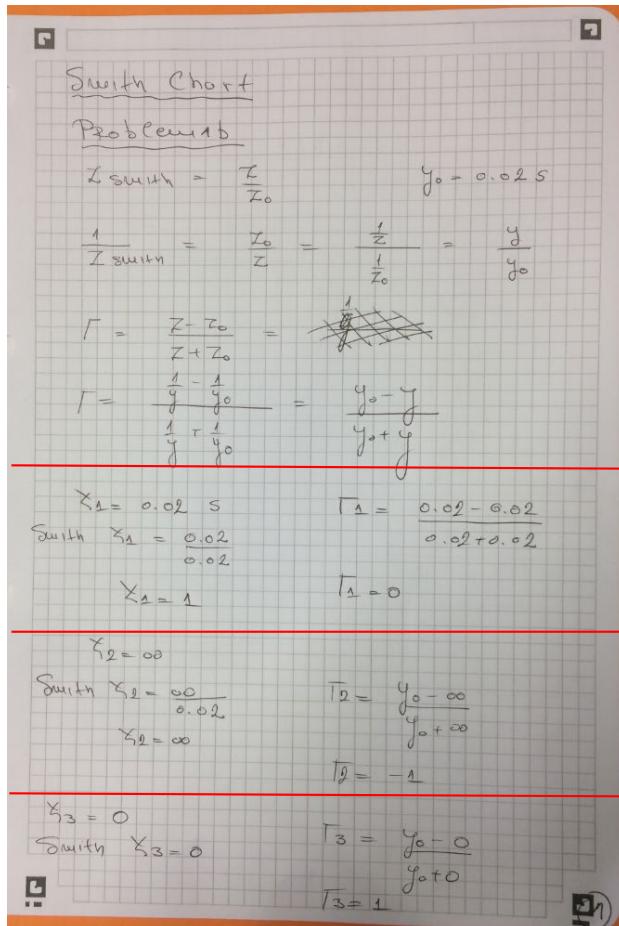

Smith Chart: Solution for Problem 1b (2/3)

$Y_1 = 0.02 \text{ S}$ (matched load)

$Y_4 = 0.02 + j 0.02 \text{ S}$

$Y_2 = \infty$ (short circuit)

$Y_5 = 0.05 - j 0.1 \text{ S}$

$Y_3 = 0$ (open circuit)

$Y_6 = 0.01 + j 0.05 \text{ S}$

$$Y_g = 0.02 + j 0.02$$

$$\text{Smith } Y_4 = \frac{0.02 + j 0.02}{0.02} = 1 + j 1$$

$$\Gamma_g = \frac{Y_o - Y}{Y_o + Y}$$

$$\Gamma_g = \frac{0.02 - 0.02 - j 0.02}{0.02 + 0.02 + j 0.02}$$

$$\Gamma_g = -j 0.02$$

$$\Gamma_g = \frac{-j 0.02}{0.02 + j 0.02}$$

$$\Gamma_g = -j$$

$$\Gamma_g = -j \frac{(2-j)}{2^2+1^2}$$

$$\Gamma_g = -1 - j \frac{2}{5} = -1 - j 0.4$$

$$Y_5 = 0.05 - j 0.1$$

$$\text{Smith } Y_5 = \frac{0.05 - j 0.1}{0.02} = 2.5 - j 5$$

$$\Gamma_5 = \frac{Y_o - Y_5}{Y_o + Y_5}$$


$$\Gamma_5 = \frac{0.02 - 0.05 + j 10^{-1}}{0.02 + 0.05 - j 10^{-1}}$$

$$\Gamma_5 = -0.03 + j 1$$

$$\Gamma_5 = -0.03 + j 1$$

$$\Gamma_5 = -121 + j 40$$

$$\Gamma_5 = 0.85 e^{j 61.5^\circ}$$

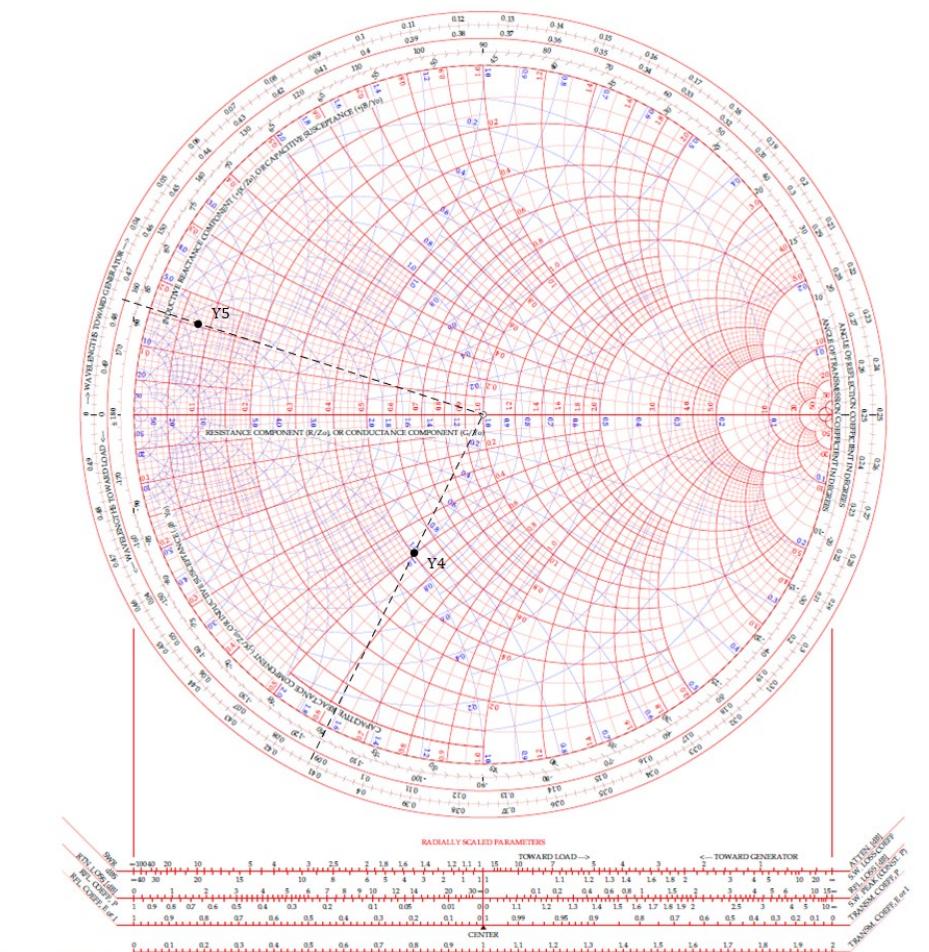

Smith Chart: Solution for Problem 1b (3/3)

$Y_1 = 0.02 \text{ S}$ (matched load)	$Y_2 = \infty$ (short circuit)	$Y_3 = 0$ (open circuit)
$Y_4 = 0.02 + j 0.02 \text{ S}$	$Y_5 = 0.05 - j 0.1 \text{ S}$	$Y_6 = 0.01 + j 0.05 \text{ S}$


$\Gamma_6 = 0.01 + j 0.05$
 $\underline{\Gamma_6} = \frac{0.01 + j 0.05}{0.02}$
 $\underline{\Gamma_6} = 0.5 + j 2.5$

$\Gamma_6 = \frac{0.02 - 0.01 - j 0.05}{0.02 + 0.01 + j 0.05}$
 $\Gamma_6 = \frac{0.01 - j 0.05}{0.03 + j 0.05} \quad | \cdot 100$

$\Gamma_6 = \frac{1 - j 5}{3 + j 5} \quad . \quad \frac{3 - j 5}{3 + j 5}$

$\Gamma_6 = \frac{-24 - j 20}{39} \quad | \cdot 10^{-3} \quad j^{-137.7}$

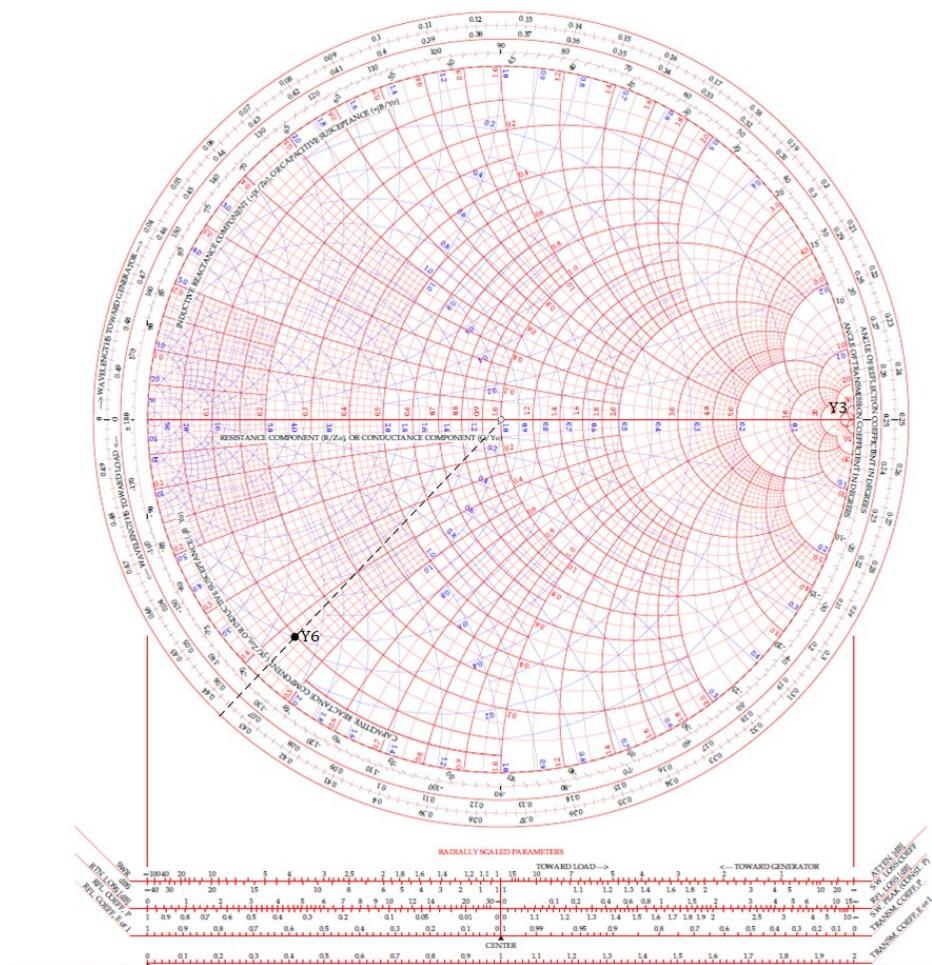$\Gamma_6 = 0.8 + e^{j \theta} \quad (3)$



Smith Chart: Problem 2

Problem 2: Transforming impedances into admittances

- a) Find the corresponding normalized admittance values for the normalized impedance of $z = 1 + j1$.
- b) Analytically calculate the normalized admittance value and compare it to your reading of the Smith chart from question a).

Smith Chart: Solution for Problem 2


Smith Chart: Problem 2

$$I = 1 + j1$$

$$Y = \frac{1}{Z}$$

$$Y = \frac{1}{1+j1} = \frac{1-j1}{(1-j1)(1+j1)} = \frac{1-j1}{2}$$

$$Y = 0.5 - j0.5$$

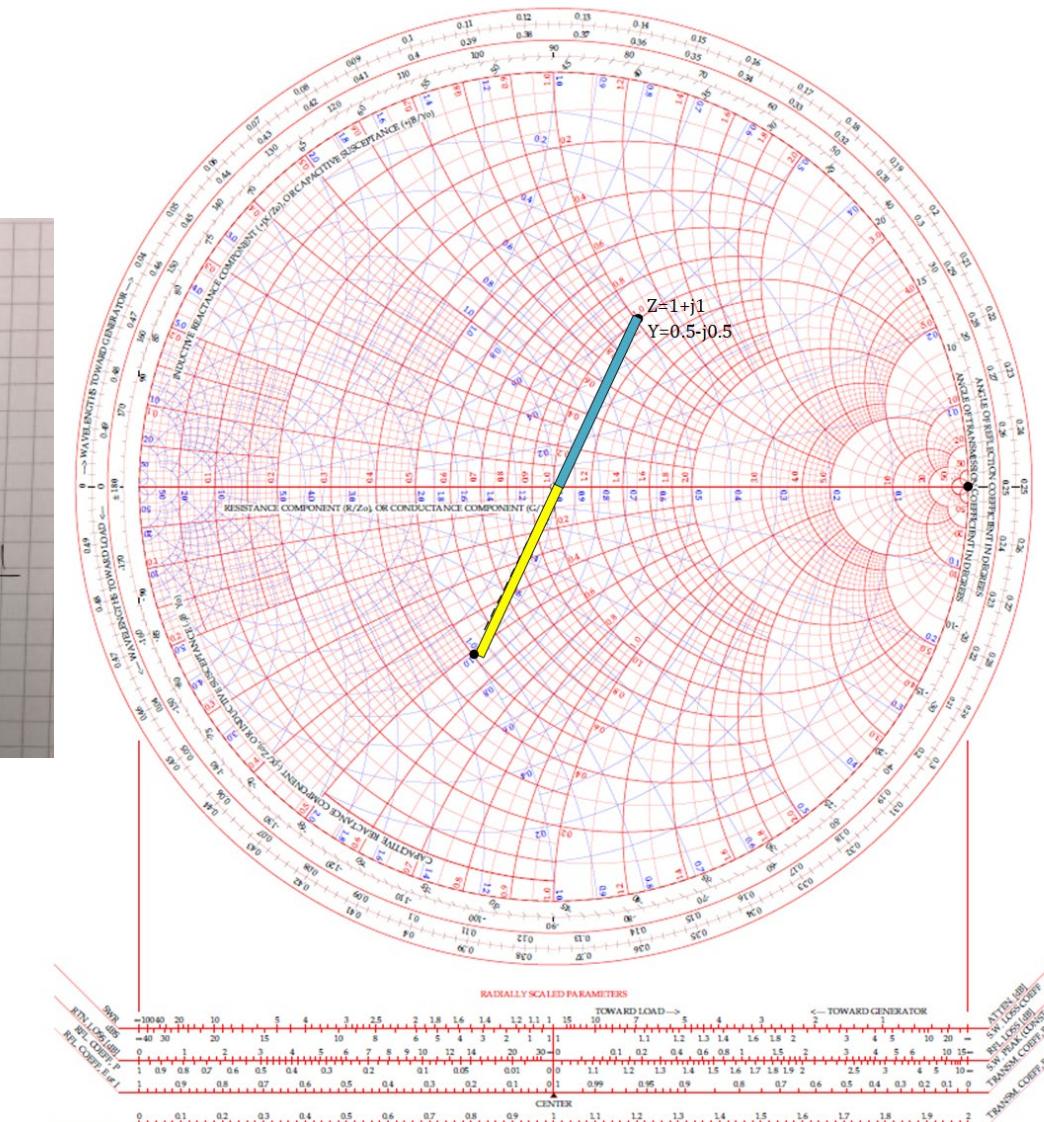


Smith Chart: Problem 3

Problem 3: From reflection coefficient to impedance and VSWR

Find the normalized input impedance whose reflection coefficient is $0.5 \angle 26^\circ$.


Determine the corresponding VSWR for this reflection coefficient in the Smith chart and by analytical calculation. Hint: Use the scale (SWR) in the Smith chart.

Smith Chart: Solution for Problem 3

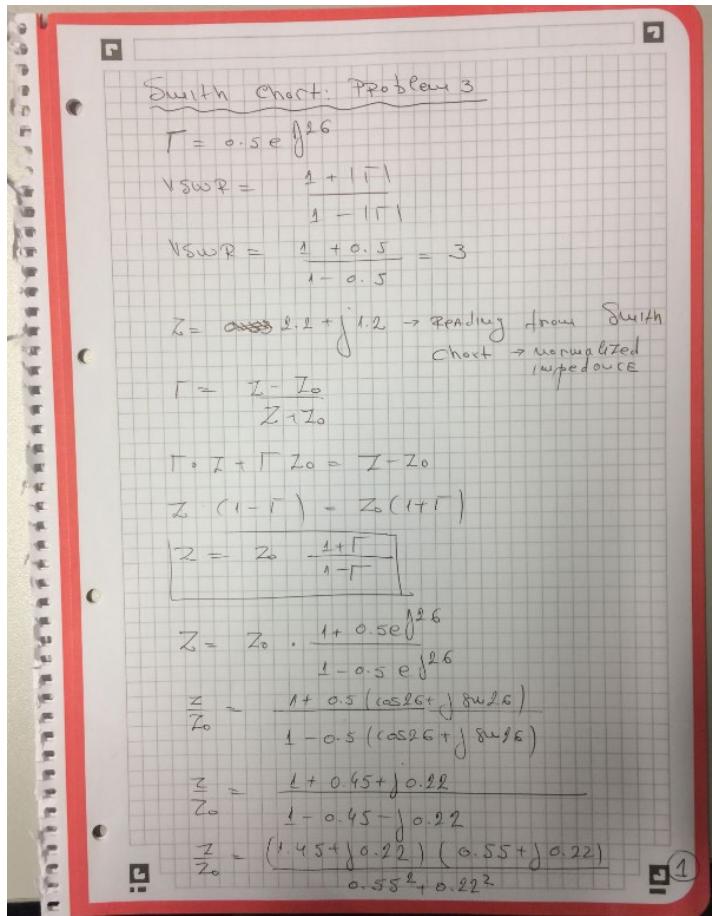

$$\frac{Z}{Z_0} = \frac{0.75 + j0.44}{0.35}$$

$$\frac{Z}{Z_0} = 2.14 + j1.25$$

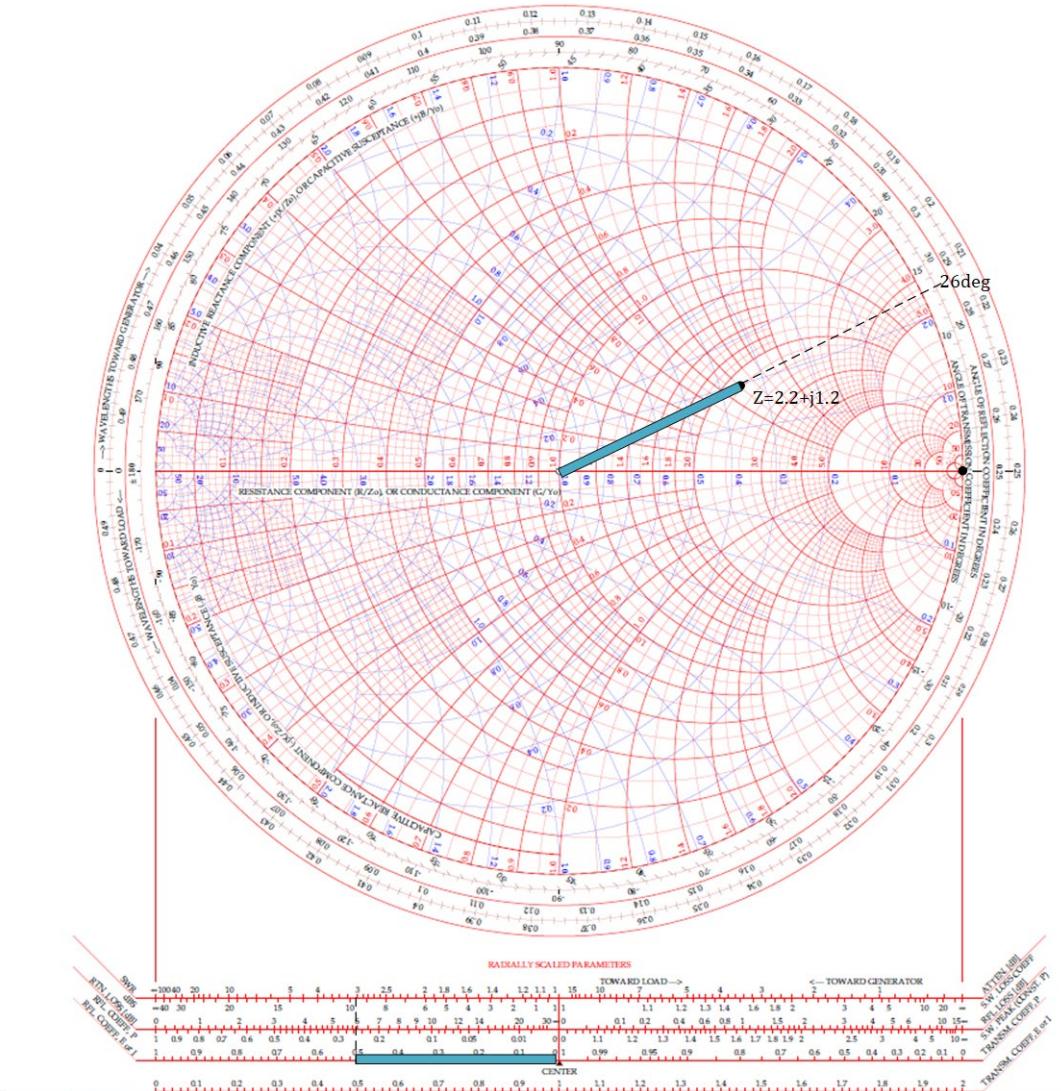


Transmission lines: Problem 4

- a) Use the Smith chart to find the input reflection coefficient, the input impedance and the VSWR for a transmission line having an electrical length of 45° and characteristic impedance of 50Ω and terminated in a load of $Z_L = 50 + j50 \Omega$.
- b) Compare the graphical solution of a) to an analytical calculation of the values.

Γ : input reflection coefficient

Z_{IN} : input impedance

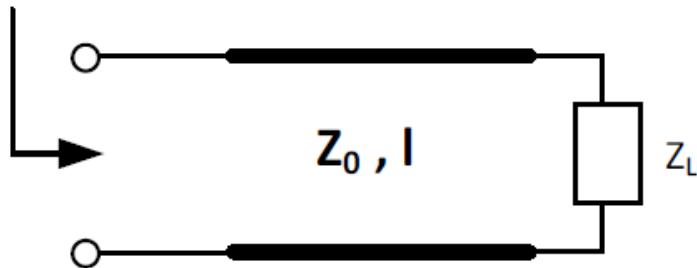

Transmission lines: Solution for Problem 4 (1/2)

Smith chart - Problem 4

a) $\beta l = \frac{\pi}{4} \rightarrow$ electrical length
 $\Rightarrow l = \frac{\pi d}{\lambda} = 0.125 \lambda$

$Z_L = 50 + j50$

$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d} / \beta = l$


$Z_{in} = Z_0 \frac{50 + j50 + j50}{50 + j(50 + j50)}$

$Z_{in} = Z_0 \frac{50 + j100}{j50}$

$Z_{in} = Z_0 \frac{1 + j2}{j} / -j$

$Z_{in} = Z_0 + j + j$

$Z_{in} = Z_0 (2 - j)$

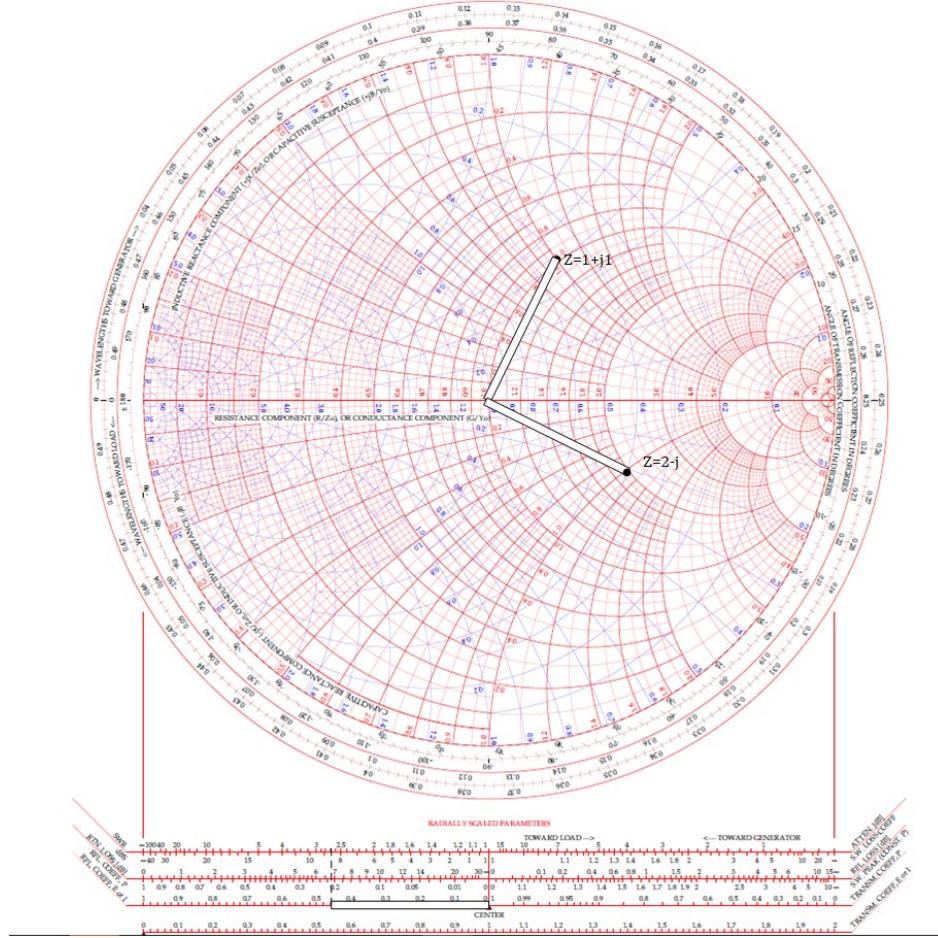

Transmission lines: Smith Chart

$$T_0 = \frac{I_L - I_0}{I_L + I_0}$$

$$T_0 = \frac{50 + j50 - 50}{50 + j50 + 50} = \frac{j50}{100 + j50} = \frac{j}{2+j}$$

$$T_0 = \frac{1 + j2}{5}$$


$$T_0 = 0.4 e^{j63.43}$$

$$V_{SWR} = \frac{1 + 0.4}{1 - 0.4} = 2.57$$

$$T_W = T_0 e^{-j2\pi fd} = T_0 e^{-j\pi/2}$$

$$T_W = 0.4 e^{j(63 - \pi/2)}$$

$$T_W = 0.4 e^{-j26.57}$$

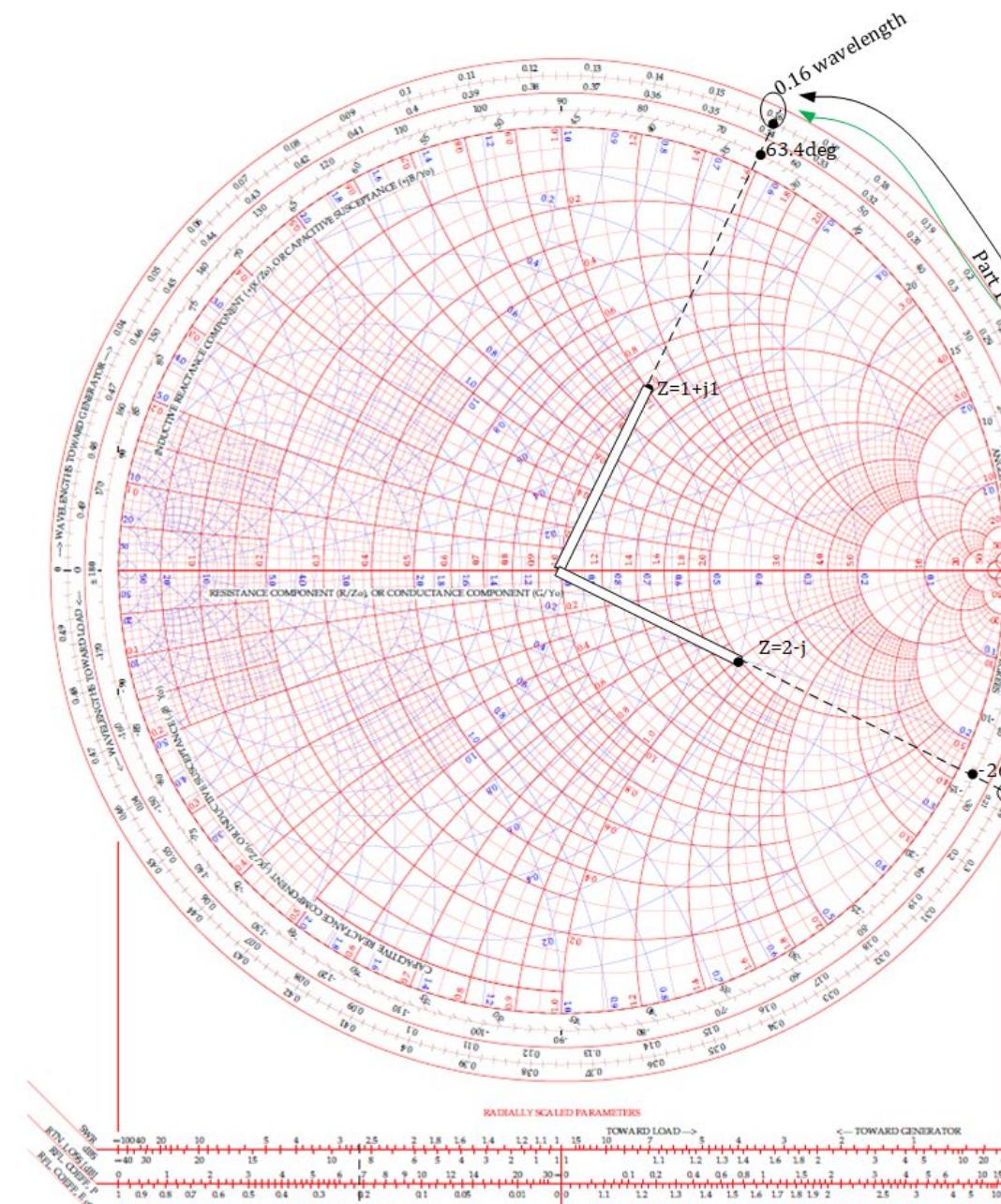

Transmission lines: Problem 5

- 5) Analytically calculate the required length l of a 50Ω short circuited transmission line to obtain an input impedance of $Z_{in}(l) = j 100 \Omega$. Express the length in terms of the wavelength λ . Determine the required length in the Smith chart and compare to your calculation.

Transmission lines: Solution for Problem 5

$$Z_{in} = Z_0 \left(\frac{Z_0 + j Z_L \tan \beta d}{Z_L + j Z_0 \tan \beta d} \right)^{-1}$$

$Z_L = 0$

$$Z_{in} = Z_0 \left(\frac{Z_0}{j Z_0 \tan \beta d} \right)^{-1}$$

~~$Z_{in} = j Z_0 \tan \beta d$~~


$$Z_{in} = j Z_0 \tan \beta d$$

$$j 100 = j 50 \tan \frac{2\pi}{\lambda} d$$

$d = \tan \frac{2\pi}{\lambda} \cdot \frac{1}{2} \quad (\pi = 180^\circ)$

$$\tan^{-1} \frac{1}{2} = 63.43^\circ = 2 \cdot 180^\circ \cdot \frac{d}{\lambda}$$

$d = 0.176 \lambda$

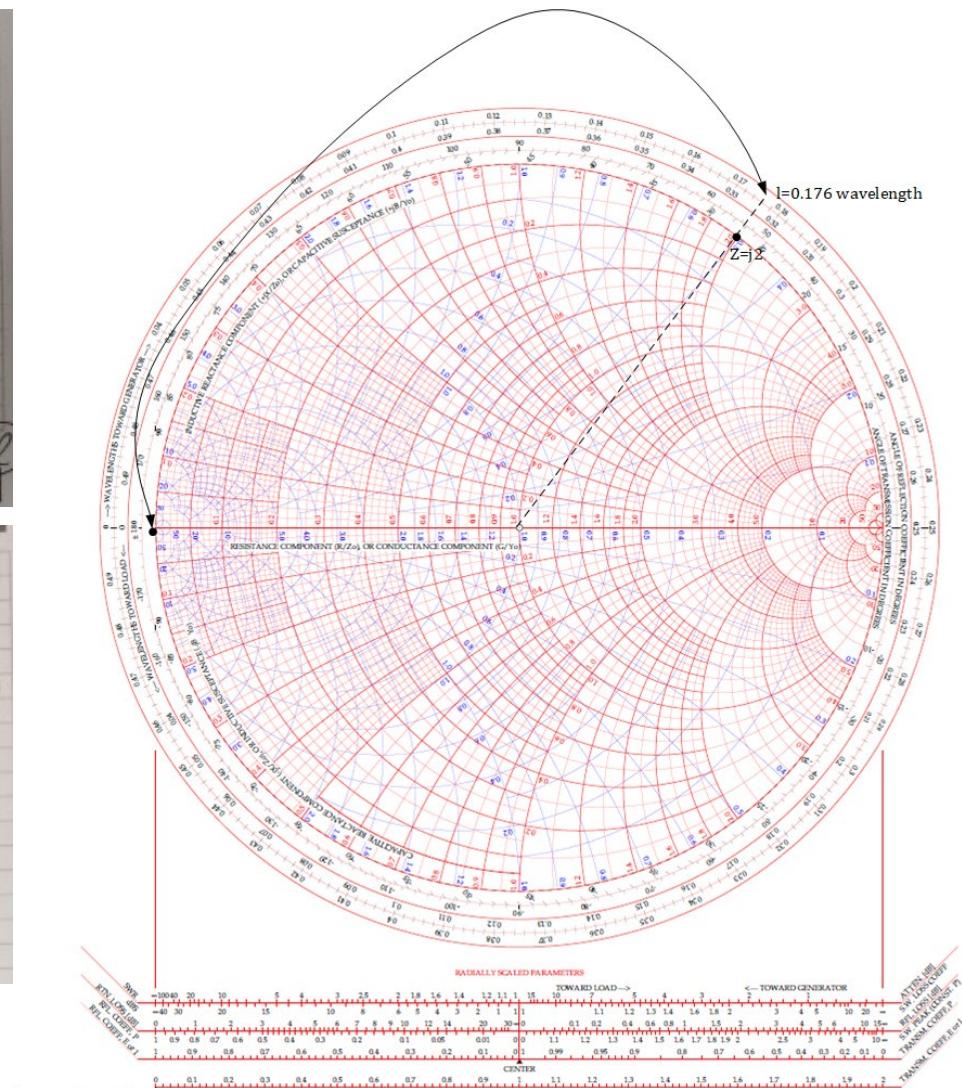

Transmission lines: Problem 6

- 6) Analytically calculate the required length l of a 50Ω open circuited transmission line to obtain an input impedance of $Z_{in}(l) = j 100 \Omega$. Express the length in terms of the wavelength λ . Determine the required length in the Smith chart and compare to your calculation.

Transmission lines: Solution for Problem 6

d) $Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \phi_d}{Z_0 + jZ_L \tan \phi_d}$

$$Z_L = \infty$$

$$Z_{in} = Z_0 \frac{1}{j \tan \phi_d}$$

$$Z_{in} = Z_0 (-j \cot \phi_d)$$


$$y_{100} = -50 \text{ } \mu\text{mho rad}$$

$$-2 = c \tan \phi_d$$

$$\phi_d = \operatorname{atan}^{-1}(-2)$$

$$2\pi d = 153.49$$

$$d = 0.426 \lambda$$

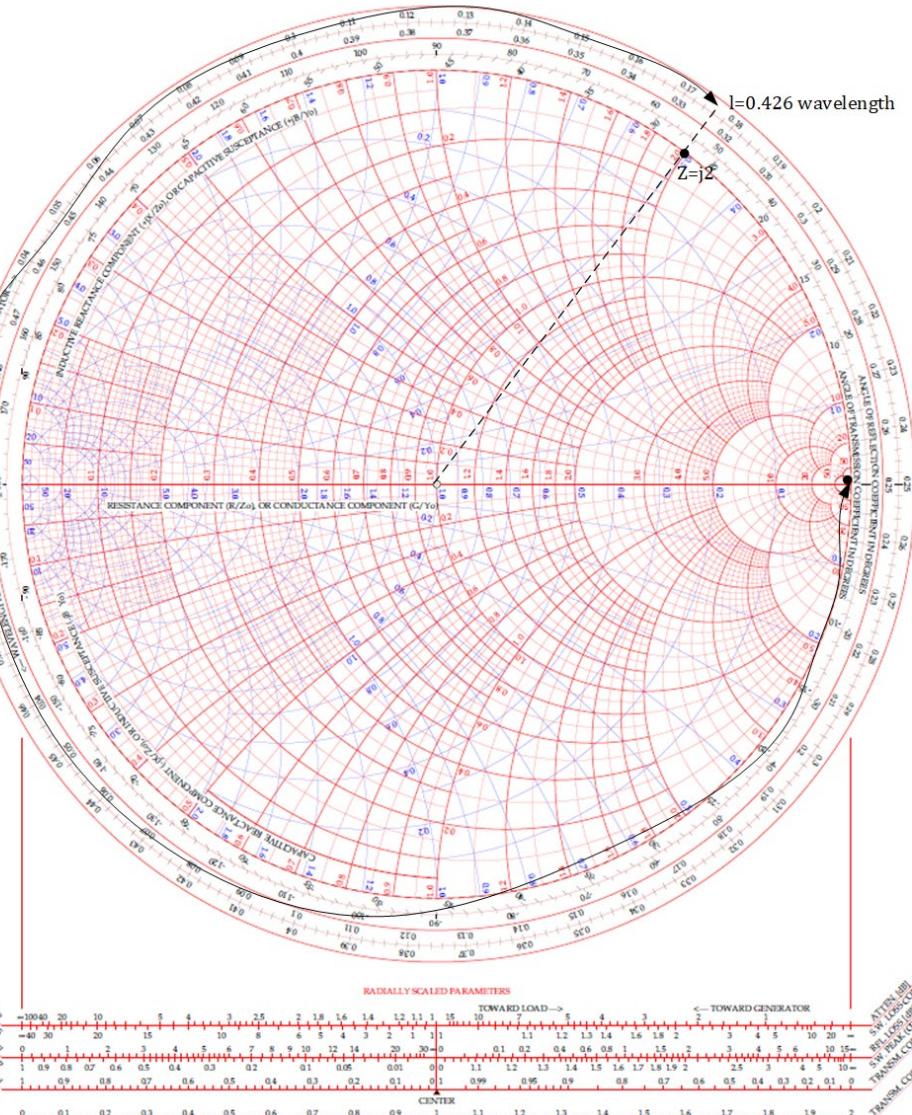

Transmission lines: Problem 7

- Book of Gonzalez: Example 1.3.1

- Find the load reflection coefficient, the input impedance, and the VSWR in the transmission line shown in Fig. 1. The length of the transmission line is $\lambda/8$ and the characteristic impedance is 50Ω .
- Evaluate $V(\lambda/8)$, $I(\lambda/8)$, $P(\lambda/8)$, $V(0)$, $I(0)$ and $P(0)$.
- Write the expression for $v(d,t)$ and $i(d,t)$ along the transmission line.
- Find the length in centimeters of the $\lambda/8$ transmission line at $f=1\text{GHz}$.


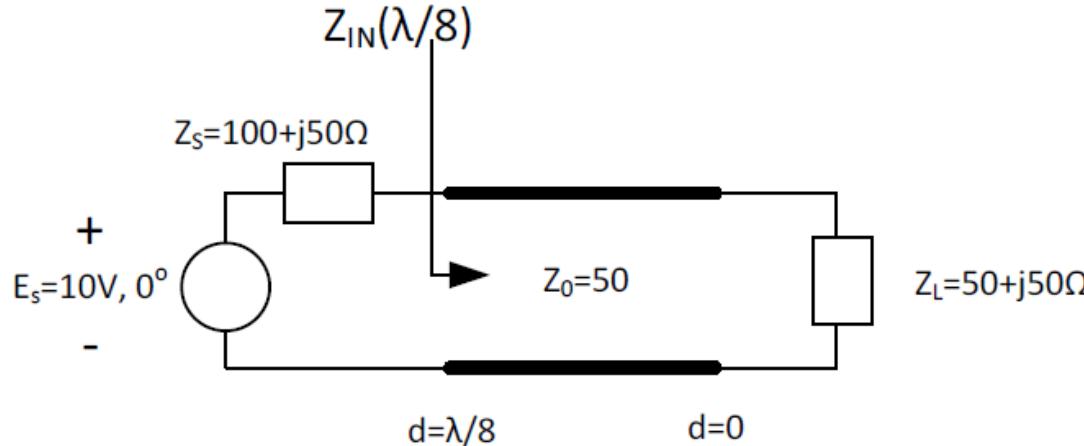


Figure 1 Transmission line circuit example problem 1.

Transmission lines: Solution for Problem 7 a

Gonzales: Example 1.3.1

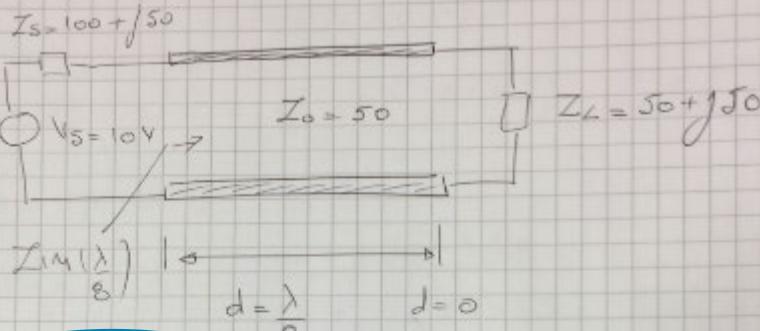

a)

$$T_0 = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$T_0 = \frac{50 + j50 - 50}{50 + j50 + 50} = \frac{j50}{100 + j50} = \frac{j}{2 + j}$$

$$T_0 = \frac{j(2-j)}{(2+j)(2-j)} = \frac{1+j2}{5}$$

$$|T_0| = \sqrt{1+2^2} = \frac{1}{\sqrt{5}} = 0.447$$

$$L T_0 = \tan^{-1}(2/1) = 63.43$$

$$T_0 = 0.447 \angle 63.43$$

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta d}{Z_0 + jZ_L \tan \beta d}$$

$$\beta = \frac{2\pi}{\lambda}, \quad d = \frac{\lambda}{8} \Rightarrow \beta d = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{8} = \frac{\pi}{4}$$

$$\tan \pi/4 = 1$$

$$Z_{in} = Z_0 \frac{50 + j50 + j50}{50 + j \cdot (50 + j50)}$$

$$Z_{in} = Z_0 \frac{50 + j100}{j50}$$

$$Z_{in} = 8 \cdot 100 + \frac{50}{j}$$

$$Z_{in} = 100 - j50$$

$$V = A_1 e^{j\beta d} + B_1 e^{-j\beta d}$$

$$V = A_1 e^{j\beta d} \cdot (1 - T_0 e^{-j2\beta d})$$

$$|V_{max}| = |A_1| (1 + |T_0|)$$

$$|V_{min}| = |A_1| (1 - |T_0|)$$

$$VSWR = \frac{|V_{max}|}{|V_{min}|} = \frac{1 + |T_0|}{1 - |T_0|}$$

$$VSWR = \frac{1 + 0.447}{1 - 0.447} = 2.62 \quad \boxed{2}$$

Transmission lines: Solution for Problem 7 b (1/3)

$$b) V = A_1 e^{j\beta d} + B_1 e^{-j\beta d}$$

$$V = A_1 e^{j\beta d} \left(1 + \frac{B_1}{A_1} e^{-j2\beta d} \right)$$

$$T_0 = \frac{B_1}{A_1}$$

$$V(d) = A_1 e^{j\beta d} \left(1 + T_0 e^{-j2\beta d} \right)$$

$$Z(d) = \frac{A_1}{T_0} e^{-j\beta d} \left(1 - T_0 e^{-j2\beta d} \right)$$

$$d = \lambda/8 \quad \beta d = \frac{\omega t}{\lambda} \cdot \frac{\lambda}{8} = \pi/4$$

$$V\left(\frac{\lambda}{8}\right) = A_1 e^{j\pi/4} \left(1 + 0.447 e^{j63.43^\circ} \right)$$

$$V\left(\frac{\lambda}{8}\right) = A_1 e^{j\pi/4} \left(1 + 0.447 e^{-j26.57^\circ} \right)$$

$$V\left(\frac{\lambda}{8}\right) = A_1 \left(e^{j\pi/4} + 0.447 e^{j18.43^\circ} \right)$$


$$V\left(\frac{\lambda}{8}\right) = A_1 \left(0.71 + j0.71 + 0.42 + j0.19 \right)$$

$$V\left(\frac{\lambda}{8}\right) = A_1 (1.13 + j0.85)$$

3

Equivalent circuit:

$$Z_S = 100 + j50$$

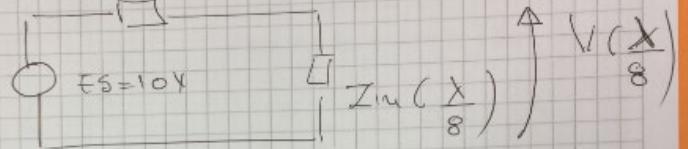

$$Z_m \left(\frac{\lambda}{8} \right) = 100 - j50$$

$$V\left(\frac{\lambda}{8}\right) = E_S \cdot \frac{Z_m \left(\frac{\lambda}{8} \right)}{Z_S + Z_m \left(\lambda/8 \right)}$$

$$V\left(\frac{\lambda}{8}\right) = E_S \cdot \frac{100 - j50}{100 + j50 + 100 - j50}$$

$$V\left(\frac{\lambda}{8}\right) = E_S \cdot \frac{100 - j50}{200}$$

$$V\left(\frac{\lambda}{8}\right) = 10 (0.5 - j0.25)$$

$$V\left(\frac{\lambda}{8}\right) = 10 \cdot \sqrt{0.5^2 + 0.25^2} \quad \left| \tan^{-1} \frac{0.25}{0.5} \right.$$

$$V\left(\frac{\lambda}{8}\right) = 5.53 \quad \left[-26.57^\circ \right]$$

4

Transmission lines: Solution for Problem 7 b (2/3)

$$I\left(\frac{\lambda}{8}\right) = \frac{E_s}{Z_s + Z_m\left(\frac{\lambda}{8}\right)}$$

$$I\left(\frac{\lambda}{8}\right) = \frac{10}{100 + j50 + 100 - j50}$$

$$I\left(\frac{\lambda}{8}\right) = \frac{10}{200} = 0.05 \text{ A}$$

$$P\left(\frac{\lambda}{8}\right) = \operatorname{Re} \left(V\left(\frac{\lambda}{8}\right) \cdot I\left(\frac{\lambda}{8}\right)^*\right)$$

$$P\left(\frac{\lambda}{8}\right) = \frac{1}{2} \operatorname{Re} \left(V\left(\frac{\lambda}{8}\right) \cdot I\left(\frac{\lambda}{8}\right) \right)$$

$$P\left(\frac{\lambda}{8}\right) = \frac{1}{2} \operatorname{Re} \left(10 \cdot (0.5 - j0.25) \cdot 0.05 \right)$$

$$P\left(\frac{\lambda}{8}\right) = \frac{1}{2} \cdot 10 \cdot 0.5 \cdot 0.05$$

$$\boxed{P\left(\frac{\lambda}{8}\right) = 12.5 \text{ mW}}$$

calculated

$$V\left(\frac{\lambda}{8}\right) = 10 \cdot (0.5 - j0.25) \rightarrow \text{on page 9}$$

$$V\left(\frac{\lambda}{8}\right) = A_1 \left(1.13 + j0.85 \right) \rightarrow \text{calculated on page 3}$$

$$A_1 = ?$$

$$10 \cdot (0.5 - j0.25) = A_1 \left(1.13 + j0.85 \right)$$

$$A_1 = 10 \frac{0.5 - j0.25}{1.13 + j0.85}$$

$$A_1 = 10 \frac{(0.5 - j0.25)(1.13 - j0.85)}{(1.13)^2 + (0.85)^2}$$

$$A_1 = 10 \frac{0.3525 - j0.4075}{2}$$

$$A_1 = 3.35 \quad \boxed{-63.45}$$

$$V(d) = 3.35 \quad \boxed{-63.45 e^{jpd}} \quad (1 + 0.497 / 63.43 e^{-jpd})$$

$$V(0) = 3.35 \quad \boxed{-63.45} (1 +$$

$$V(d) = 3.35 \quad \boxed{-63.45 e^{jpd} + 1.77 e^{-jpd}}$$

$$I(d) = 3.35 \quad \boxed{-63.45 e^{jpd} - 1.77 e^{-jpd}}$$

50

⑥

Transmission lines: Solution for Problem 7 b (3/3)

$$V(d) = 3.55 [-63.45 e^{j\beta d} + 1.77 e^{-j\beta d}]$$

$$V(0) \Rightarrow d = 0$$

$$V(0) = 3.55 e^{j63.45} + 1.77$$

$$V(0) = 3.55 \cos(63.45) + j3.55 \sin(63.45) + 1.77$$

$$V(0) = 3.53 + j3.53$$

$$\boxed{V(0) = 3.53 (1+j) = 5 \cdot e^{j45^\circ}}$$

$$I(0) = \frac{V(0)}{50 + j50} = \frac{3.53(1-j)}{50(1+j)}$$

$$P(0) = \frac{1}{2} \operatorname{Re} \{ V(0) \cdot I(0)^* \}$$

$$P(0) = \frac{1}{2} \operatorname{Re} \{ 5 e^{-j45^\circ} \cdot 0.0706 e^{j\pi/2} \}$$

$$P(0) = \frac{1}{2} \cdot 0.353 \cos(45^\circ)$$

$$P(0) = 125 \text{ mW}$$

Transmission lines: Solution for Problem 7 c,d

c) $V(d,t) = \operatorname{Re} \left\{ (3.95 L - 63.45 e^{j\beta d} + 1.77 e^{-j\beta d}) e^{j\omega t} \right\}$

$$V(d,t) = \operatorname{Re} \left\{ 3.95 e^{j\beta d - j63.45 + j\omega t} + 1.77 e^{-j\beta d + j\omega t} \right\}$$

$$V(d,t) = 3.95 \cos(\omega t + \beta d - 63.45) + 1.77 \cos(\omega t - \beta d)$$

$$V(d,t) = 3.95 [\cos(\omega t + \beta d) \cdot \cos(63.45) + \sin(\omega t + \beta d) \sin(63.45)] + 1.77 \cos(\omega t - \beta d)$$

$$V(d,t) = 3.95 \cdot 1.76 \cos(\omega t + \beta d) + 3.53 \sin(\omega t + \beta d) + 1.77 \cos(\omega t - \beta d)$$

$$V(d,t) = 1.76 (\cos \omega t \cdot \cos \beta d - \sin \omega t \cdot \sin \beta d) + 3.53 (\sin \omega t \cos \beta d + \cos \omega t \sin \beta d) + 1.77 (\cos \omega t \cos \beta d + \sin \omega t \sin \beta d)$$

$$V(d,t) = 3.54 \cos \beta d \cos \omega t + 3.54 \quad (7)$$

$$+ 3.54 \sin \beta d \cos \omega t$$

$$+ 3.54 \cos \beta d \sin \omega t$$


d) $f = 1 \text{ GHz}$

$$\lambda = c/f = 0.3$$

$$\frac{\lambda}{8} = 3.75 \text{ cm.}$$


Matching network: Problem 9

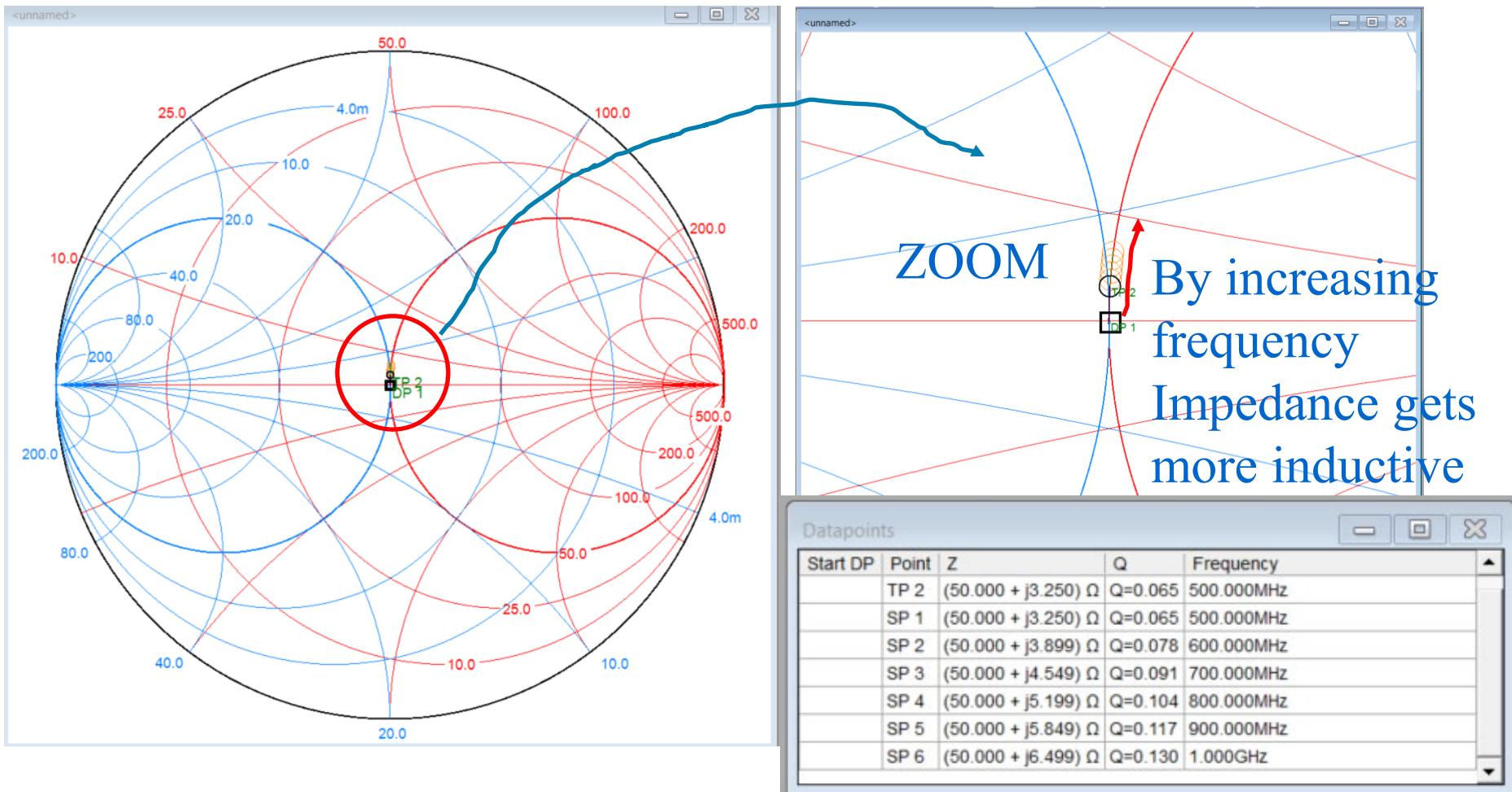For a series R-L network draw the path in the ZY-Smith chart for the frequency range 500 MHz to 1 GHz for $R=50 \Omega$ and $L=1 \text{ nH}$.




Matching network: Problem 10

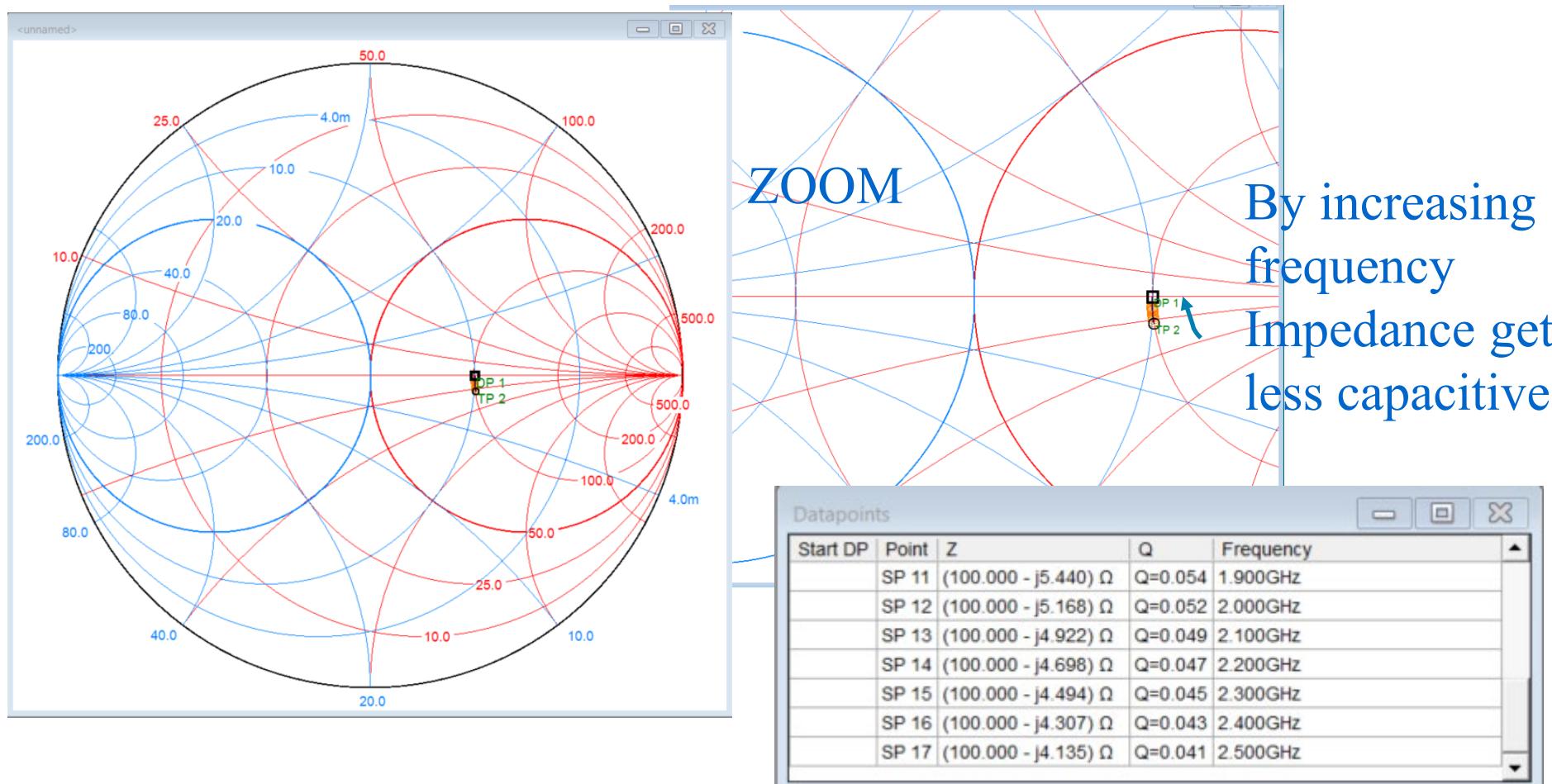For a series R-C network draw the path in the 50Ω ZY-Smith chart for the frequency range 900 MHz to 2.5 GHz for $R=100 \Omega$ and $C=1.5 \text{ pF}$.



Matching: Problem 11

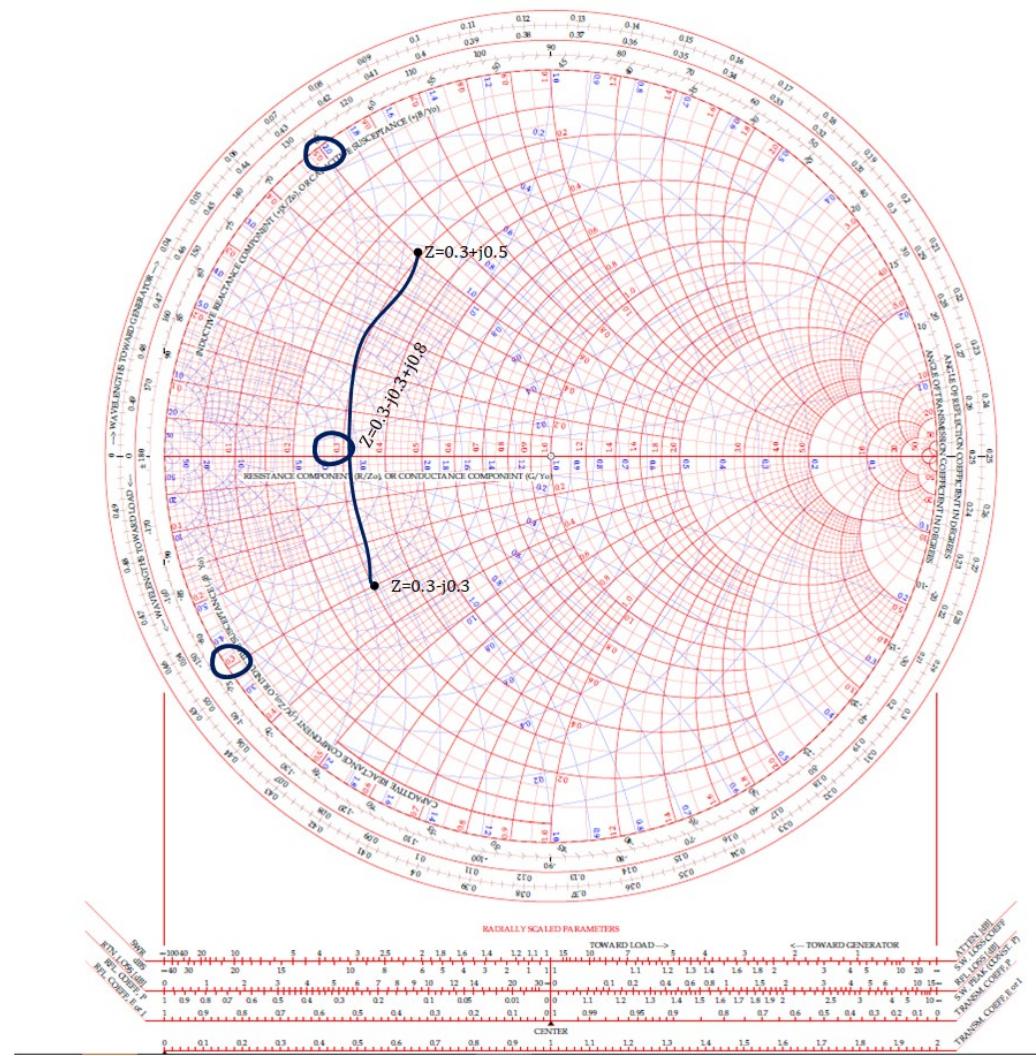
In the Smith chart, illustrate the effect of adding a series inductor L ($z_L=j 0.8$) to an impedance $z=0.3 - j0.3$.



Matching: Problem 12

- d) Illustrate the effect of adding a shunt inductor L ($y_L = -j2.4$) to an admittance $y = 1.6 + j1.6$ in the ZY Smith chart.
- e) Illustrate the effect of adding a shunt capacitor C ($y_{LC} = j3.4$) to an admittance $y = 1.6 + j1.6$ in the ZY Smith chart.

Matching: Problem 12 - solution

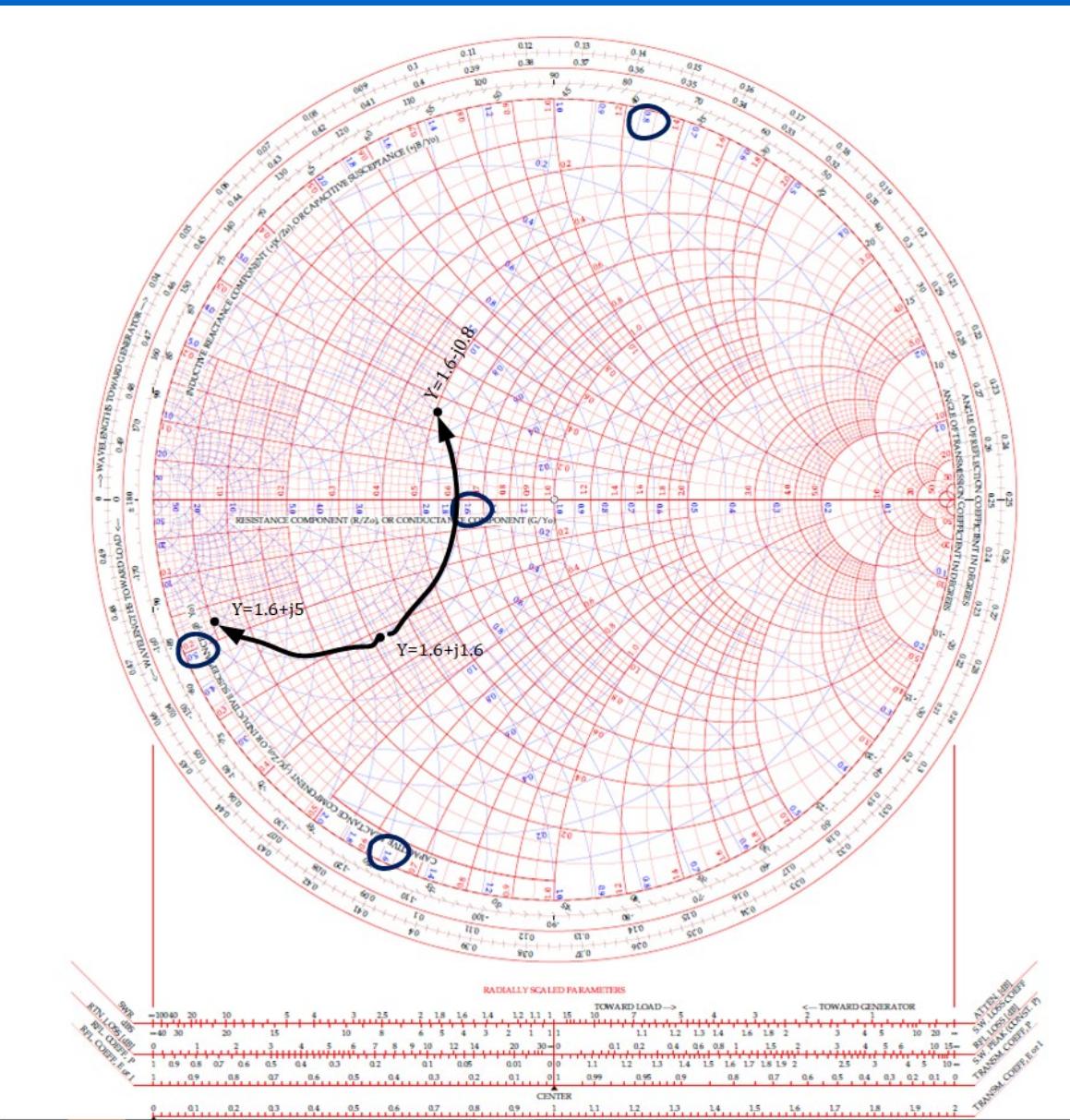


Smith Chart: Problem 13

A load of impedance $Z_{LOAD} = 10 + j10\Omega$ is to be matched to a 50Ω line for the frequency $f=500$ MHz.

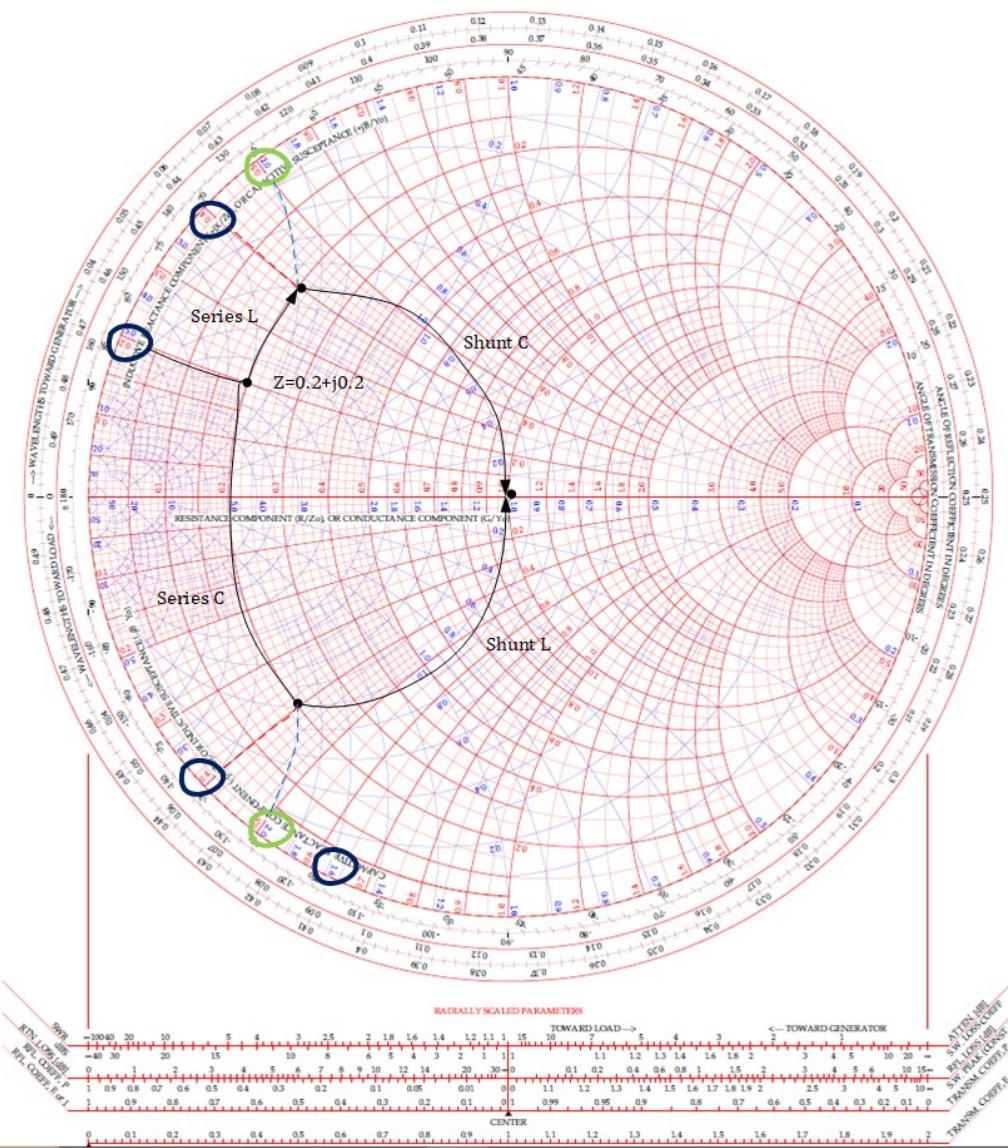- a) Use the Smith chart and design two 2-element L-C matching networks and specify the values of L and C. Illustrate your answer in the Smith chart.
- b) Find the values of L and C by an analytical calculation (without the Smith chart).

Matching network: Problem 13 – solution (1/2)



a) option 1:

$$Z_{in} = 50 \Omega$$

$$\frac{Z_{in}}{Z_L} = \frac{50}{0.2 + j0.2}$$

$$Z_L = 10 \Omega + j10 \Omega$$

$$Z_L = 0.2 + j0.2$$

$$WL = 0.4 - 0.2 = 0.2$$

$$L = \frac{0.2}{2\pi \cdot 500 \cdot 10^6 H_z} = 3.18 \text{ nH}$$

$$WC = 2 \cdot 0.02 = 0.04$$

$$C = \frac{0.04}{2\pi \cdot 500 \cdot 10^6} = 12.7 \text{ pF}$$

option 2:

$$Z_{in} = 50 \Omega$$

$$\frac{Z_{in}}{Z_L} = \frac{50}{0.2 + j0.2}$$

$$Z_L = 10 \Omega + j10 \Omega$$

$$Z_L = 0.2 + j0.2$$

$$\frac{1}{WL} = (0.2 - (-0.4)) \cdot 50 \Omega = 30 \Omega$$

$$\rightarrow C = \frac{1}{2\pi \cdot 500 \cdot 10^6 \cdot 30 \Omega} = 10.6 \text{ pF}$$

$$\frac{1}{WL} = 2 \cdot 0.02 = 0.04$$

$$L = \frac{1}{2\pi \cdot 500 \cdot 10^6 \cdot 0.04} = 7.96 \text{ nH}$$

Matching network: Problem 13 – solution (2/2)

b) option 1:

$$50 \Omega = Z_{in} = ((Z_L + j\omega L)^{-1} + j\omega C)^{-1}$$

$$0,02 = \frac{1}{Z_L + j\omega L} + j\omega C$$

$$= \frac{1}{R + j(Im(Z_L) + \omega L)} + j\omega C$$

$$= \frac{R - j(Im(Z_L) + \omega L)}{R^2 + (Im(Z_L) + \omega L)^2} + j\omega C$$

$$\text{condition 1: } \frac{R}{R^2 + (Im(Z_L) + \omega L)^2} = 0,02 \quad (1)$$

$$\text{condition 2: } \frac{-Im(Z_L) - \omega L}{R^2 + (Im(Z_L) + \omega L)^2} + \omega C = 0 \quad (2)$$

$$(1) \Rightarrow R = 0,02 (R^2 + (Im(Z_L) + \omega L)^2)$$

$$\pm \sqrt{\frac{R}{0,02} - R^2} = (Im(Z_L) + \omega L)$$

$$\Rightarrow \omega L = \pm \sqrt{\frac{R}{0,02} - R^2} - Im(Z_L)$$

$$\omega L = (\pm 20 - 10) \Omega$$

$$= 10 \Omega, \text{ as } \omega L > 0$$

$$L = 3,18 \cdot 10^{-9} H$$

$$= 3,18 nH$$

$$\text{with } L = 3,18 nH : \quad \omega C = \frac{Im(Z_L) + \omega L}{R^2 + (Im(Z_L) + \omega L)^2} = 0,04$$


$$C = 12,7 pF$$

Similar procedure for option ②

Matching network: Problem 14

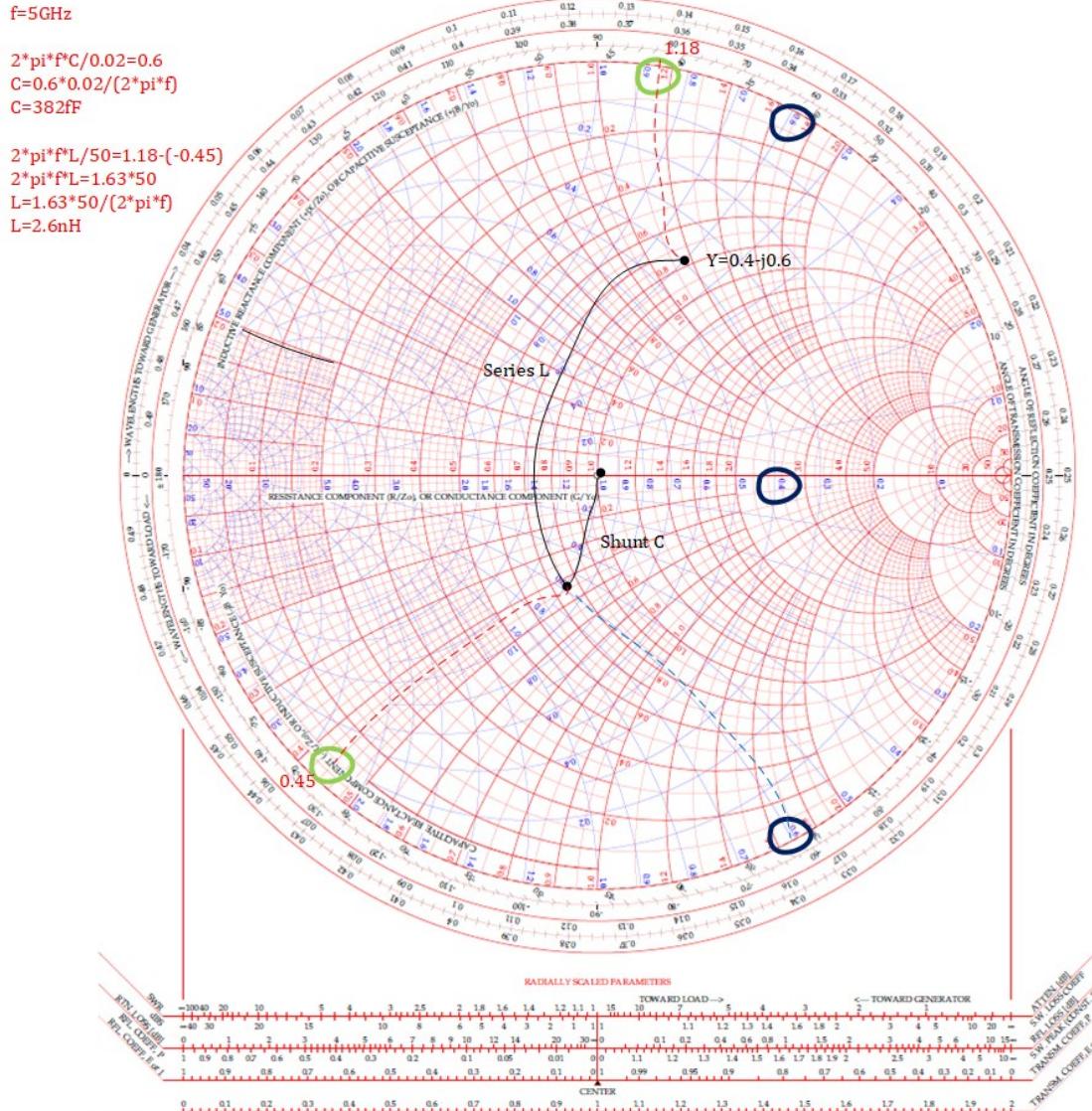- a) Design a matching network for $f = 5 \text{ GHz}$ composed of an inductor L and a capacitor C to transform a 50Ω load at the input to an admittance $Y_{\text{OUT}}=(8 - j12) \cdot 10^{-3} \text{ S}$ at the output.
- b) Illustrate your solution in the Smith chart.

Matching network: Problem 14 –solution (1/2)



Matching network: Problem 14 –solution (2/2)

