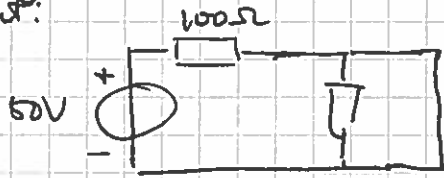


Question 1 TRANSMISSION LINES

- ①A Steady state, before $t=0$. \Rightarrow TL's "do not matter"
Circuit:



$$V_{\text{steady}, Z_0} = V_{\text{steady}, Z_1} = 0 \text{ [V]}$$

$$I_{\text{steady}, Z_0, Z_1} = \frac{50}{100} = 0.5 \text{ [A]}$$

(note: all the current flowing in the short.)

- ①B The decomposition can be done in two ways

① Using the "standard" equations:

$$V_{\text{steady}}^+ = \frac{Z_L + Z}{2(Z_L + Z)} V_g \quad V_{\text{steady}}^- = \frac{Z_L - Z}{2(Z_L + Z)} V_g$$

$$\Rightarrow \text{for } Z_0: \quad V_{\text{steady}}^+ = \frac{100}{200} \cdot 50 = 25 \text{ [V]}$$

$$V_{\text{steady}}^- = \frac{-100}{200} \cdot 50 = -25 \text{ [V]}$$

$$(\Sigma = 0 \quad \leftarrow)$$

$$\Rightarrow \text{for } Z_1: \quad V_{\text{steady}}^+ = \frac{200}{200} \cdot 50 = 50 \text{ [V]}$$

$$V_{\text{steady}}^- = \frac{-200}{200} \cdot 50 = -50 \text{ [V]}$$

$$(\Sigma = 0 \quad \leftarrow)$$

② Using the decomposition matrix

$$\begin{pmatrix} V_{\text{steady}}^+ \\ V_{\text{steady}}^- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & Z \\ 1 & -Z \end{pmatrix} \begin{pmatrix} V_{\text{steady}} \\ I_{\text{steady}} \end{pmatrix}$$

$$\Rightarrow \text{for } Z_0: \quad \begin{pmatrix} V_{\text{steady}}^+ \\ V_{\text{steady}}^- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & 100 \\ 1 & -100 \end{pmatrix} \begin{pmatrix} 0 \\ 0.5 \end{pmatrix} = \begin{pmatrix} 25 \text{ V} \\ -25 \text{ V} \end{pmatrix}$$

$$\Rightarrow \text{for } Z_1: \quad \begin{pmatrix} V_{\text{steady}}^+ \\ V_{\text{steady}}^- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & 200 \\ 1 & -200 \end{pmatrix} \begin{pmatrix} 0 \\ 0.5 \end{pmatrix} = \begin{pmatrix} 50 \text{ V} \\ -50 \text{ V} \end{pmatrix}$$

$$\underline{I_{\text{steady}}}: \Rightarrow \text{for } Z_0: \quad I_{\text{steady}}^+ = \frac{V_{\text{steady}}^+}{Z} = \frac{25}{100} = 0.25 \text{ [A]}$$


$$I_{\text{steady}}^- = \frac{V_{\text{steady}}^-}{Z} = \frac{-25}{100} = -0.25 \text{ [A]}$$

$$(\Sigma = 0.5 \text{ [A]} \quad \leftarrow)$$

$$\Rightarrow \text{for } Z_1: \quad I_{\text{steady}}^+ = 0.25 \text{ [A]} \quad \text{and} \quad I_{\text{steady}}^- = -0.25 \text{ [A]}$$

(1c) The new circuit for $t > 0$ is:

(2)

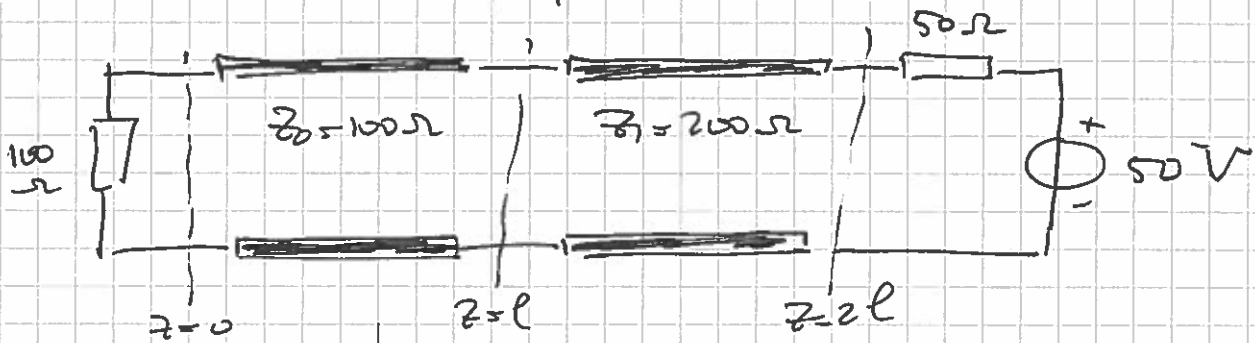

We have to calculate the compensating voltage amplitude.
The voltage over the line for $t < 0 = 0V$!

at $z=0$ \Rightarrow not a lot will happen. It was zero and no additional wave is generated
 \rightarrow still $0V$, so no wave

at $z=2l$ \Rightarrow There will be a step of voltage $50V$ over $Z_2 = 50\Omega$ and the transmission line with $Z_1 = 200\Omega$

\rightarrow gives a wave of $\frac{200}{200+50} \cdot 50 = 40V$

The wave is propagating from $z=2l$ in the negative z -direction

(1d) Bouncing diagram for $0 < t < 2\mu s$

first: timing. $l = 90m \Rightarrow 0.3\mu s$
 $2l = 180m \Rightarrow 0.6\mu s$

second: reflection and transmission coefficients.

$$\Gamma_0 = \frac{100 - 100}{100 + 100} = 0 \quad (\text{matched})$$




$$\Gamma_{2l} = \frac{50 - 200}{50 + 200} = -\frac{3}{5}$$

$$\Gamma_{\rightarrow l} = \frac{200 - 100}{200 + 100} = \frac{1}{3} \quad \Rightarrow \quad T_{\rightarrow l} = \frac{4}{3}$$

$$\Gamma_{\leftarrow l} = \frac{100 - 200}{100 + 200} = -\frac{1}{3} \quad \Rightarrow \quad T_{\leftarrow l} = \frac{2}{3}$$


Now we can draw the bounce diagram.

3

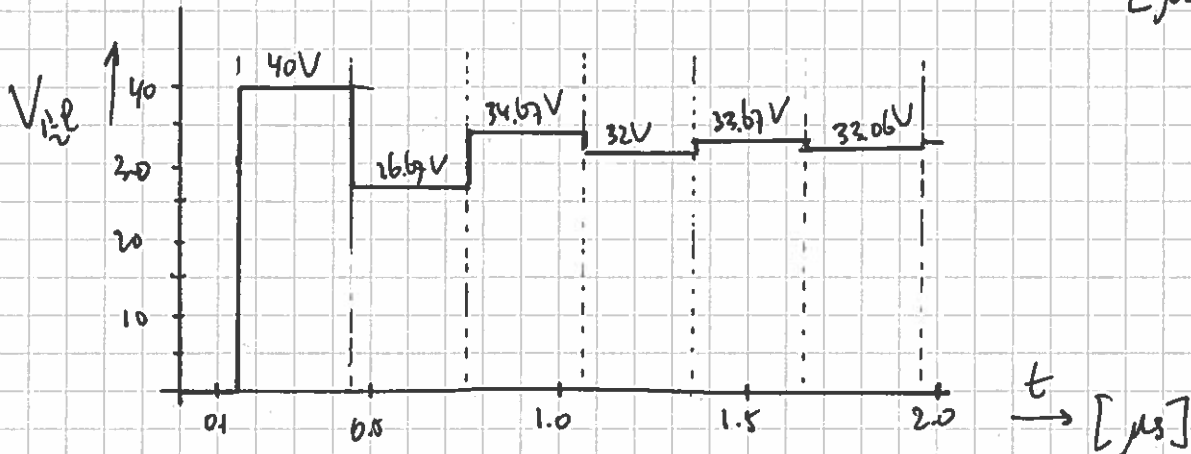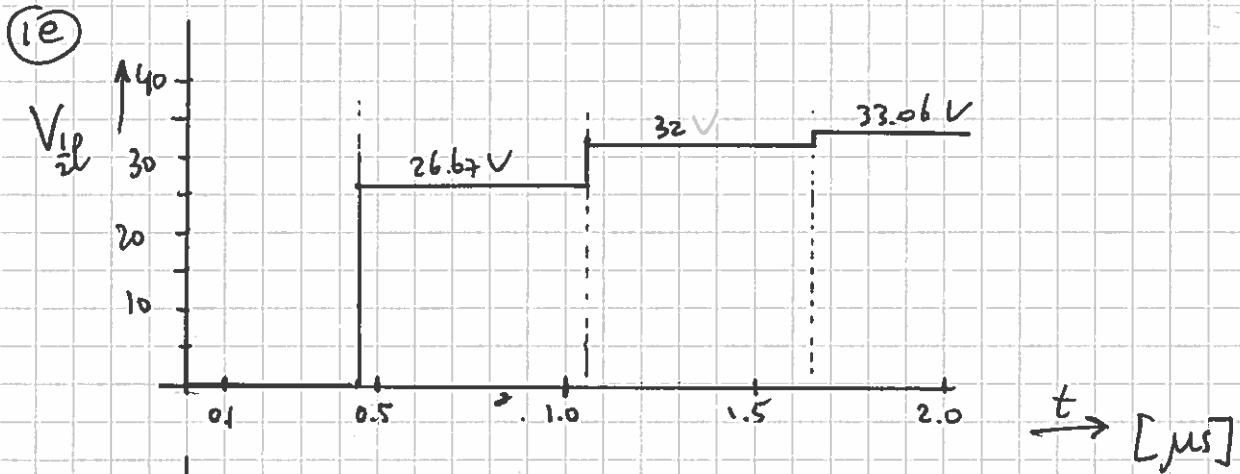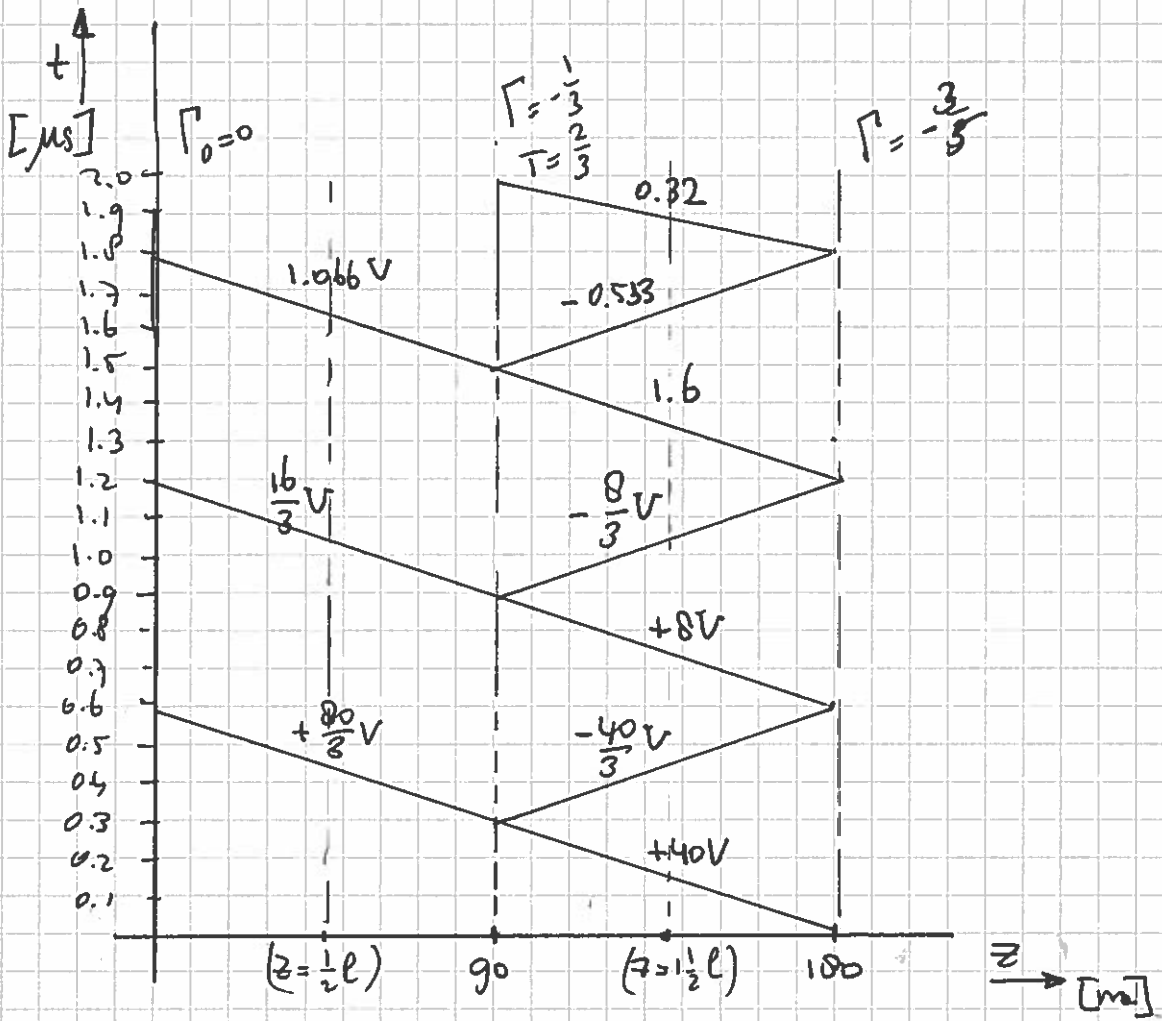

(1f) for $t \rightarrow \infty$ the circuit will be:

(4)

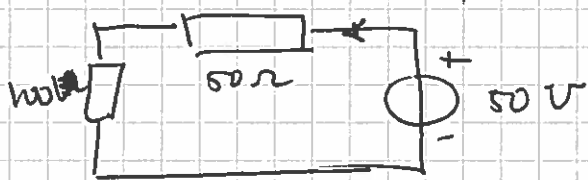


$$V_{\text{steady}} = \frac{100}{150} \cdot 50 = 33\frac{1}{3} [V]$$

$$I_{\text{steady}} = \frac{50}{150} = 0.33 [A]$$

This current is flowing in the negative z -direction so, formally it is $-0.33 [A]$.

You can also see this V_{steady} in the plots of (1e)

Question 2

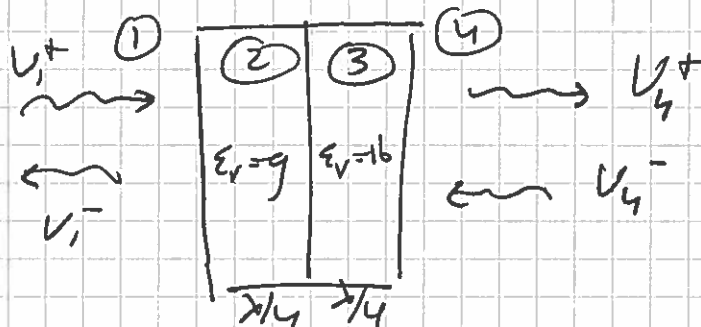

(2A)
$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = T \begin{pmatrix} V_4 \\ I_4 \end{pmatrix} = \begin{pmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{pmatrix} \begin{pmatrix} V_4 \\ I_4 \end{pmatrix}$$

mention something like: a transfer matrix gives the voltage and current at one side (medium 1) given the voltage and current of another side (medium 2)

(2B) given voltages: V_1^+ , V_1^- , V_4^+ and V_4^-

Transfer matrix
$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = T_2 T_3 \begin{pmatrix} V_4 \\ I_4 \end{pmatrix}$$

now
$$\begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & Z_1 \\ 1 & -Z_1 \end{pmatrix} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} \quad (\text{decomposition matrix})$$

and
$$\begin{pmatrix} V_4 \\ I_4 \end{pmatrix} = \begin{pmatrix} 1 & 1 \\ Y_4 & -Y_4 \end{pmatrix} \begin{pmatrix} V_4^+ \\ V_4^- \end{pmatrix} \quad (\text{composition matrix})$$

filling in:
$$\begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 1 & Z_1 \\ 1 & -Z_1 \end{pmatrix} T_2 T_3 \begin{pmatrix} 1 & 1 \\ Y_4 & -Y_4 \end{pmatrix} \begin{pmatrix} V_4^+ \\ V_4^- \end{pmatrix}$$

(or
$$\begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = D_1 T_2 T_3 C_4 \begin{pmatrix} V_4^+ \\ V_4^- \end{pmatrix}$$
)

(2c) Both medium 2 and 3 are $\lambda/4$ long

(5)

$$\Rightarrow k \cdot l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \frac{1}{2} \pi \quad (\text{in both media})$$

So: $T_2(l, l_1) = T_2(0, \frac{\lambda}{4}) = \begin{pmatrix} 0 & jZ_2 \\ jZ_2^{-1} & 0 \end{pmatrix}$

$$T_3(l, l_2) = T_3(l, l + \frac{\lambda}{4}) = \begin{pmatrix} 0 & jZ_3 \\ jZ_3^{-1} & 0 \end{pmatrix}$$

$$\Rightarrow T_2 T_3 = \begin{pmatrix} 0 & jZ_2 \\ jZ_2^{-1} & 0 \end{pmatrix} \begin{pmatrix} 0 & jZ_3 \\ jZ_3^{-1} & 0 \end{pmatrix} = \begin{pmatrix} -Z_2/Z_3 & 0 \\ 0 & -Z_3/Z_2 \end{pmatrix}$$

Now we look if we can replace this with a single medium 5

$$k_5 \cdot l_5 = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \pi \Rightarrow \sin(k_5 l_5) = 0$$
$$\Rightarrow \cos(k_5 l_5) = -1$$

$$T_5 = \begin{pmatrix} -1 & 0 \\ 0 & -1 \end{pmatrix}$$

So, never T_5 will be equal to $T_2 T_3$...

yeah perhaps if $Z_2 = Z_3$, ... However

$$Z_2 = 40\pi \quad \text{and} \quad Z_3 = 30\pi$$

Conclusion: this isn't possible.

(2d)

So, we have $T_2 T_3 = \begin{pmatrix} -Z_2/Z_3 & 0 \\ 0 & -Z_3/Z_2 \end{pmatrix}$

to calculate the scatter matrix, we use the A-matrix and reshuffle the parameters

$$\vec{A} = D_1 T C_4$$

with

$$Z_1 = Z_4 = 120\pi$$

$$Z_2 = 40\pi$$

$$Z_3 = 30\pi$$

$$\Rightarrow T = \begin{pmatrix} -4/3 & 0 \\ 0 & -3/4 \end{pmatrix}$$

$$\textcircled{6} \quad \tilde{A} = \underbrace{\begin{pmatrix} \frac{1}{2} & 60\pi \\ \frac{1}{2} & -60\pi \end{pmatrix} \begin{pmatrix} -\frac{4}{3} & 0 \\ 0 & -\frac{3}{4} \end{pmatrix}}_{\begin{pmatrix} -\frac{4}{6} & -45\pi \\ -\frac{4}{6} & 45\pi \end{pmatrix}} \underbrace{\begin{pmatrix} 1 & 1 \\ \frac{+1}{120\pi} & \frac{-1}{120\pi} \end{pmatrix}}_{\begin{pmatrix} 1 & 1 \\ \frac{1}{120\pi} & \frac{-1}{120\pi} \end{pmatrix}} \\
= \begin{pmatrix} -\frac{2}{3} - \frac{3}{8} & -\frac{2}{3} + \frac{3}{8} \\ -\frac{2}{3} + \frac{3}{8} & -\frac{2}{3} - \frac{3}{8} \end{pmatrix} = \begin{pmatrix} -\frac{25}{24} & -\frac{7}{24} \\ -\frac{7}{24} & -\frac{25}{24} \end{pmatrix}$$

$$\underline{\text{So}} \quad \begin{pmatrix} V_1^+ \\ V_1^- \end{pmatrix} = \begin{pmatrix} -\frac{25}{24} & -\frac{7}{24} \\ -\frac{7}{24} & -\frac{25}{24} \end{pmatrix} \begin{pmatrix} V_4^+ \\ V_4^- \end{pmatrix}$$

$$\Rightarrow \begin{aligned} V_1^+ &= -\frac{25}{24} V_4^+ - \frac{7}{24} V_4^- \\ V_1^- &= -\frac{7}{24} V_4^+ - \frac{25}{24} V_4^- \end{aligned}$$

$$\Rightarrow 24V_1^+ = -25V_4^+ - 7V_4^- \quad (1)$$

$$24V_1^- = -7V_4^+ - 25V_4^- \quad (2)$$

$$25 \times (2): \quad 600V_1^- = -175V_4^+ - 625V_4^- \quad (3)$$

$$7 \times (1): \quad 168V_1^+ = -175V_4^+ - 49V_4^- \quad (4)$$

$$(4) \text{ in } (3) \quad 600V_1^- = 168V_1^+ + 49V_4^- - 625V_4^-$$

$$\Rightarrow \boxed{V_1^- = \frac{168}{600} V_1^+ - \frac{576}{600} V_4^-} \quad (5)$$

(5) in (3)

$$600 \left(\frac{168}{600} V_1^+ - \frac{576}{600} V_4^- \right) = -175V_4^+ - 625V_4^-$$

$$-175V_4^+ = 168V_1^+ + 49V_4^-$$

$$\Rightarrow \boxed{V_4^+ = -\frac{168}{175} V_1^+ - \frac{49}{175} V_4^-}$$

⑦

So, the scatter matrix is

$$\begin{pmatrix} \nu_1^- \\ \nu_4^+ \end{pmatrix} = \begin{pmatrix} \frac{7}{25} & \frac{-24}{25} \\ \frac{-24}{25} & -\frac{7}{25} \end{pmatrix} \begin{pmatrix} \nu_1^+ \\ \nu_4^- \end{pmatrix}$$

~~h~~